

# TAPPING TRANSFORMERS

DAVE VE300I

FEBRUARY 2023




"Went outside the envelope -- faster than the speed for which it was designed." - Chuck Yeager

The speed was so great that Yeager lost control and the aircraft tumbled about 50,000 feet -- turning wildly. Yeager banged his helmeted head so hard on the "canopy" of the cockpit that he dented it. Yet he saved himself and the plane.

# THE PROBLEM
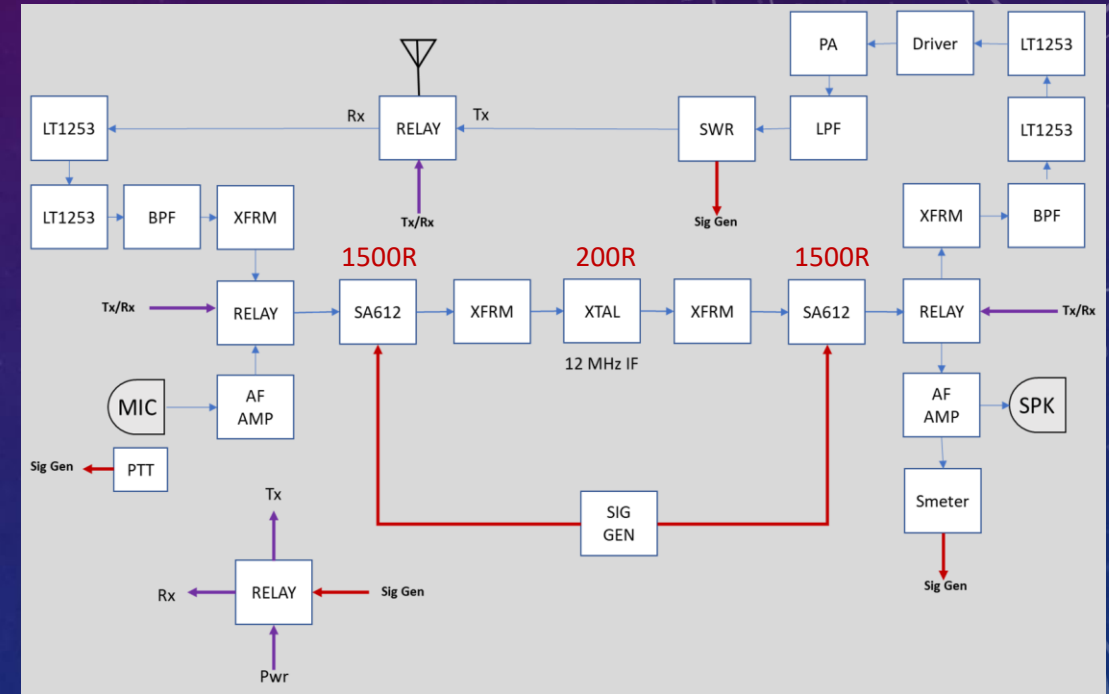
## Background

- Peter and I build the Dueling 612 Transceiver
- SA612 has impedance of 1500R and Crystal Filter has impedance of the order of 200R
- Had issues measuring performance of mixer and crystal filter using Spectrum Analyzer
- We discussed methods of measuring performance
  1. Tap coupling transformers
  2. Using a resistor divider
- The resistor divider was “off the cuff” suggestion




# AGENDA

This is not a tutorial on transformers

- Its not about how transformers work
- Its not about transformers equations. Just accept the equations

This is about simple physics

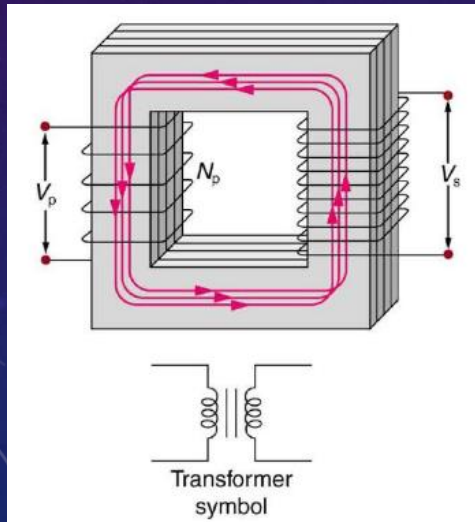

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

$$\frac{I_p}{I_s} = \frac{N_s}{N_p}$$

$$\left(\frac{N_p}{N_s}\right)^2 = \frac{Z_p}{Z_s}$$

Power in a Transformer

$$\text{Power}_{\text{Primary}} = \text{Power}_{\text{Secondary}}$$

$$P_p = I_p V_p = I_s V_s = P_s$$



# PHYSICS

## Simple Physics


- ✓ The power output to a transformer MUST be equal or less than the power input into a transformer. If not, you can make a perpetual motion machine and the world is flat and JFK was shot by aliens
- ✓ This is governed by the laws of thermodynamics

### The Laws of Thermodynamics

**1st Law of Thermodynamics** - Energy cannot be created or destroyed.

**2nd Law of Thermodynamics** - For a spontaneous process, the entropy of the universe increases.

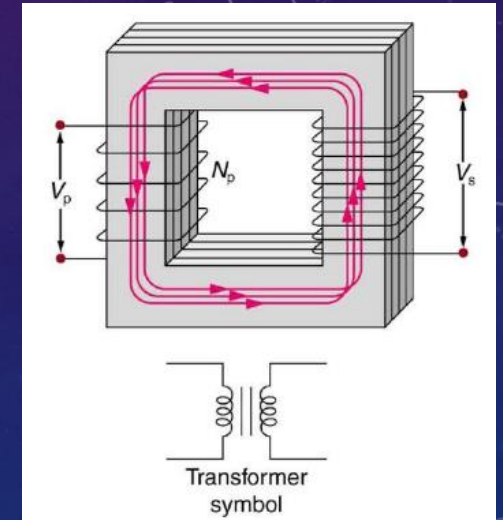**3rd Law of Thermodynamics** - A perfect crystal at zero Kelvin has zero entropy.



As we now know that energy is the capacity to do work, with the standard unit used for energy (and work) being the **Joule**. A joule of energy is defined as the energy expended by one ampere at one volt, moving in one second. Electric current results from the movement of electric charge (electrons) around a circuit, but to move charge from one node to another there needs to be a force to create the work to move the charge, and there is: *voltage*.







### What is Electric Power?

**Electric power Definition** – It is the rate at which work is done or energy is transformed in an **electrical circuit**. Simply put, it is a measure of how much energy is used in a span of time.

In physics, the rate of transfer of electrical energy by an electrical circuit per unit time is called electrical power. Here electrical energy can be either kinetic energy or potential energy. In most of the cases, potential energy is considered, which is the energy stored due to the relative positions of charged particles or electric fields. Electrical power is denoted by  $P$  and measured using Watt.

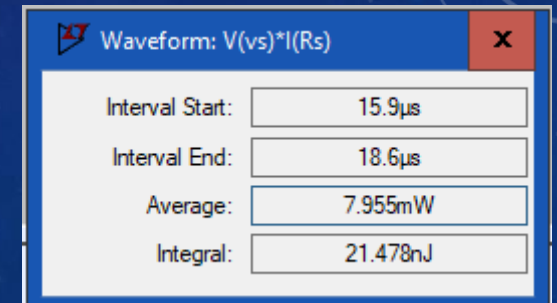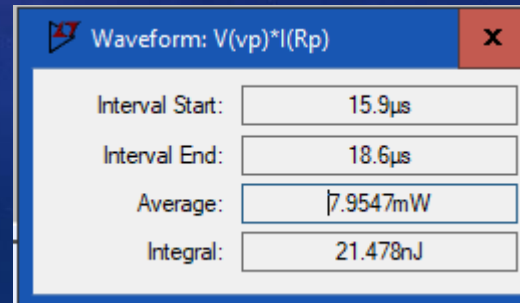
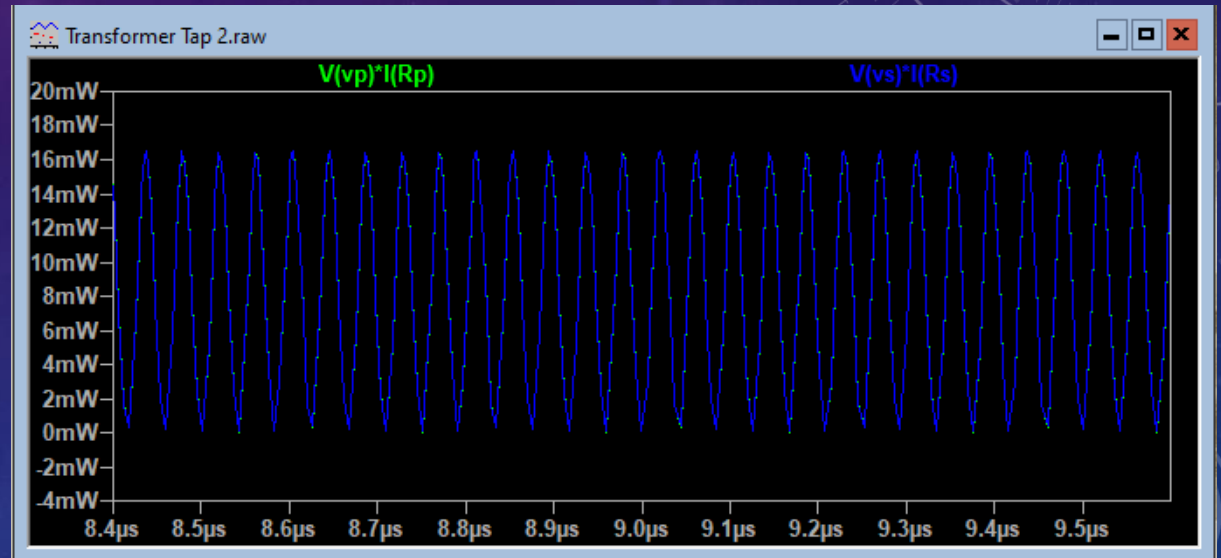
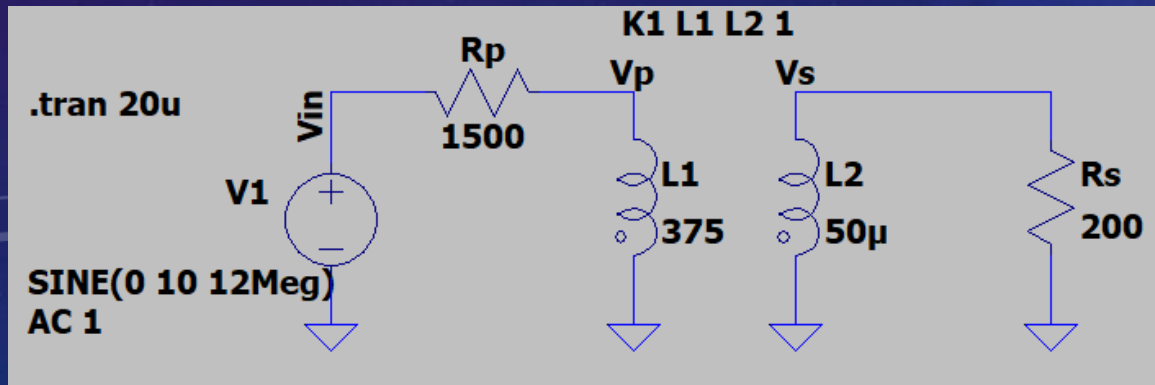
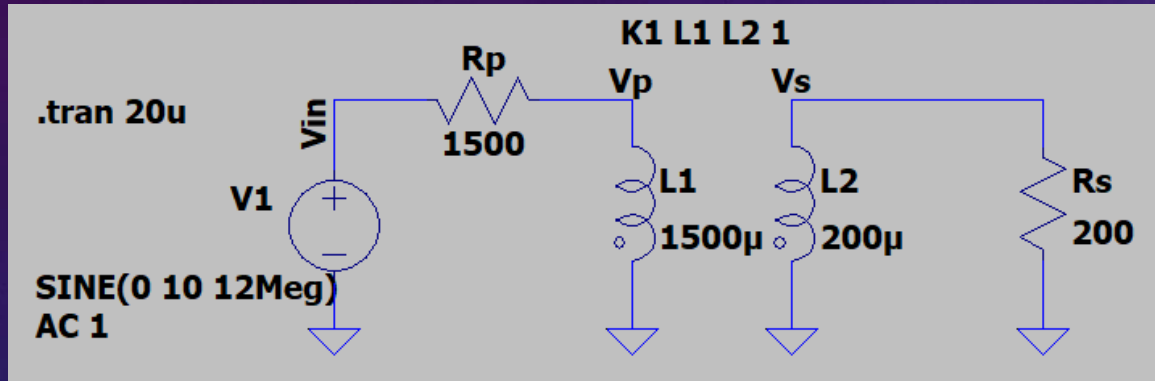
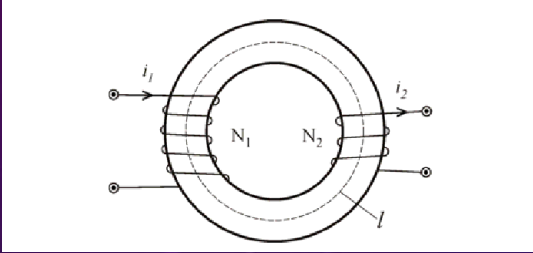
# WHAT DOES THIS MEAN?

Simple Physics: Power Transfer – 1<sup>st</sup> Law of Thermodynamics







# WHAT DOES THIS MEAN?
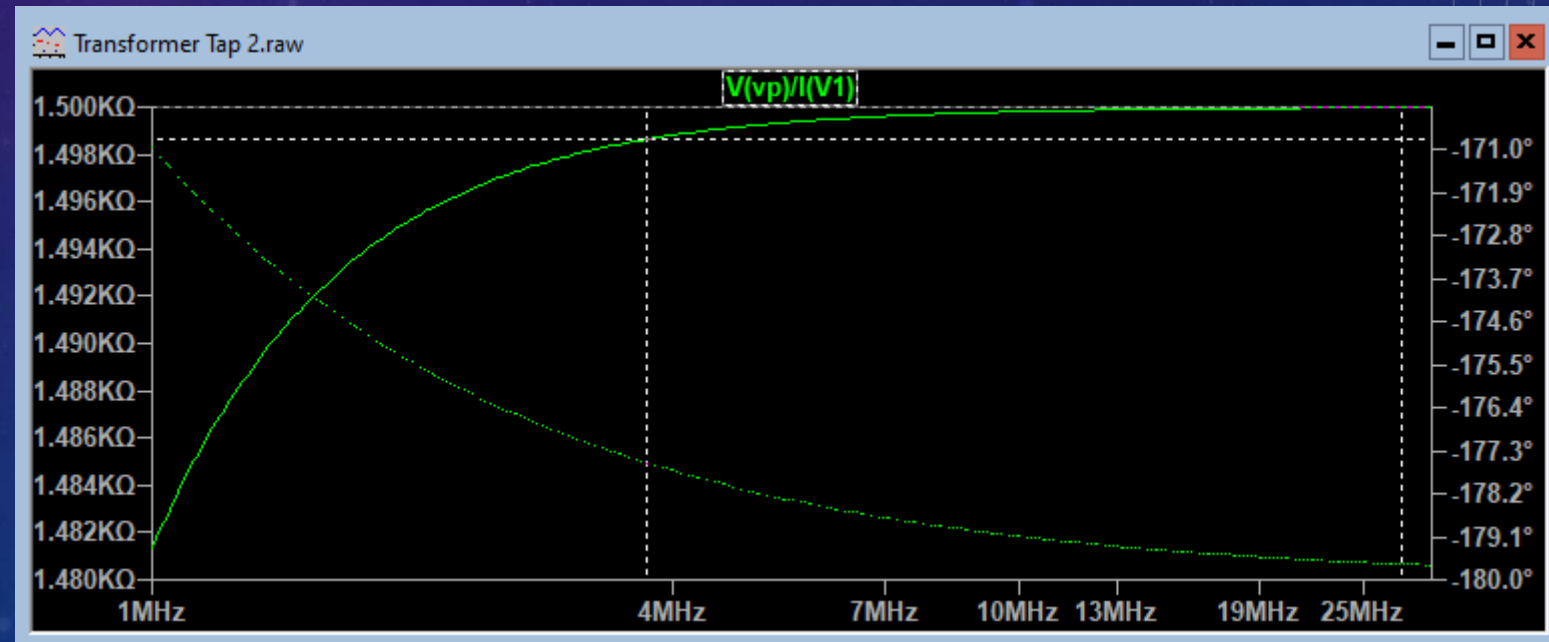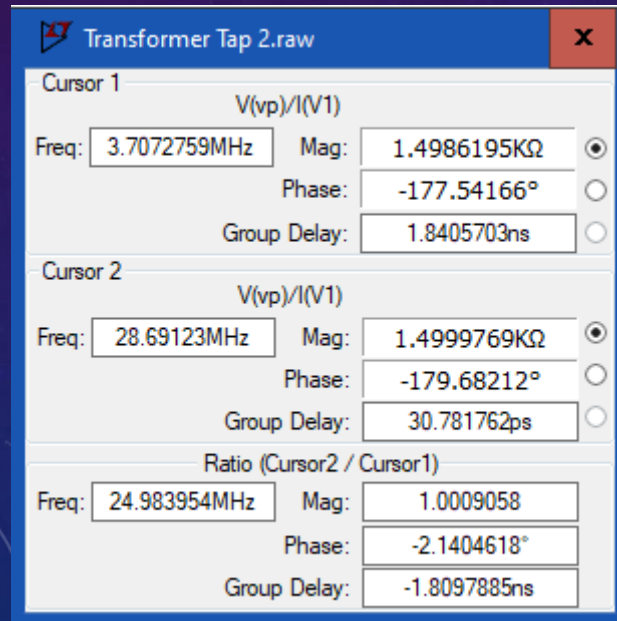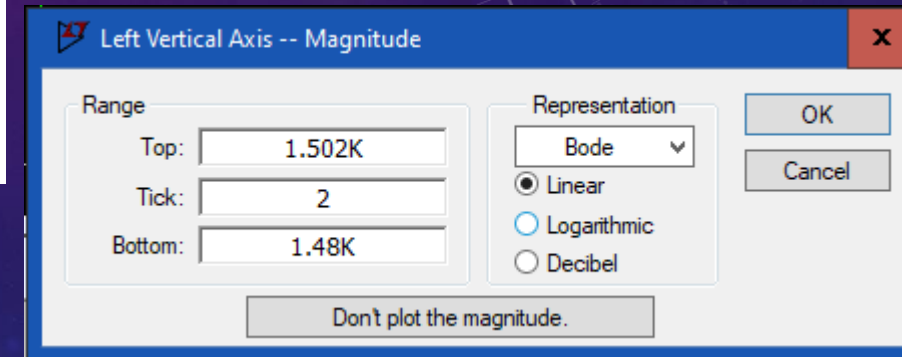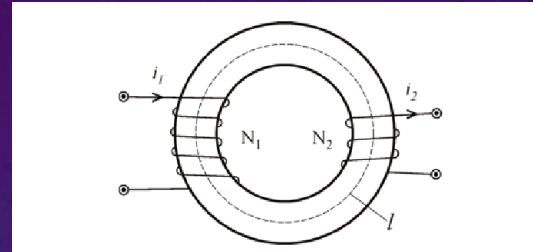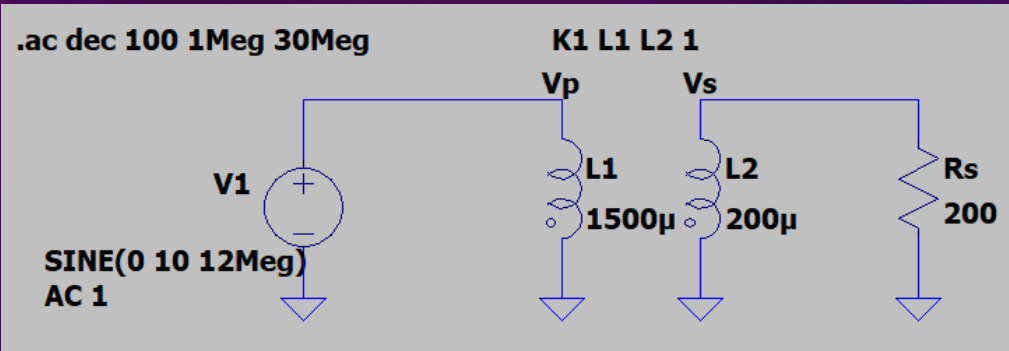
## Simple Physics: Impedance Transformation



# WHAT DOES THIS MEAN?

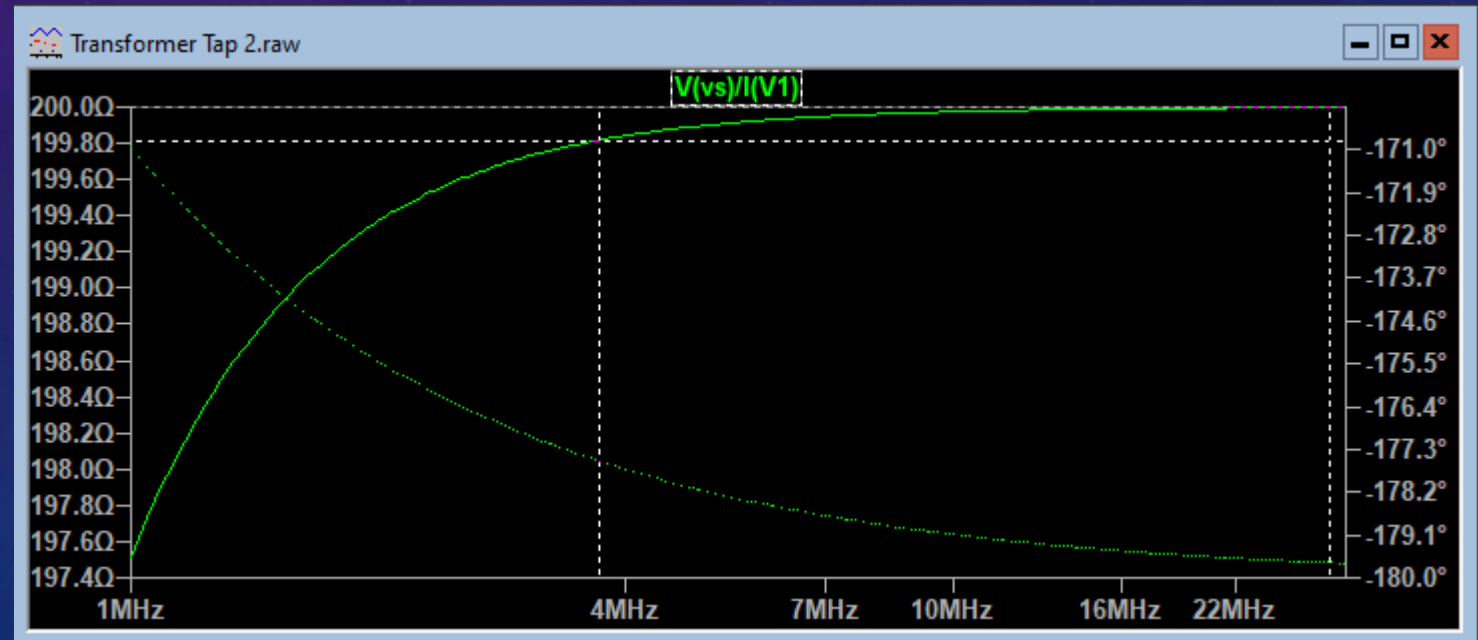
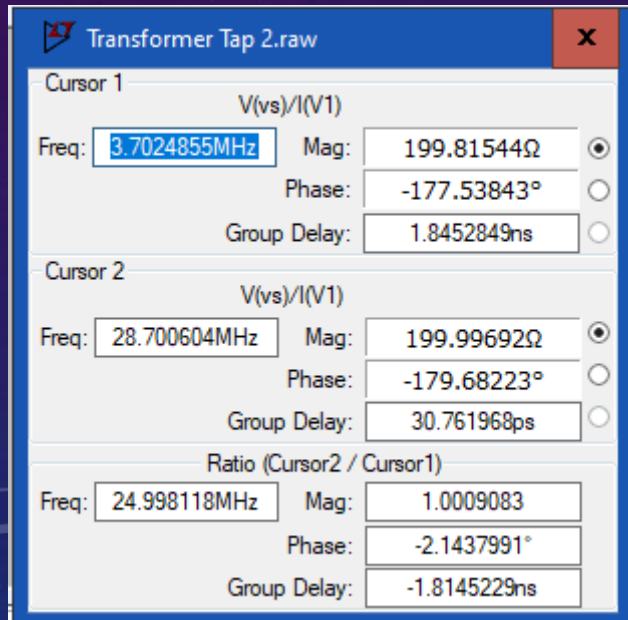
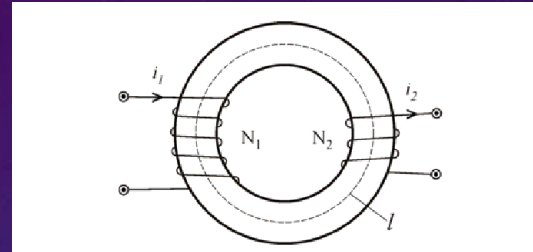
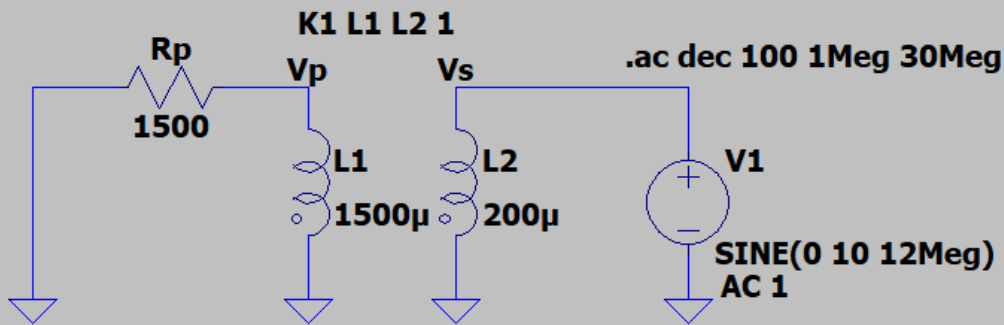
## Simple Physics: Impedance Transformation




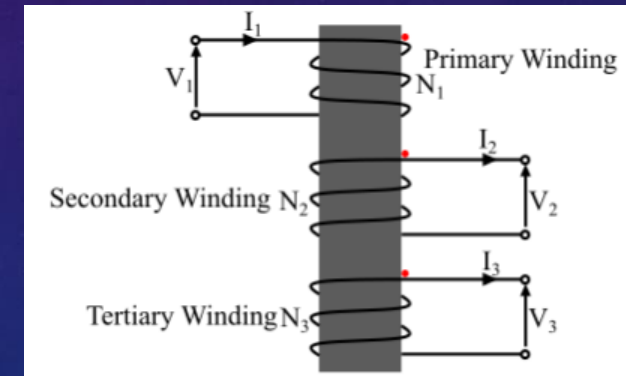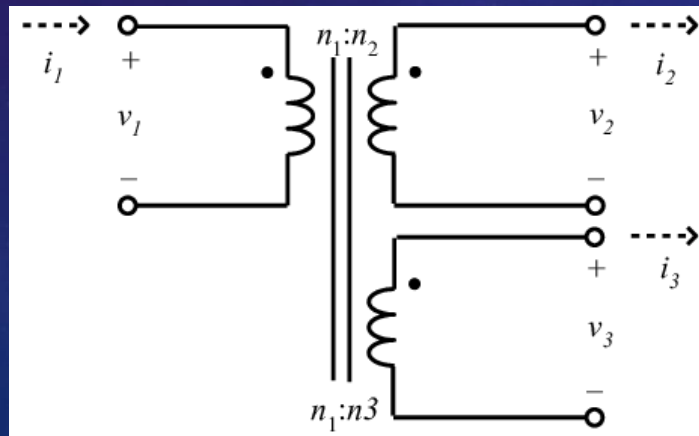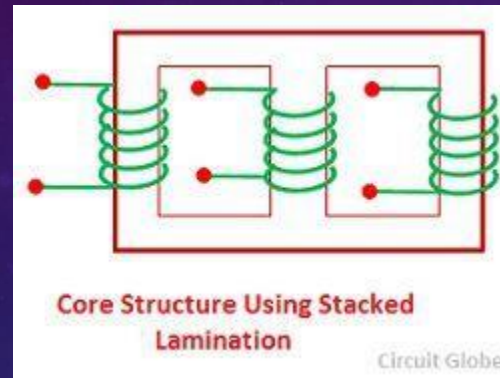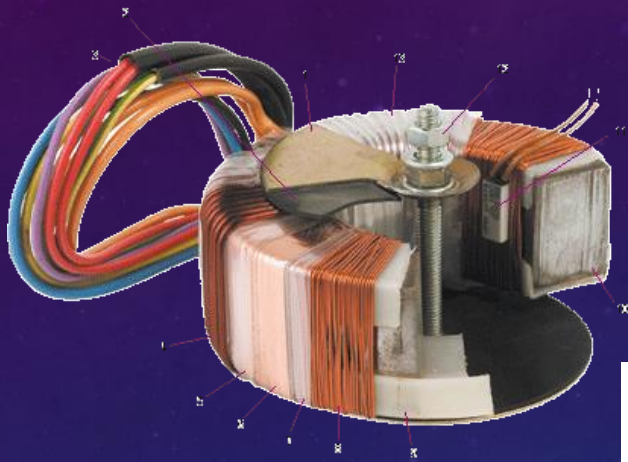
# WHAT HAPPENS IF YOU ADD A TAP?

- ✓ 1<sup>st</sup> Law of Thermodynamics: Power in = Power out (for ideal transformer)
- ✓ Impedance reflected is based on turns ratio of **all turns and taps**



$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$







$$\frac{V_3}{V_1} = \frac{N_3}{N_1}$$

$$N_1 I_1 = N_2 I_2 + N_3 I_3$$


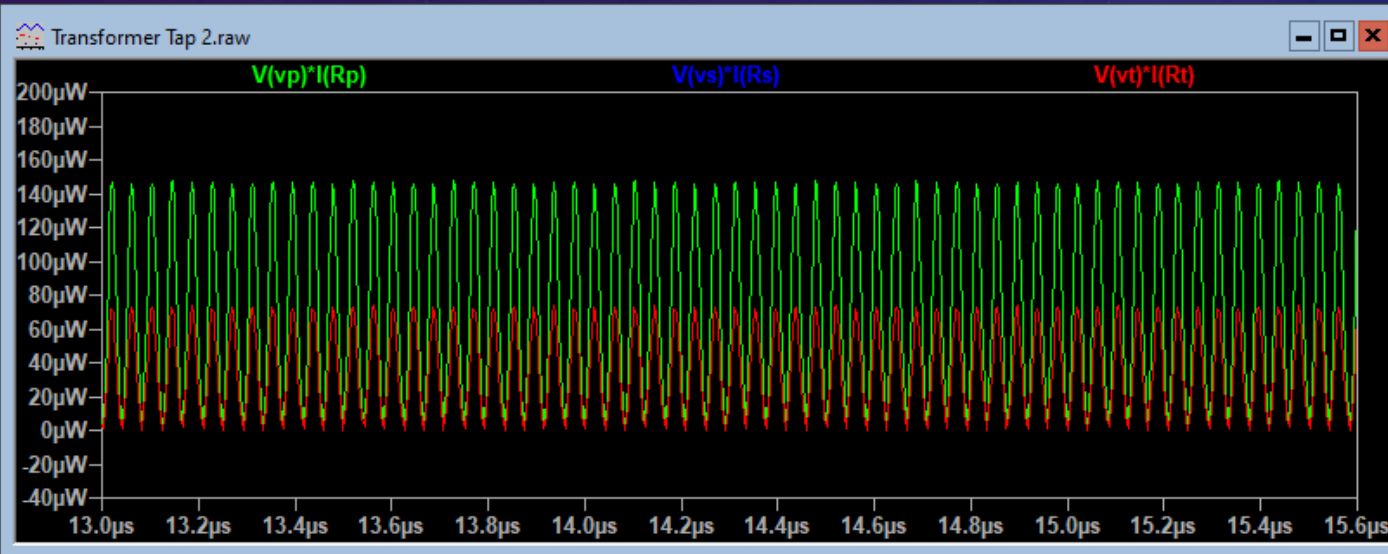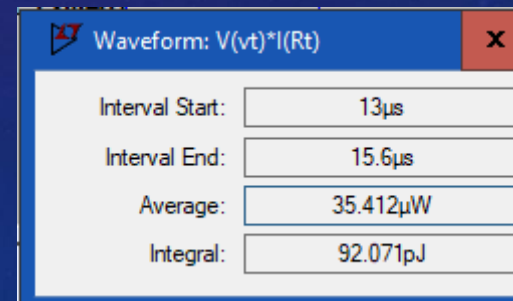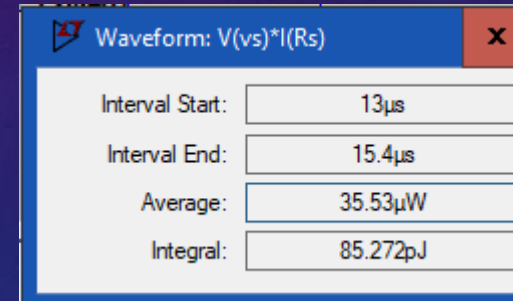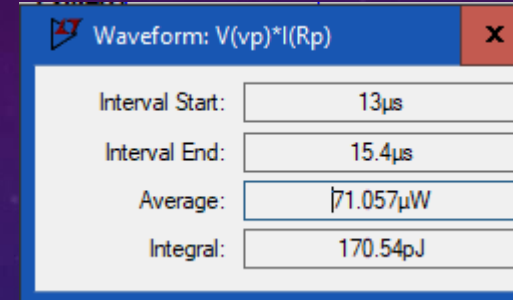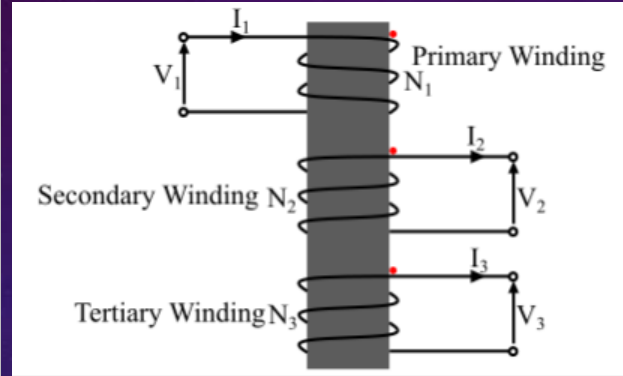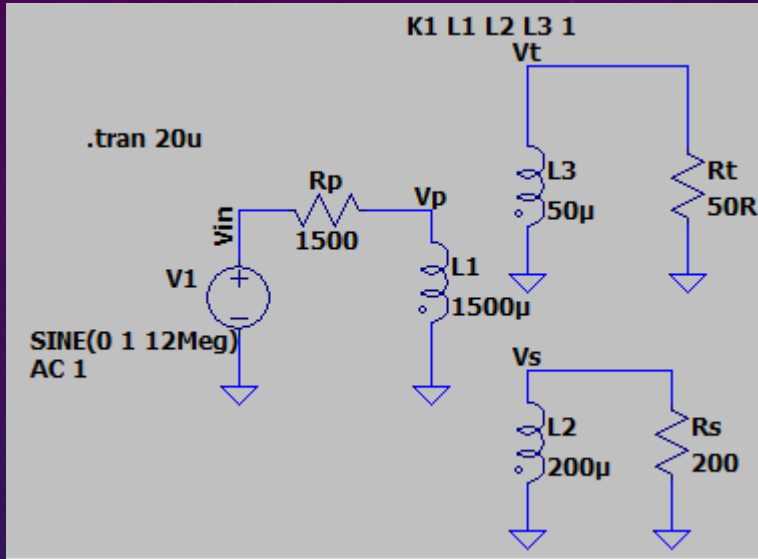
# ADDING 50R TAP

**SIMPLE/COMPLEX** Physics: Power Transfer – 1<sup>st</sup> Law of Thermodynamics









$$35.5\mu\text{W} + 35.4\mu\text{W} = 70.9\mu\text{W} \text{ (71}\mu\text{W)}$$



# ADDING 50R TAP
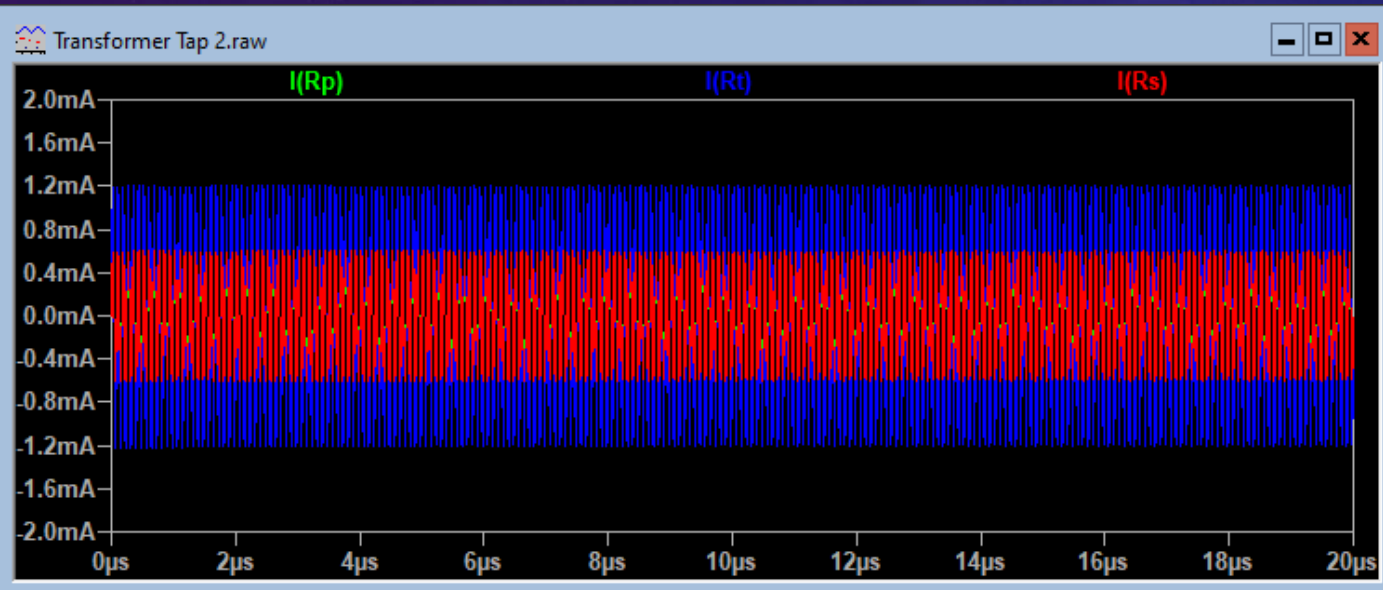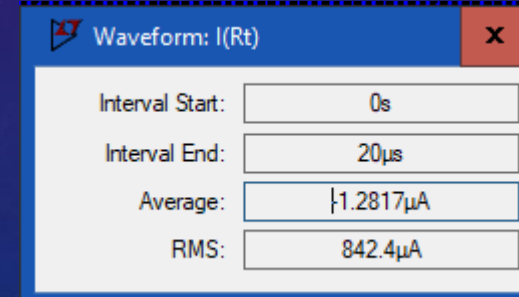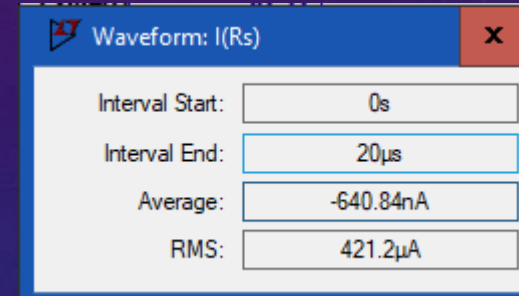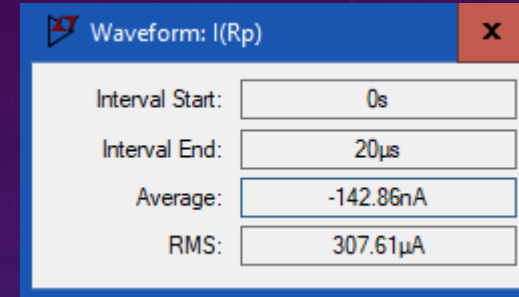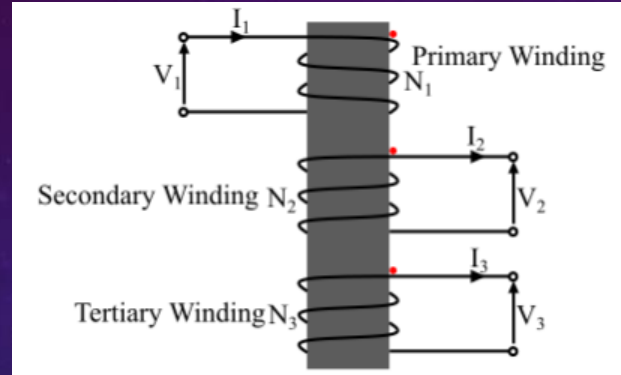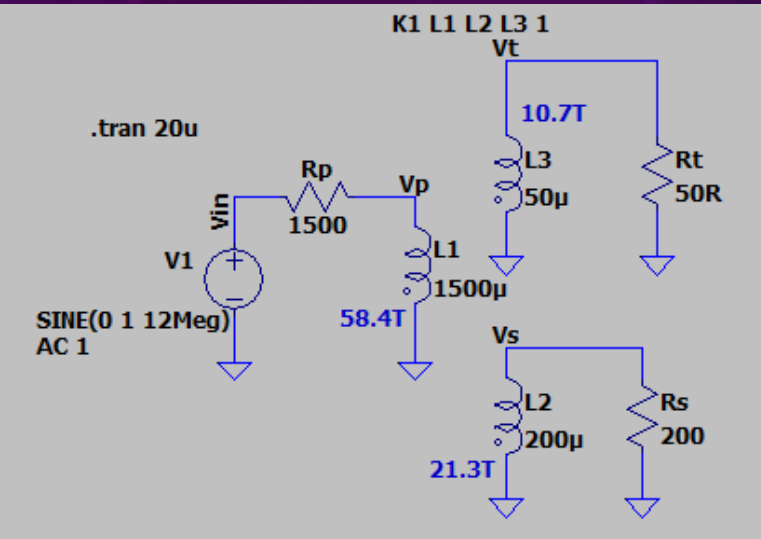
## SIMPLE/COMPLEX Physics: Current Distribution



$$N_1 I_1 = N_2 I_2 + N_3 I_3$$




$$308 \times 58.4 = 17963$$

$$421 \times 21.3 + 842 \times 10.7 = 17985$$



# ADDING 50R TAP
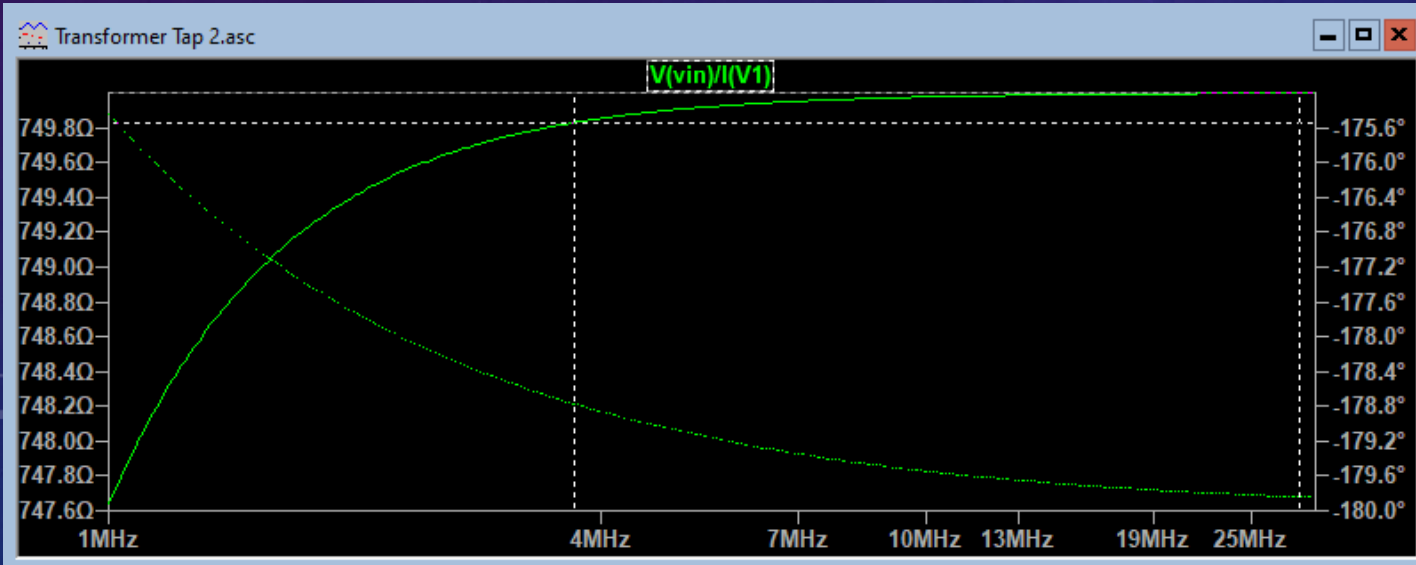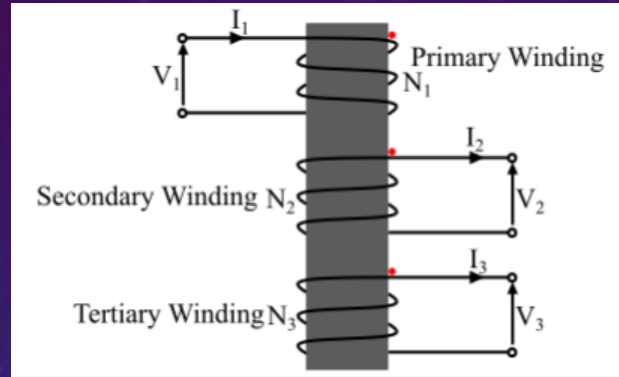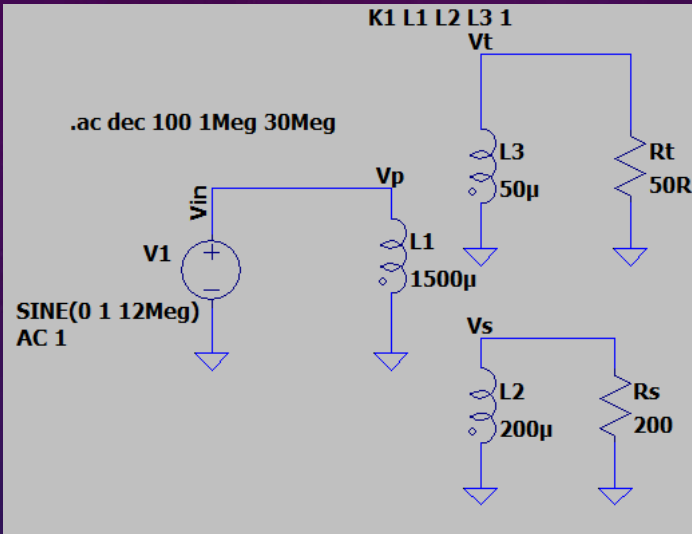
## COMPLEX Physics: Impedance Transformation






Cursor 1		$V(vin)/I(V1)$	
Freq:	3.7127462MHz	Mag:	749.82778 $\Omega$
		Phase:	-178.77211 $^\circ$
		Group Delay:	918.85686ps
Cursor 2		$V(vin)/I(V1)$	
Freq:	28.700604MHz	Mag:	749.99712 $\Omega$
		Phase:	-179.84109 $^\circ$
		Group Delay:	15.379339ps


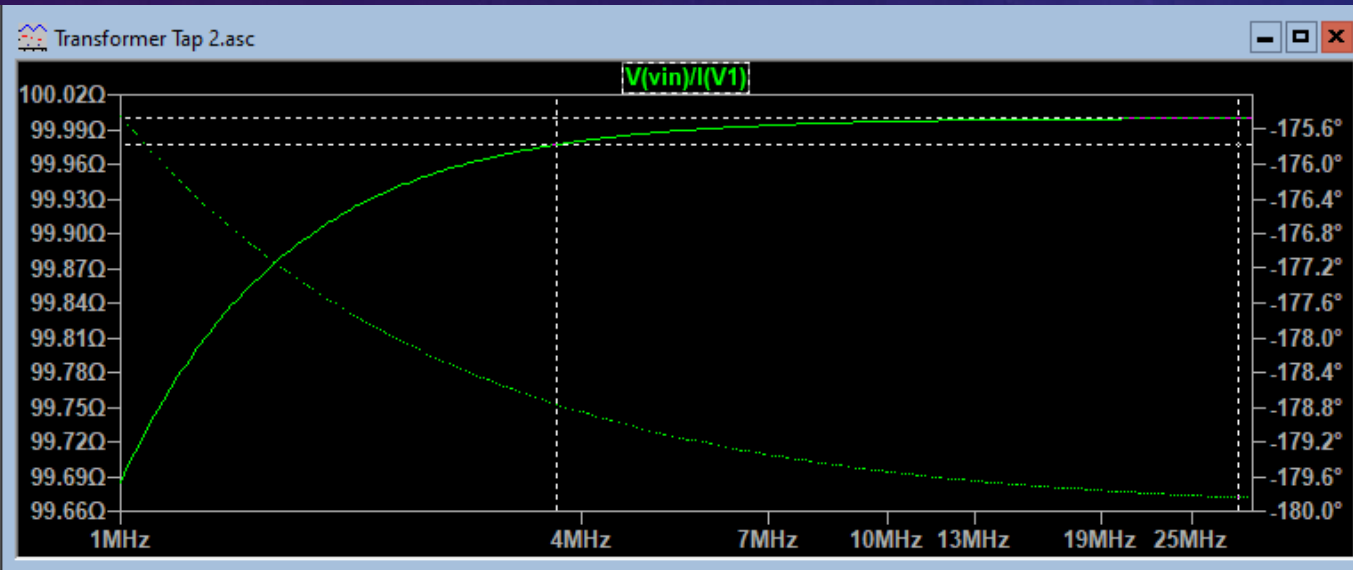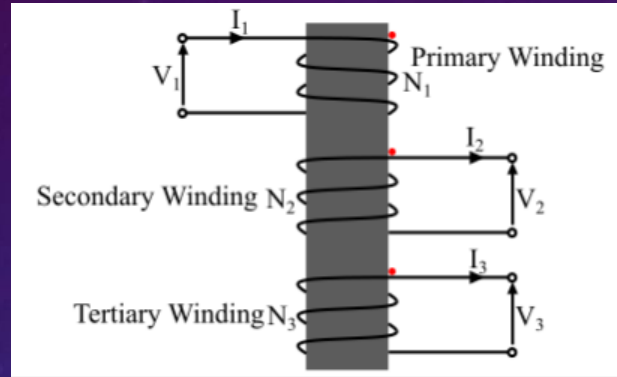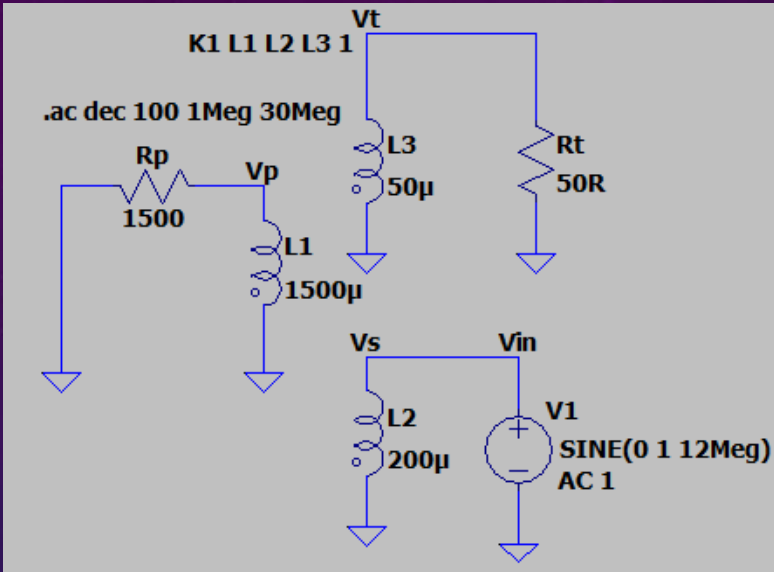
# ADDING 50R TAP

COMPLEX Physics: Impedance Transformation






Cursor 1			
V(vin)/I(V1)			
Freq:	3.7127462MHz	Mag:	99.977037Ω
		Phase:	-178.77211°
		Group Delay:	918.85686ps
Cursor 2			
V(vin)/I(V1)			
Freq:	28.700604MHz	Mag:	99.999616Ω
		Phase:	-179.84109°
		Group Delay:	15.379339ps



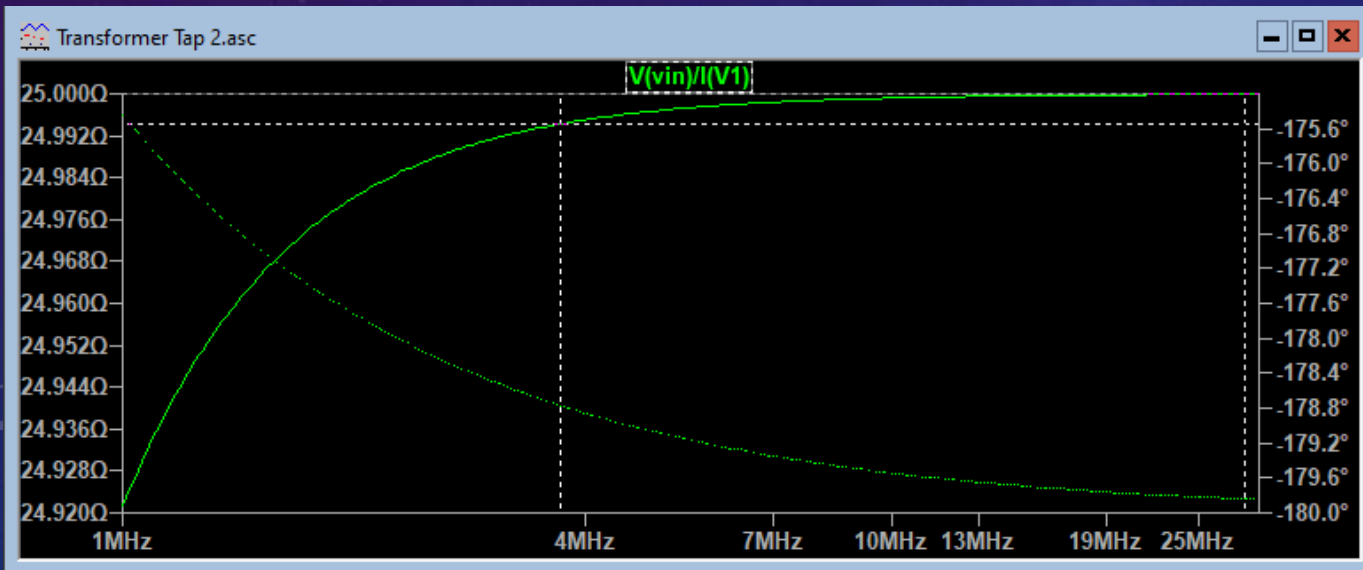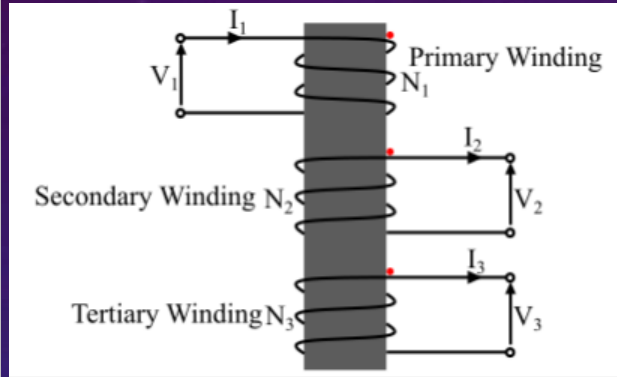
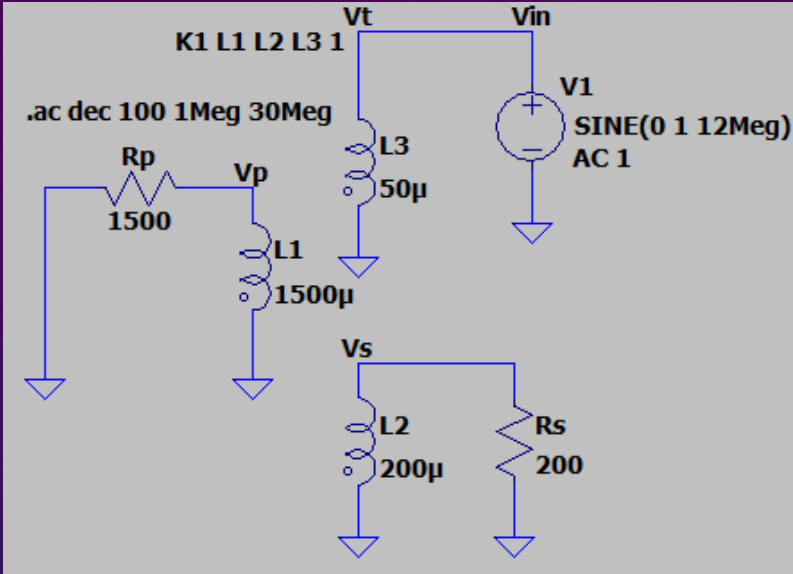
# ADDING 50R TAP

COMPLEX Physics: Impedance Transformation




Cursor 1			
$V(vin)/I(V1)$			
Freq:	3.7096448MHz	Mag:	24.994249Ω
		Phase:	-178.77106°
		Group Delay:	920.38721ps
Cursor 2			
$V(vin)/I(V1)$			
Freq:	28.693325MHz	Mag:	24.999904Ω
		Phase:	-179.84105°
		Group Delay:	15.387025ps

# CRYSTAL FILTER Q VS LOADING

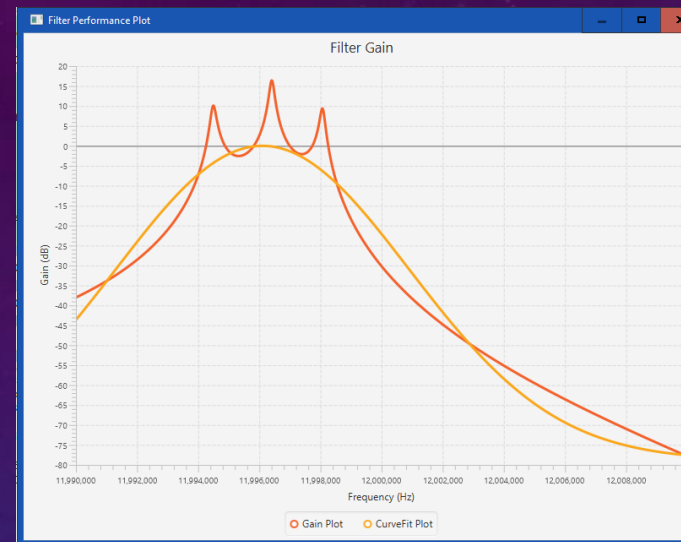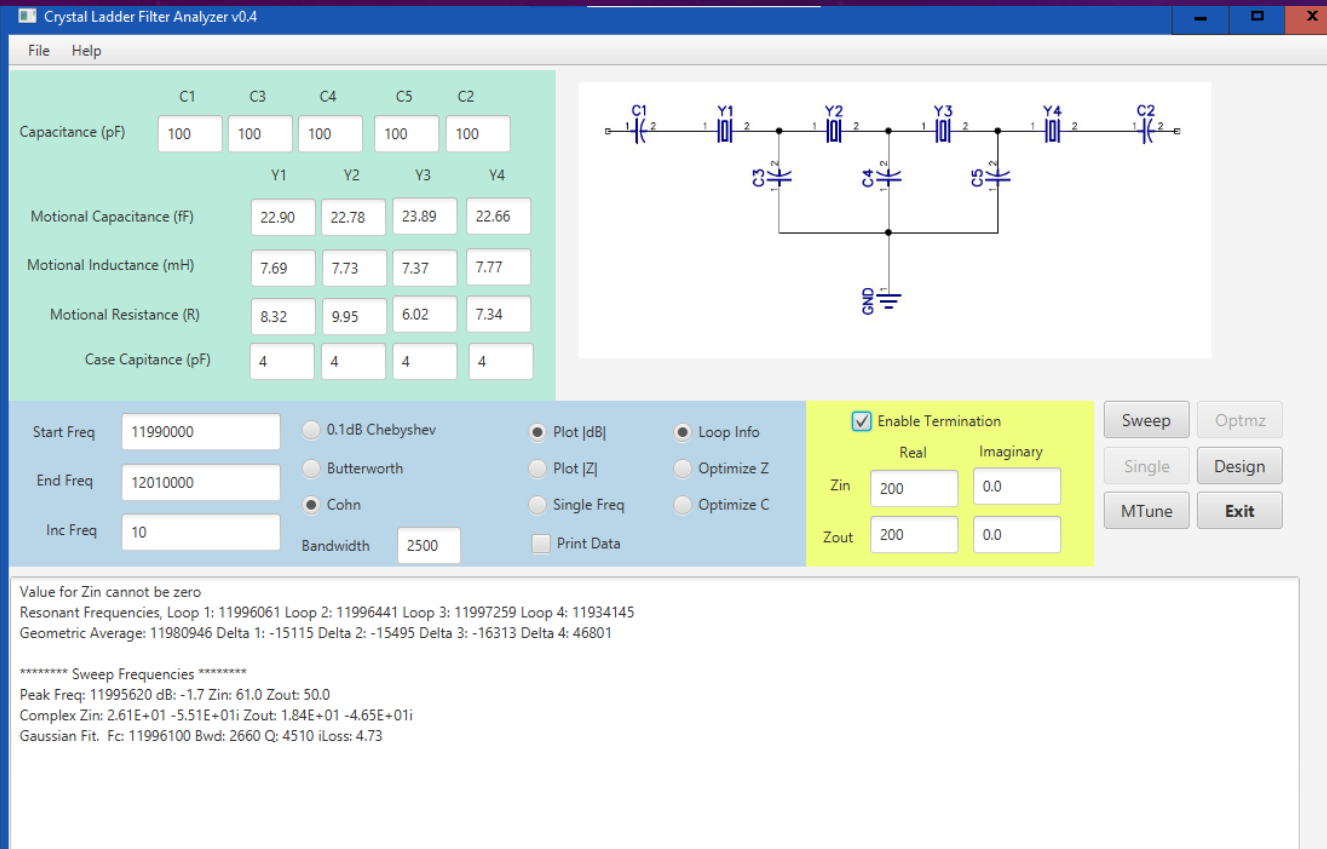


Unterminated

200R Terminated

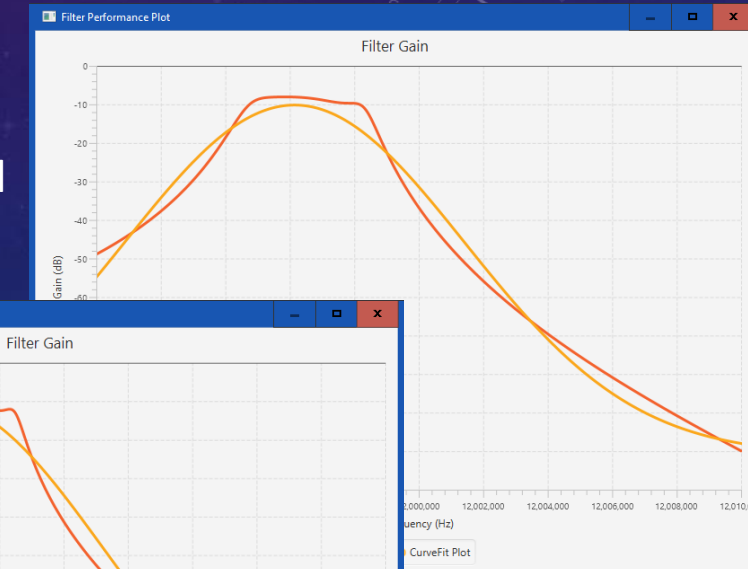







100R Terminated

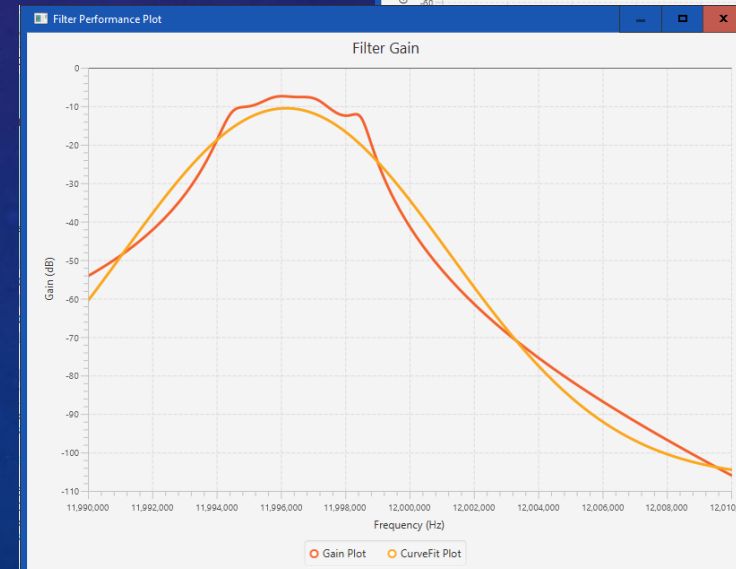

Filter Analysis Java Program written in circa 2018  
Used to fine tune Crystal Filter used in D612 Transceiver

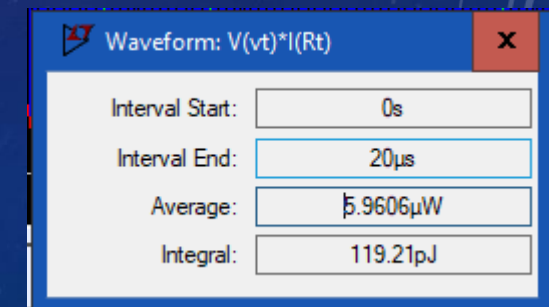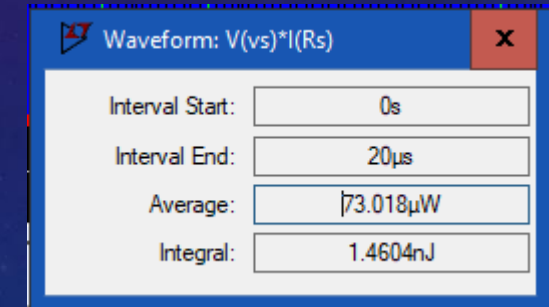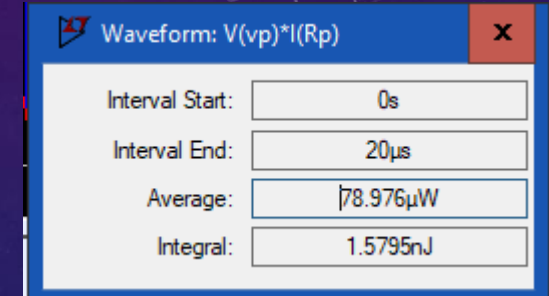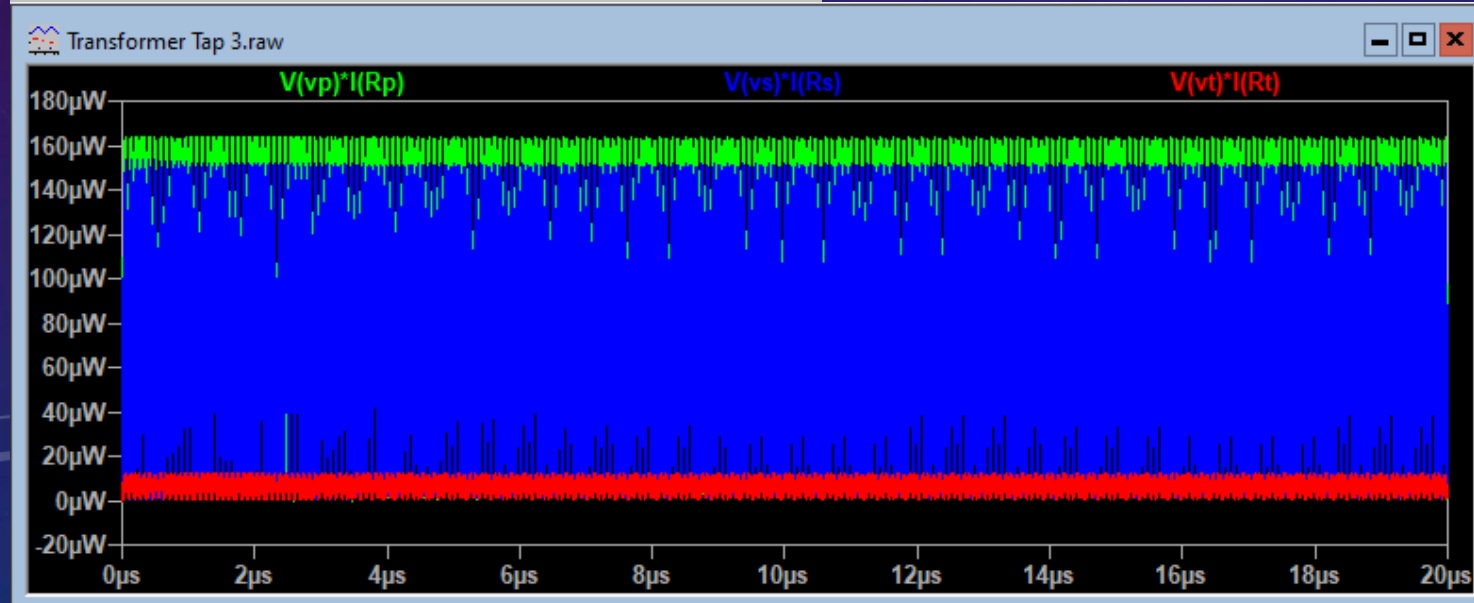
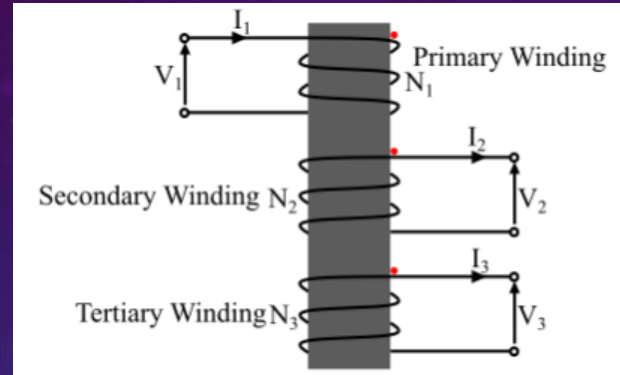
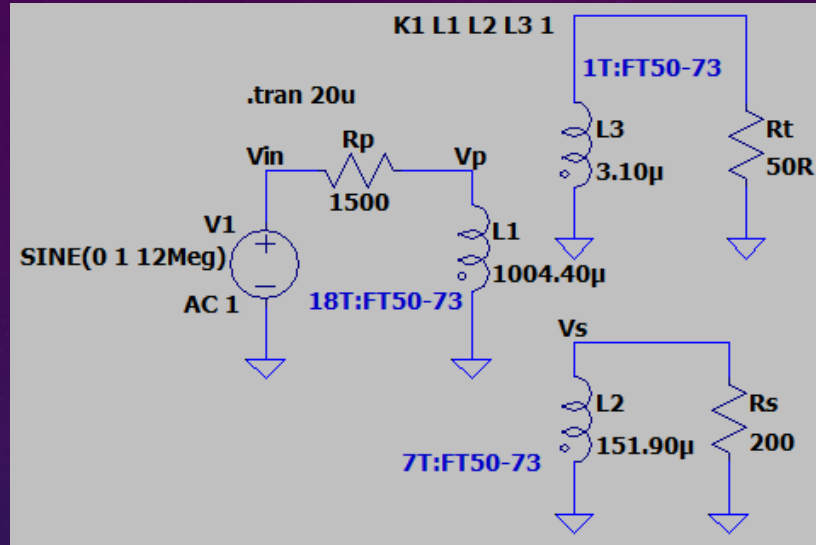
# ADDING 1 TURN TAP

COMPLEX Physics: Power Transfer – 1st Law of Thermodynamics


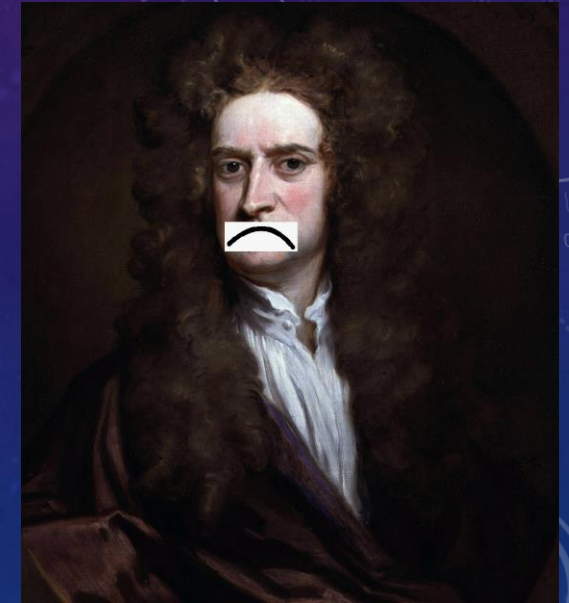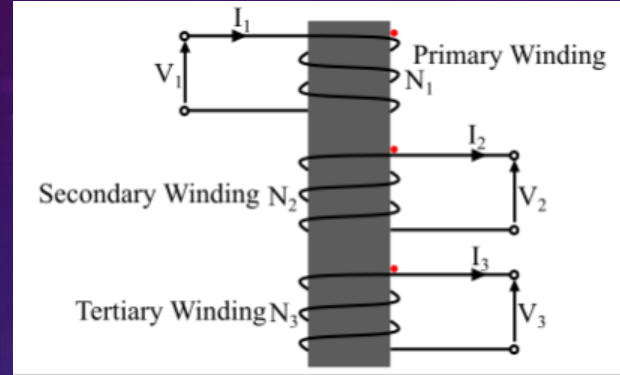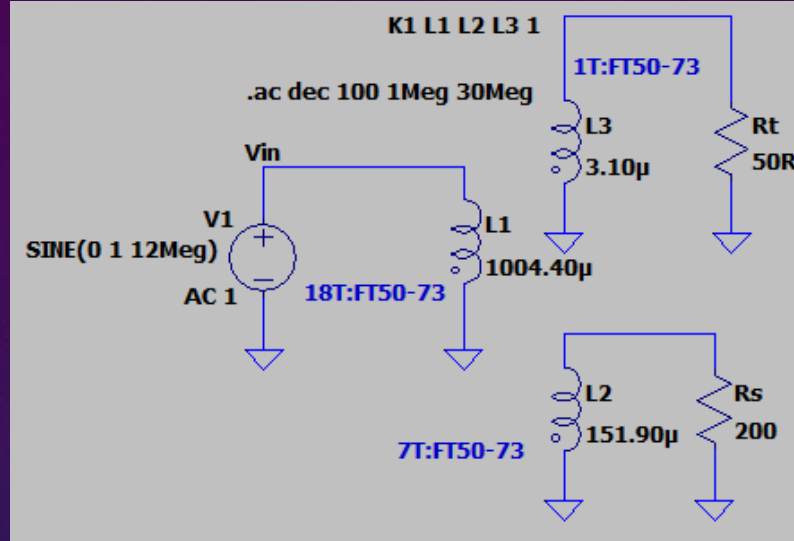
# ADDING 1 TURN TAP

COMPLEX Physics: Impedance Transformation



Cursor 1			
V(vin)/I(V1)			
Freq:	3.7048419MHz	Mag:	1.220973KΩ
		Phase:	-177.00639°
		Group Delay:	2.2414249ns
Cursor 2			
V(vin)/I(V1)			
Freq:	28.702669MHz	Mag:	1.2226137KΩ
		Phase:	-179.61322°
		Group Delay:	37.441139ps

Cursor 1			
V(vin)/I(V1)			
Freq:	3.7048419MHz	Mag:	207.27004Ω
		Phase:	-176.63933°
		Group Delay:	2.5150633ns
Cursor 2			
V(vin)/I(V1)			
Freq:	28.702669MHz	Mag:	207.62115Ω
		Phase:	-179.5657°
		Group Delay:	42.041823ps

Cursor 1			
V(vin)/I(V1)			
Freq:	3.7048419MHz	Mag:	2.1682178Ω
		Phase:	-178.27811°
		Group Delay:	1.2908131ns
Cursor 2			
V(vin)/I(V1)			
Freq:	28.702669MHz	Mag:	2.1691811Ω
		Phase:	-179.77765°
		Group Delay:	21.521953ps





Small impact on Mixer and Crystal Filter

SA or TG seeing 2R (Short Circuit!)



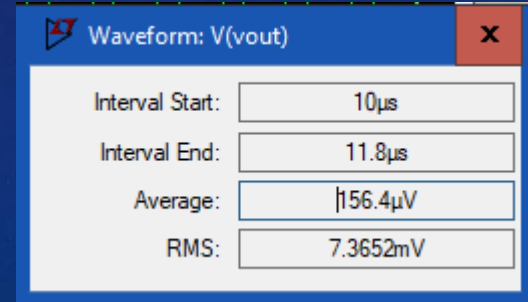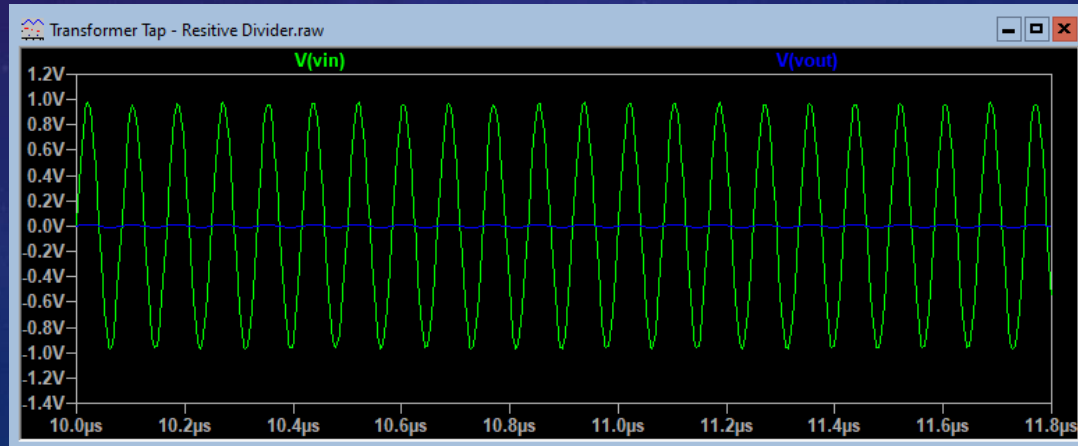
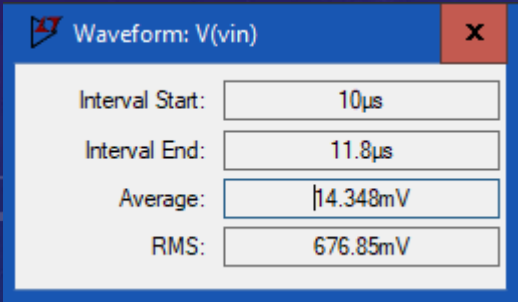
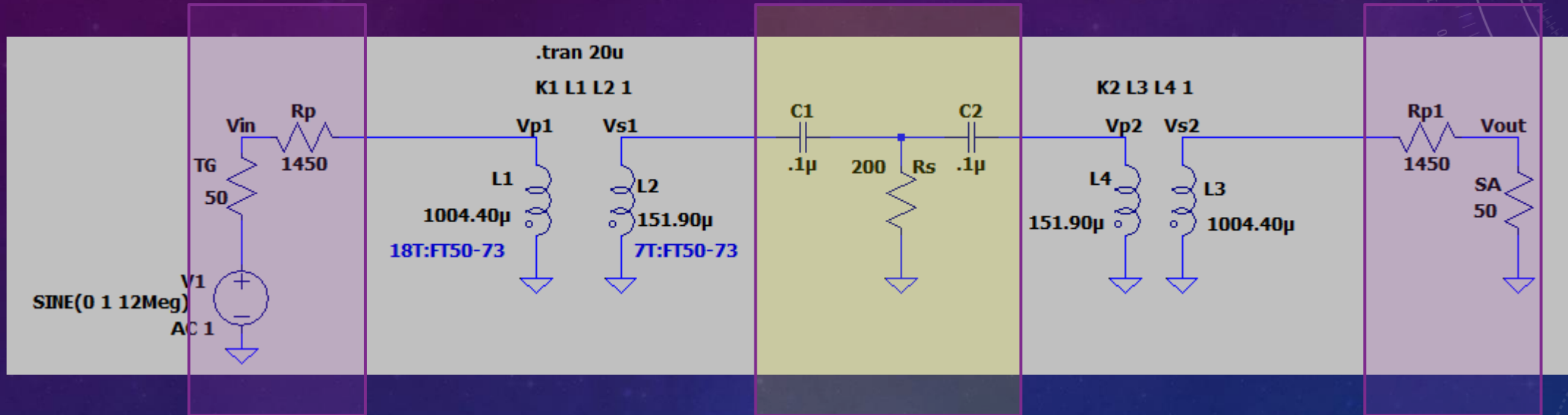
# SUGGESTION

- ✓ **Best Approach:** Best to use a 50R:1500R transformer or a 50R:200R transformer
- ✓ **Quick and Dirty Approach:** Maybe use resistive voltage divider to your advantage. Frequency independent.


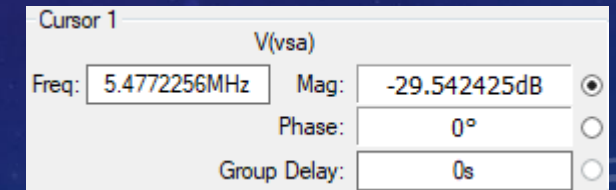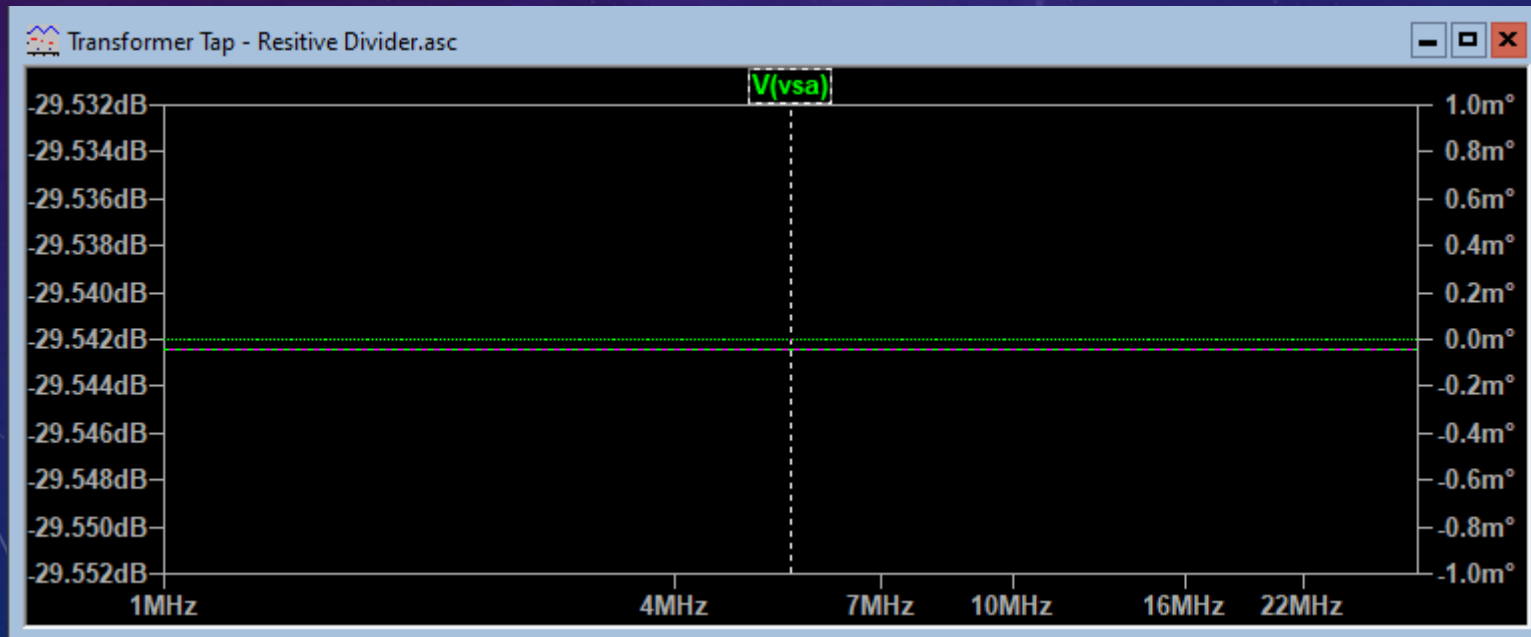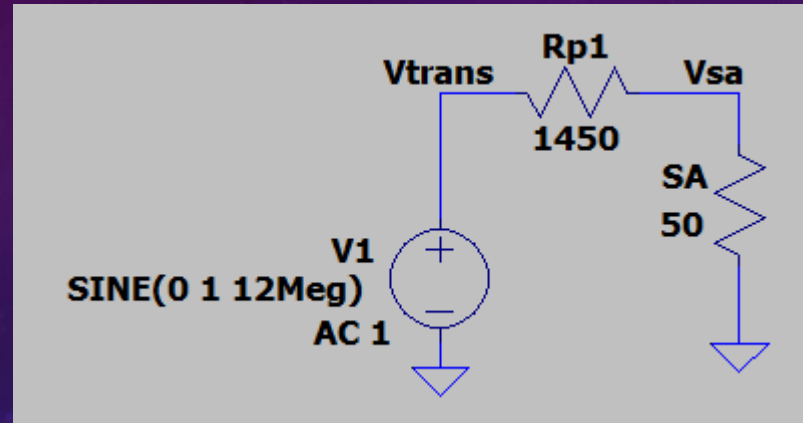
# SUGGESTION

- ✓ **Best Approach:** Best to use a 50R:1500R transformer or a 50R to 200R transformer
- ✓ **Quick and Dirty Approach:** Maybe use resistive voltage divider to you advantage. Frequency independent.



Act like a 29dB attenuator to SA

