



PARC HB

# OPAMPS SIMPLIFIED (with LTSpice)

Dave VE3OOI

Feb 2021


# **FOLLOW AND LEARN**

- 1. This is not a “traditional” tutorial**
- 2. Its “Hands-On”, experimental approach.**
- 3. Build experience using LTSpice**
- 4. Present a “Principal” then clarify with experiment with LTSpice**







# FUNDEMANNTALS

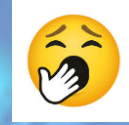

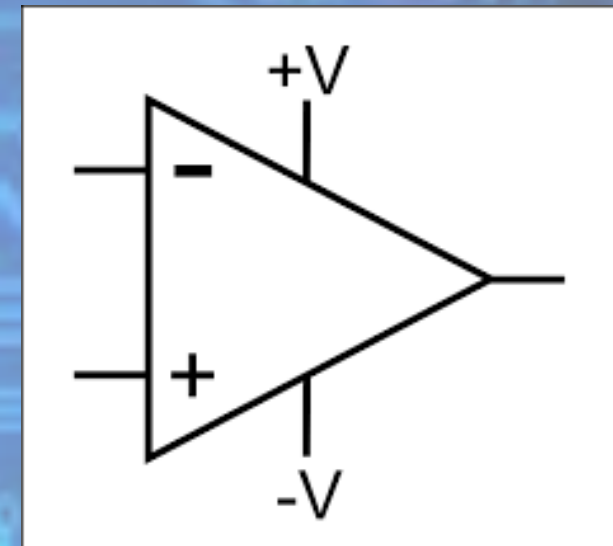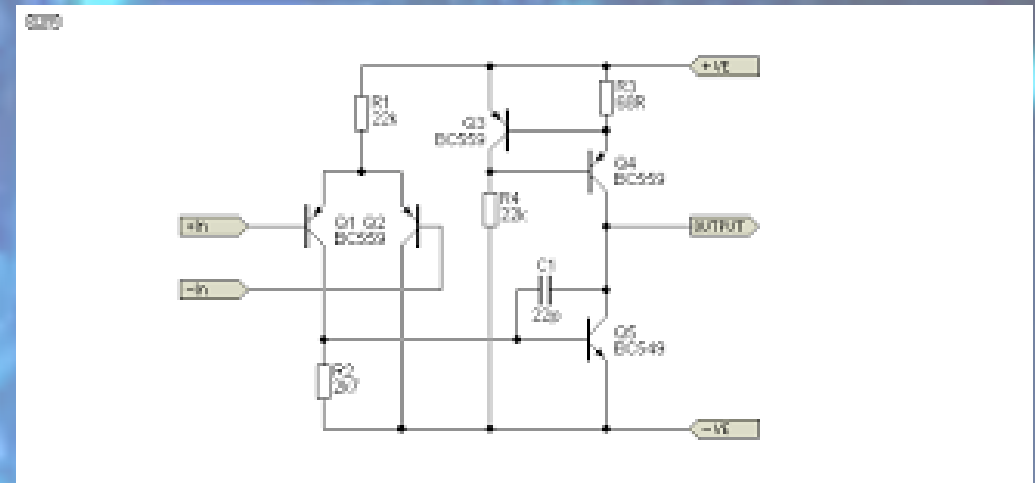1. Based on a bunch of transistors
2. Have 2 inputs + (non-inverting) and – (inverting)
3. Have Positive Supply (+V) and a Negative Supply (-V). Lets call this positive or negative voltage “**rails**”
4. Output is based on difference.
  - ✧ **Output is 0 if difference between inputs is 0**
  - ✧ **Generally, output a voltage between voltage rails based on difference of inputs**



# Principal 1: Input Offset Voltage

1. If voltage at + input is greater than - input, output is set to Positive Rail
2. If voltage at - input is greater than + input, output is set to Negative Rail
3. Real opamp has input offset due to mismatched parts and tolerances.
  - 0 voltage difference applied to both terminal does NOT produce 0 volts output
  - Typical offset between inputs to trigger output to hit Positive or Negative Rail

An ideal op-amp amplifies the differential input; if this input difference is 0 volts (i.e. both inputs are at the same voltage), the output should be zero. However, due to manufacturing process, the differential input transistors of real op-amps may not be exactly matched. This causes the output to be zero at a non-zero value of differential input, called the input offset voltage.





SYMBOL	PARAMETER	CONDITIONS	LT1013AM/AC LT1014AM/AC			LT1013C/D/I/M LT1014C/D/I/M			UNITS
			MIN	TYP	MAX	MIN	TYP	MAX	
V <sub>os</sub>	Input Offset Voltage	LT1013		40	150		60	300	μV
		LT1014		50	180		60	300	μV
		LT1013D/I, LT1014D/I					200	800	μV

LT1013 is replacement of LM358




# Experiment 1: Input Offset Voltage

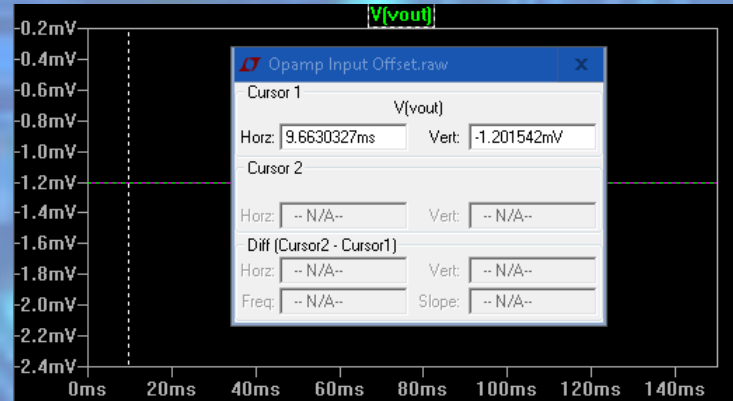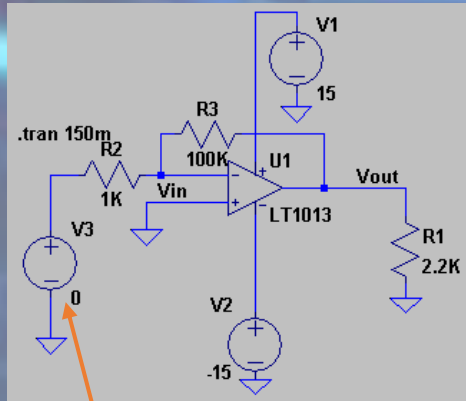





- 1.2mV at output. What input offset is needed?
  - For Gain = 100, input =  $1.201542/100 \text{ mV} = 12 \text{ uV}$
- An input offset of 12uV is needed to make output zero.
- This is a simulation. Data sheet says typically 40 – 150 uV and due to MANUFACTURING.

Offset set to -12.0156µV

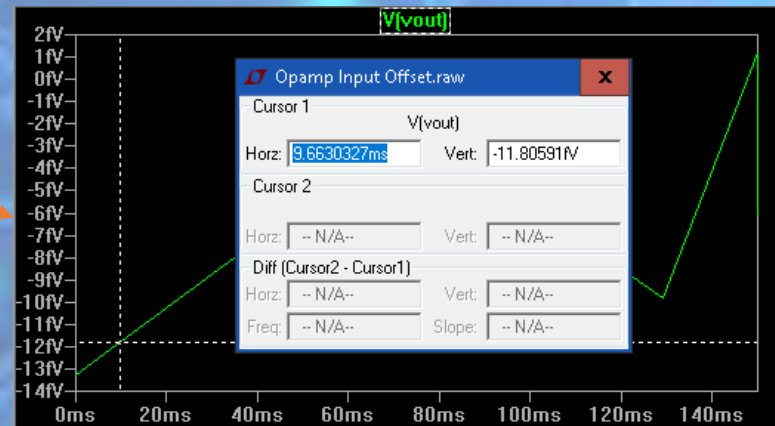

SYMBOL	PARAMETER	CONDITIONS	LT1013AM/AC LT1014AM/AC			LT1013C/D/I/M LT1014C/D/I/M			UNITS
			MIN	TYP	MAX	MIN	TYP	MAX	
Vos	Input Offset Voltage	LT1013		40	150	60	300		µV
		LT1014		50	180	60	300		µV
		LT1013D/I, LT1014D/I				200	800		µV

# Experiment 2: Input “Offset” Voltage

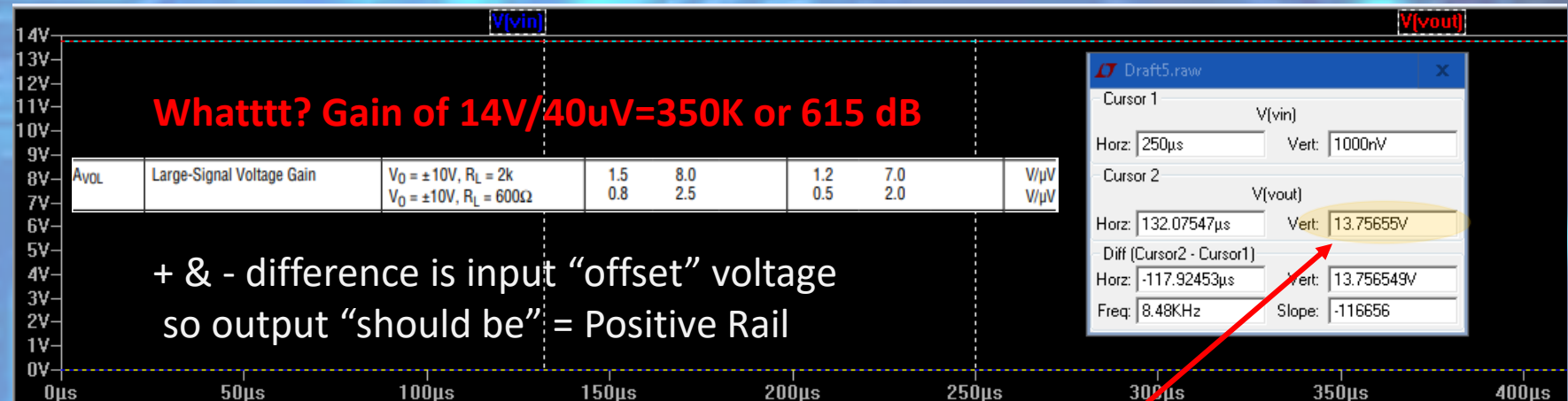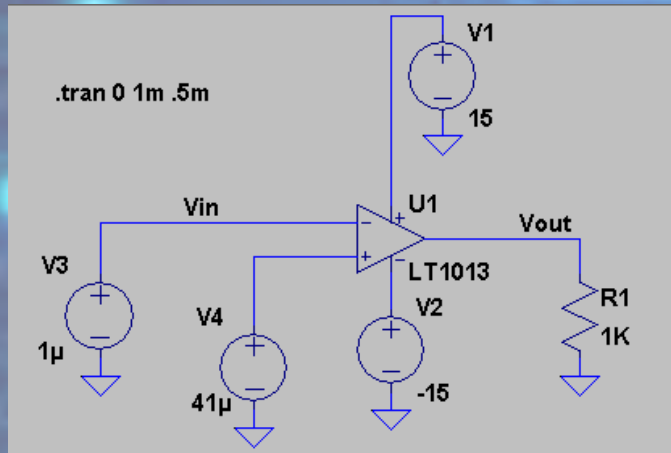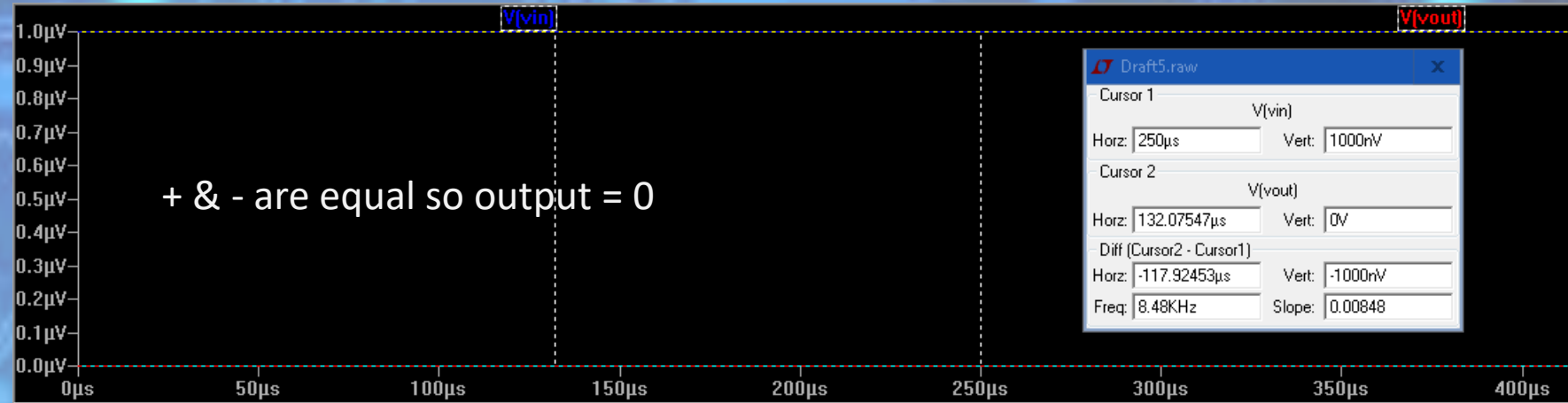
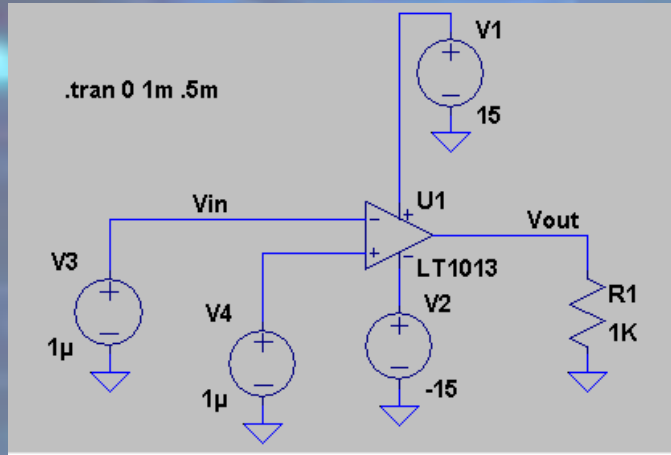


## HOMEWORK:


1. Vary the input. Is it linear between 0-40μV?
2. What happens if you ground the negative supply?

Huh?
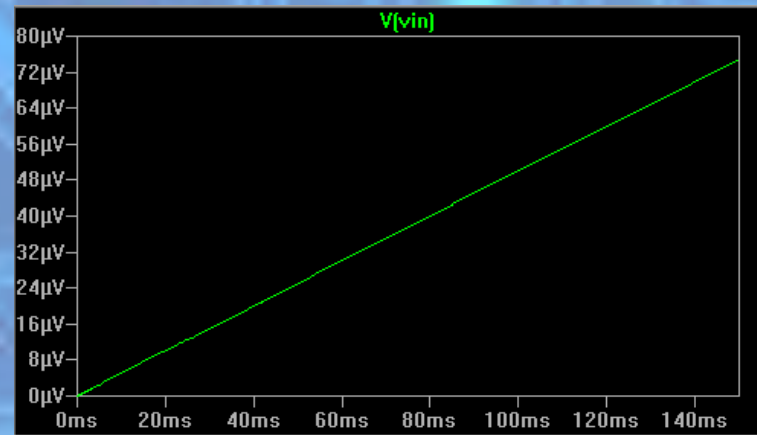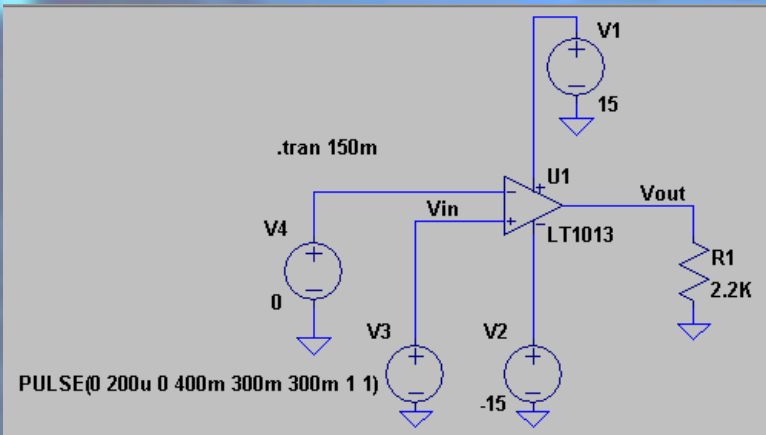
# Experiment 3: Alternate View of “Offset”



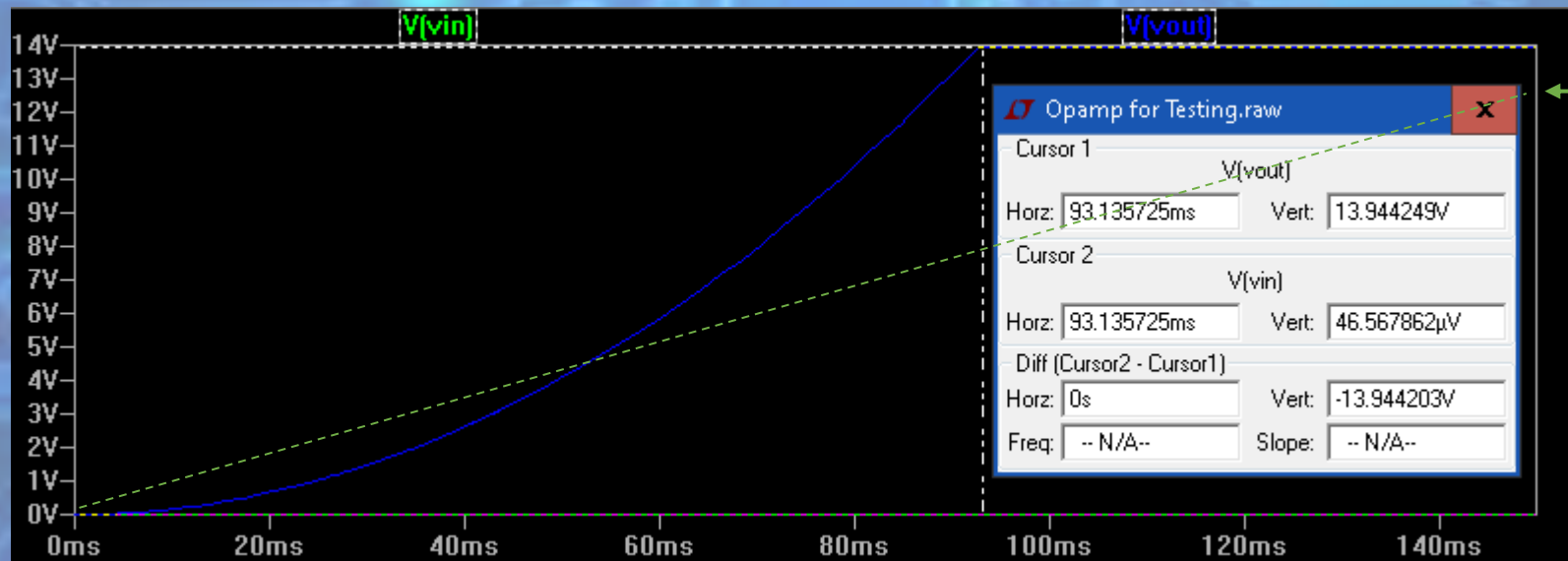Opamp **DOES NOT** set output to positive or negative rail with a small offset. Huh?



75uV

CONDITIONS	LT1013AM/AC LT1014AM/AC		
	MIN	TYP	MAX
LT1013		40	150
LT1014		50	180
LT1013D/I, LT1014D/I			

# LTSPICE MINUTE: PULSE SOURCE

**Independent Voltage Source - V4**

Functions

- ☐ (none)
- ☒ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- ☐ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- ☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- ☐ SFFM(Voff Vamp Fcar MDI Fsig)
- ☐ PWL(t1 v1 t2 v2...)
- ☐ PWL FILE:

Initial[V]:   
Von[V]:   
Tdelay[s]:   
Trise[s]:   
Tfall[s]:   
Ton[s]:   
Tperiod[s]:   
Ncycles:

Make this information visible on schematic: ☒

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(AC)


AC Amplitude:   
AC Phase:

Make this information visible on schematic: ☒

Parasitic Properties

Series Resistance[Ω]:   
Parallel Capacitance[F]:

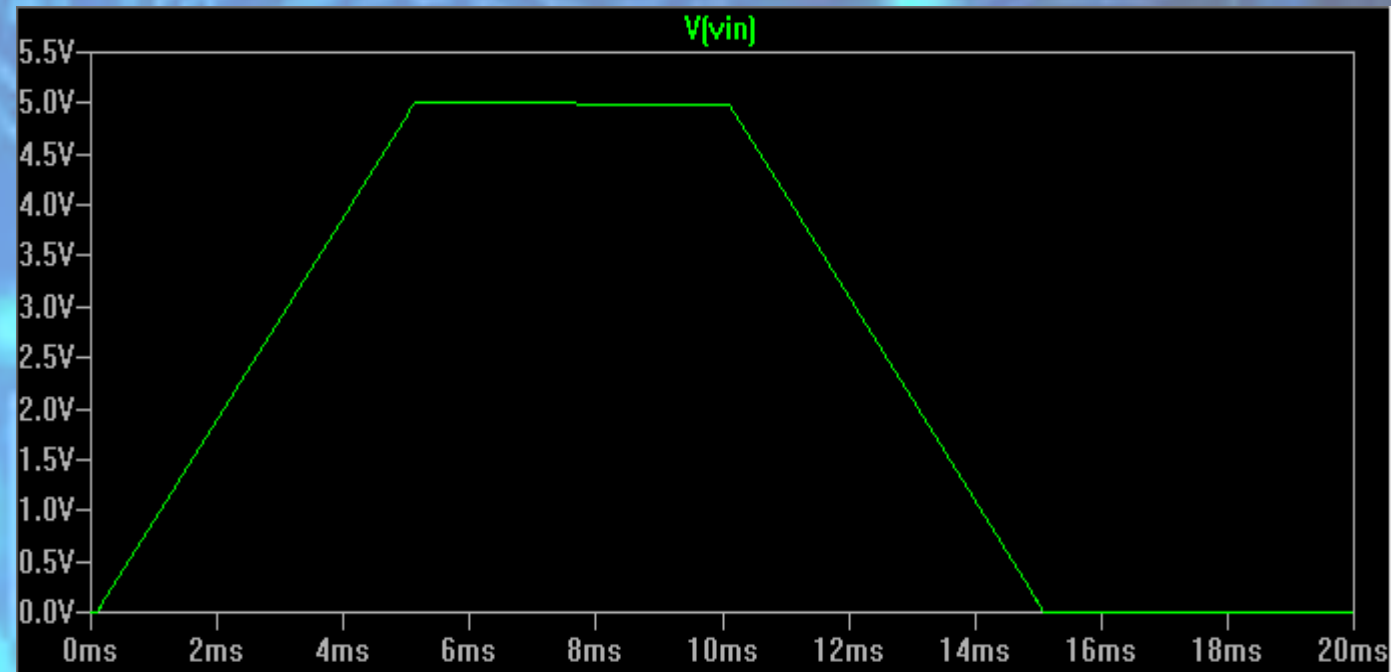Make this information visible on schematic: ☒





# Rail to Rail

$V_{OUT}$	Output Voltage Swing	$R_L = 2k$	$\pm 13$	$\pm 14$	$\pm 12.5$	$\pm 14$	V
-----------	----------------------	------------	----------	----------	------------	----------	---



- 1. Many opamps don't swing to the voltage rails. This reduces the useful limit of an opamp. BEWARE!!**
- 2. Opamps that swing to both rails are called “rail-to-rail” opamps**

## FINDING 1:

- Opamps have a HUGE gain!
- Small input voltage can create output close to or equal to rail voltage
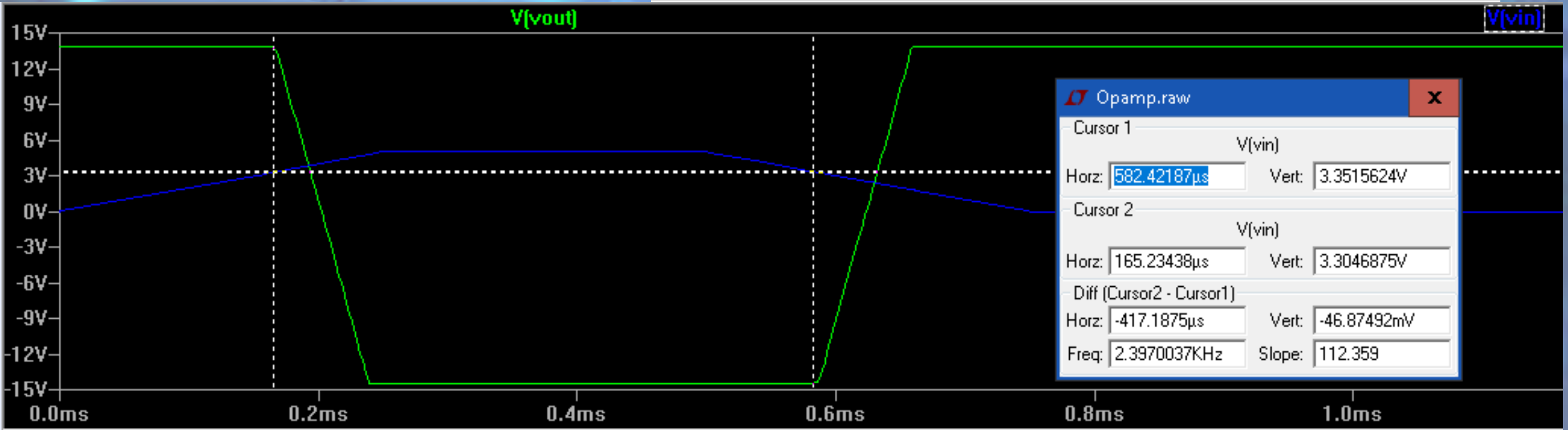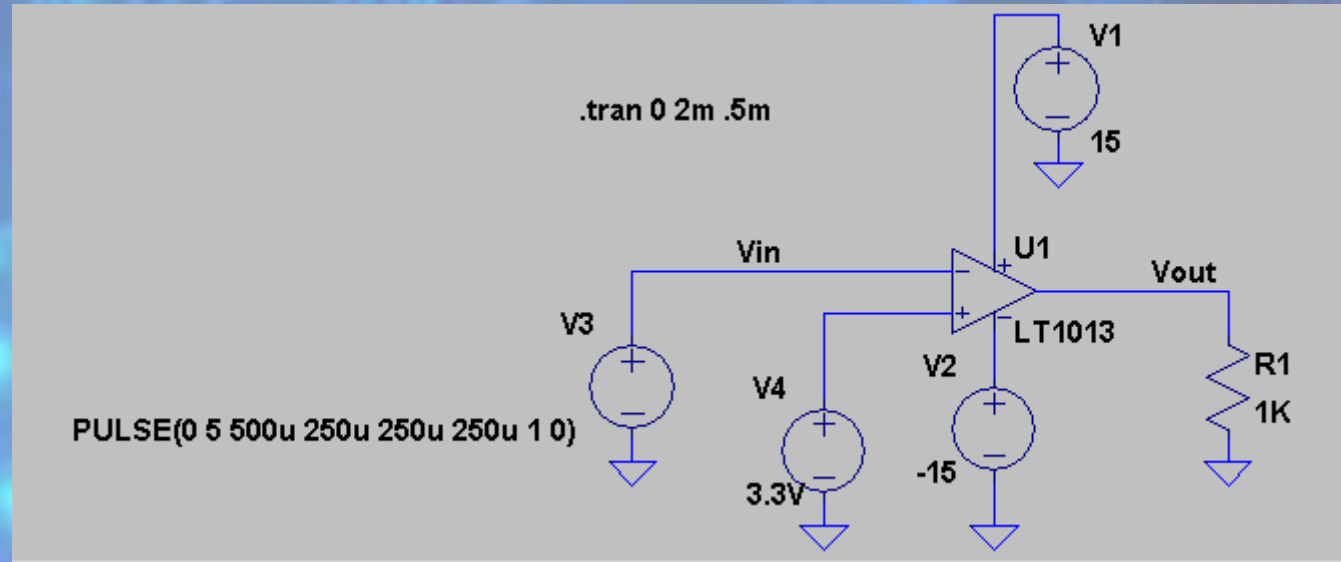
# Experiment 4: Comparator


Can be used to identify when a voltage is below, at or above a reference voltage



# Principal 2: Input Bias Current

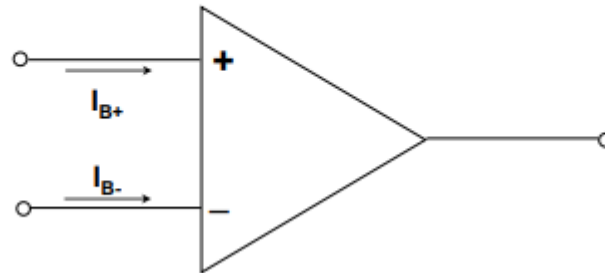1. Ideal Opamps have a infinite input impedance
2. Ideal Opamps should therefore have NO current should flow at inputs

Ideally, no current flows into the input terminals of an op amp. In practice, there are always two *input bias currents*,  $I_{B+}$  and  $I_{B-}$ . (see Figure 1).



$I_B$	Input Bias Current		12	20	15	30	nA
	Input Resistance – Differential Common Mode	(Note 2)	100 5	400 5	70 4	300 4	MΩ GΩ


- Differential Mode: Input voltages relative to each other. Voltage different at terminals
- Common Mode: Input voltages relative to ground. Same voltage at inputs

**Note 2:** This parameter is guaranteed by design and is not tested.





# Experiment 5: Input Bias Current

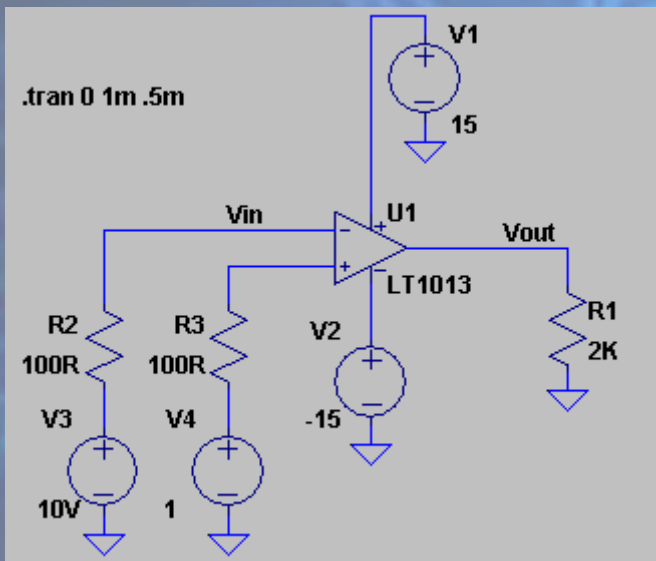


$I_B$	Input Bias Current	12	20	15	30	nA
-------	--------------------	----	----	----	----	----

## FINDING 2:


- Opamps consume negligible amount of current at input – this makes math EASY!!

# Experiment 6: Output Current

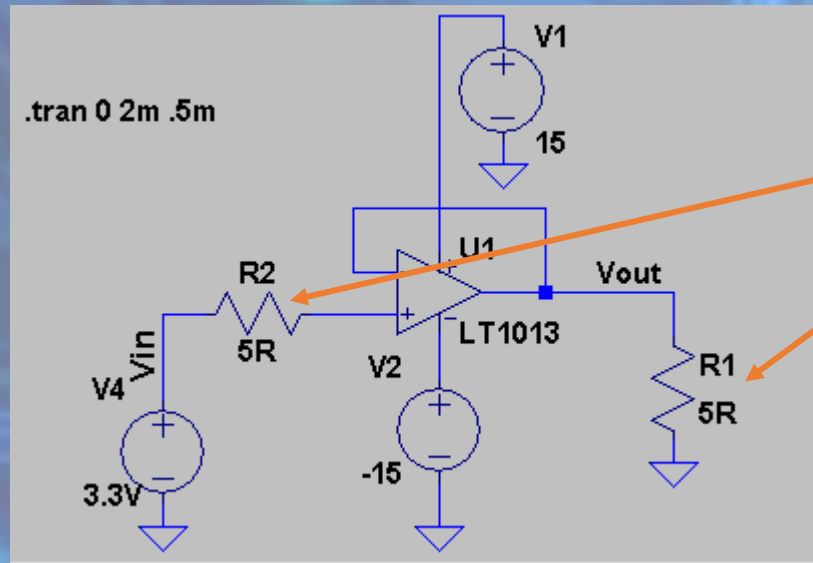



Use 2 current sensing resistors to measure input and output current.

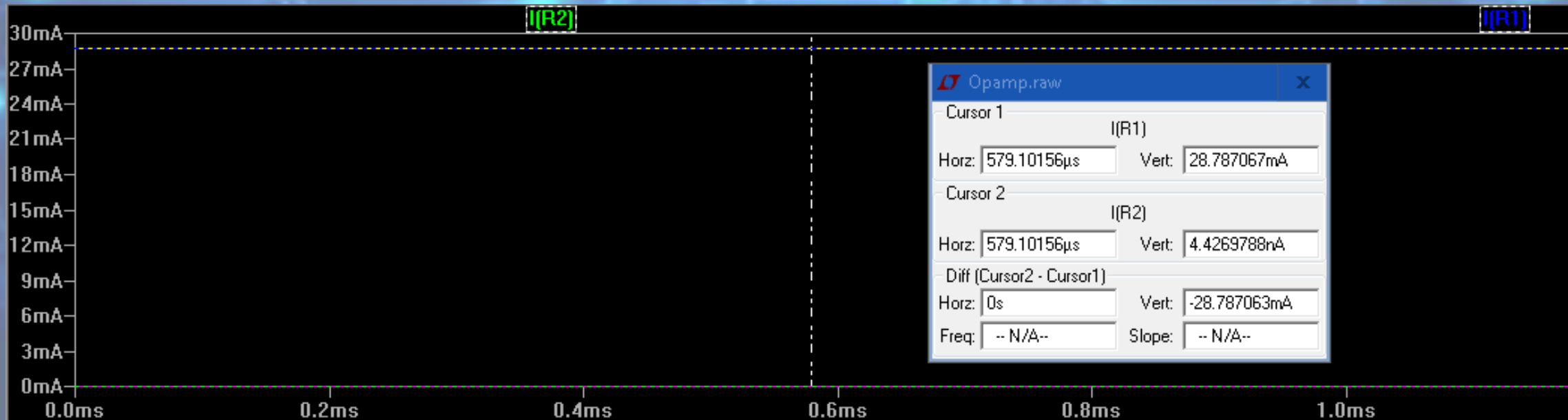**FINDING 4: Opamps can have huge current gain!**


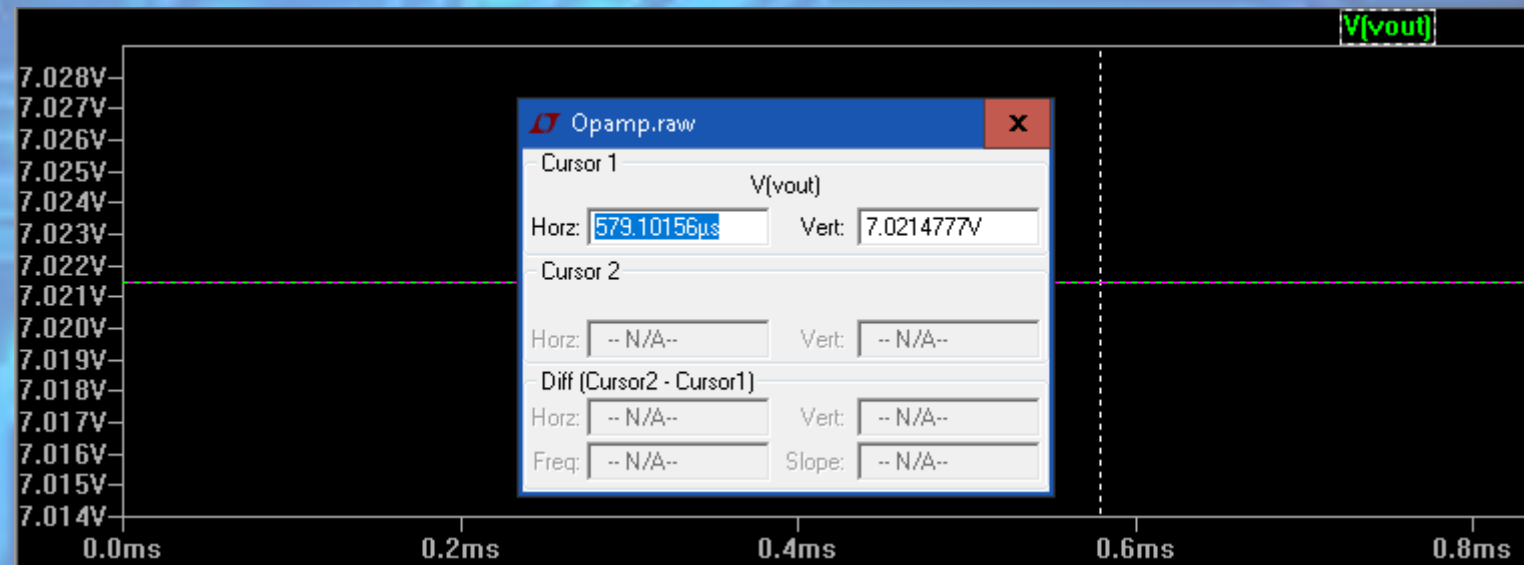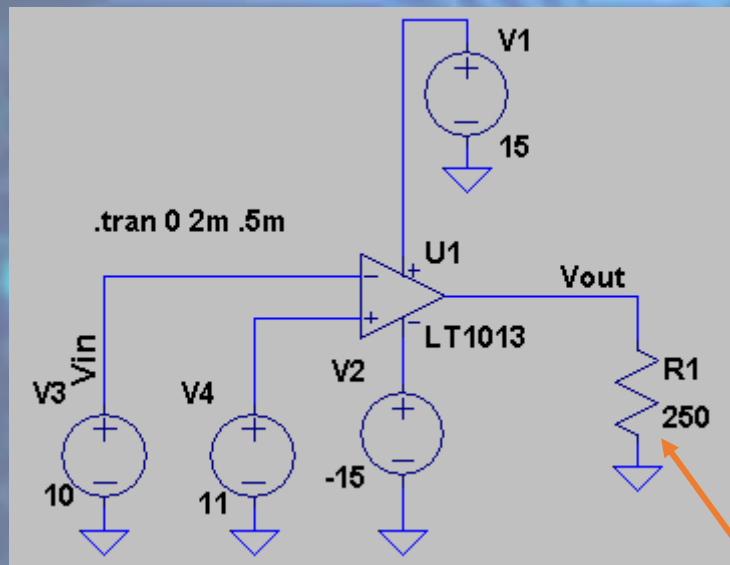
# Experiment 7: Output Impedance

The overall op amp circuit output impedance is normally low and usually purely resistive. However aspects like the drive capability of the op amp need to be carefully considered as most chips have a very limited capability as they are not expected to drive large loads. Where large loads and high currents are needed, additional components can be added to provide the additional capability, or high power op amp chips can be used.




Change load resistor until you get ½ of maximum output (Rail voltage ~ 14V)




# Principal 2: Negative Feedback

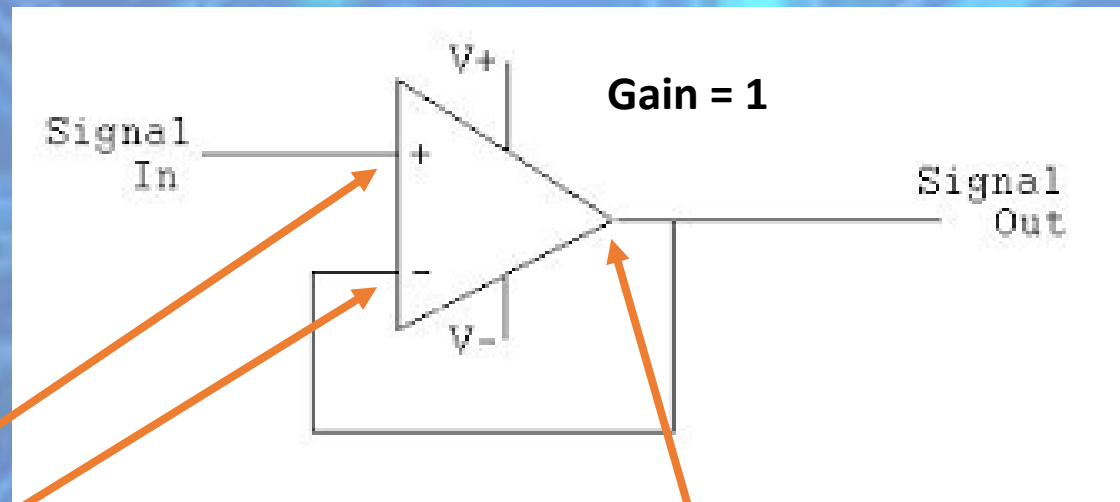1. Can use negative feedback to control the gain.
2. With feedback, the opamp alters output so that input offset is between (+) and (-) input are the same




If (+) > (-), output raises to positive rail. Once output is within "Input Offset Voltage" of (+), then output = (+)


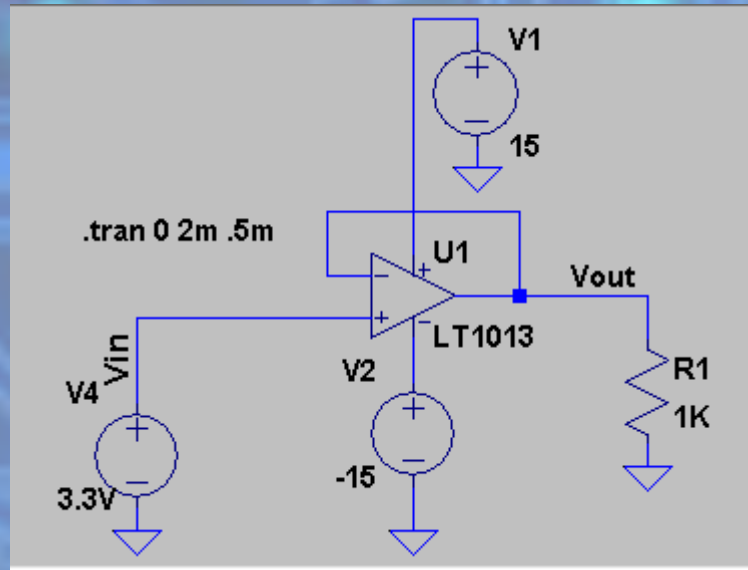
# Experiment 8: DC Voltage Follower or Buffer



SYMBOL	PARAMETER	CONDITIONS	LT1013AM/AC LT1014AM/AC			LT1013C/D/I/M LT1014C/D/I/M			UNITS
			MIN	TYP	MAX	MIN	TYP	MAX	
Vos	Input Offset Voltage	LT1013		40	150		60	300	$\mu\text{V}$
		LT1014		50	180		60	300	$\mu\text{V}$
		LT1013D/I, LT1014D/I					200	800	$\mu\text{V}$

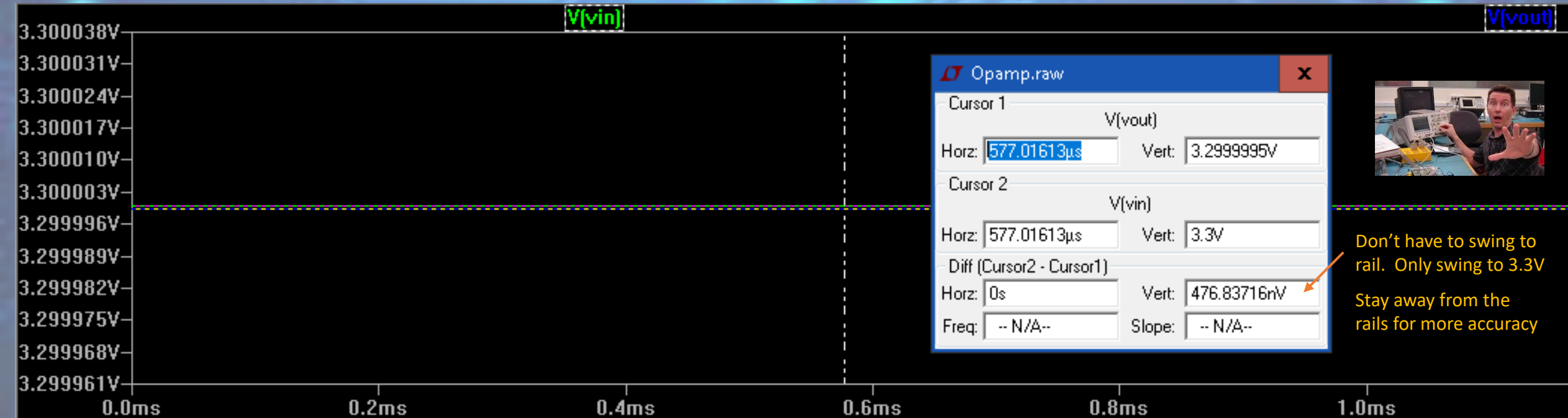

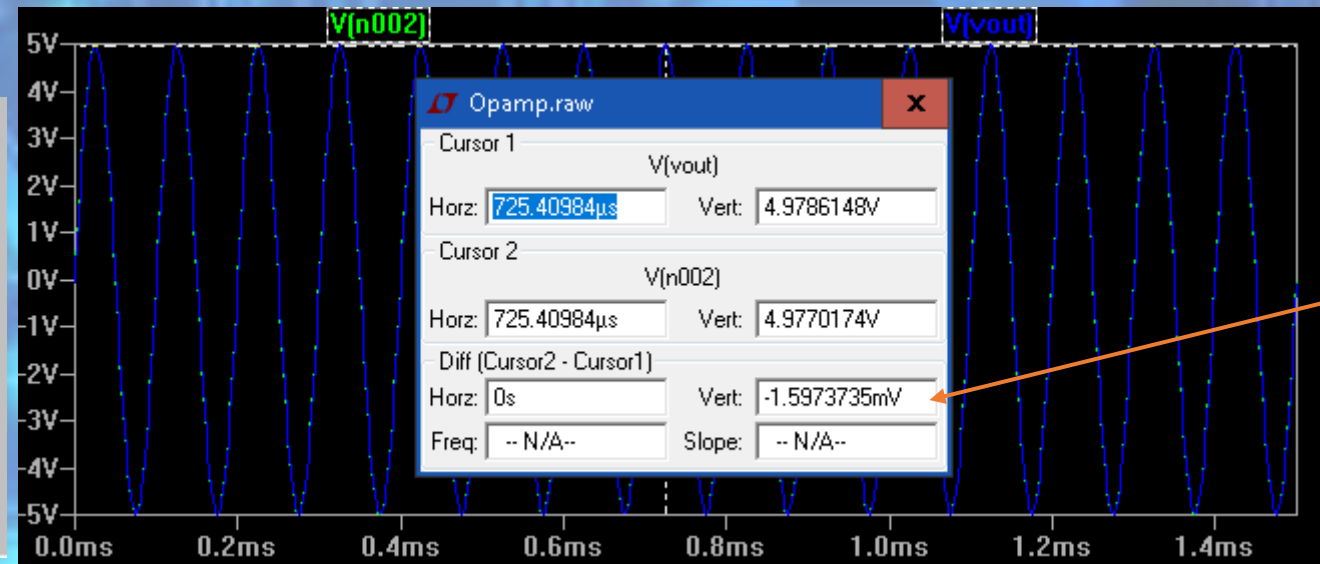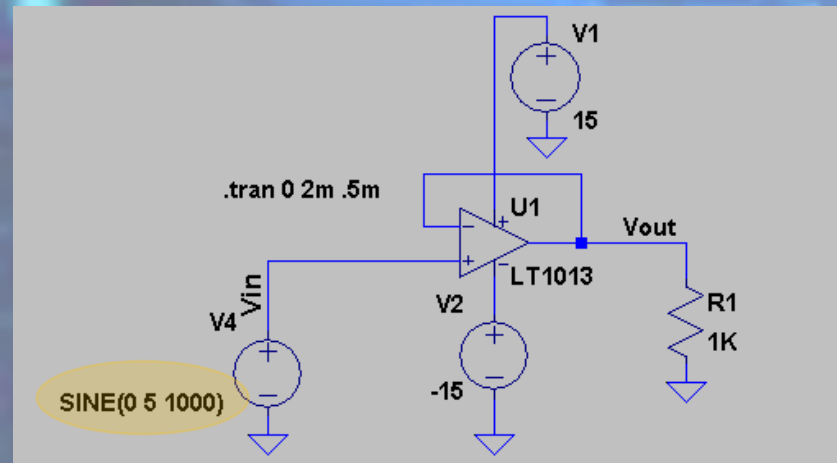
# Experiment 9: AC Voltage Follower or Buffer



Don't have to swing to rail. Only swing to 5V  
Difference larger for 5V than 3.3V. Slew Rate?

## HOMEWORK:

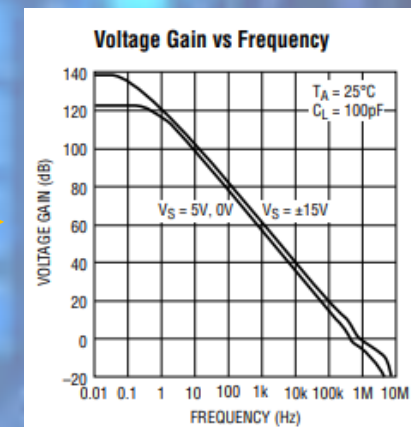1. Create a voltage follower with a low frequency AC
2. Increase frequency and what happens to output when frequency is above 20 KHz?




$$\text{Slew rate} = 2 \pi f V$$



# Principal 3: Gain and Negative Feedback
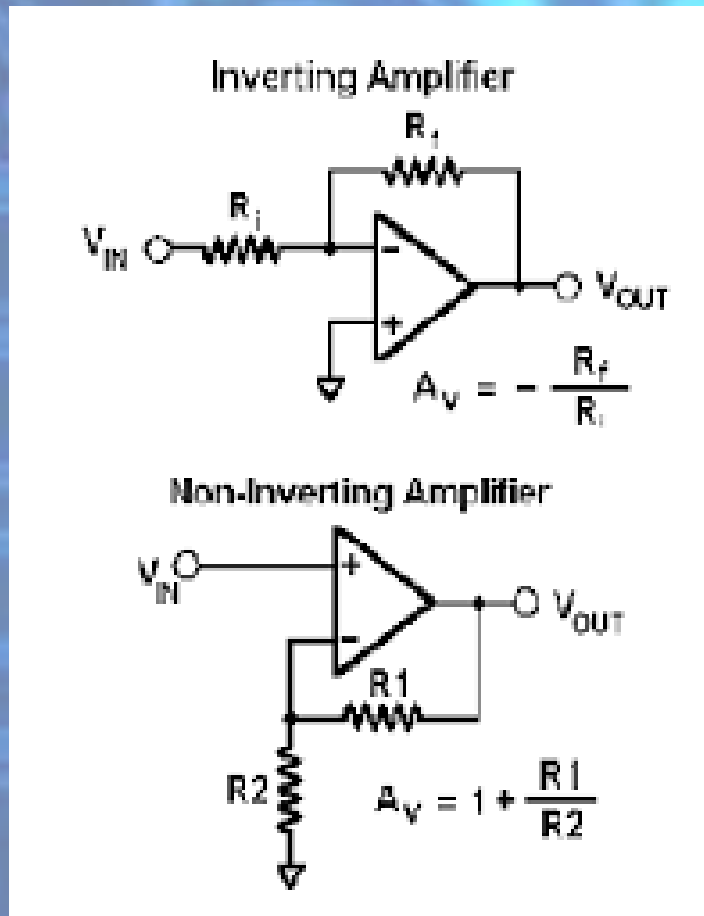
## 1. Feedback can be used to create gain for an inverting configuration or a non inverting configuration





**With feedback, the opamp alters output so that input offset is between (+) and (-) input are the same**

**Use a voltage divider to feedback a fraction of the output voltage**

**Caveat emptor: Opamp may have low noise. Resistors add noise (thermal). Choose them wisely**

# Experiment 10: Inverting Amplifier

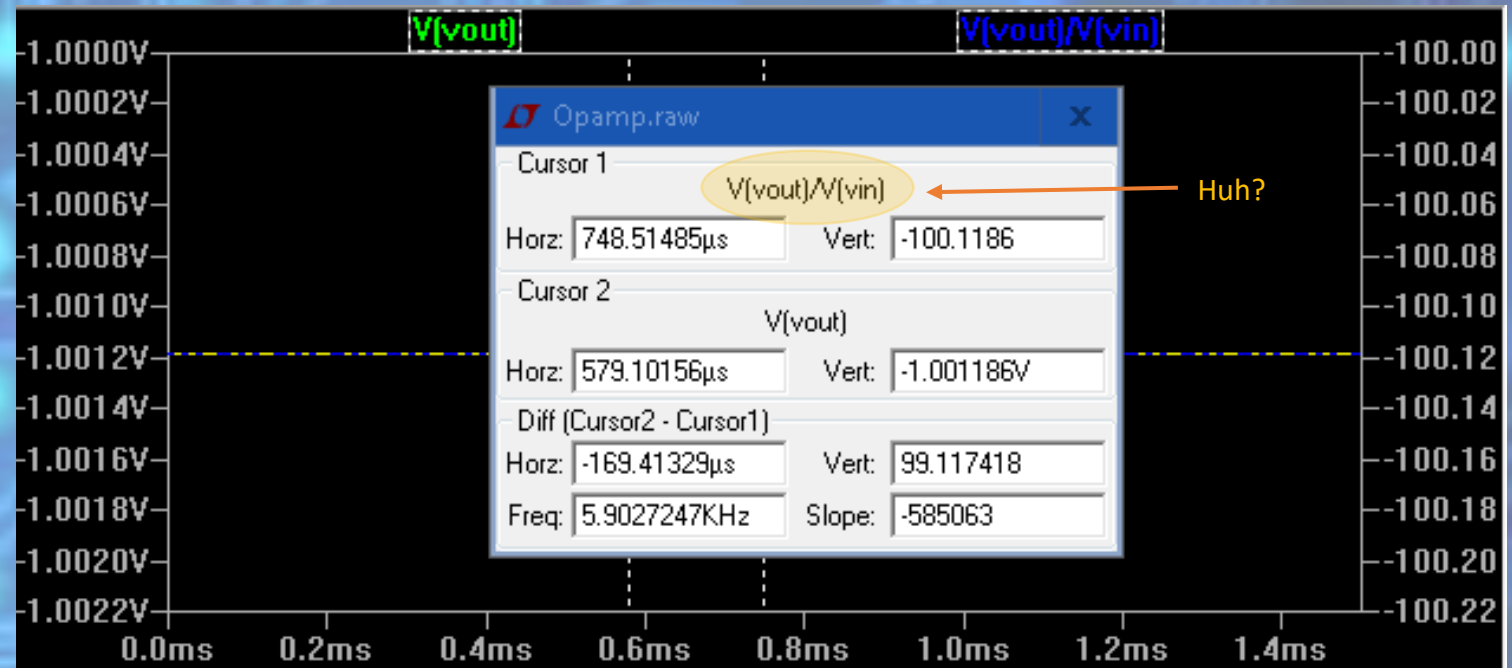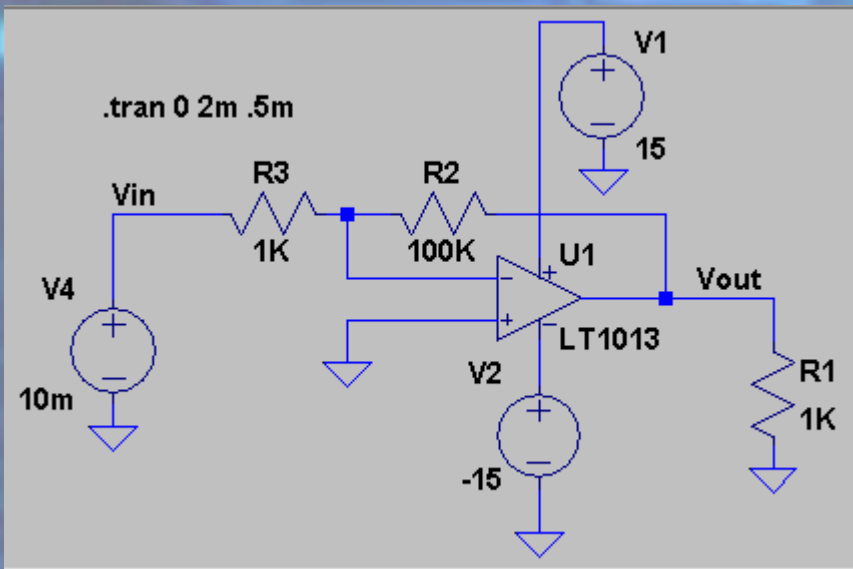

- Inverting Gain =  $-R2/R1 = -100K/1K = 100$
- For 10mV input, output should be  $-10mV \times 100 = -1V$

## HOMEWORK:

1. Change input voltage. At what point does the voltage clip (i.e., hit the negative rail)
2. Change  $R2$  and  $R3$ . What is the max gain you can get.
3. Introduce a small AC signal and see if gain is the same as DC gain

# LTSPICE MINUTE: TRACE CALCULATION

	Zoom Area	Ctrl+Z
	Zoom Back	Ctrl+B
	Zoom to Fit	Ctrl+E
	Pan	
	Autorange Y-axis	Ctrl+Y
	Manual Limits	
	Aut-ranging	
<b>Visible Traces</b>		
	Add Trace	Ctrl+A
	Delete Traces	F5
	Select Steps	
<b>Add Plot Pane</b>		
	Delete this Pane	
	Sync. Horiz. Axes	
<b>Marching Waveforms</b>		
Grid		
	Reset Colors	
	Mark Data Points	
Eye Diagram		
View		

Add Traces to Plot


☒ Asterisks match colons

Available data:

V(vin)	Ix(U1:OUT)
V(vout)	Ix(U1:V+)
V(n001)	Ix(U1:V-)
V(n002)	
V(n003)	
V(n004)	
I(R1)	
I(R2)	
I(R3)	
I(V1)	
I(V2)	
I(V4)	
time	
Ix(U1:In+)	
Ix(U1:In-)	

Expression(s) to add:

☒ AutoRange


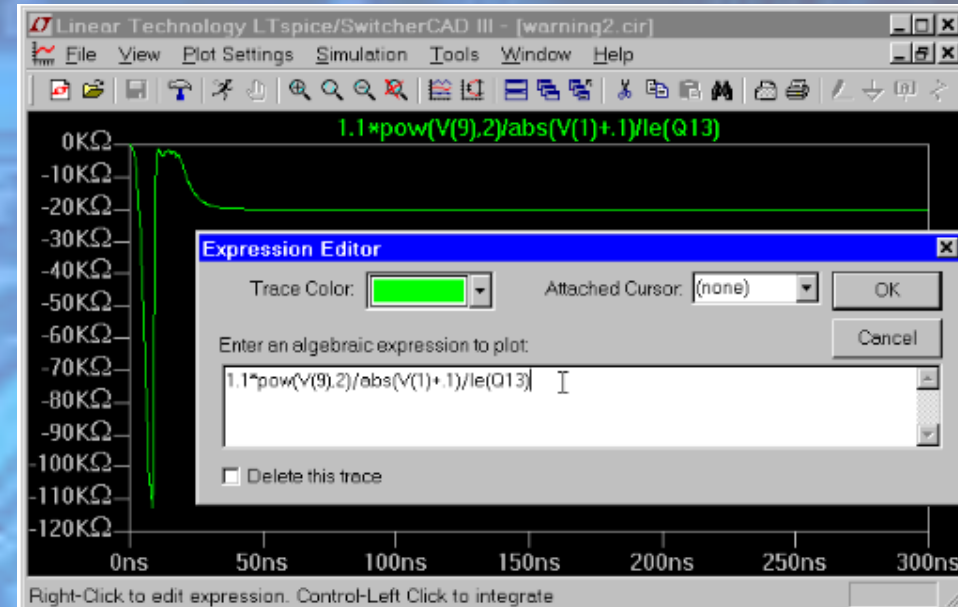


Operand	Description
&	Convert the expressions to either side to Boolean, then AND.
	Convert the expressions to either side to Boolean, then OR.
^	Convert the expressions to either side to Boolean, then XOR.
>	TRUE if expression on the left is greater than the expression on the right, otherwise FALSE.

Function Name	Description
abs(x)	Absolute value of x
acos(x)	Arc cosine of x
arccos(x)	Synonym for acos()
acosh(x)	Arc hyperbolic cosine
asin(x)	Arc sine
arcsin(x)	Synonym for sin()
asinh(x)	Arc hyperbolic sine
atan(x)	Arc tangent of x



# Experiment 11: Non-Inverting Amplifier


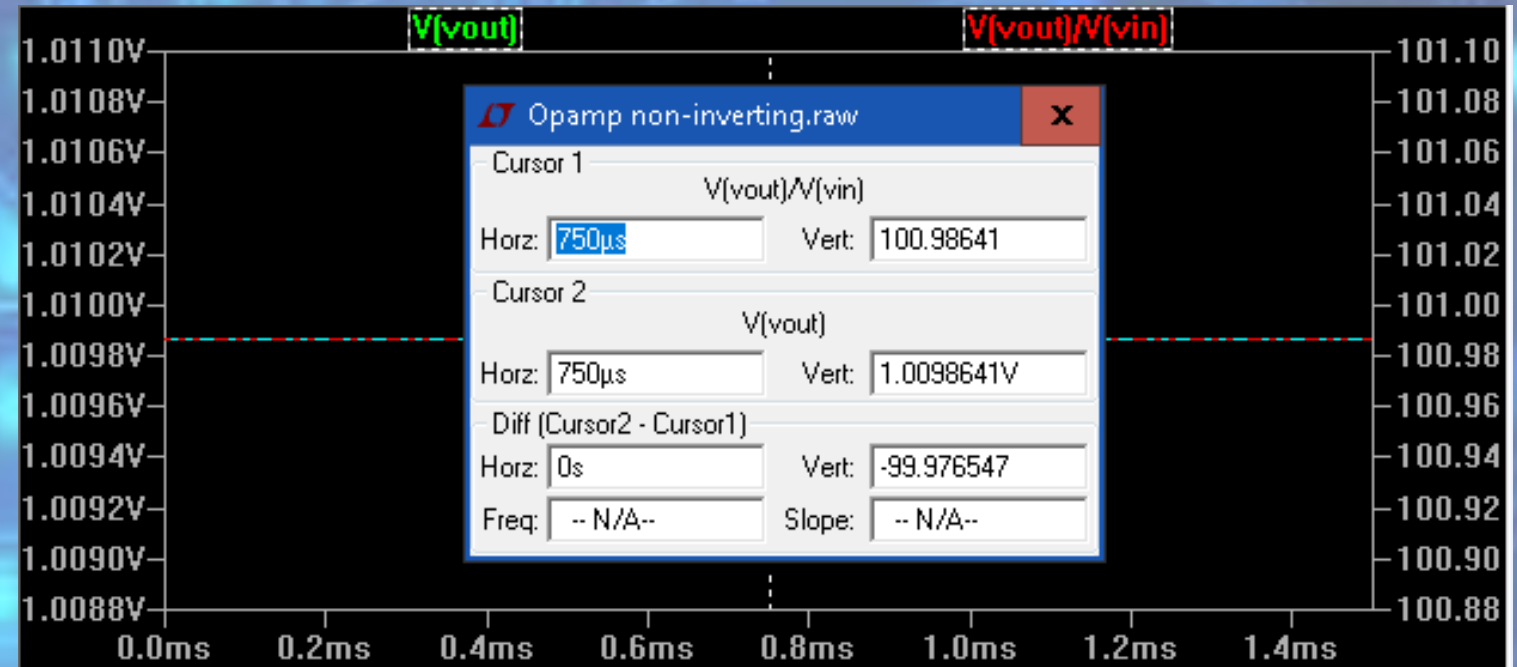
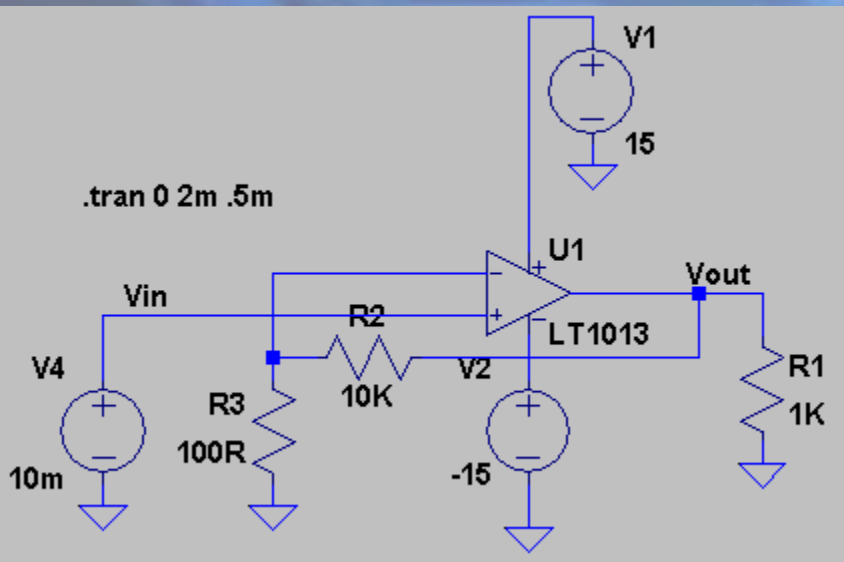


- Non-Inverting Gain =  $1 + R2/R1 = 1 + 10K/100 = 101$
- For 10mV input, output should be  $10m \times 101 = +1.01V$




## HOMEWORK:

1. Same as inverting amplifier
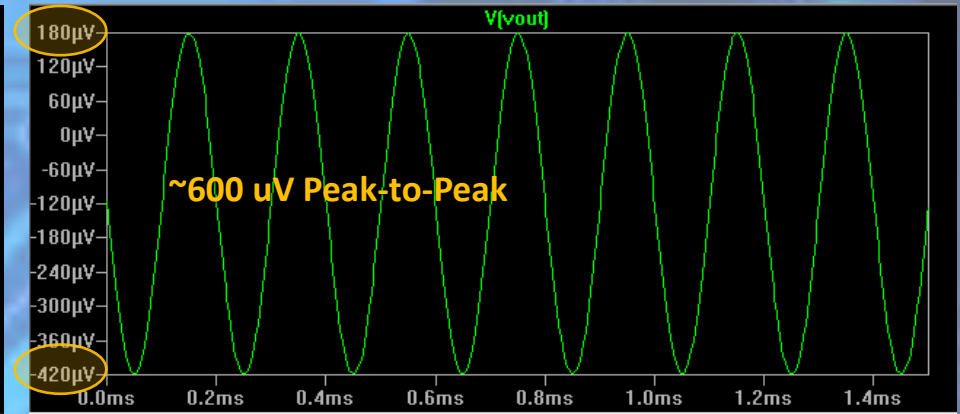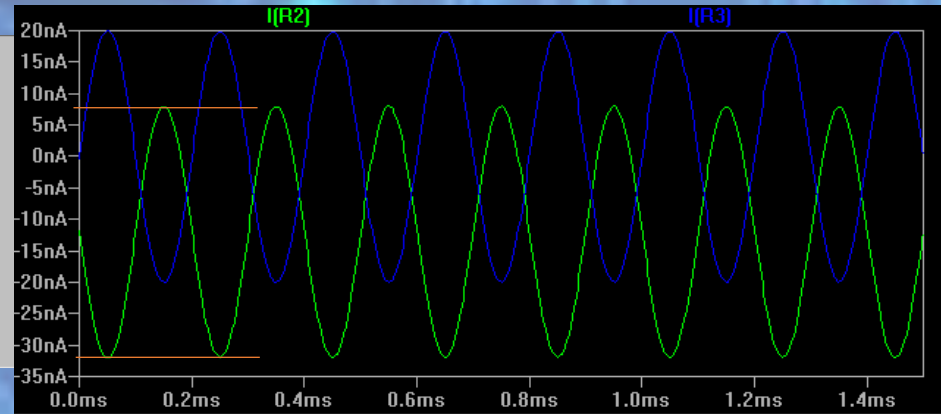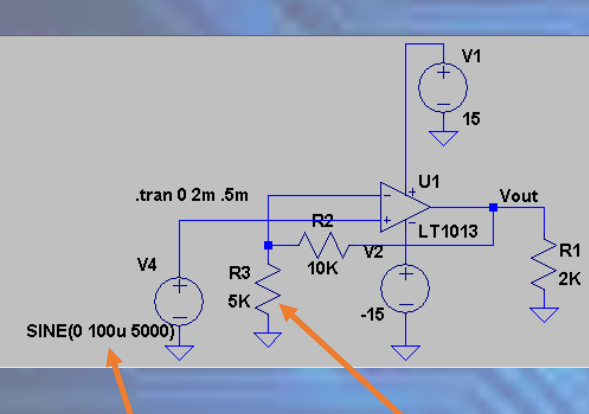
# Finding 4: Current Sink Will f\*\*\* you up!



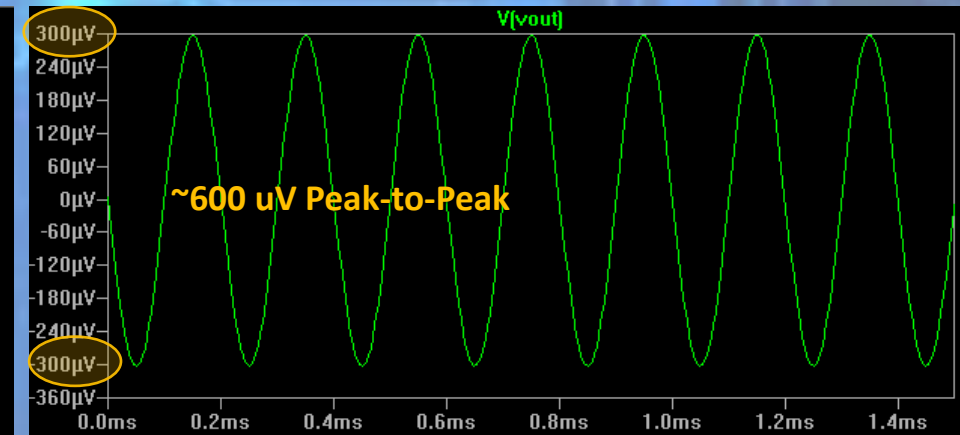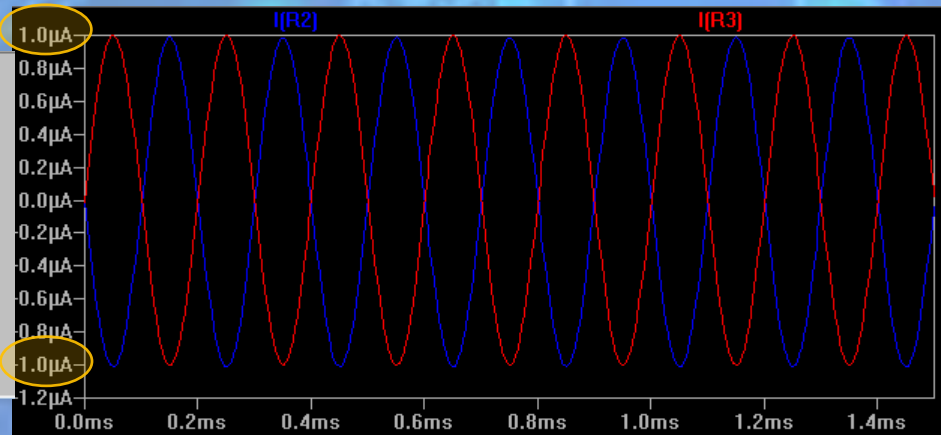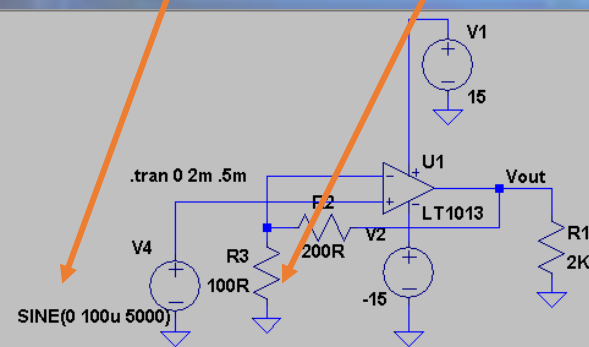
Resistor needs to be low enough to sink current for Non-Inverting Opamp





Small Signal

# Single Supply

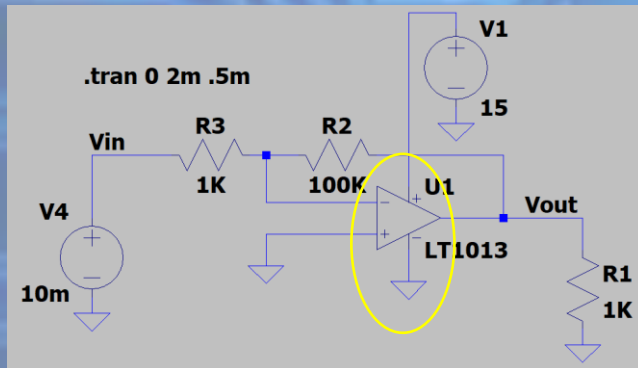1. Opamps swing between Positive Rail and Negative Rail
2. For +Rail and -Rail, swing is around 0
3. Negative rails allows voltages to swing below 0





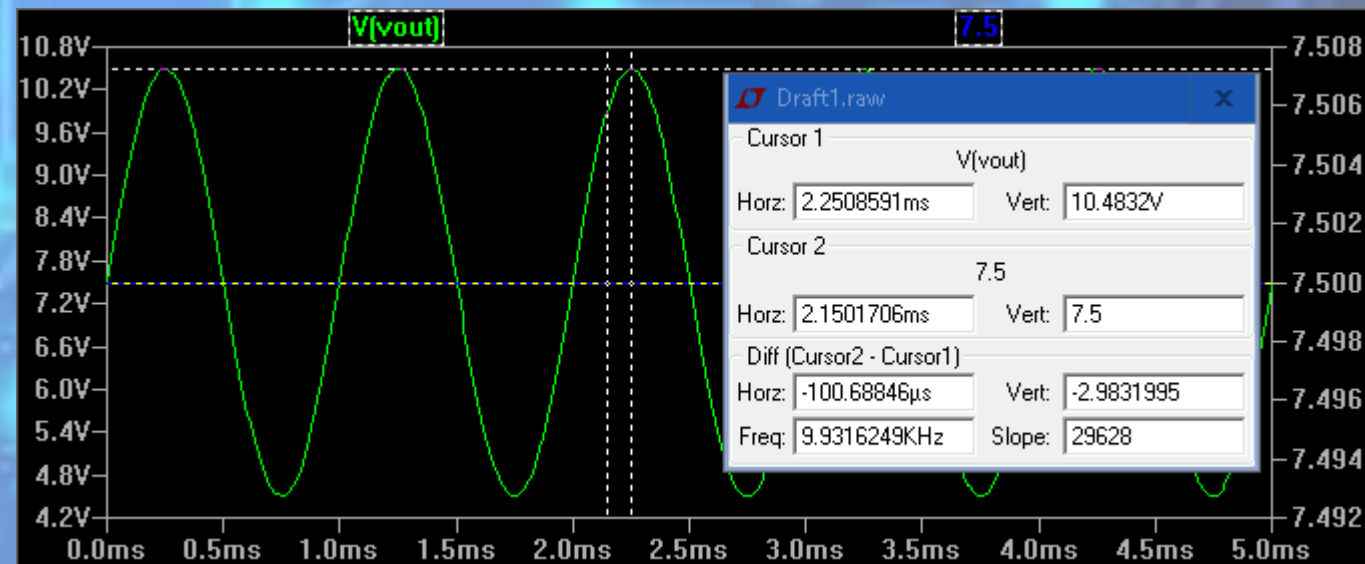
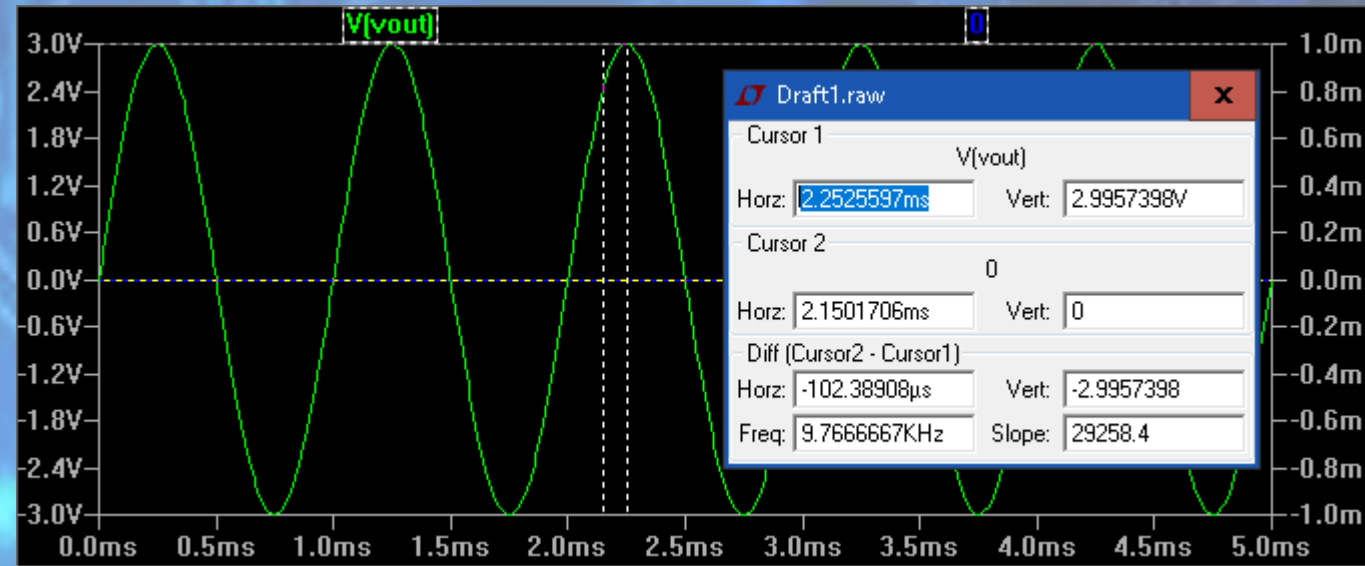
1. For single supply swing needs to be between +Rail and Gnd
2. Need to add  $\frac{1}{2}$  supply offset to input





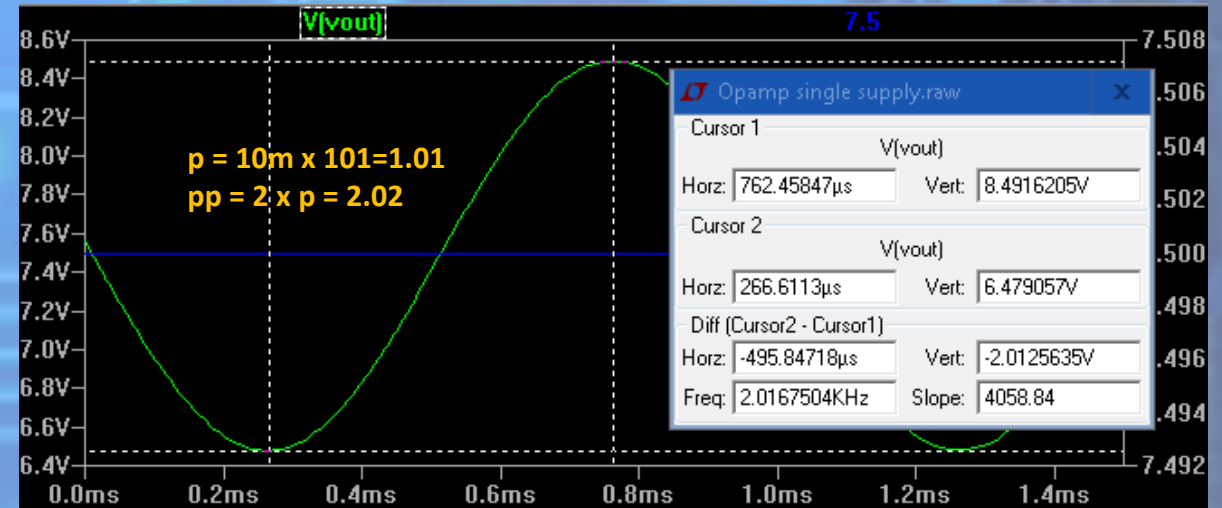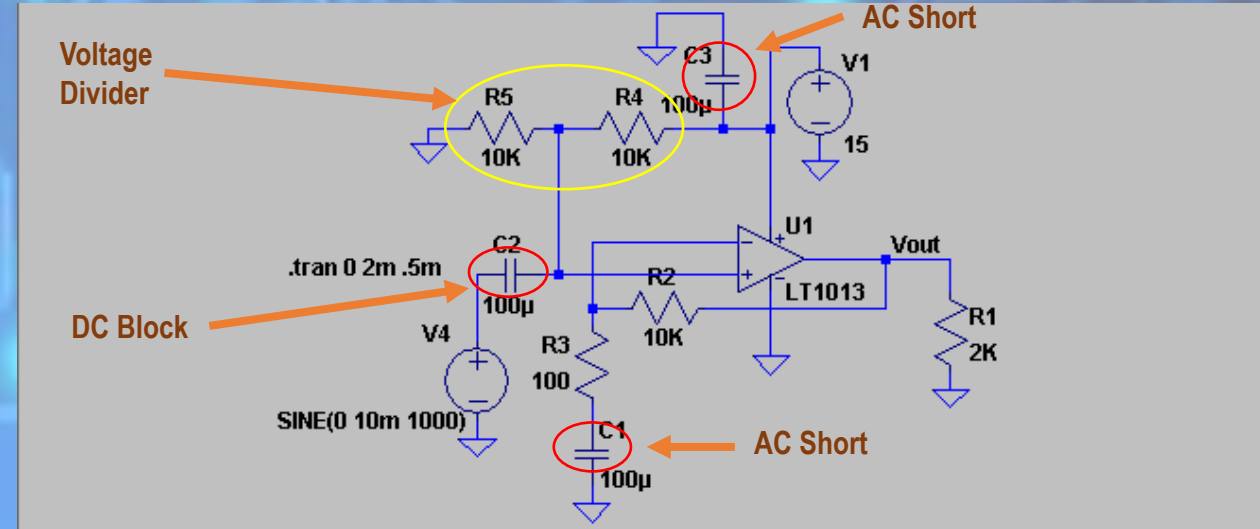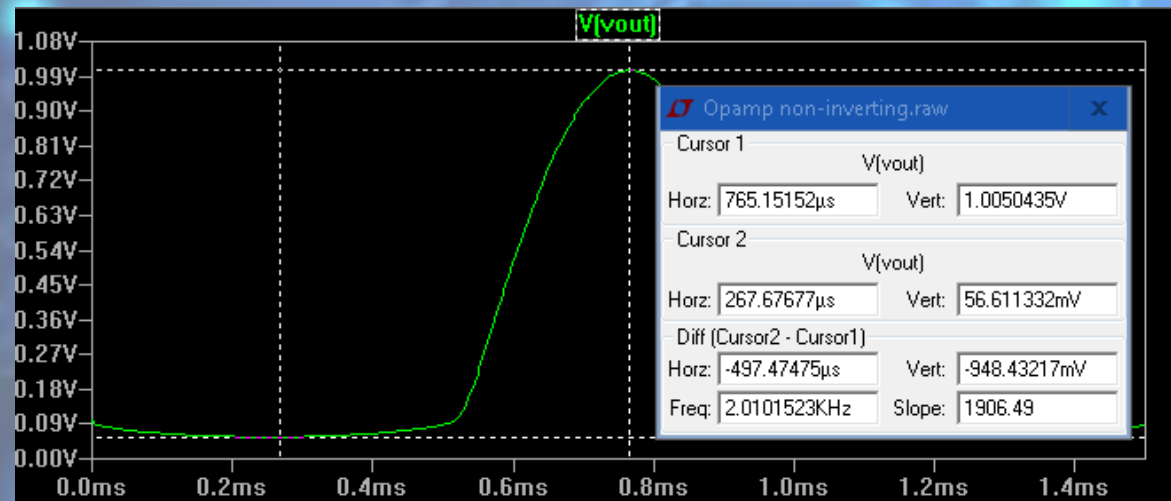
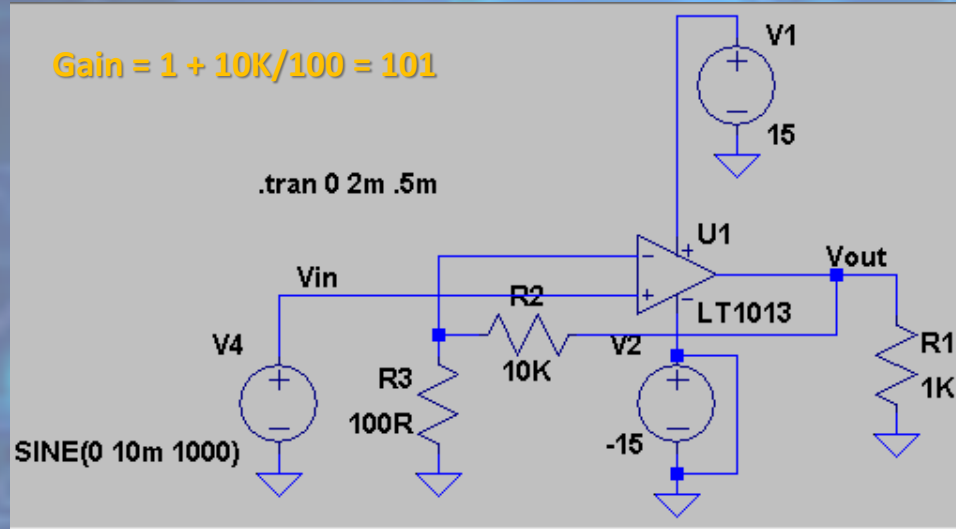
# Experiment 12: Single Supply

What happens if -Rail is 0 (ground)? What happens to the swing?



# Experiment 13: Distortion

**What happens If gain is too high?**

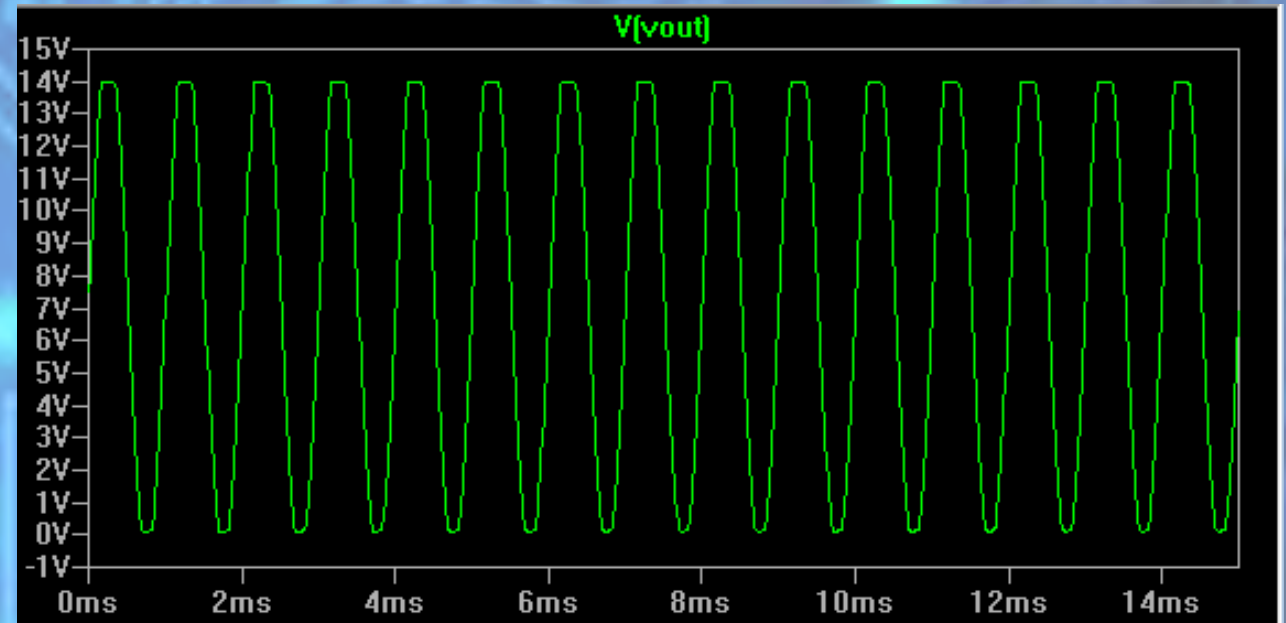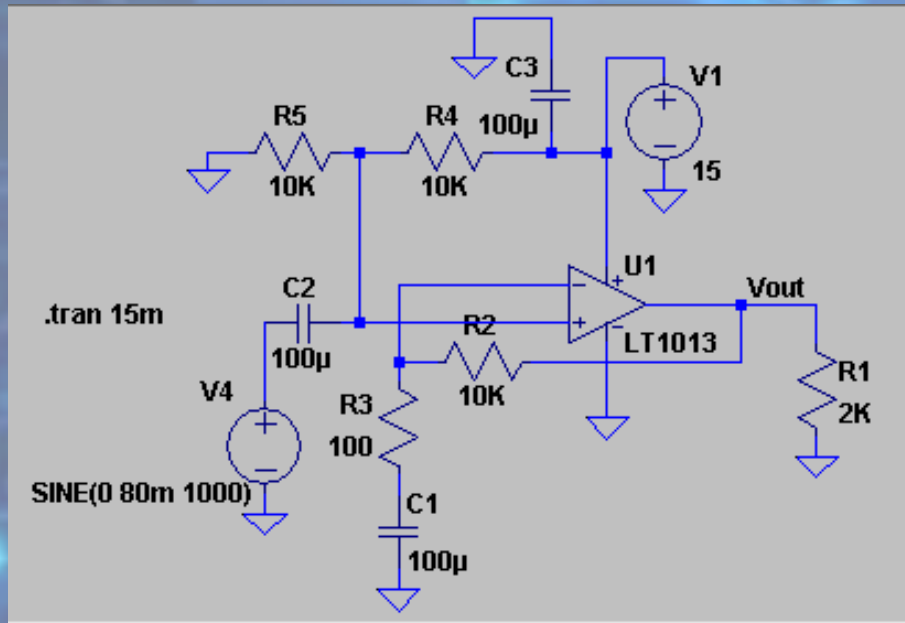

- 1. Gain is 100x. Input is 80mV, Output is 8V.**
- 2. Voltage swing is from 7.5V->0 and 7.5V -> 14**
- 3. Not enough room to accommodate necessary swing so it clips at Rails**

# **OPAMP LIMITATIONS**

**1. Frequency Limitation – Gain Bandwidth Product**


**2. Frequency & Output Voltage Limitation - Slew Rate**

**3. Noise**






# Experiment 14: Gain Bandwidth Product

## Opamps gain vary with Frequency

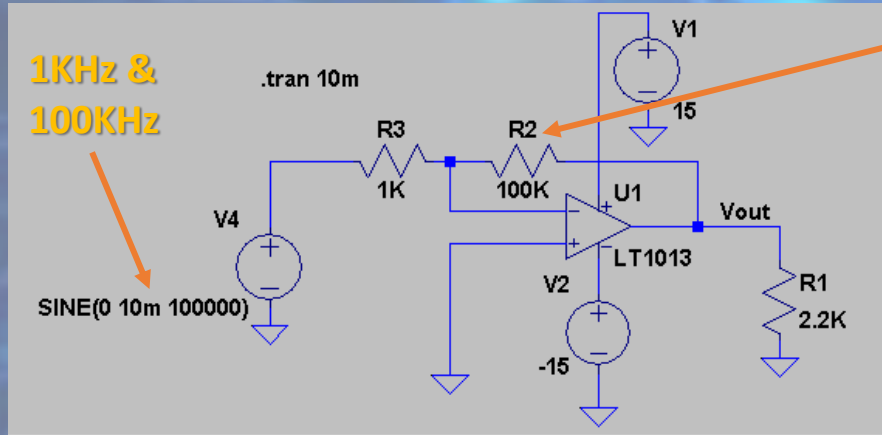
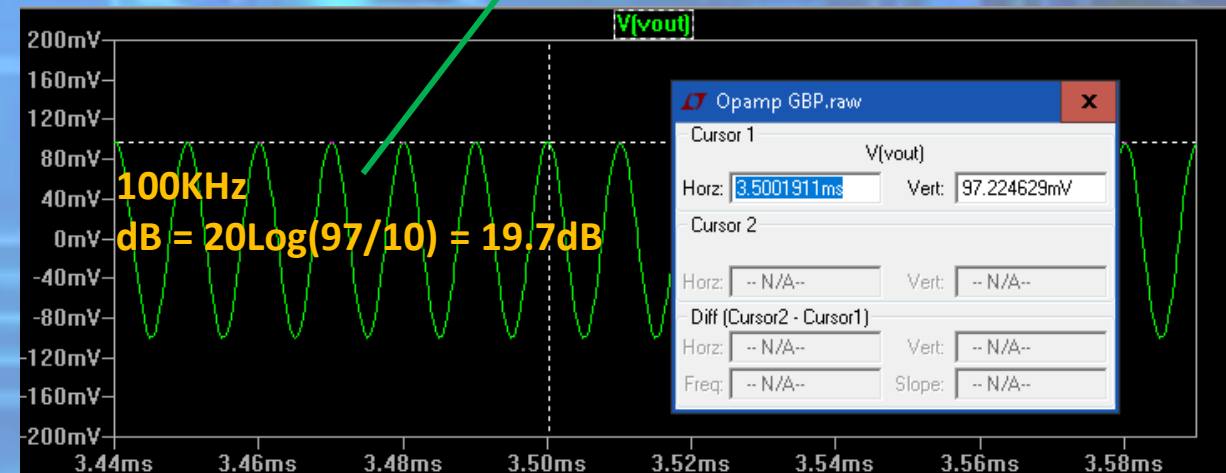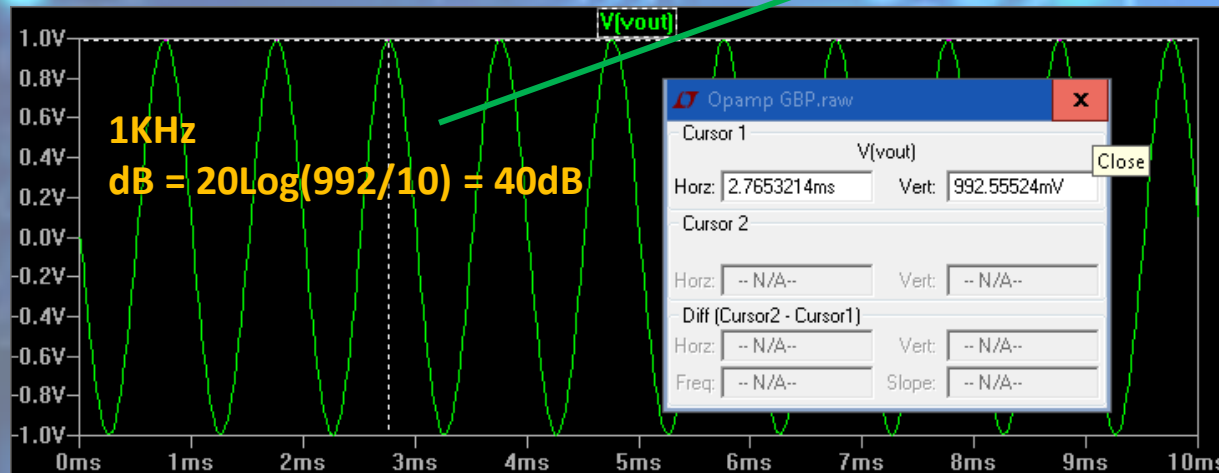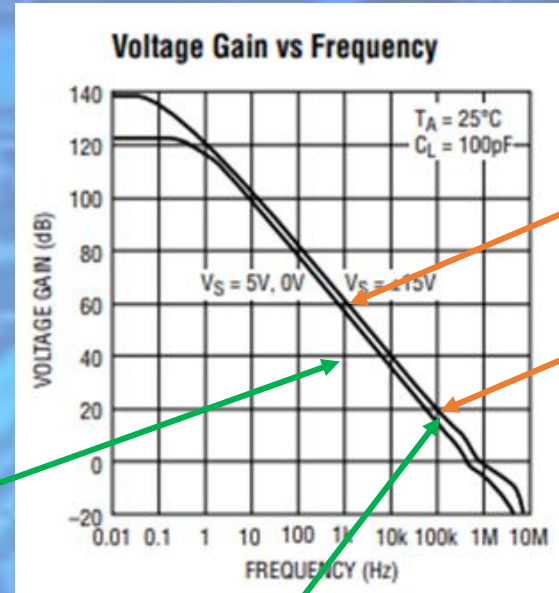
$$\text{Gain} = 20\log(100/10) = 40\text{dB}$$





# Experiment 15: Slew Rate

Will f\*\*\*\* you up!



The output of an operational amplifier can only change by a certain amount in a given time. This limit is called the slew rate of the op-amp, and although slew rate is not always mentioned, it can be a critical factor in ensuring that an amplifier is able to provide an output that is a faithful representation of the input..

$$\text{Slew rate} = 2 \pi f V$$

Slew Rate		0.2	0.4	0.2	0.4	V/ $\mu$ s
-----------	--	-----	-----	-----	-----	------------



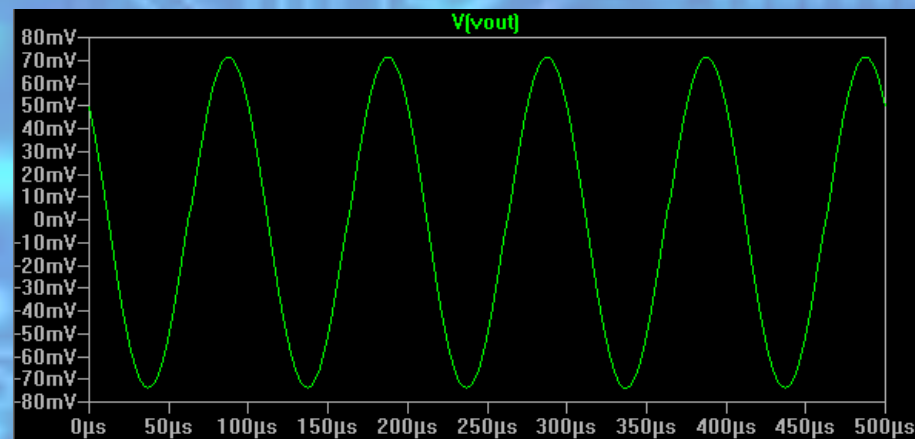
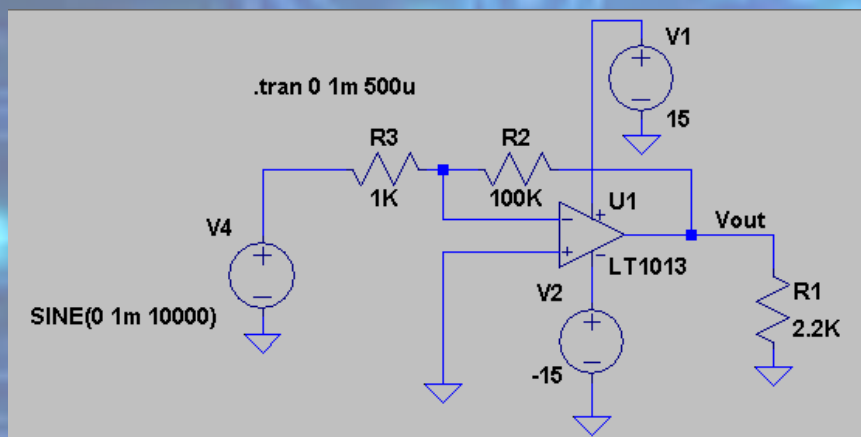


10 KHz

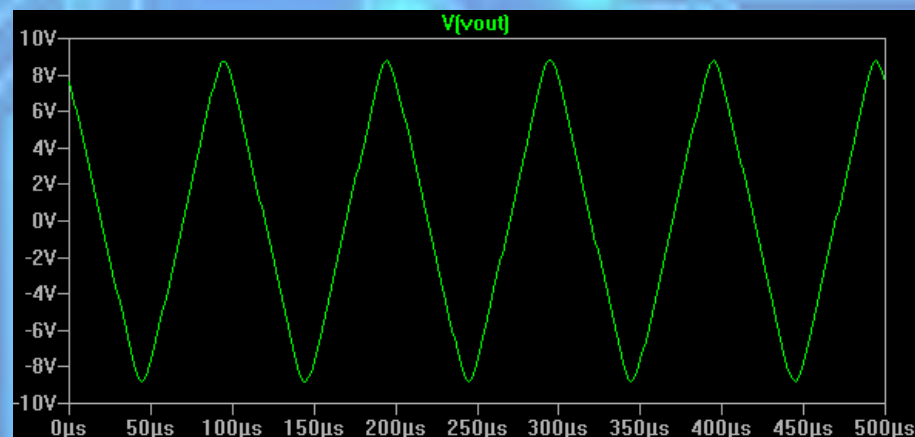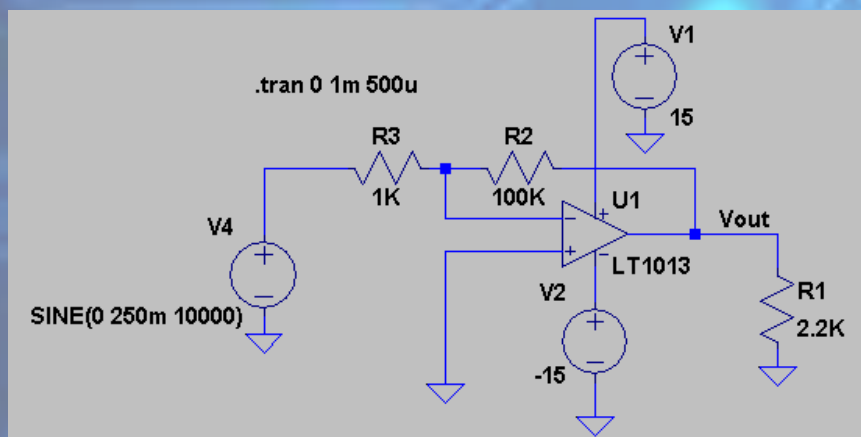

20 KHz

# Experiment 16: SR Simplification

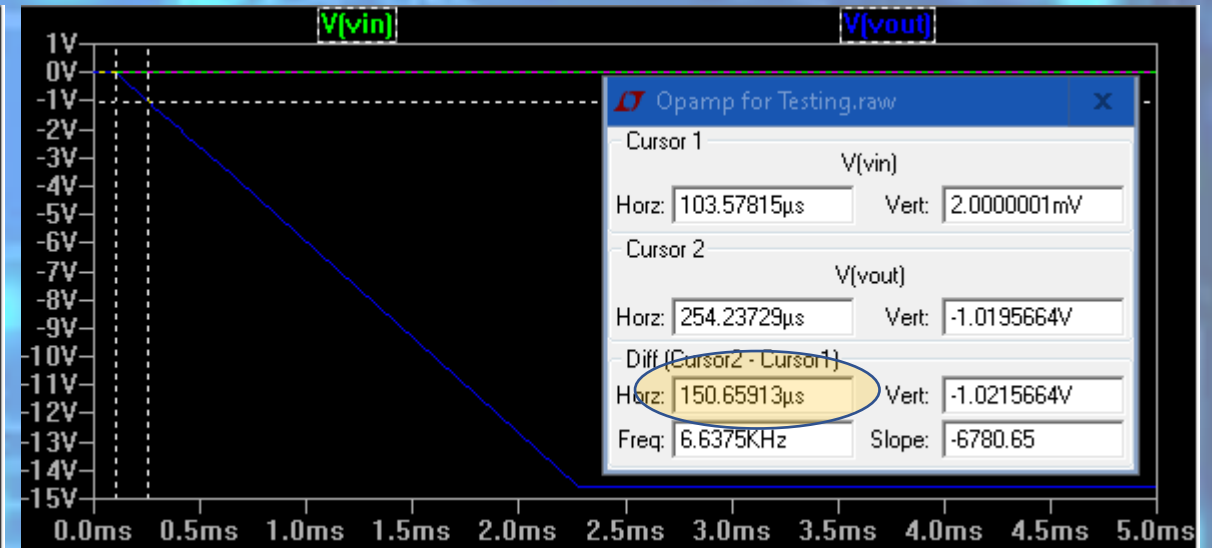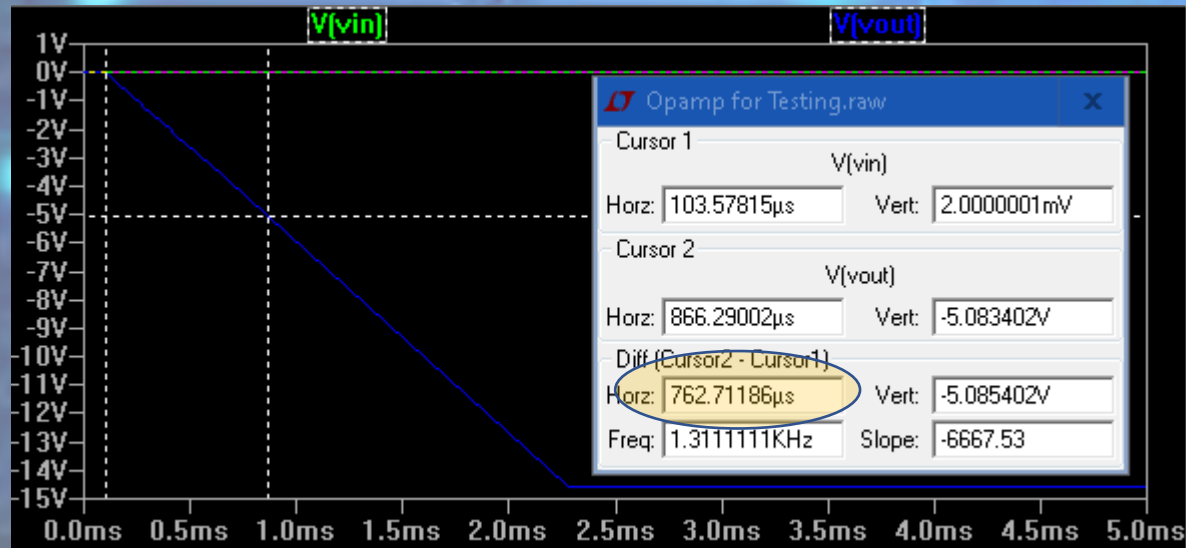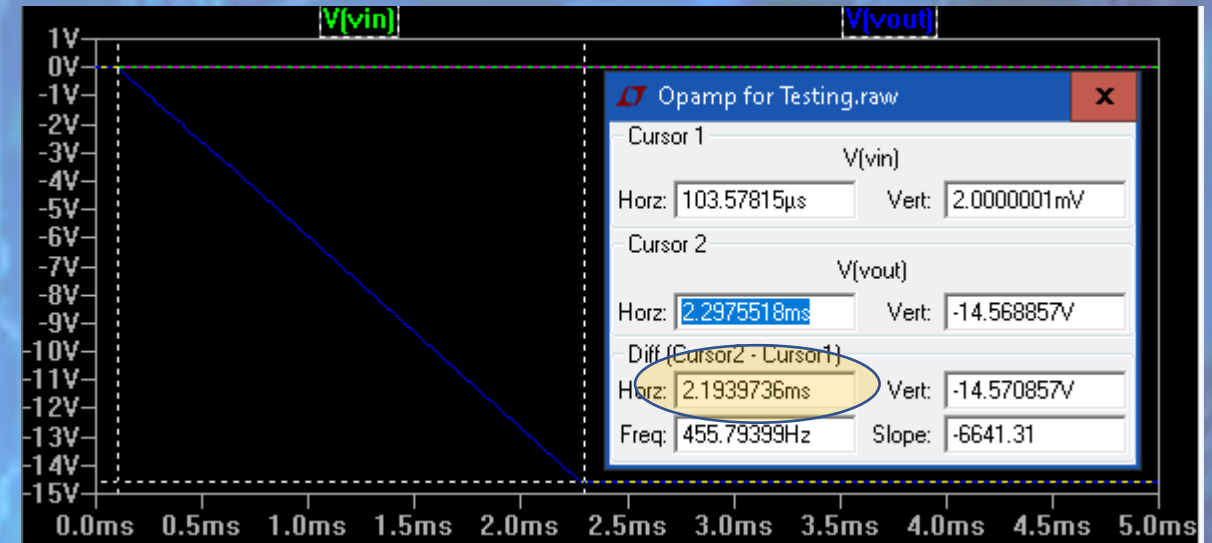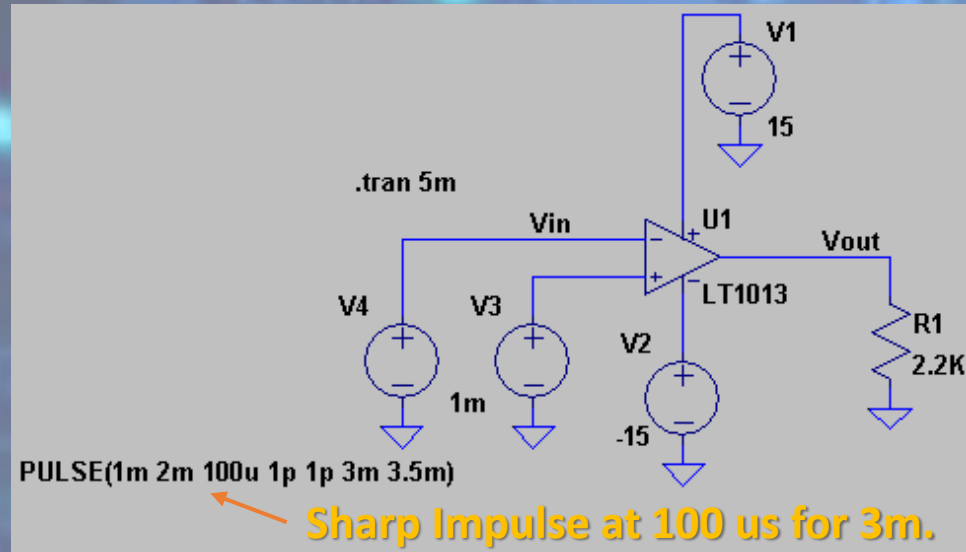

**Homework: Add feedback to this circuit and measure time**



# Finding 4: Slew Rate Calculation

$$\text{Slew rate} = 2 \pi f V$$

Slew Rate		0.2	0.4	0.2	0.4	V/ $\mu$ s
-----------	--	-----	-----	-----	-----	------------

**Slew Rate = 0.3 V/ $\mu$ s = 300,000 V/s**

**1. For 13 Volts,**

$$\mathbf{F = SR / (2 * \pi * V) = 300,000 / (2 * 3.14 * 13) = 3.675 \text{ KHz}}$$

**2. For 1 Volt, F = 47.771 KHz**


**3. For 5 Volts, F = 9.554 KHz**

**Homework: Create test circuit with gain and see how the output is impacted after these frequencies and voltages.**

**\*\*Don't forget gain bandwidth product**

# Principal 4: Opamp Noise

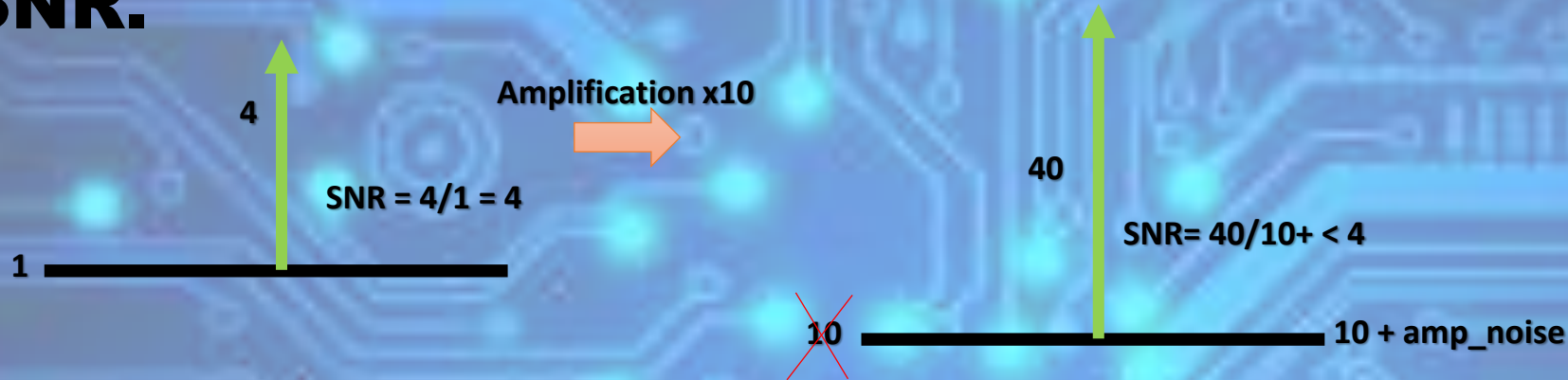**1. All amplifiers introduce noise into a circuit that reduces SNR.**




1. Opamp
2. Feedback Network

**2. Opamps introduce “White” Noise and “Pink” Noise. Noise is subject to gain with voltage and current noise added to input.**

### 3. Feedback network introduces White Noise from resistors – Usually Largest

$e_n$	Input Noise Voltage	0.1Hz to 10Hz	0.55	0.55	$\mu V_{p-p}$
$e_n$	Input Noise Voltage Density	$f_0 = 10\text{Hz}$	24	24	$nV/\sqrt{Hz}$
		$f_0 = 1000\text{Hz}$	22	22	$nV/\sqrt{Hz}$
$i_n$	Input Noise Current Density	$f_0 = 10\text{Hz}$	0.07	0.07	$pA/\sqrt{Hz}$

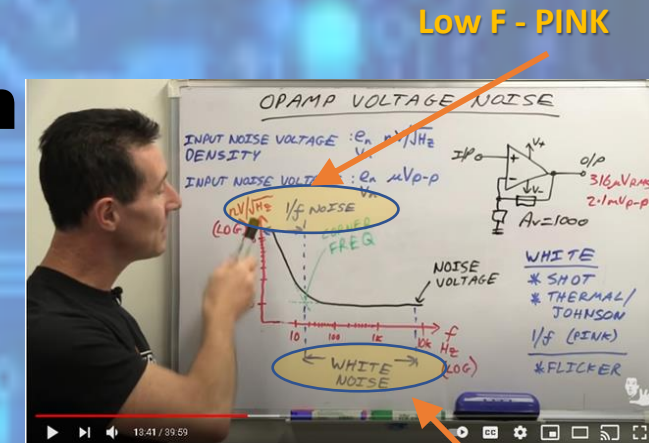


## Spectral Noise Density

## Higher F - White



# Modeling Noise in Opamps

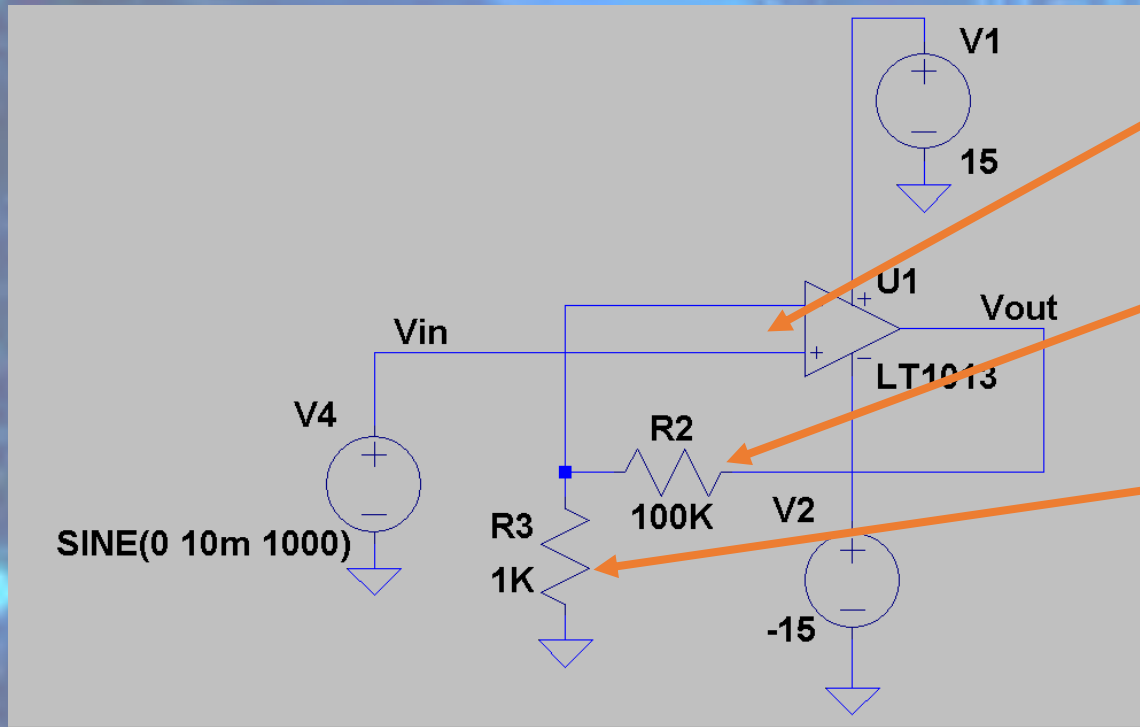

Current Noise and Voltage Noise

Resistor Voltage Noise

Resistor Voltage Noise

$$E = \sqrt{4 \cdot R \cdot k \cdot T \cdot \Delta F}$$

Where  $E$  is the RMS noise signal in volts,  $R$  is the resistance in ohms,  $k$  is Boltzmann's constant,  $T$  is the temperature in Kelvin and  $\Delta F$  is the bandwidth in Hz. The equation shows that the noise level can be decreased by reducing the resistance, the temperature or the bandwidth. Knowing Boltzmann's constant, the formula is

**Resistor noise is about 4nV/rHz for 1K Resistor at room temp**



# Experiment 17: Calculate Opamp Noise

At the output: Spectral Noise Density:

1. Noise from resistors:

- R1: 40nV/rHz
- R2: 400nV/rHz


2. LT1013 Opamp current noise

- 7nV/rHz


3. LT1013 Opamp voltage noise

- 2200nV/rHz



Sum of Squares: 2236 nV/rHz (2.2uV/rHz)

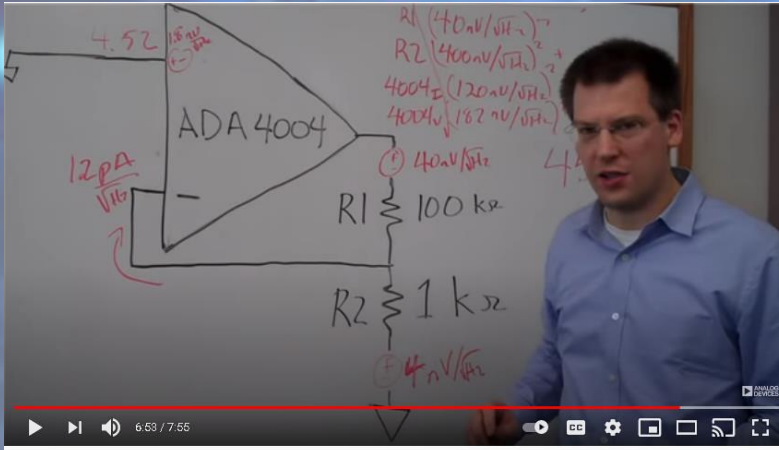



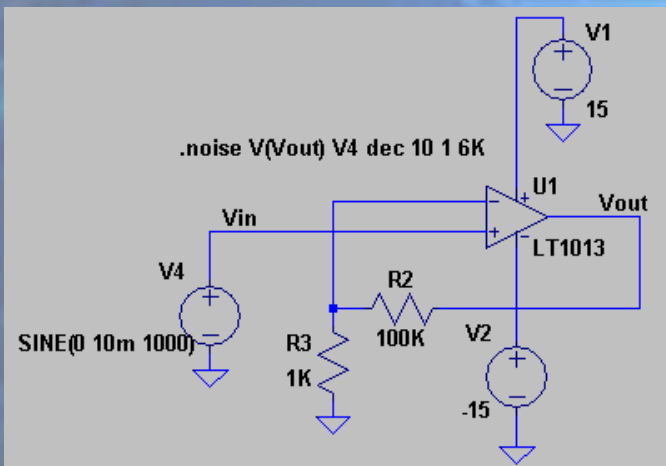
Noise of a Non-inverting Operational Amplifier Circuit




Bandwidth

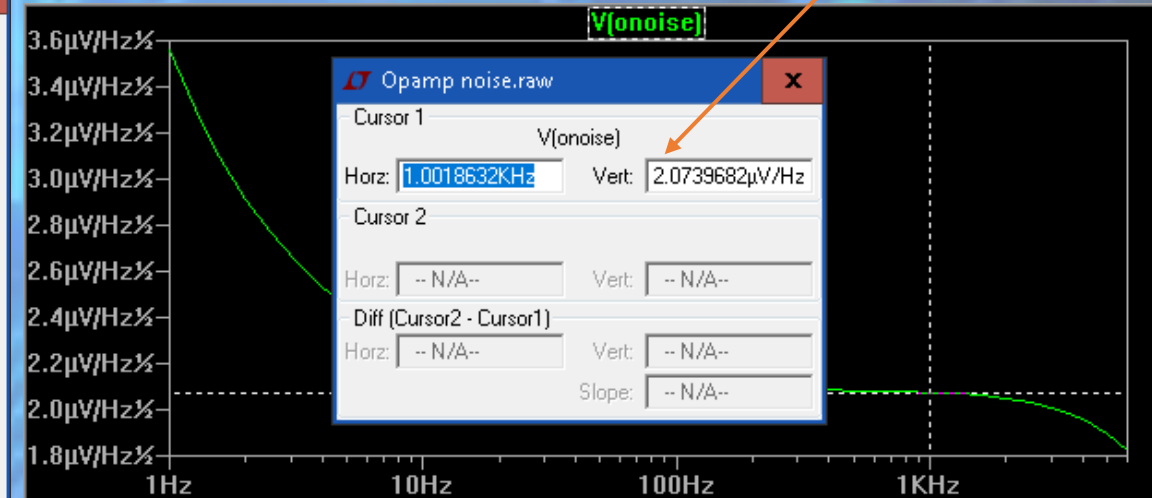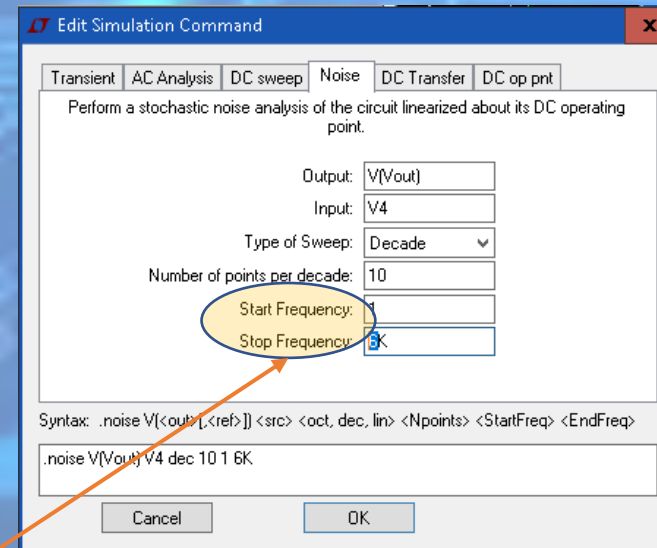

# Experiment 18: Noise in Audio Range

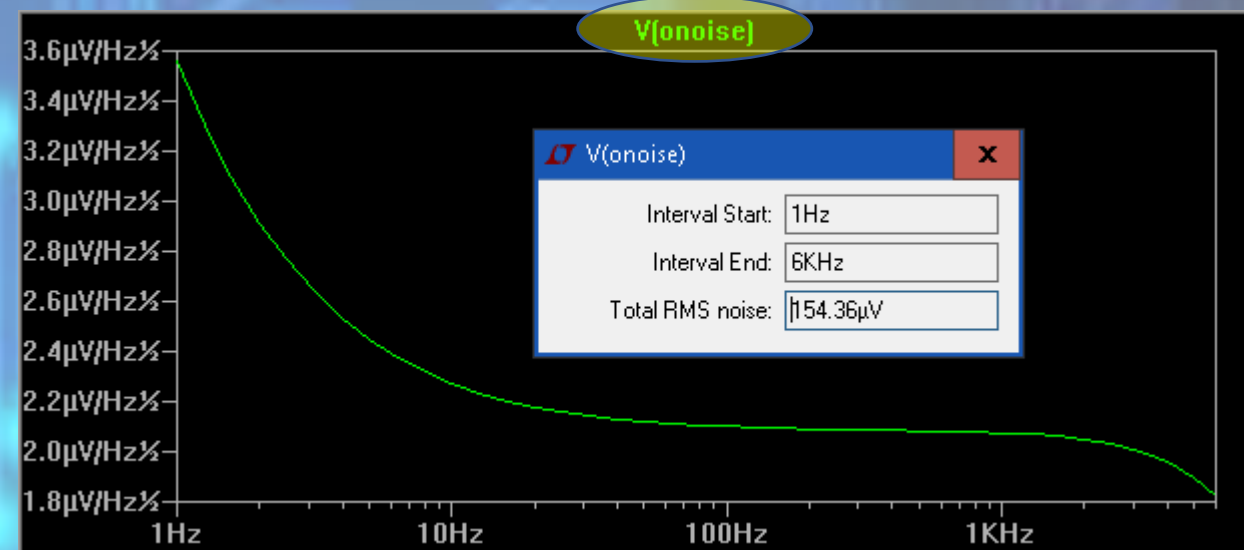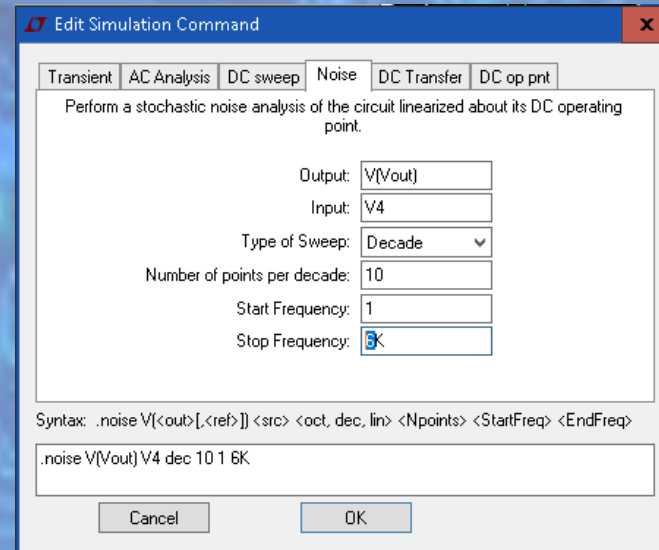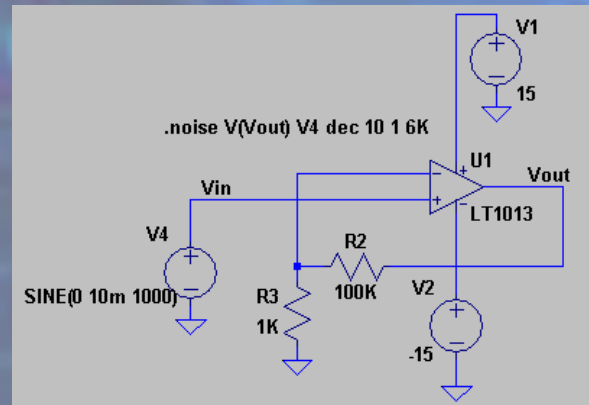


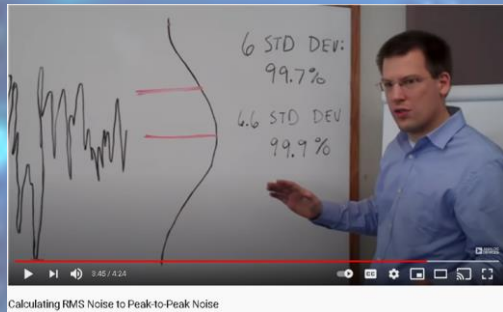**Point to Trace Name and Press CTL-Click**



**Dumb it down: Multiply RMS noise by 6.6 to get peak-peak voltage**

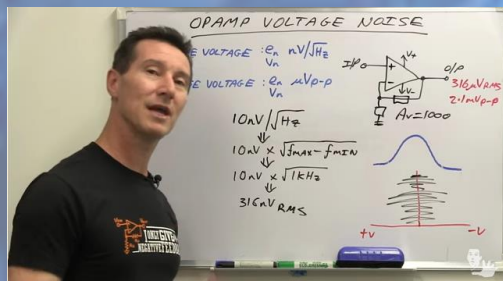
**Peak-Peak Noise:  $6.6 \times 154 \mu\text{V} = 1.02 \text{ mVpp}$**





# NOISE WRAP UP

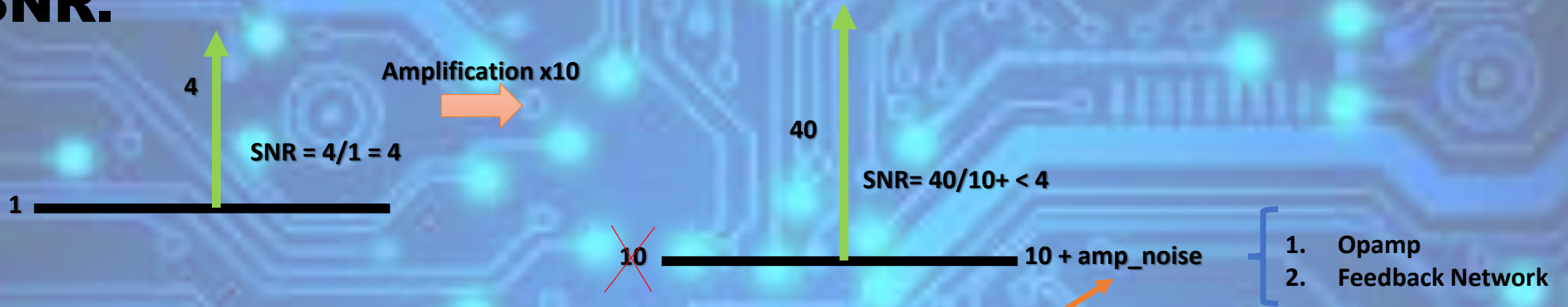**1. All amplifiers introduce noise into a circuit that reduces SNR.**



**We now know how much noise opamp will add!!**





**FIN**