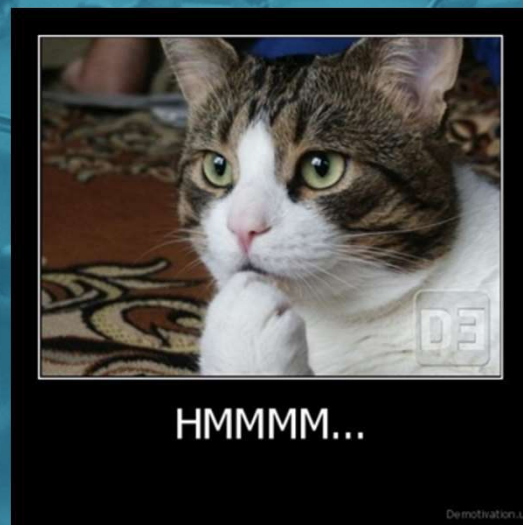


What are Load Cells?



DAVE VE3OOI
APRIL 2022

Agenda

1. Why I did this?



2. Wheatstone Bridge Basics



3. Load Cells, Stain Gauges and all that



4. Load Cell Measurements/Simulation

5. What about SWR?

Danger Will Robinson



This is my journey:

- Preceding are my rambling
- This is not an engineering tutorial
- Quote Charlie Morris, ZL2CTM:



This NOT a tutorial. Its a log of my journey. Right or wrong.



HOW THIS STARTED...

- I have crashed MANY airplanes and Helicopters
- Many due to stupidity...
- Others due to underpowered aircraft.
 - ❖ Thrust-to-Weight ratio too small
- Needed a mechanism to measure thrust from motor & propeller.




Built a "Thrust Measurement Bench"


The Final Product

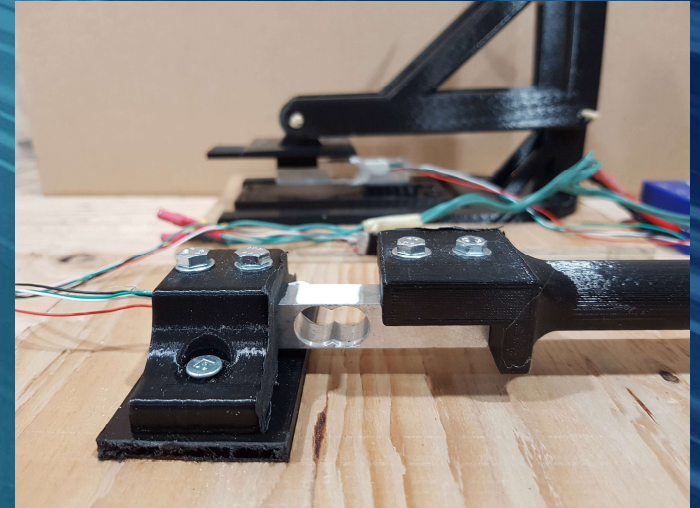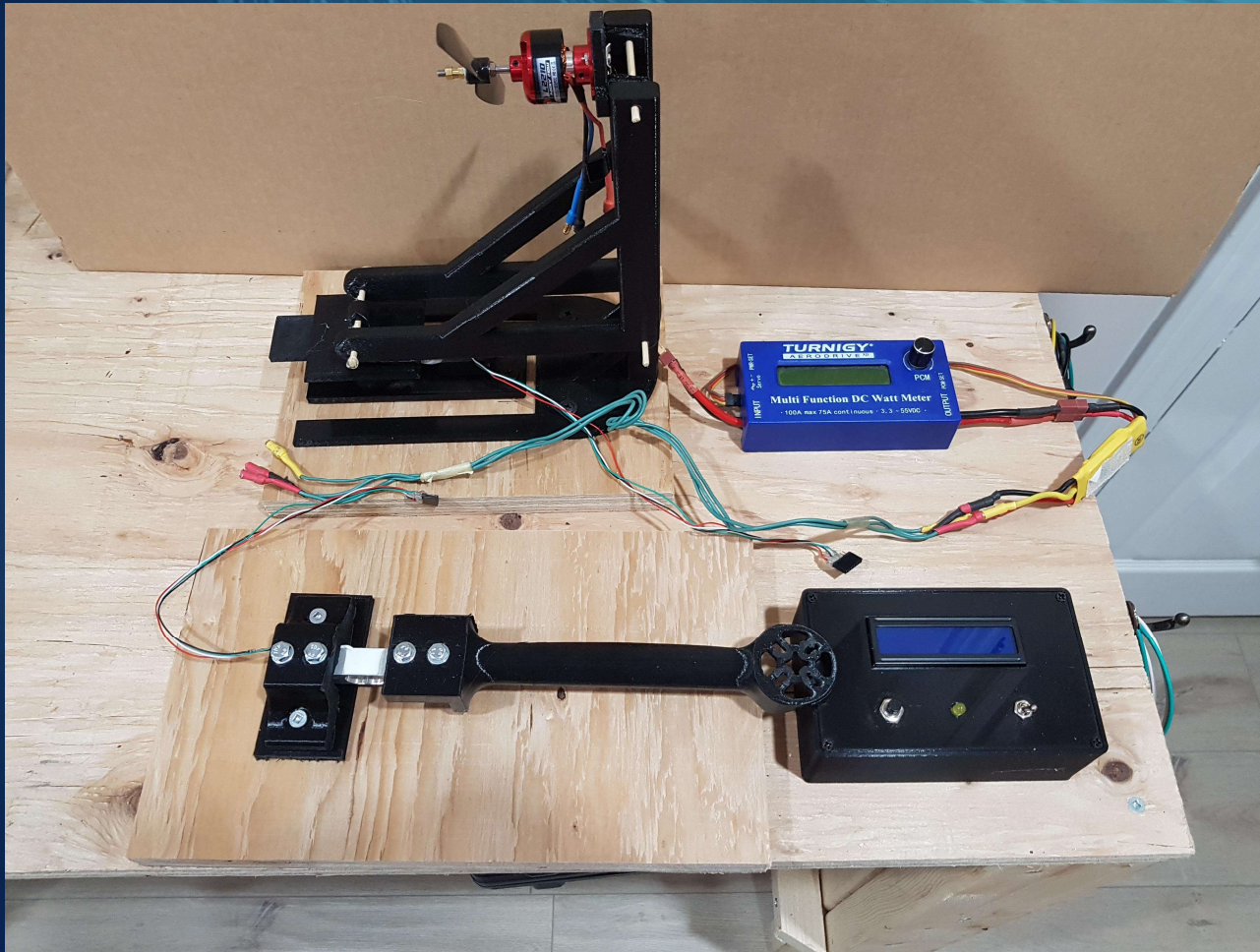

Wheatstone Bridge

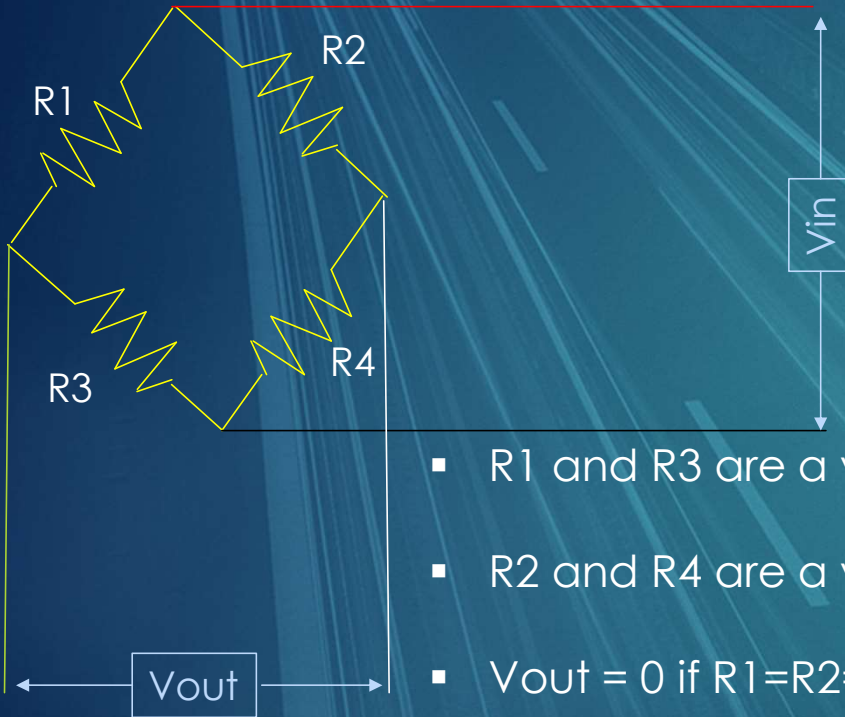

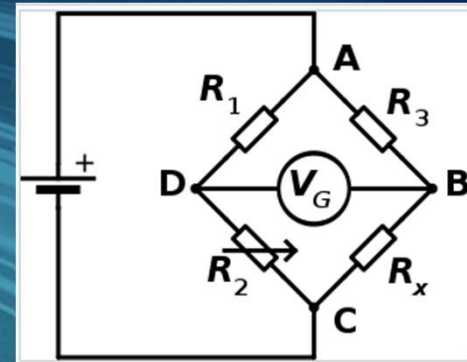
- R1 and R3 are a voltage divider for V_{in}
- R2 and R4 are a voltage divider for V_{in}
- $V_{out} = 0$ if $R1=R2=R3=R4$
- If any R changed by small amount, there will be a small voltage at V_{out}
- **Temperature tolerant**




Wheatstone bridge circuit diagram. The unknown resistance R_x is to be measured; resistances R_1 , R_2 and R_3 are known, where R_2 is adjustable. When the measured voltage V_G is 0, both legs have equal voltage ratios: $R_2/R_1 = R_x/R_3$ and $R_x = R_3 R_2 / R_1$.

Load Cell

LOAD CELL WIRING

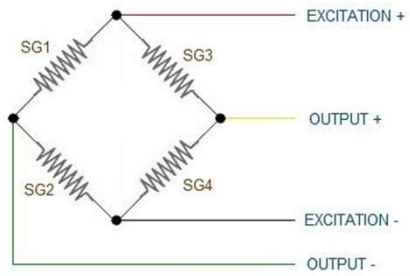


Wheatstone Bridge Calculations

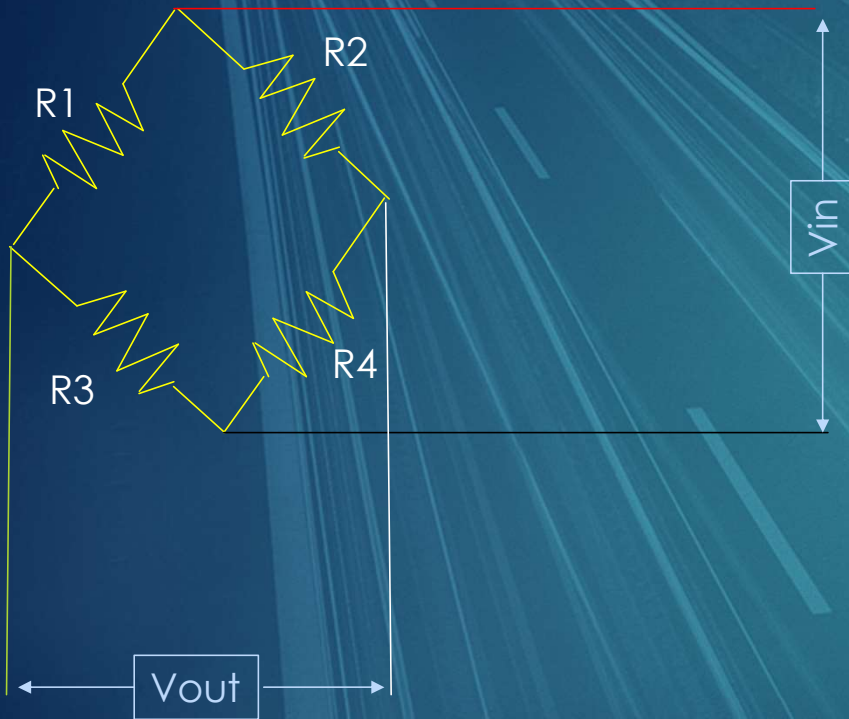


From Video,

- Resistances measured 997 and 748 ohms
- ✓ If resistance between Red and Black is 997 (i.e. $R2+R4//R1+R3$)
- ✓ If resistance between White and Black is 748 (i.e. $R4//R1+R2+R3$)
- ✓ If $R1=R2=R3=R4$, then
 - $997 = R2+R4//R1+R3$
 - $748 = R4//R1+R2+R3$
 - $997 = R+R//R+R$, $R=997$
 - $748 = R//R+R+R$, $R=997$

So for my Load Cell, $R=997$ ohms

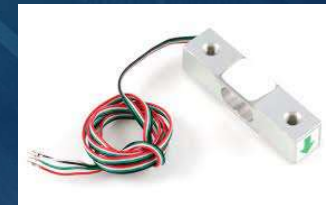

Load Cell Calculations


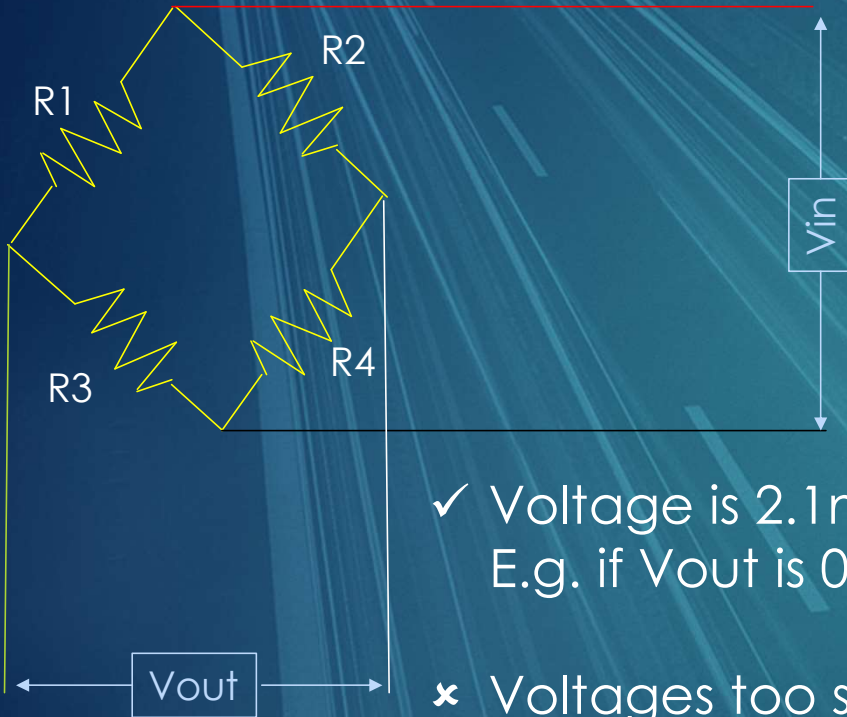


From Video,


- V_{out} measured 2.1mV for 600g

✓ Voltage is 2.1mV for 600g or 3.5uV/g or 0.286g/uV
E.g. if V_{out} is 0.5 mV, weight is 143g

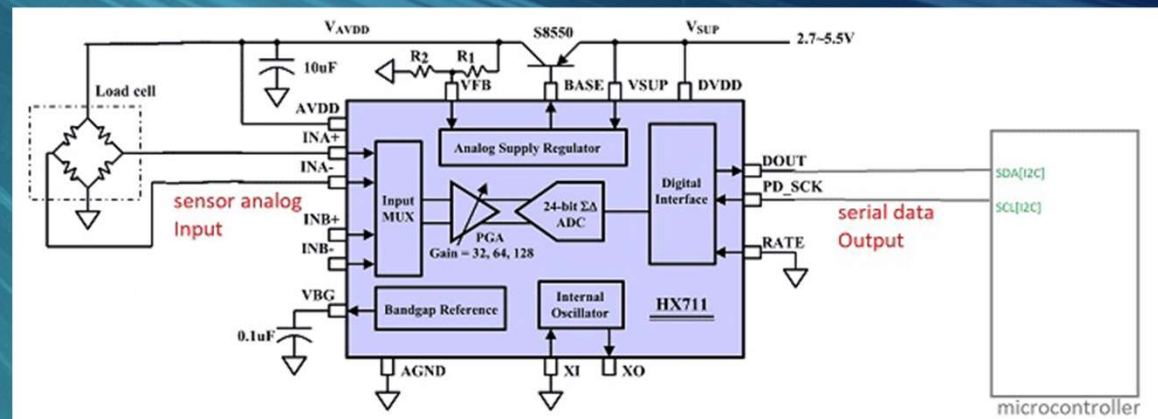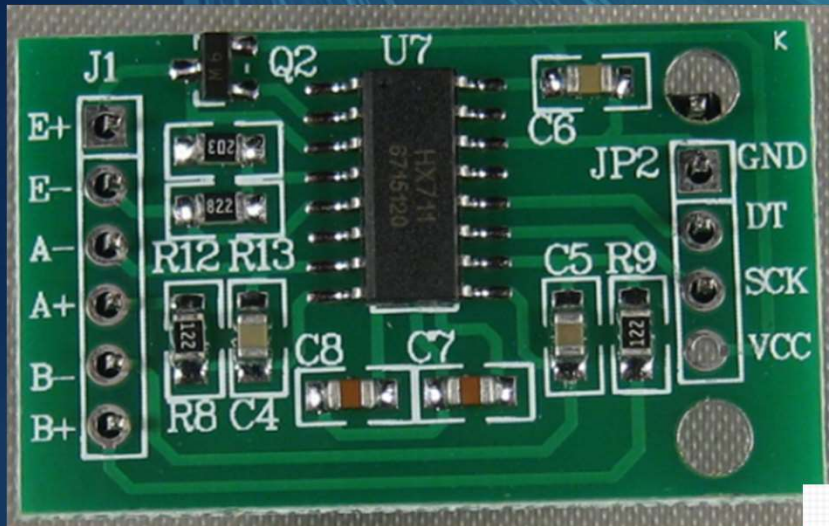✗ Voltages too small to measure with uC. Need amplification.
Us HX777 amplifier and 24bit ADC



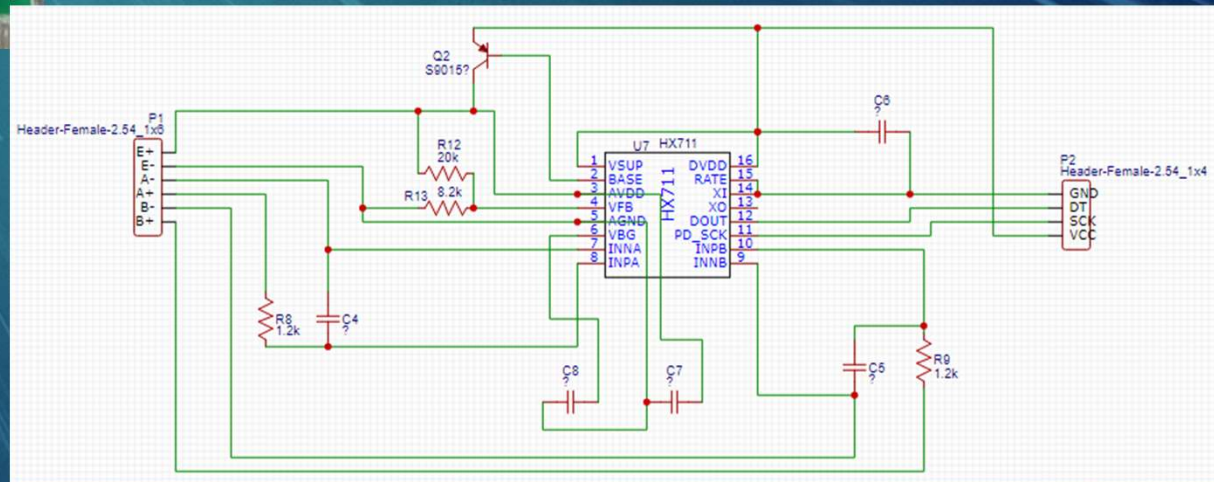
$$V_{AVDD} = V_{BG} * (R1 + R2) / R1$$
$$= 1.25 * (20 + 8.2) / 20$$
$$= 1.7625 \text{ V}$$



Load Cell & LTSpice

```
.param Ag=128
.param ADC=1677216/1.7625
.param GF 457

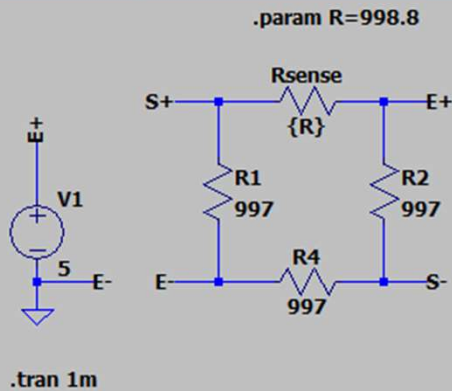.meas TRAN Vp AVG V(S+)
.meas TRAN Vn AVG V(S-)
.meas TRAN Vd PARAM (Vn - Vp)
.meas TRAN Vm PARAM Vd*Ag
.meas TRAN Vadc PARAM Vm*ADC
.meas TRAN SF PARAM Vadc/600
.meas TRAN Gms PARAM Vadc/GF
```




```
vp: AVG(v(s+))=2.49775 FROM 0 TO 0.001
vn: AVG(v(s-))=2.5 FROM 0 TO 0.001
vd: (vn - vp)=0.00225472
vm: vd*ag=0.288605
vadc: vm*adc=274640
sf: vadc/600=457.733
gms: vadc/gf=600.962
```



Cursor 1		V(s-) - V(s+)	
Horz:	236.8214µs	Vert:	2.2547245mV
Cursor 2			
Horz:	-- N/A --	Vert:	-- N/A --
Diff (Cursor2 - Cursor1)			
Horz:	-- N/A --	Vert:	-- N/A --
Freq:	-- N/A --	Slope:	-- N/A --


SWR with Wheatstone Bridge

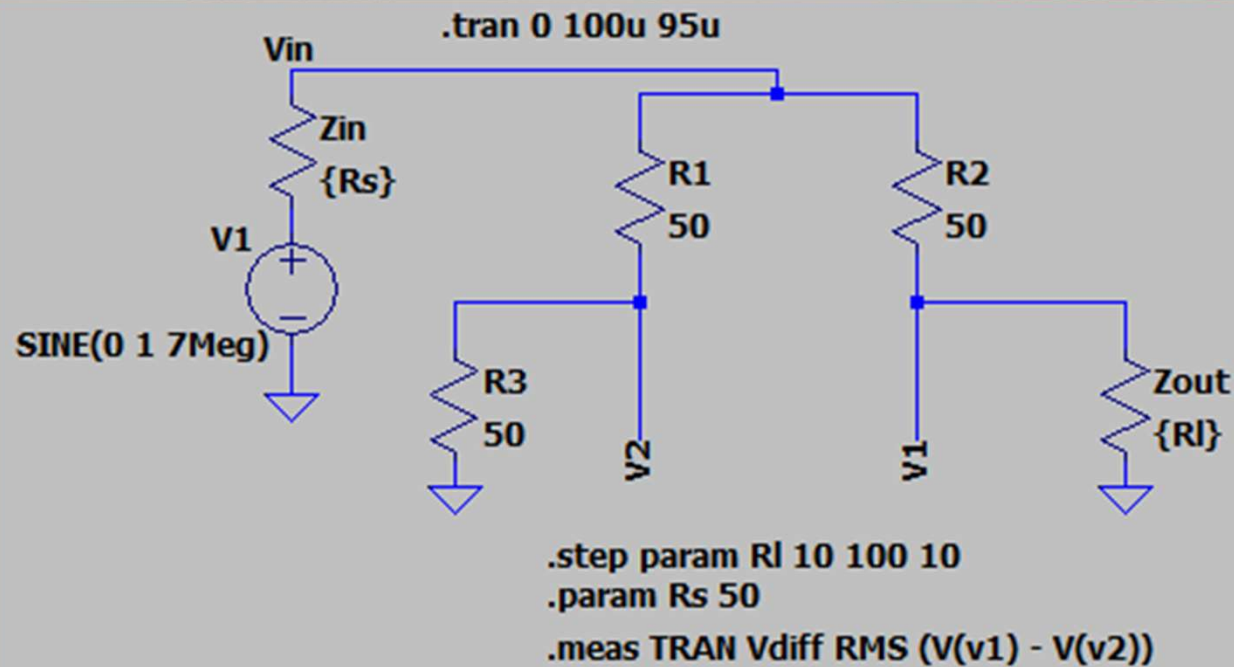

Measurement: vdiff

step	RMS (v(v1) - v(v2))
1	0.0986397
2	0.0668205
3	0.0406164
4	0.0186616
5	0
6	0.0160576
7	0.0300208
8	0.0422742
9	0.0531137
10	0.0627707

Detector

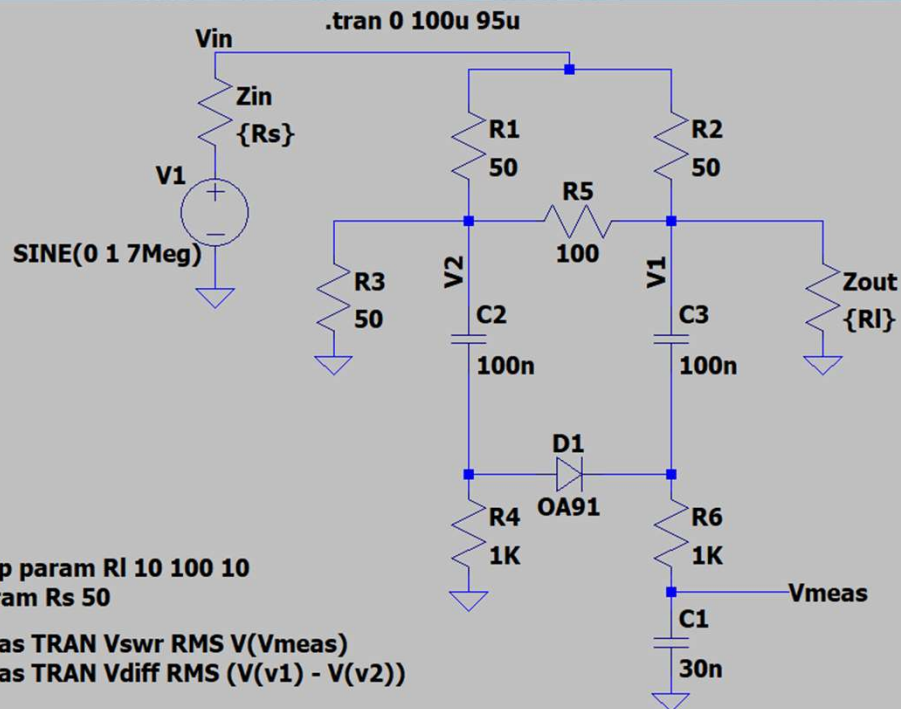


Measurement: vdiff

step	RMS(v(v1) - v(v2))
1	0.0700472
2	0.0454747
3	0.0267262
4	0.0120013
5	1.96664e-006
6	0.00989201
7	0.0181911
8	0.0252524
9	0.031334
10	0.036642

Measurement: vswr

step	RMS(v(vmeas))
1	0.00516979
2	0.00217436
3	0.000863429
4	0.000148736
5	0.000121162
6	0.000138377
7	0.000224854
8	0.000488699
9	0.000851575
10	0.00128201

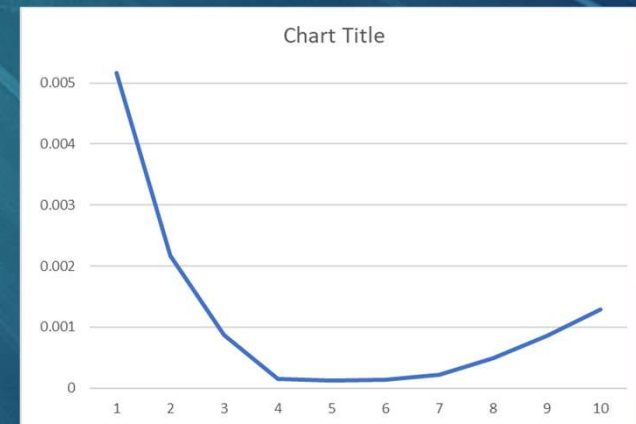



Fin