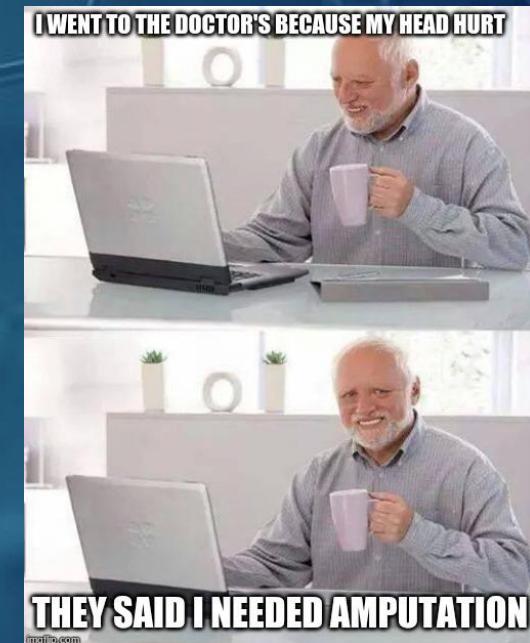


# Journey Down Rabbit Holes

## Why my head hurts

DAVE VE3OOI

DEC 2021 – FEB 2022



# Danger Will Robinson...



Members of the Accelerator Laboratory. Drs. Cameron, Kuehner and Waddington were teaching classes when this photo was taken.

Preceding are the ramblings of an 'old' Experimental Physicist.

This is not an engineering tutorial




Quote Charlie Morris, ZL2CTM:  
This NOT a tutorial. Its a log of my journey.


Right or wrong.
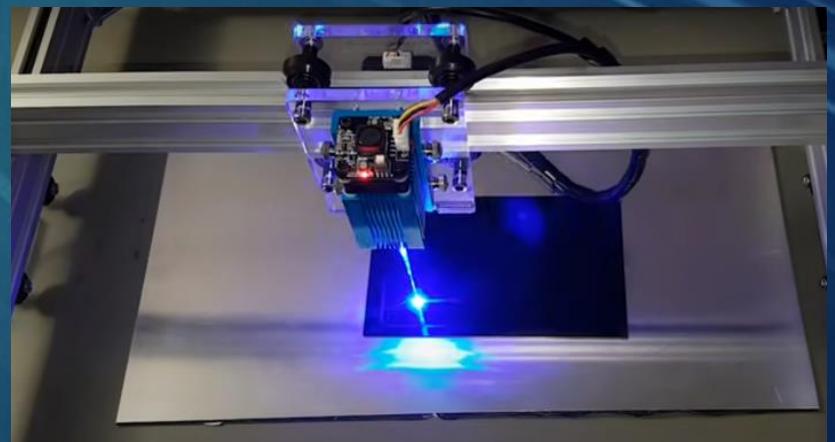
# How It All Started...



- Purchased an Ender 3D Printer
- Discovered laser module for printer
  - Useful to cut parts from thin plywood
  - **Etch PCB boards!**
- Investigation of how laser modules work
  - Use laser diodes
  - Require low voltage but higher current (e.g., 3V and several amps)
- Use PWM to control voltage (Laser Power)
- Use a buck step-down converter to control voltage and higher current



# The Rabbit Holes...

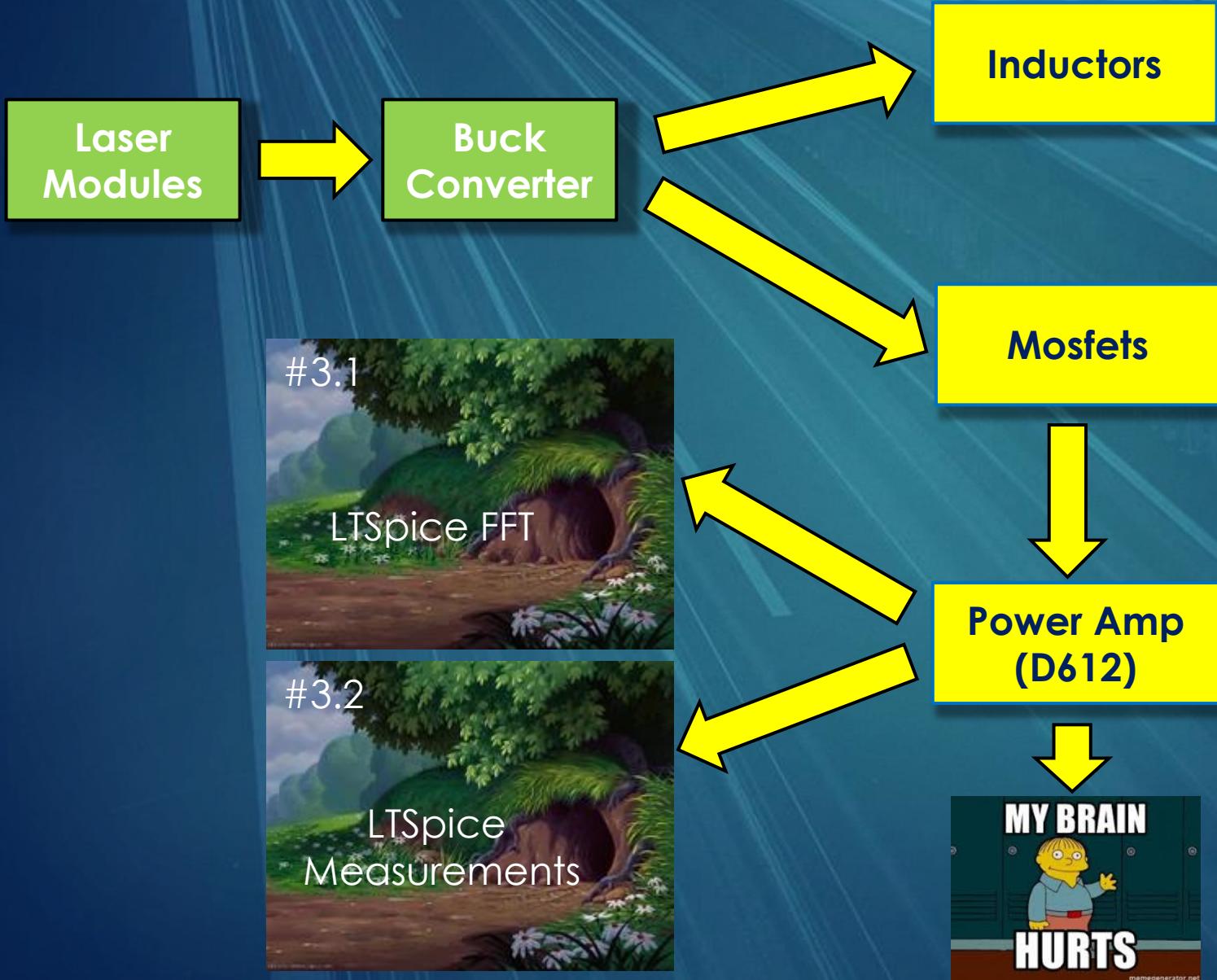


# Buck Converter: How It Works

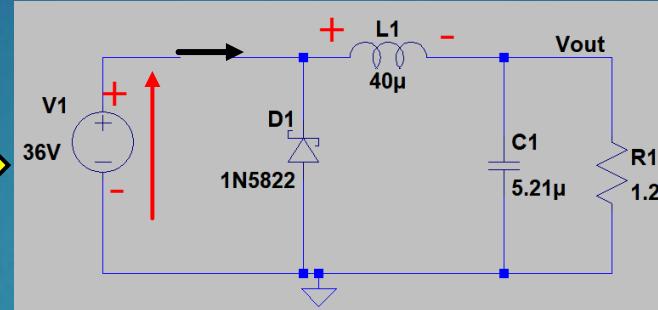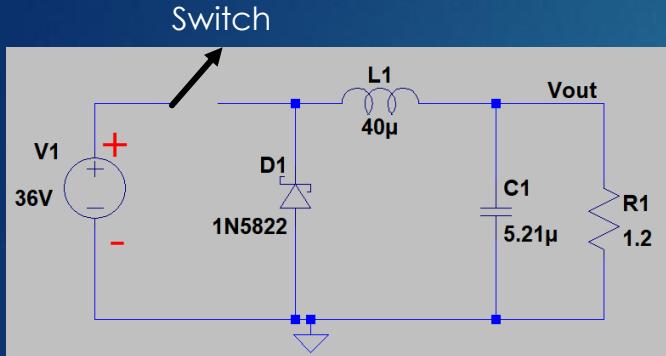


1. Switch Closed. Current slowly flows through inductor.
2. Inductor opposes current increase
3. Capacitor Charges
4. Current slowly increases through  $R_1$


Switch opens

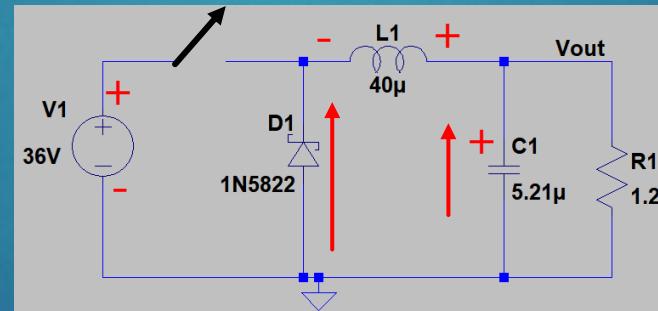

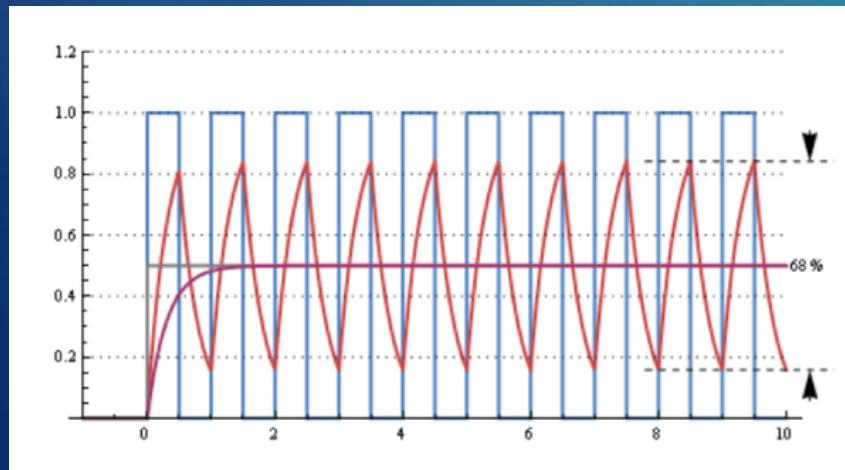1. Current rapidly decreases through inductor.
2. Inductor opposes current decrease
3. Capacitor and inductor act as a battery
4. Current continue to flow through  $R_1$



# Buck Converter: Testing

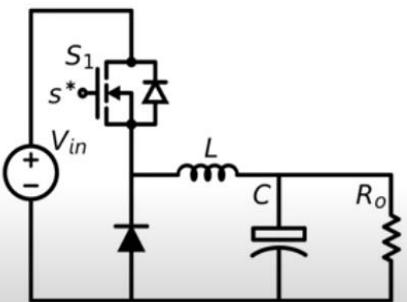

$$V_{in} = 36 \text{ V}$$


$$V_o = 12 \text{ V}$$

$$f_{sw} = 100 \text{ kHz}$$

$$R_{o,min} = 1.2 \Omega$$

$$\Delta i_L = 20 \%$$

$$\Delta v_o = \pm 2 \%$$

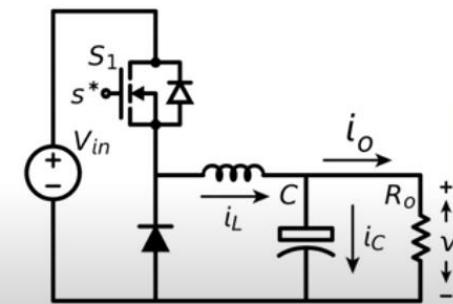

$$D = \frac{12 \text{ V}}{36 \text{ V}} = 0.33 \quad (4)$$

$$I_{L,max} = \frac{12 \text{ V}}{1.2 \Omega} = 10 \text{ A} \quad (5)$$



$$L = \frac{(36 \text{ V})(1 - 0.33)(0.33)}{(2 \text{ A})(100 \text{ kHz})} = 40 \mu\text{H} \quad (6)$$

$$C = \frac{(36 \text{ V})(1 - 0.33)(0.33)}{8(40 \mu\text{H})(0.48 \text{ V})(100 \text{ kHz})^2} = 5.21 \mu\text{F} \quad (7)$$

$$I_{LB} = I_{oB} = \frac{\Delta i_L}{2} = 1 \text{ A}$$

$$R_{oB} = \frac{V_o}{I_{oB}} = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$$

# Buck Converter: Simulation

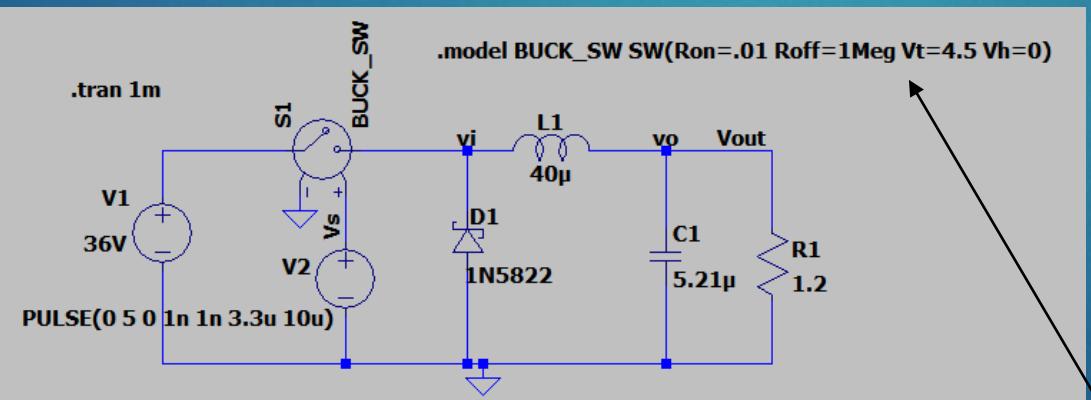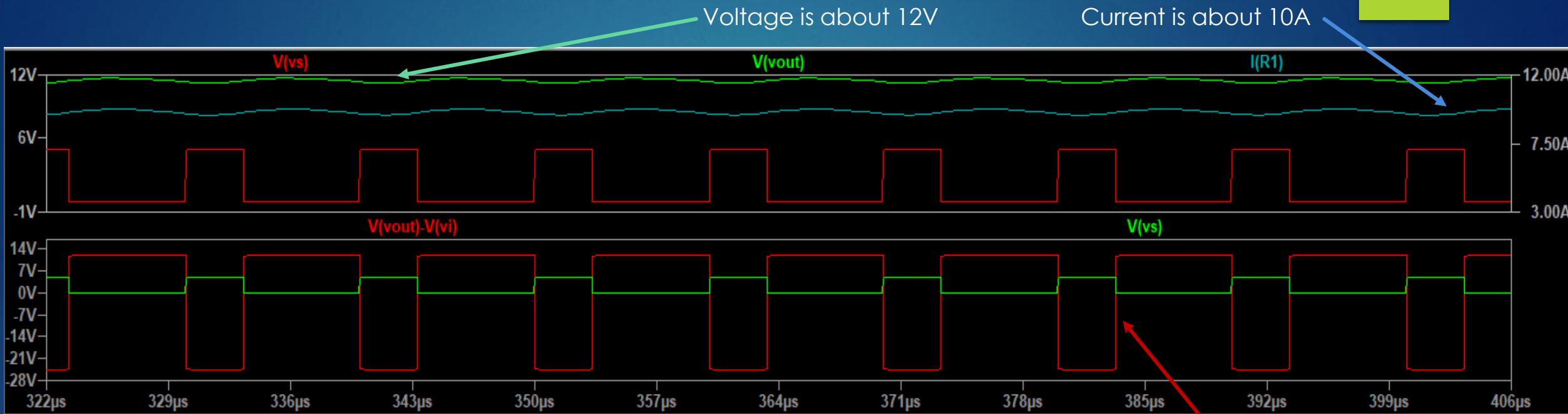


1. This is voltage across inductor ( $V_o - V_i$ )
2. Switch closed:
  - Inductor voltage is negative.
  - i.e.  $V_i > V_o$  (i.e. + to -)
3. Switch open:
  - Inductor voltage is positive.
  - i.e.  $V_o > V_i$  (i.e. - to +)




LTSpice Trick:

✓ right clk Select "Add Plot Plane"

# WTF?!

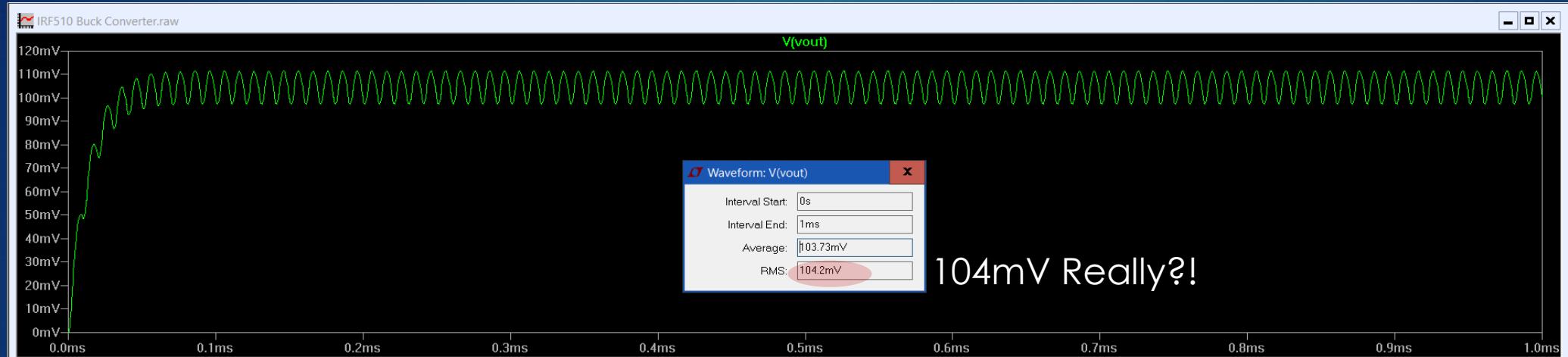

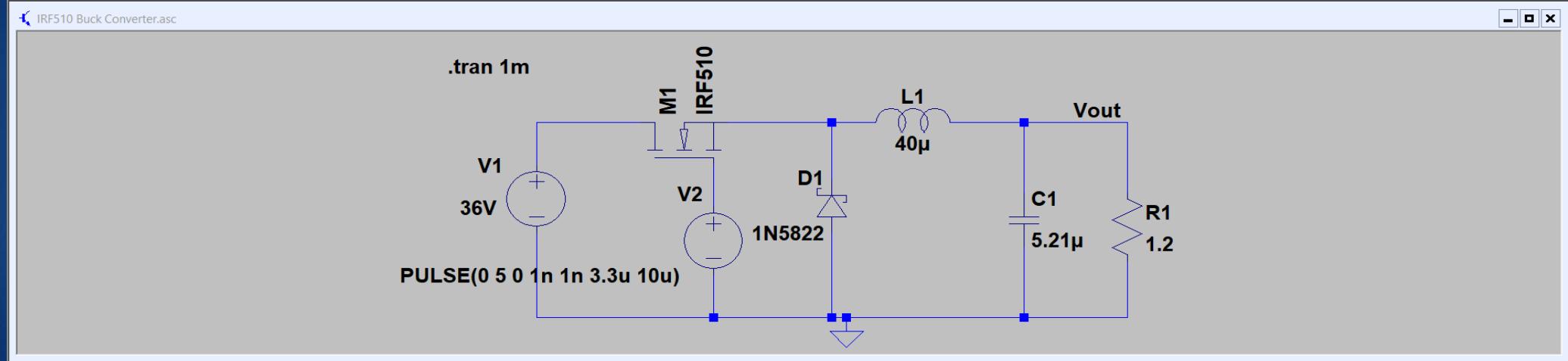LTSpice Trick:  
✓ `ctl + left clk` for RMS



After Rabbit Hole #3: Its actually "Vgs" Threshold. Gate voltage must be (at least) 4V higher than source voltage to turn on.



# Rabbit Hole #1: Inductors






This is something you probably already understood but may have forgotten or misunderstood....

# Agenda



1. Magnetic Fields around a Wire
2. Faraday's Law of Induction
3. Lenz's Law of Induced Magnetic Fields



# Magnetic Fields Around A Wire

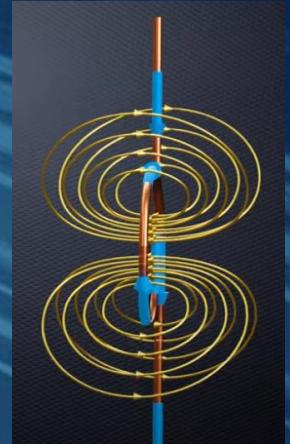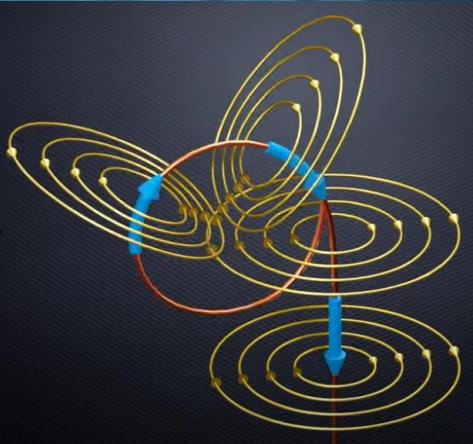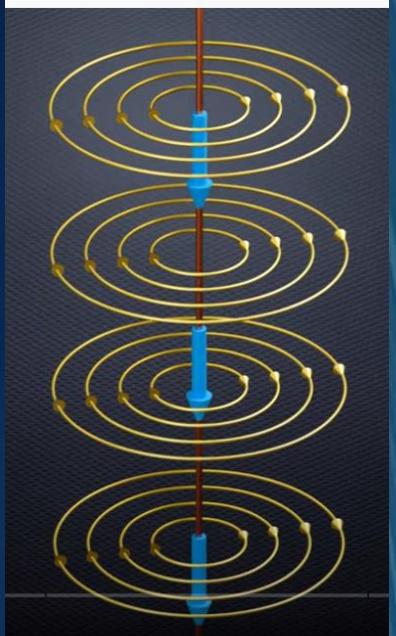


STEADY STATE: STATIC FIELD CREATED

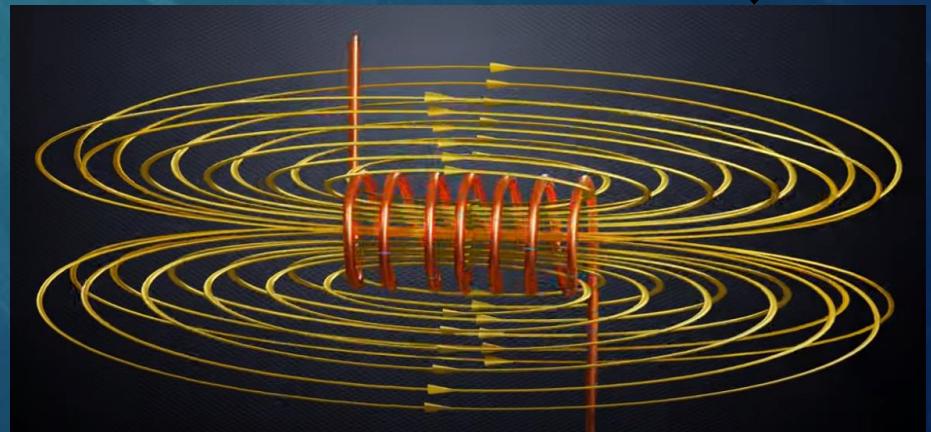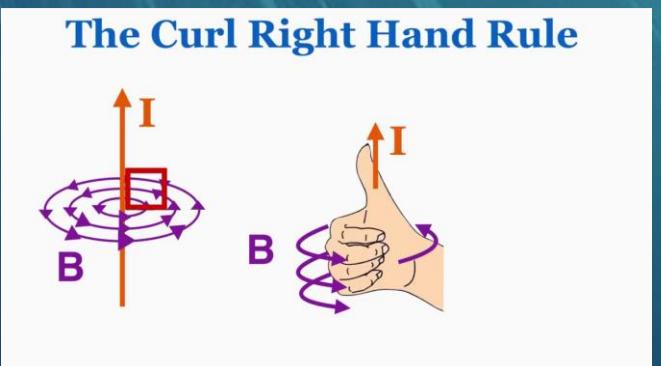


# Faraday's Law

## FARADAY'S LAW

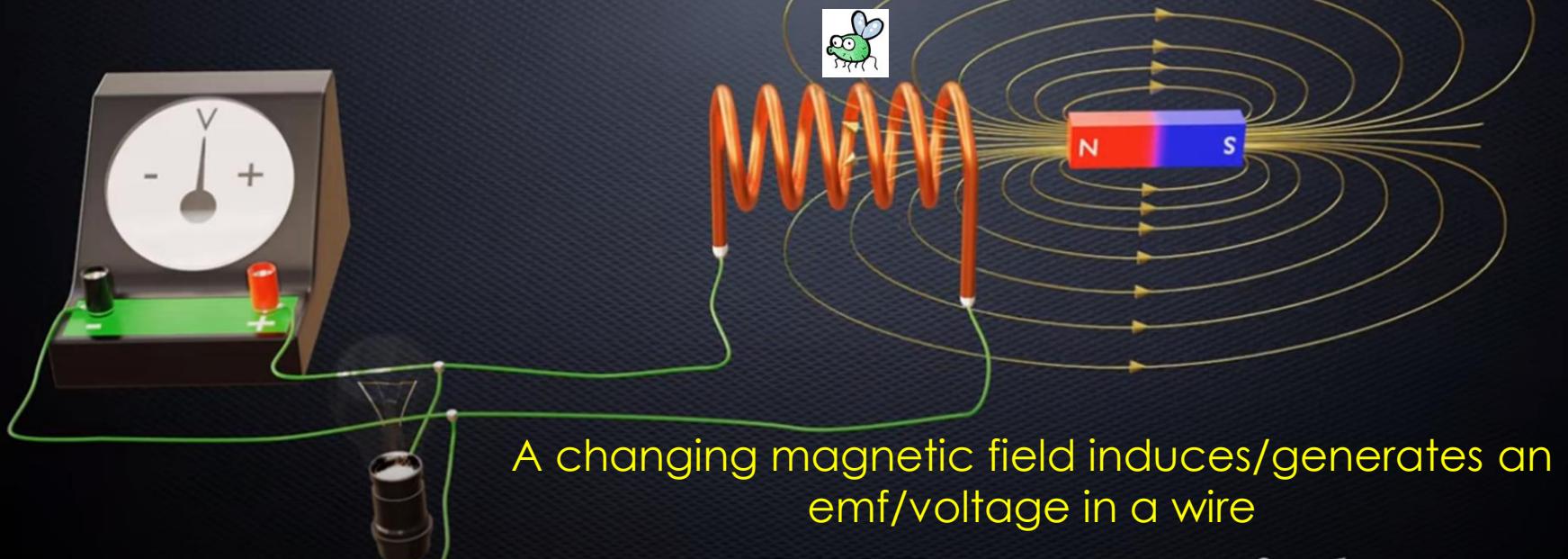


Motion of magnet creates a changing magnetic field

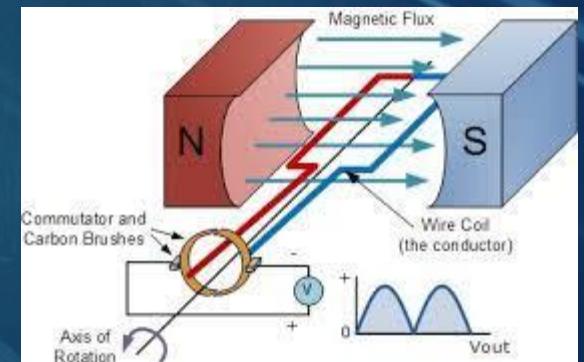Generator and Alternators generate voltages by spinning wire amateur inside a magnetic field




# Faraday's Law

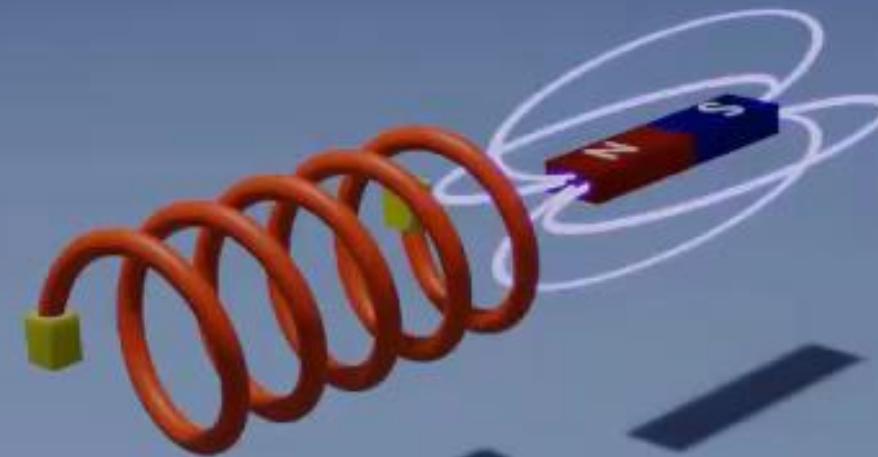


1. As magnetic field around permanent magnet moves near the coil, the coil "sees" a changing magnetic field.
2. An EMF and current is "induced" in the coil  
i.e., a changing magnetic field induces an EMF in a conductor (e.g., coil)

# Lenz's Law: Increasing Fields

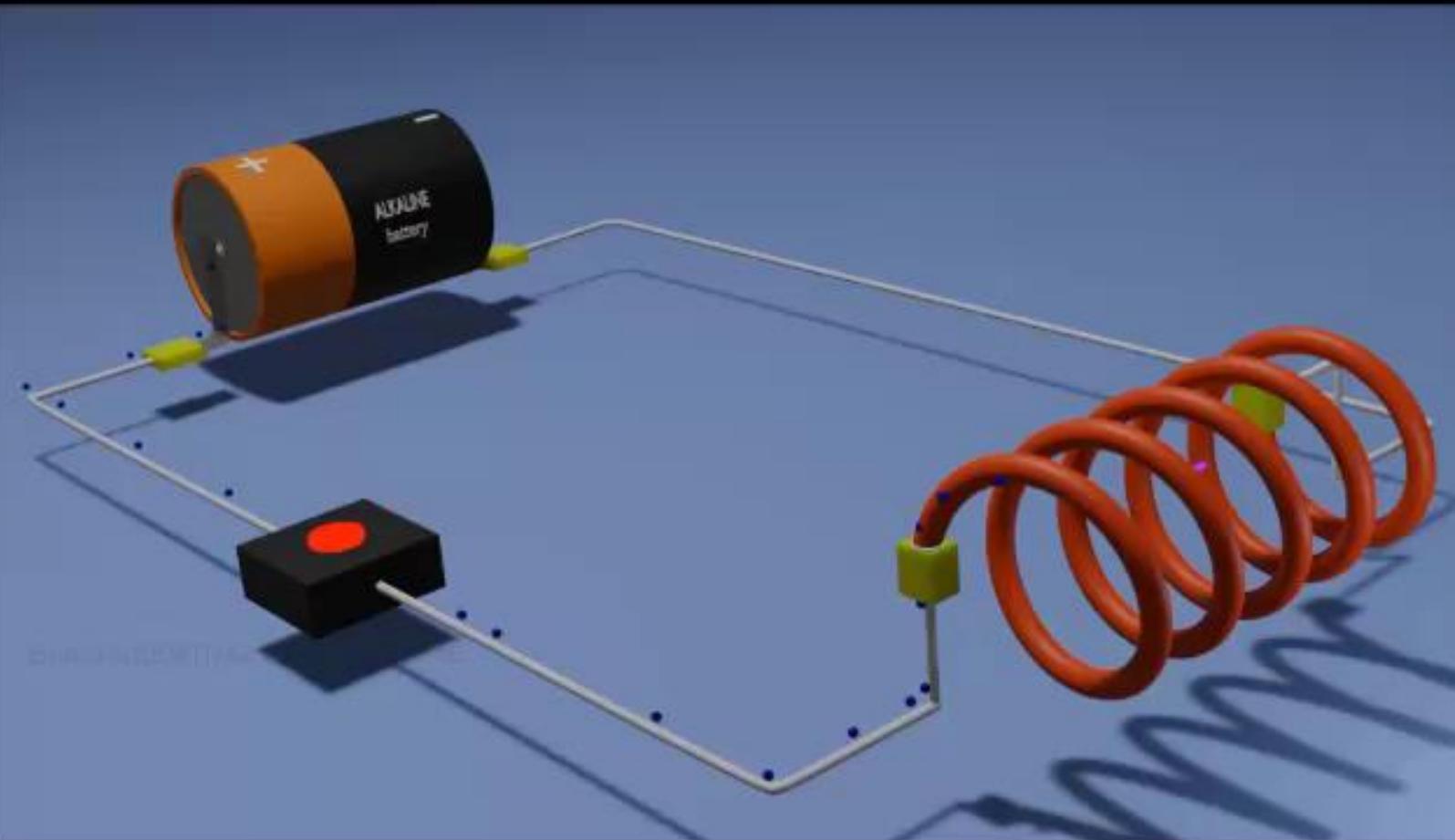

1. As current flows through the coil, a magnetic field builds.
  - ✓ Magnetic field not created instantly
2. The magnetic field changes and therefore induces an EMF and current based on Faraday's Law
  - ✓ This is called self induction.
3. Does the induced current field enhance or oppose the current from the battery?
4. Lenz's Law: The induced current imposes the original current.
  - ✓ Actually, the induced current generates a magnetic field that opposed the original magnetic field.
  - ✓ This is why we are told, "An inductor opposes a change in current"
5. With a DC source, the magnetic field eventually becomes constant. When constant, there is no induced current.


# Lenz's Law: Decreasing Fields

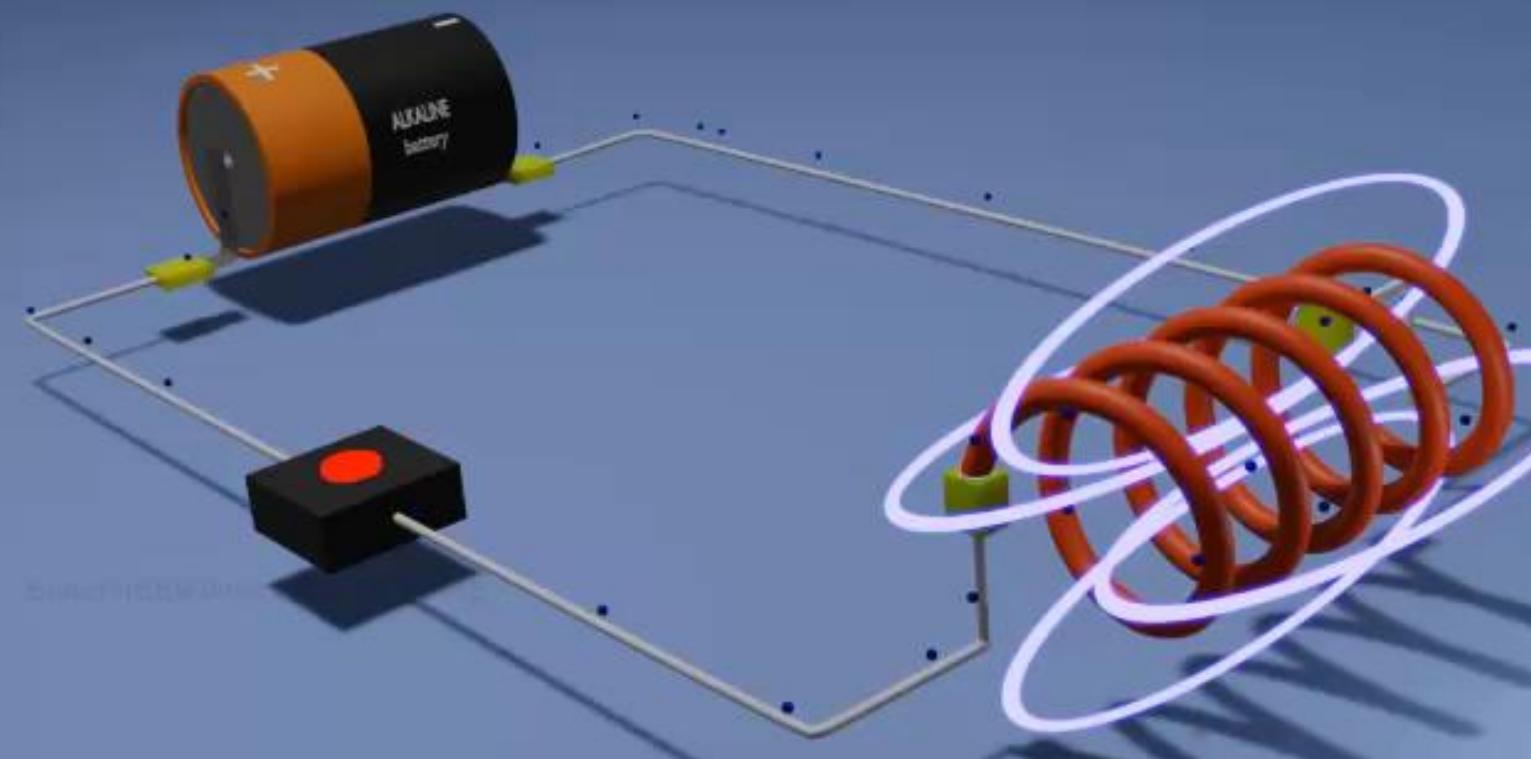


1. When current to inductor is turned off, the established static magnetic field reduces
2. The magnetic field changes and therefore induces an EMF and current based on Faraday's Law
  - ✓ This is called self induction.
3. Lenz's Law: The induced current imposes the original current.
4. If there is now path for the induced current to flow, the voltage can grow very large
  - ✓ This is why you need a diode across a relay coil.

# Increasing VS Decreasing Current

Increasing Field/Increasing Current

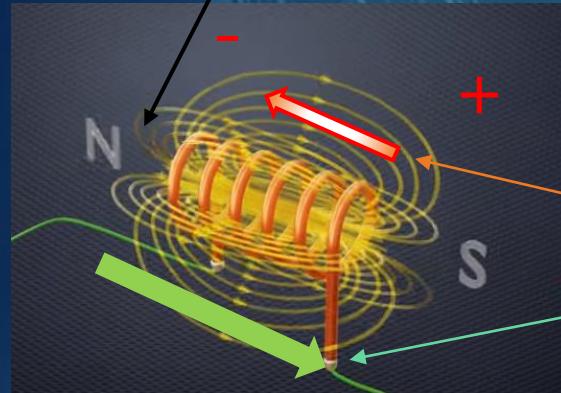

Decreasing Field/Decreasing Current


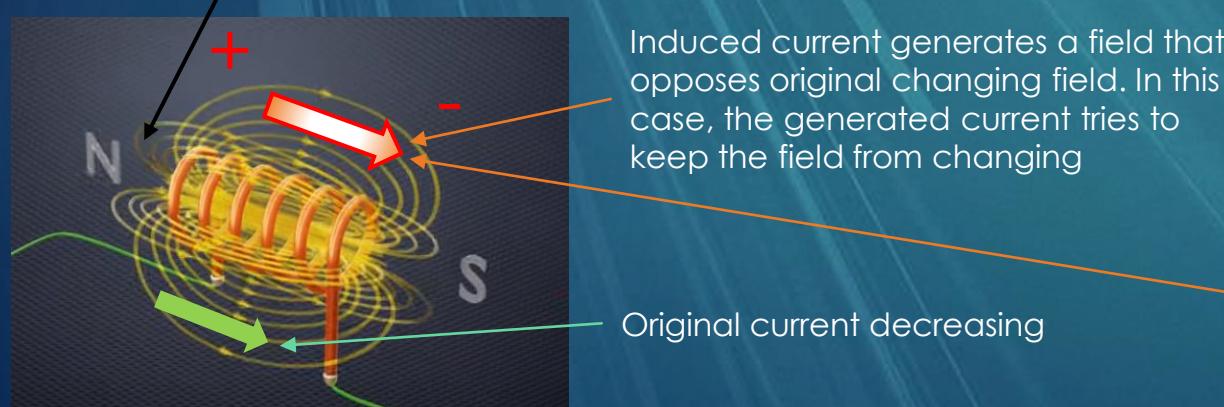


Lenz's Law: The induced current imposes the change in original current.


➤ The induced current generates a magnetic field that opposes the original magnetic field.

Note: If this current has no where to flow very large EMF results (large voltage)

# Charge & Discharge


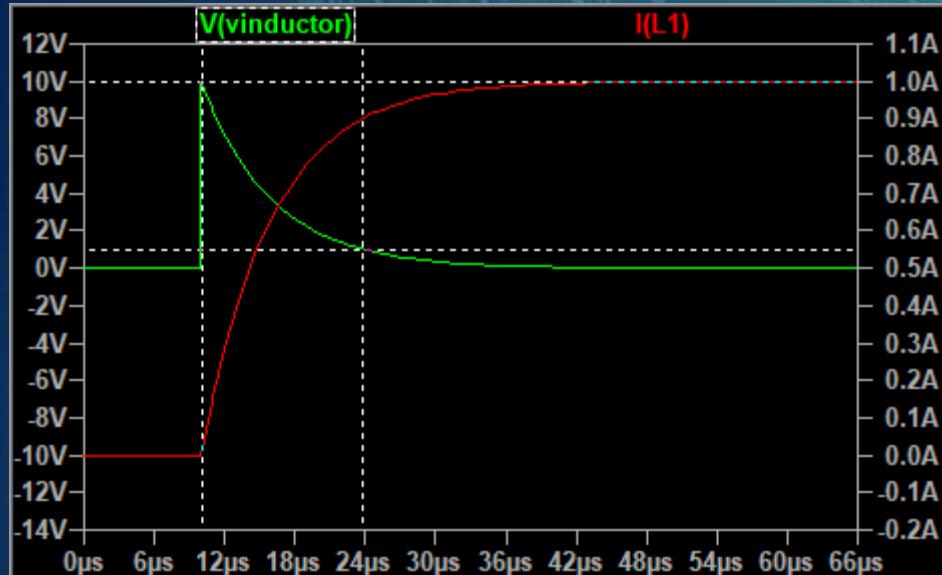
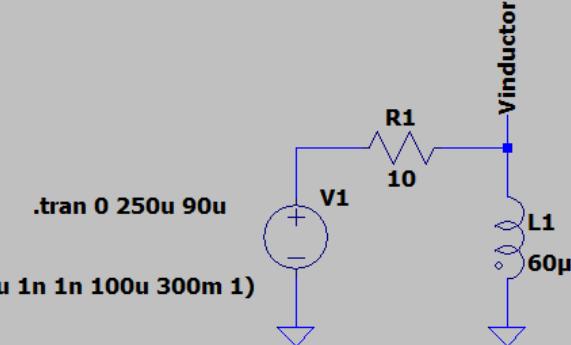


Cursor 1	V(vinductor)
Horz:	10.015848μs
Vert:	9.9744621V
Cursor 2	V(vinductor)
Horz:	23.81876μs
Vert:	1.0021487V
Diff (Cursor2 - Cursor1)	
Horz:	13.802912μs
Vert:	-8.9723134V
Freq:	72.44848KHz
Slope:	-650030

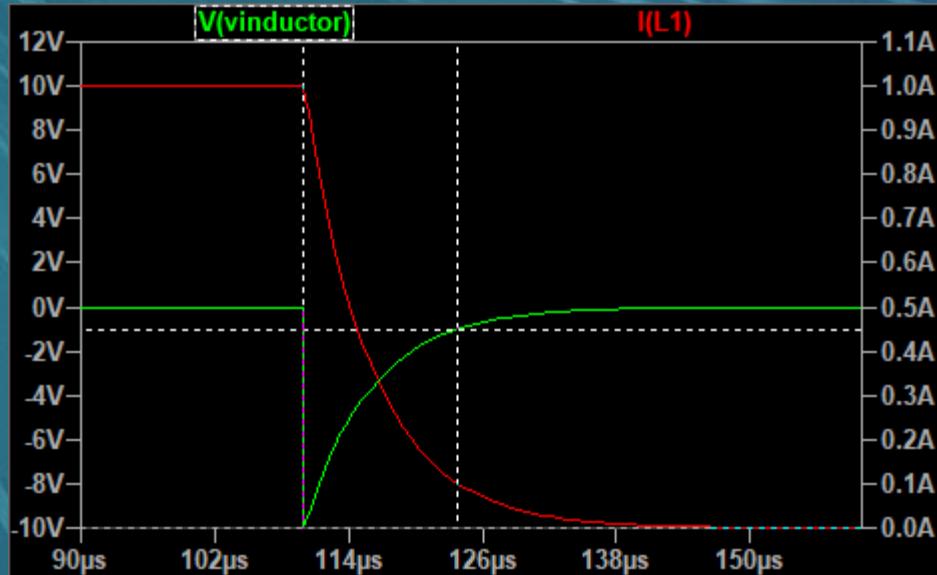

Cursor 1	V(vinductor)
Horz:	110.002μs
Vert:	-9.9981623V
Cursor 2	V(vinductor)
Horz:	123.74359μs
Vert:	-1.0138262V
Diff (Cursor2 - Cursor1)	
Horz:	13.74159μs
Vert:	8.9843361V
Freq:	72.771784KHz
Slope:	653806

# Summary:

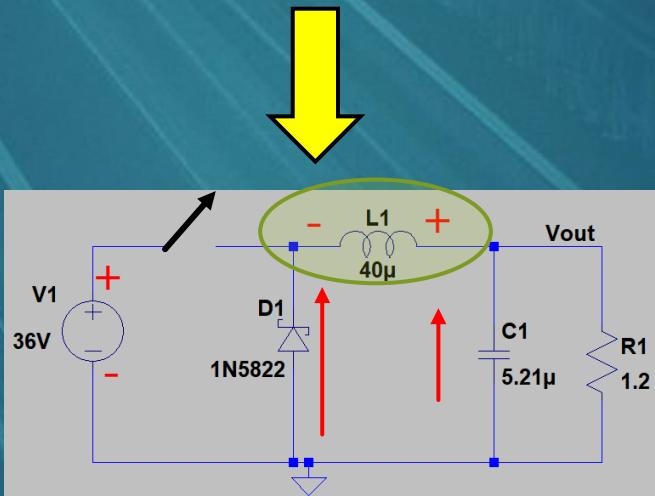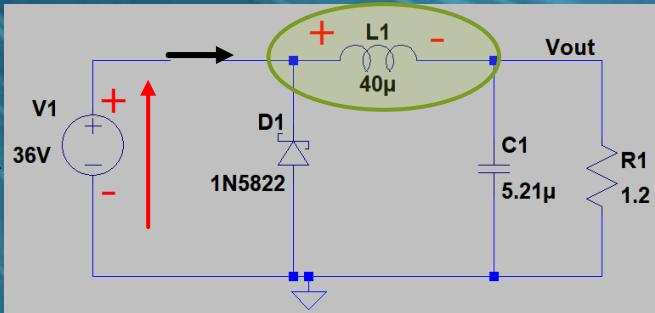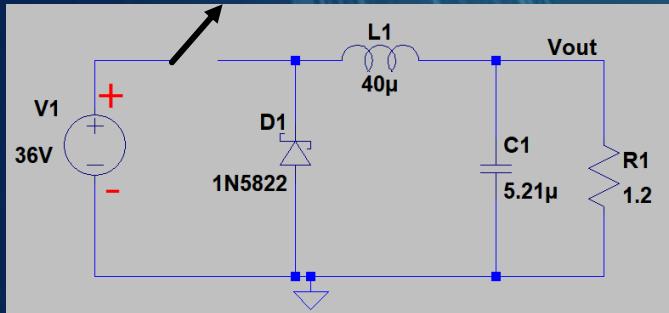

1. Switch Closed. Current slowly flows through inductor.
2. Inductor opposes current increase
3. Capacitor Charges
4. Current slowly increases through R1

1. Current rapidly decreases through inductor.
2. Inductor opposes current decrease
3. Capacitor and inductor act as a battery
4. Current continues to flow through R1


# Rabbit Hole #2: Mosfets



# Agenda

1. Mosfet Parameters and Buck Converter
2. High Side & Low Side Switching
3. Mosfet Construction
4. Capacitance
5. Mosfet Model in LTSpice

# Recall: Buck Converter Design

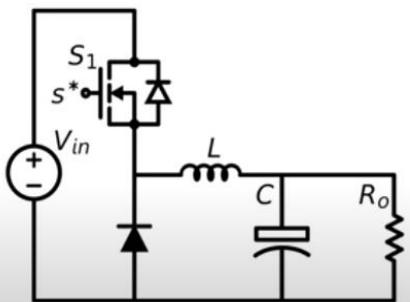

$$V_{in} = 36 \text{ V}$$


$$V_o = 12 \text{ V}$$

$$f_{sw} = 100 \text{ kHz}$$

$$R_{o,min} = 1.2 \Omega$$

$$\Delta i_L = 20 \%$$

$$\Delta v_o = \pm 2 \%$$

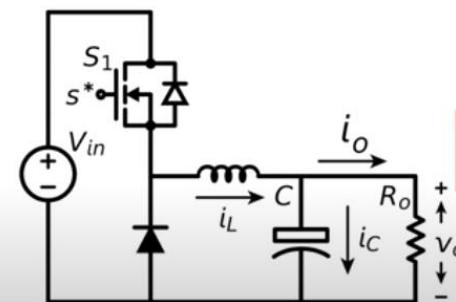

$$D = \frac{12 \text{ V}}{36 \text{ V}} = 0.33 \quad (4)$$

$$I_{L,max} = \frac{12 \text{ V}}{1.2 \Omega} = 10 \text{ A} \quad (5)$$




$$L = \frac{(36 \text{ V})(1 - 0.33)(0.33)}{(2 \text{ A})(100 \text{ kHz})} = 40 \mu\text{H} \quad (6)$$

$$C = \frac{(36 \text{ V})(1 - 0.33)(0.33)}{8(40 \mu\text{H})(0.48 \text{ V})(100 \text{ kHz})^2} = 5.21 \mu\text{F} \quad (7)$$

$$I_{LB} = I_{oB} = \frac{\Delta i_L}{2} = 1 \text{ A}$$

$$R_{oB} = \frac{V_o}{I_{oB}} = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$$

# In our last episode...

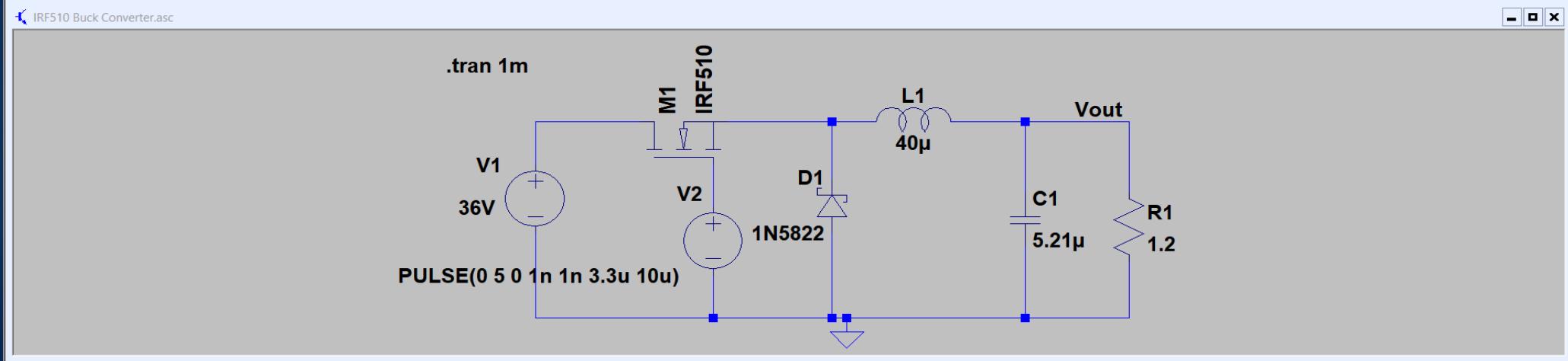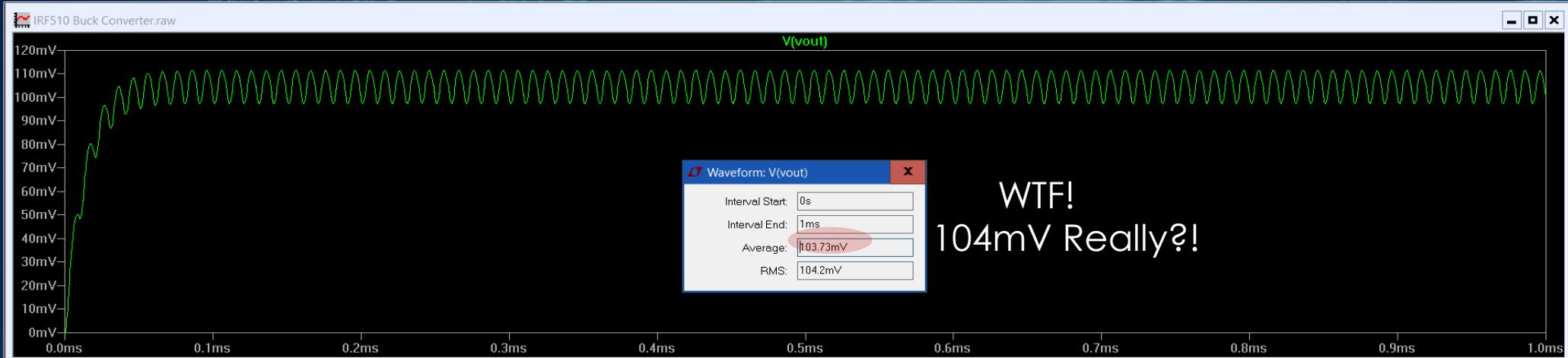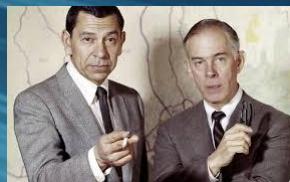

Its actually "Vgs" Threshold.

Gate voltage must be (at least) 4V higher than source voltage to turn on.


# Key Parameters for Buck Converter

## SPECIFICATIONS ( $T_J = 25^\circ\text{C}$ , unless otherwise noted)


PARAMETER	SYMBOL	TEST CONDITIONS	MIN.	TYP.	MAX.	UNIT
<b>Static</b>						
Drain-source breakdown voltage	$V_{DS}$	$V_{GS} = 0 \text{ V}, I_D = 250 \mu\text{A}$	100	-	-	V
$V_{DS}$ temperature coefficient	$\Delta V_{DS}/T_J$	Reference to $25^\circ\text{C}$ , $I_D = 1 \text{ mA}$	-	0.12	-	$^\circ\text{C}$
Gate-source threshold voltage	$V_{GS(\text{th})}$	$V_{DS} = V_{GS}, I_D = 250 \mu\text{A}$	2.0	-	4.0	V
Gate-source leakage	$I_{GSS}$	$V_{GS} = \pm 20 \text{ V}$	-	-	$\pm 100$	nA
Zero gate voltage drain current	$I_{DSS}$	$V_{DS} = 100 \text{ V}, V_{GS} = 0 \text{ V}$	-	-	25	$\mu\text{A}$
		$V_{DS} = 80 \text{ V}, V_{GS} = 0 \text{ V}, T_J = 150^\circ\text{C}$	-	-	250	
Drain-source on-state resistance	$R_{DS(on)}$	$V_{GS} = 10 \text{ V}$   $I_D = 3.4 \text{ A}^b$	-	-	0.54	$\Omega$
Forward transconductance	$g_{fs}$	$V_{DS} = 50 \text{ V}, I_D = 3.4 \text{ A}^b$	1.3	-	-	S

1. Gate threshold ( $V_{GS}$ ) is relative to source.
  - ✓ E.g. If Source Grounded, Gate needs to be between 2 to 4 Volts
  - ✓ E.g. If Source is at 5V, Gate needs to be between 7 to 9 Volts
2. If  $V_{GS}$  is 10V, and  $I_D$  is 3.4A,  $R_{ON}$  is 0.54 ohms


# High Side vs Low Side Mosfet Switch

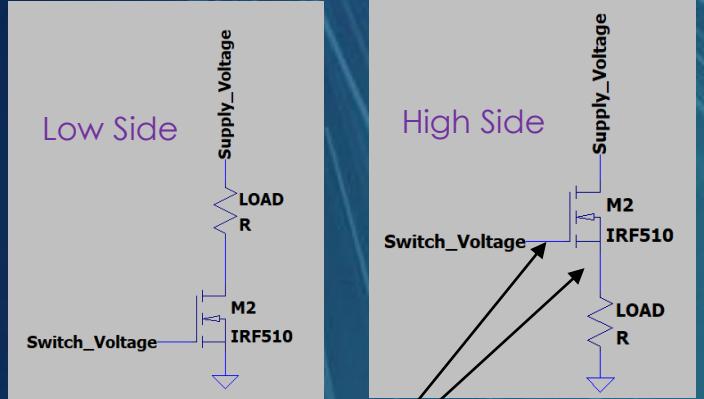


$V_g \gg V_s$  by  $V_{gs}$

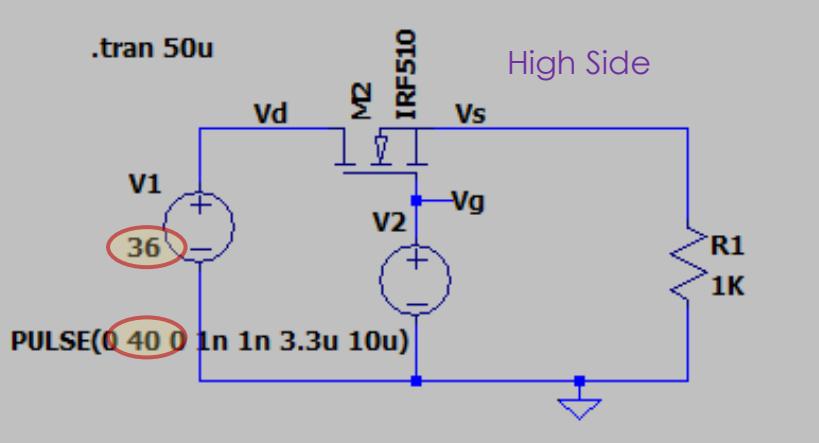

$V_g \gg V_s$  by  $V_{gs}=4V$

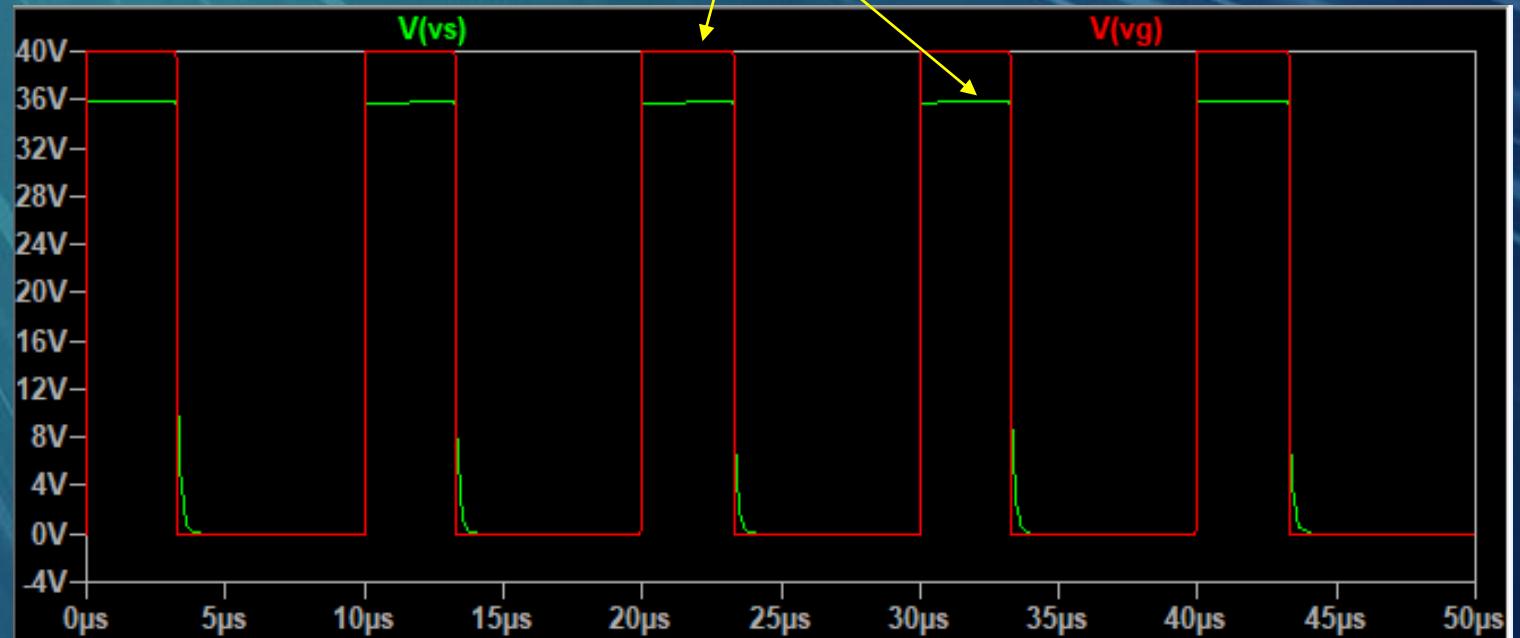


# Back to the Buck...


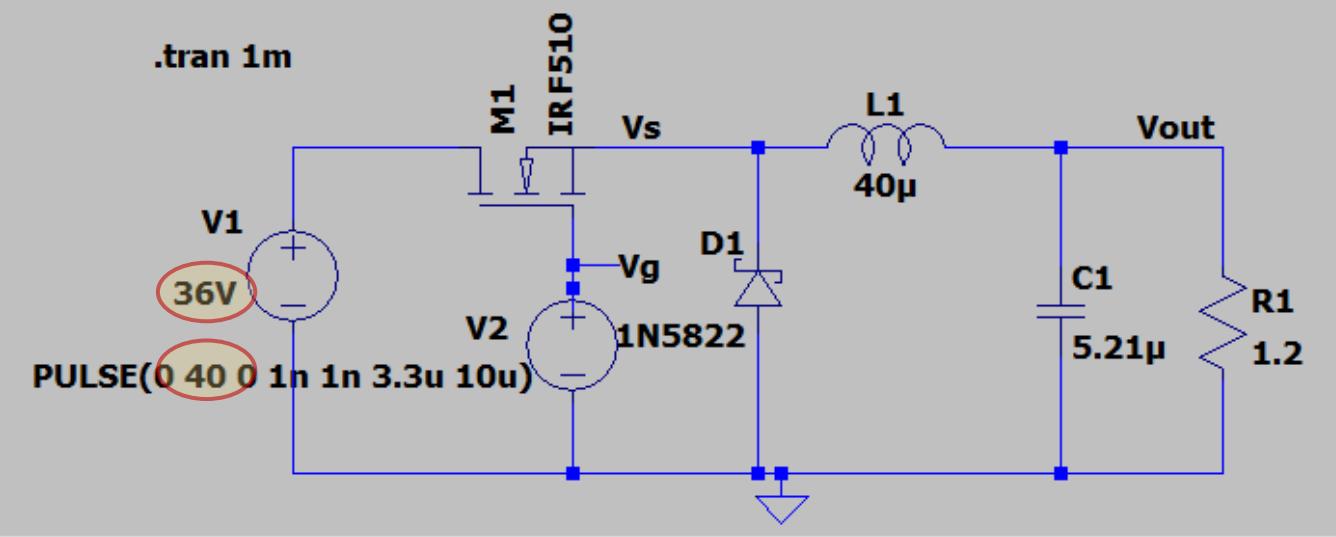


Huh? 8ish A?  
Should be 10A

Huh? 10V?  
Should be 12V

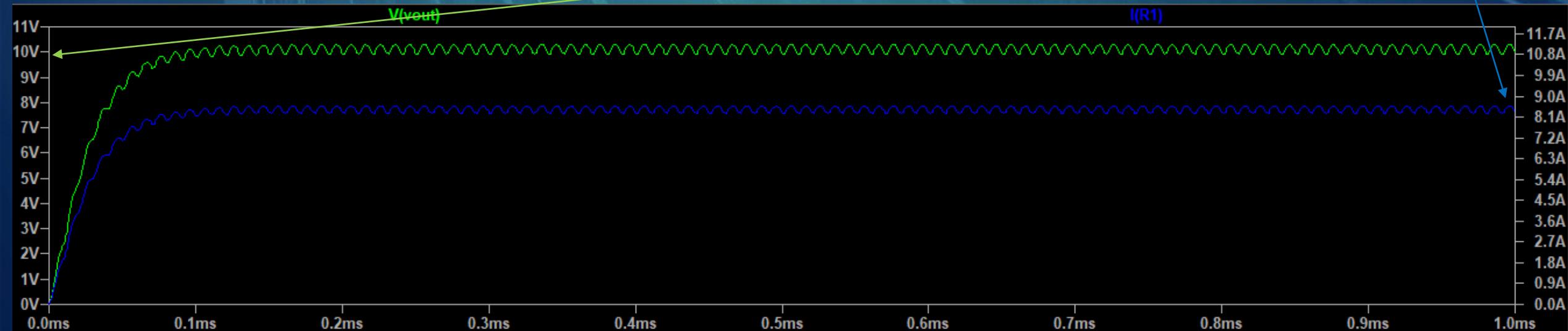


# Doh....

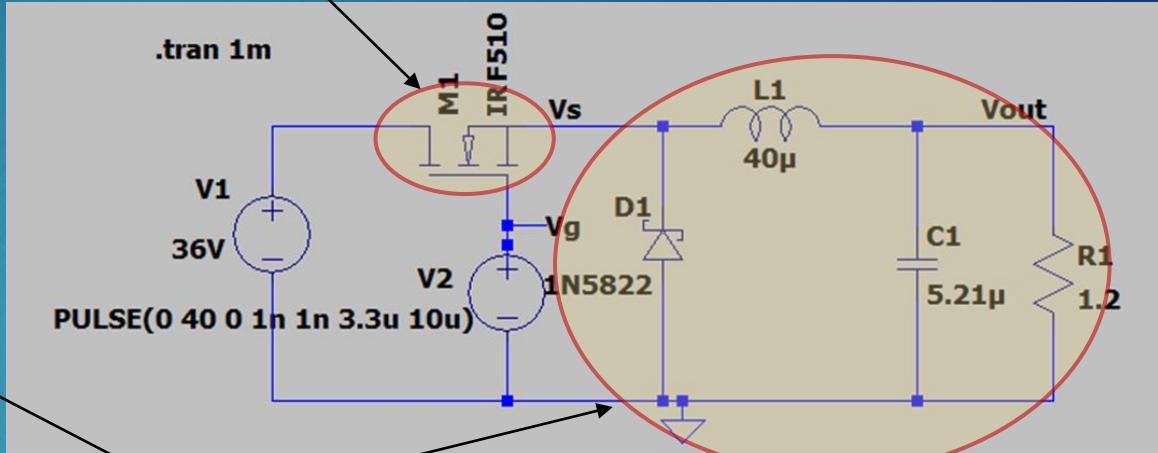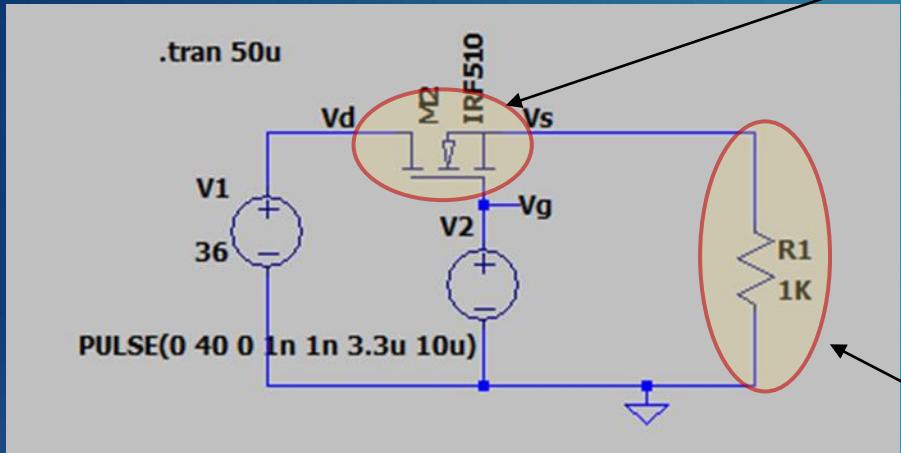

R1

R2

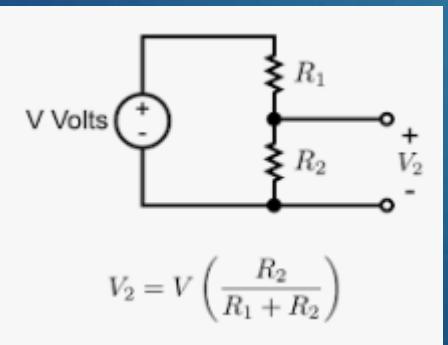

Drain-source on-state resistance

$R_{DS(on)}$

$V_{GS} = 10\text{ V}$



$I_D = 3.4\text{ A}^b$

R1


0.54

$\Omega$




# SUCCESS!!!!!!

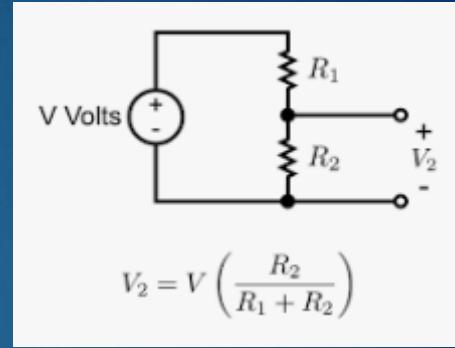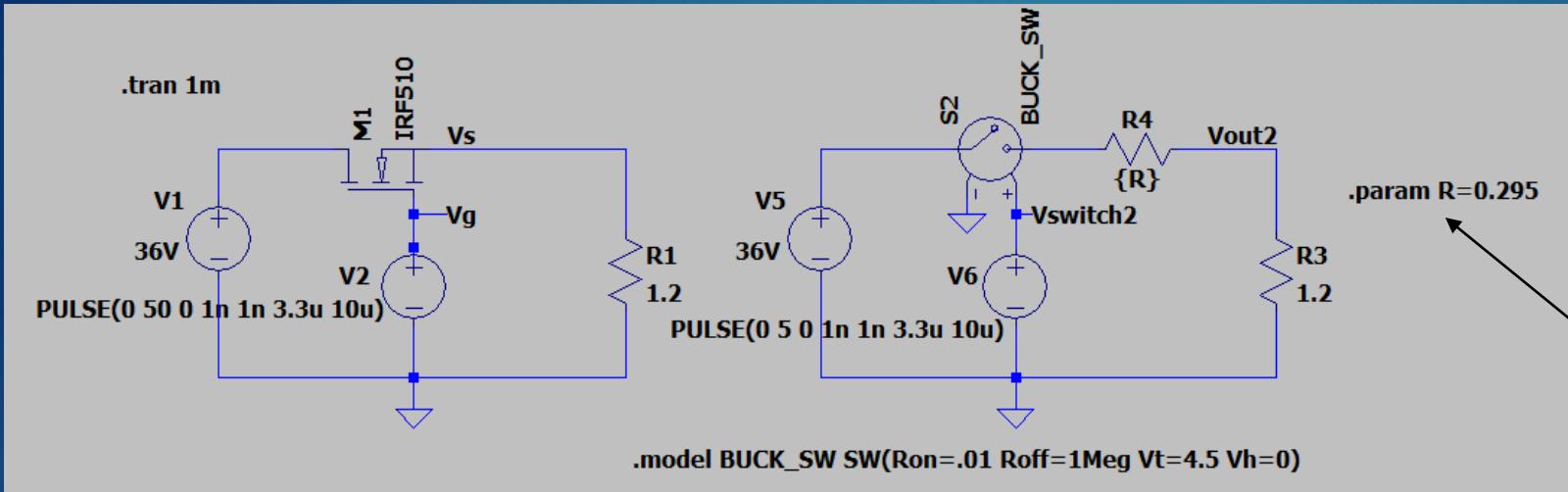

With some math...Ron is 0.3 ohms

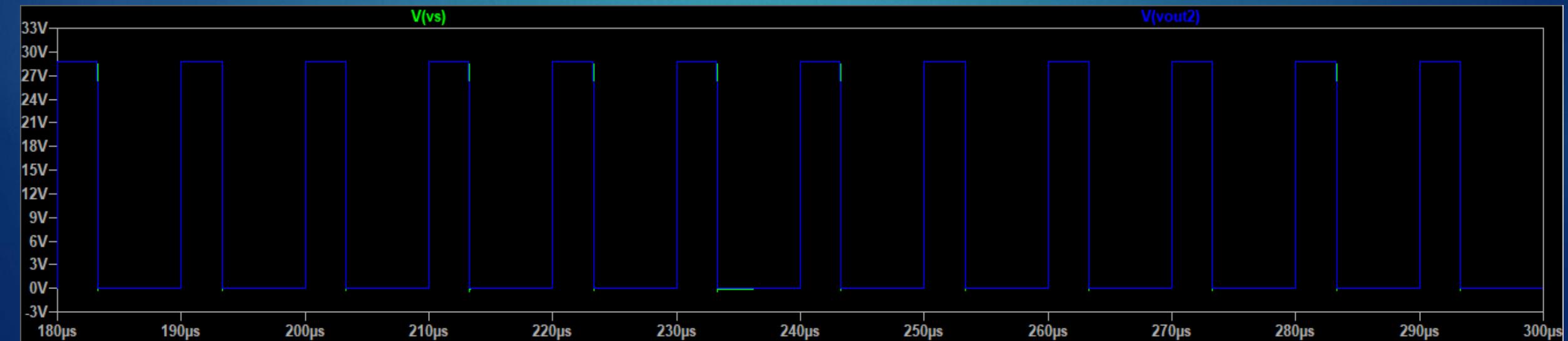

# High Side Bootstrap

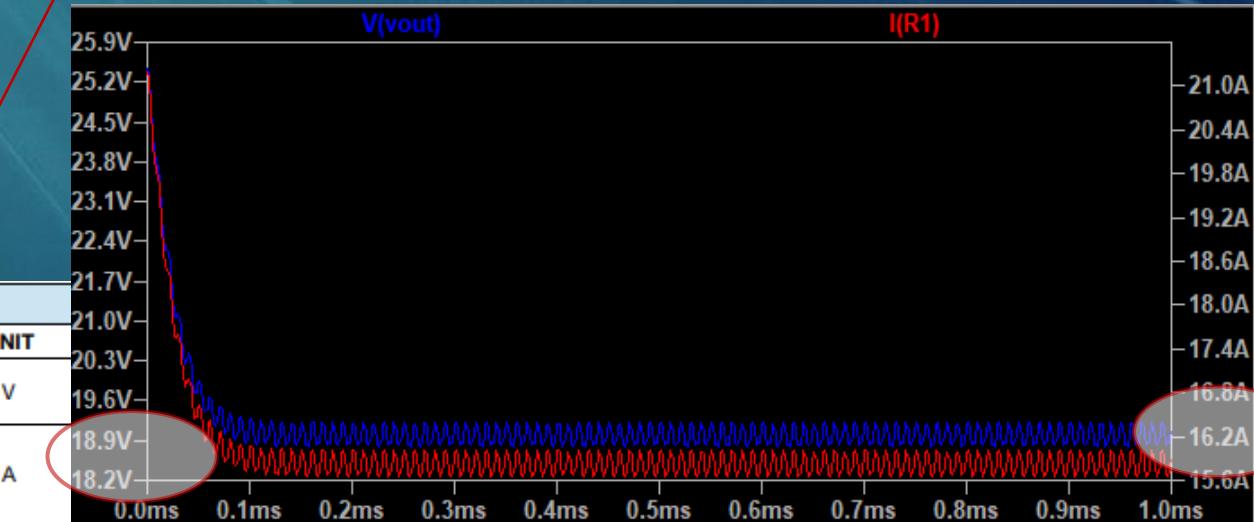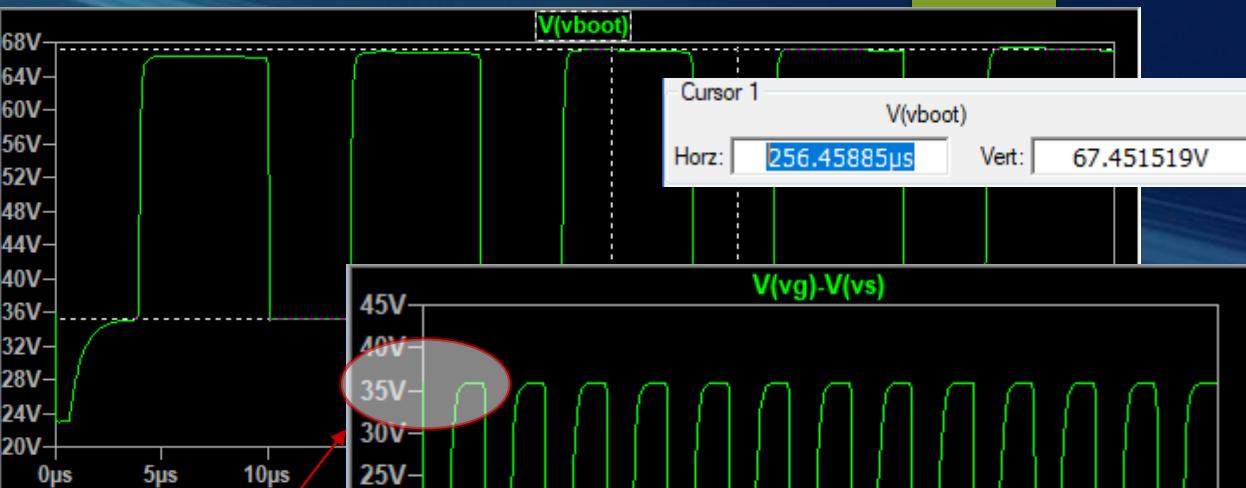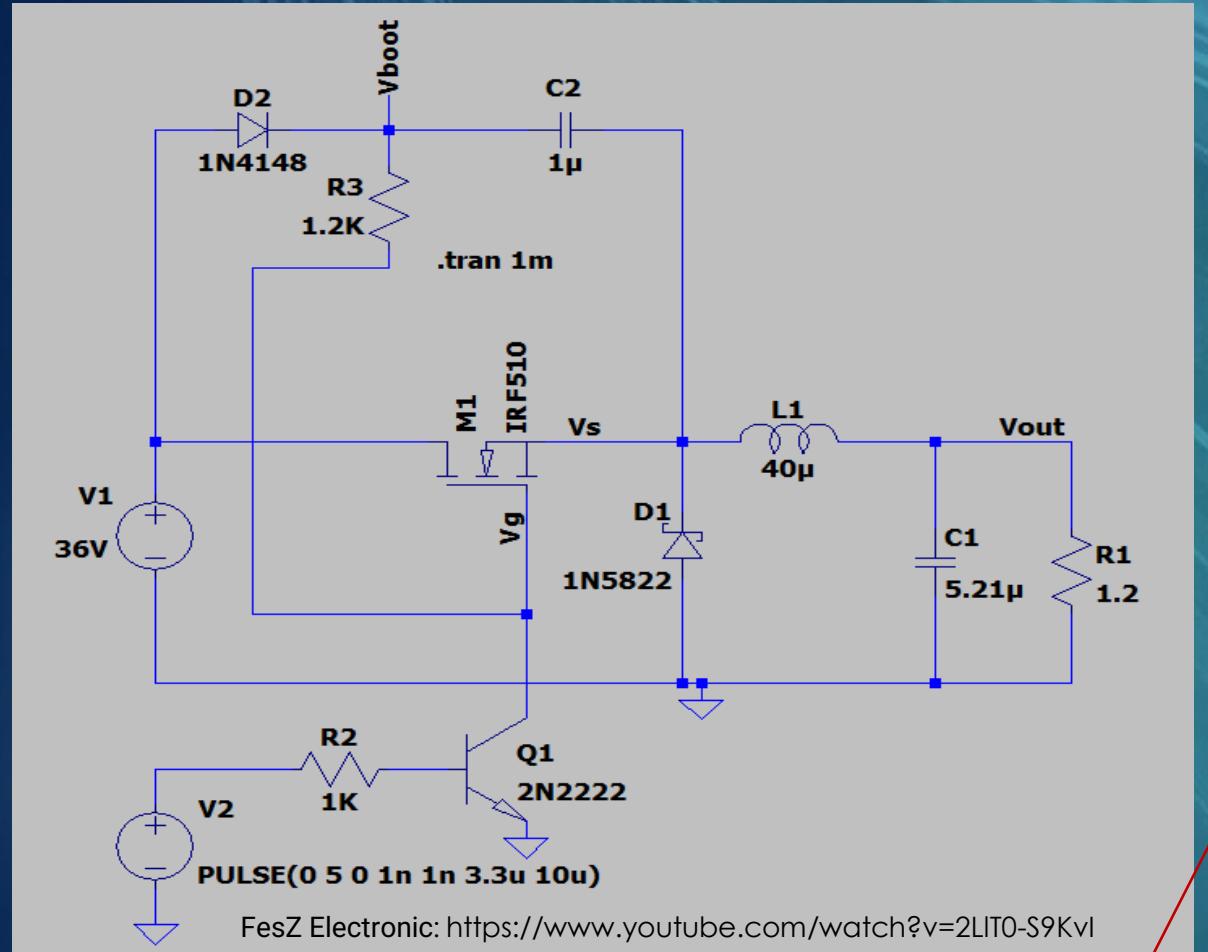

## ABSOLUTE MAXIMUM RATINGS ( $T_C = 25^\circ\text{C}$ , unless otherwise noted)

PARAMETER	SYMBOL	LIMIT	UNIT
Drain-source voltage	$V_{DS}$	100	V
Gate-source voltage	$V_{GS}$	$\pm 20$	V
Continuous drain current	$I_D$	5.6	A
		4.0	
Pulsed drain current <sup>a</sup>	$I_{DM}$	20	A
		18.9	
		18.2	

<sup>a</sup> Continuous drain current rating at  $T_C = 25^\circ\text{C}$ . Pulsed drain current rating at  $T_C = 100^\circ\text{C}$ .

# Proper Buck Converter



Voltage Divider  
to produce  $V_g$   
so that  $V_s$  is 36V

LTS spice Trick:

- ✓ Press ALT Key + Click component (pwr plot)
- ✓ Press CTL Key + Click on trace (integrate/rms)


Interval Start:	0s
Interval End:	1ms
Average:	99.044W
Integral:	99.044mJ

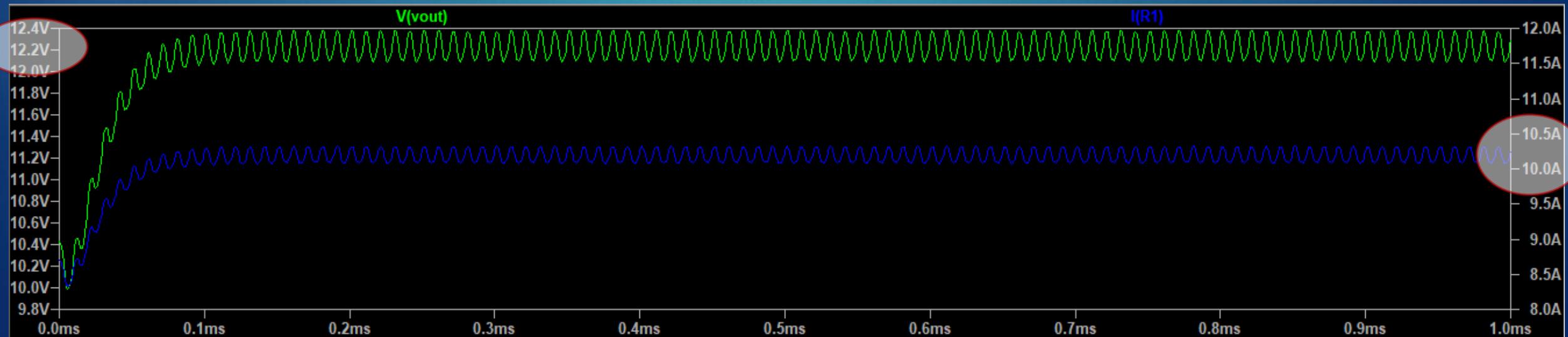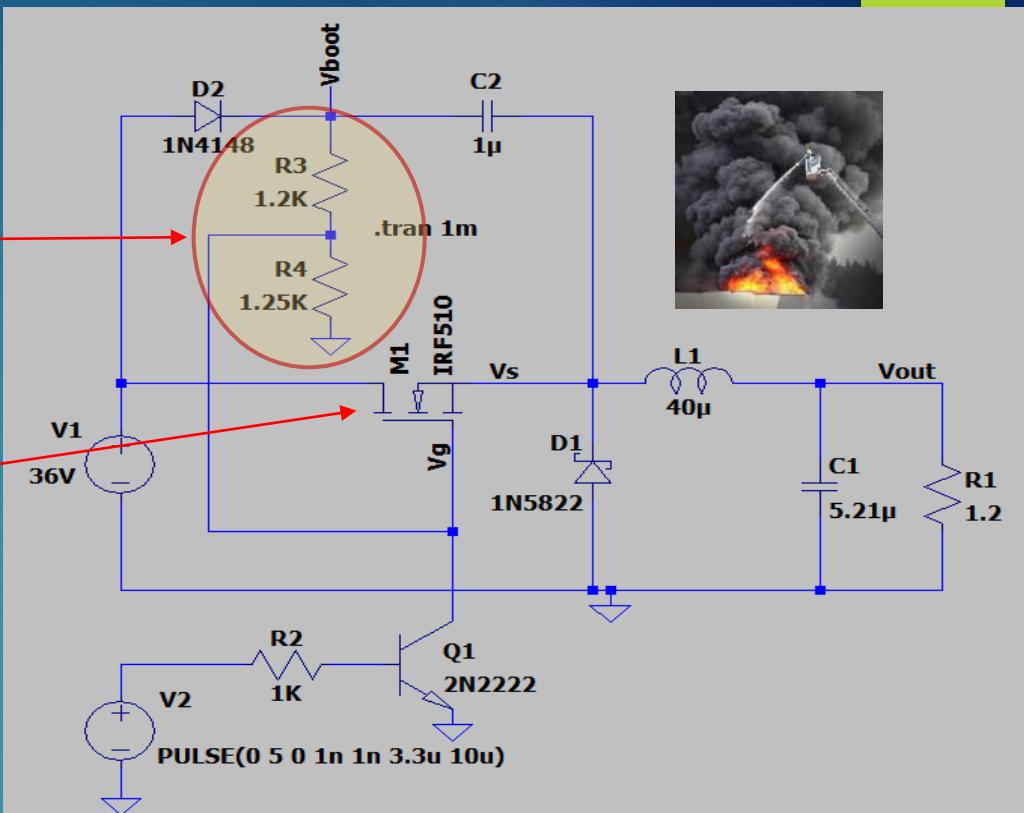Maximum power dissipation       $T_C = 25^\circ\text{C}$        $P_D$       43      W





# MOSFET CONSTRUCTION

N Channel  
Enhancement Mode


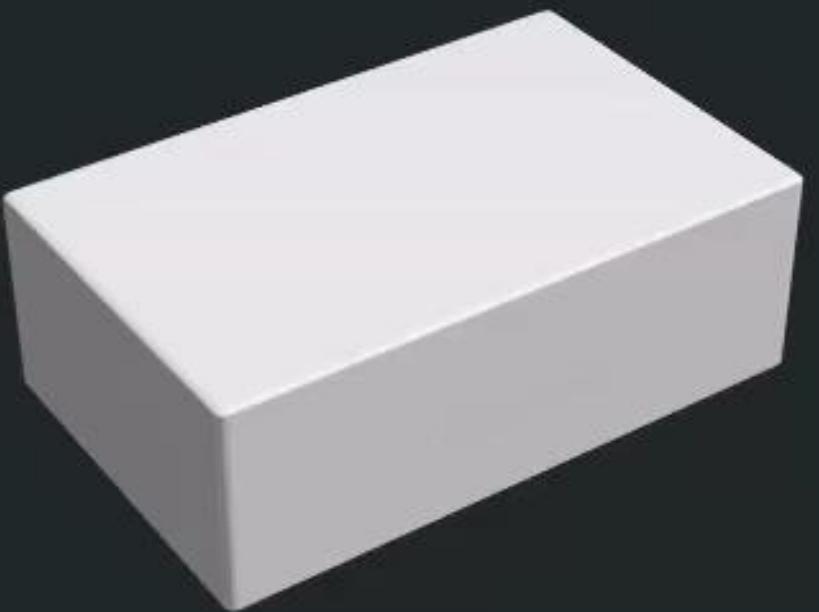


1. Created by applying two “N” doped semiconductors to a based on “P” doped semiconductor
2. N-Doped has impurity added with excess electrons and P-Doped has impurity added with more holes (missing electrons)
3. The N doped semiconductors are source and drain (Collector/Emitter)
4. A metal plate with an insulator is added to the P-doped base to create a capacitor.
5. When a voltage is applied to the gate with **respect to the source**, elections are attracted to the gate, and a channel is formed.
6. Once a threshold gate voltage is applied, current flows between drain and source



# Capacitors

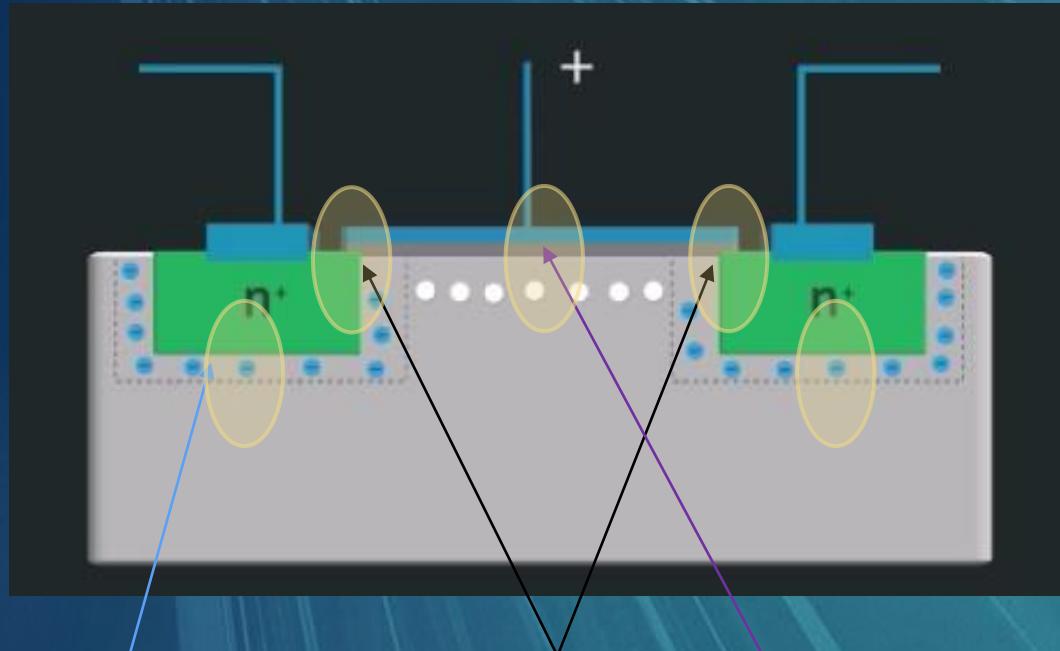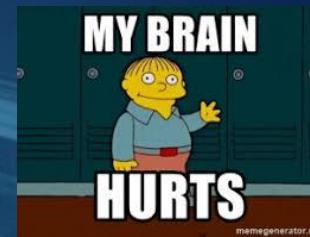

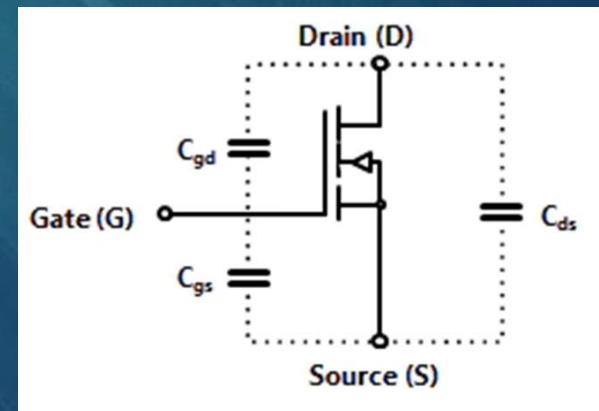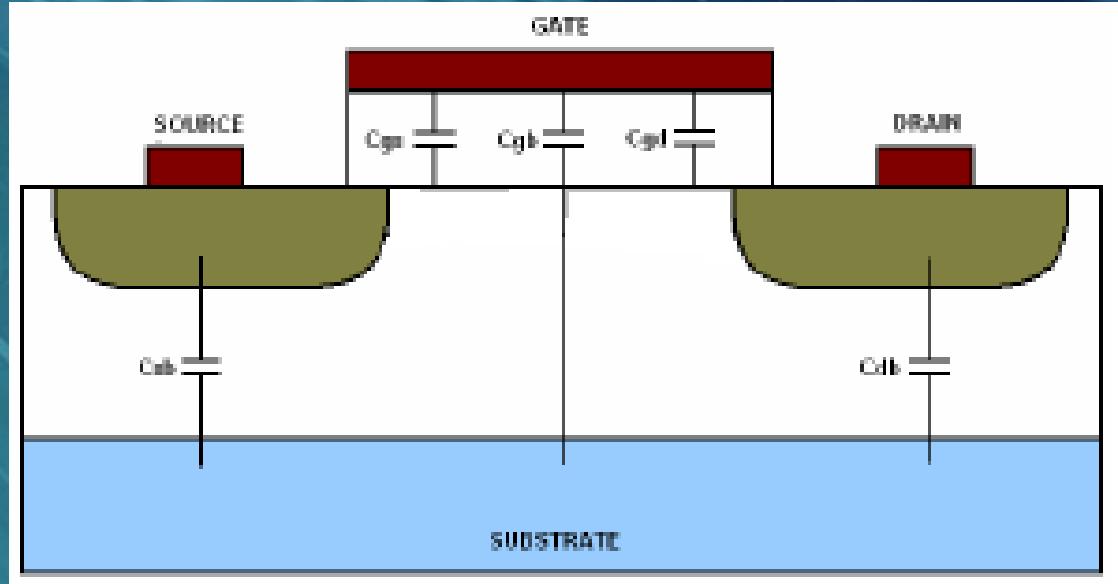Depletion region      Overlap      Oxide/dielectric




# MOSFET CAPACITANCE DEFINED

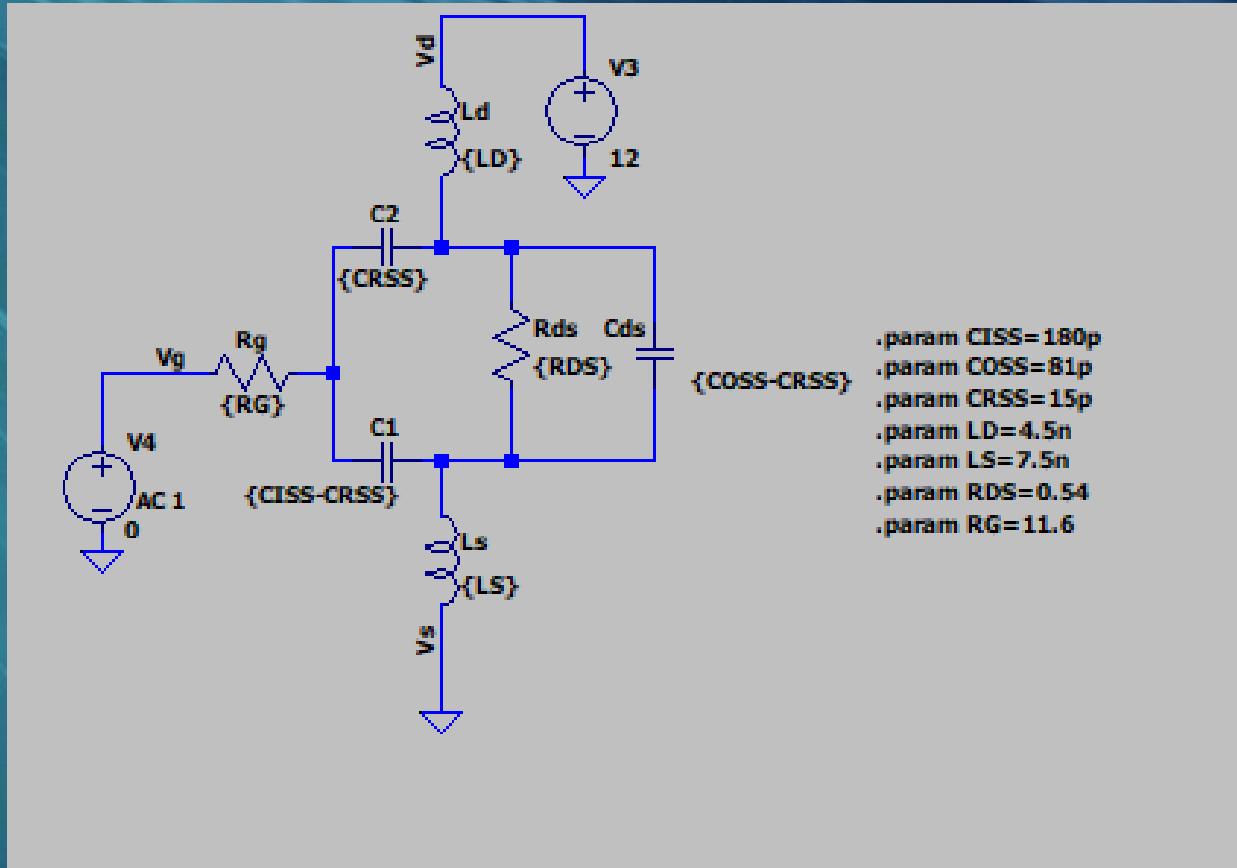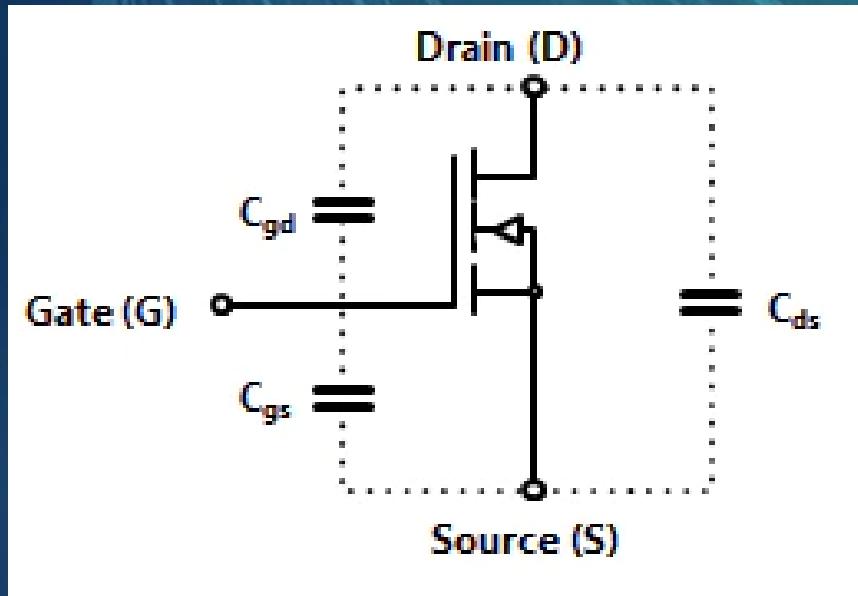


Dynamic		$V_{GS} = 0 \text{ V},$ $V_{DS} = 25 \text{ V},$ $f = 1.0 \text{ MHz, see fig. 5}$		$\text{pF}$
Input capacitance	$C_{iss}$			
Output capacitance	$C_{oss}$			
Reverse transfer capacitance	$C_{rss}$			

# Model Comparison

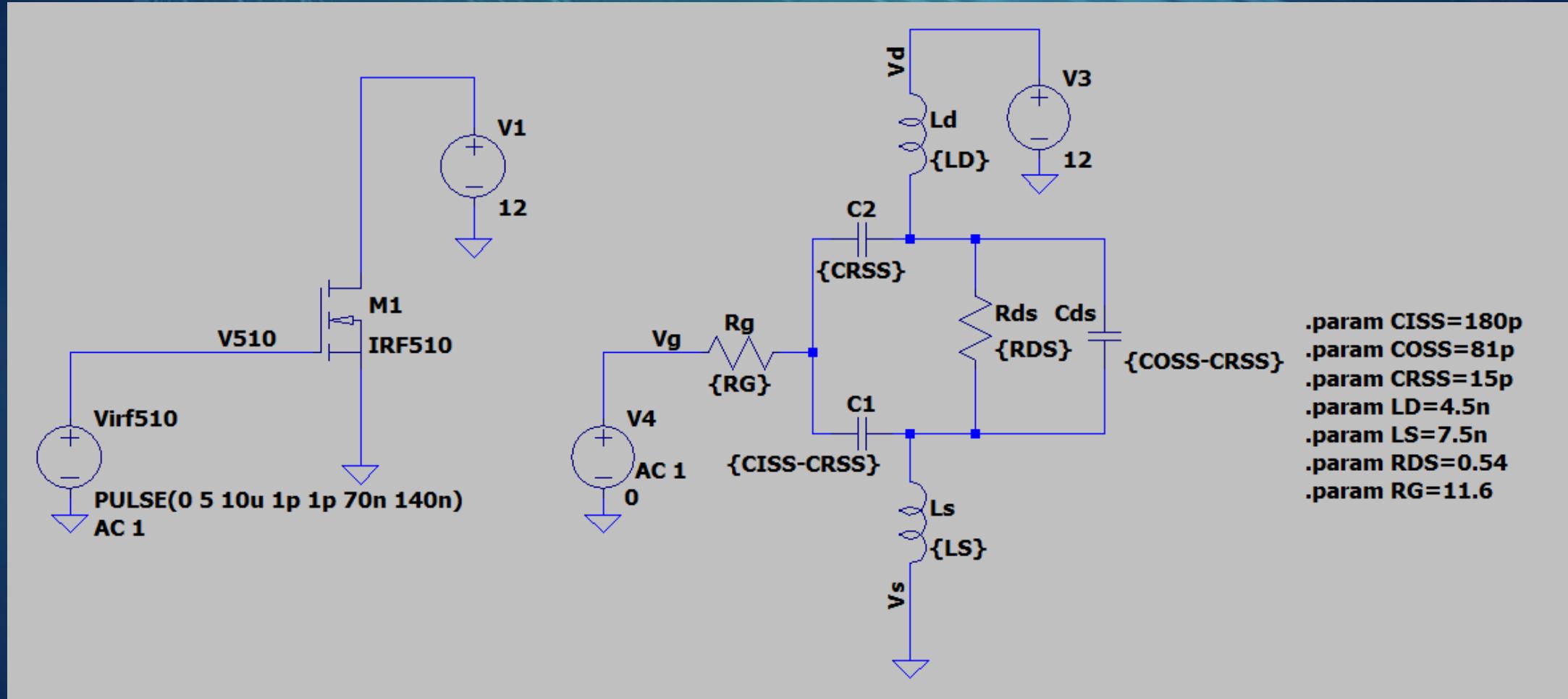


# Winner... Winner...

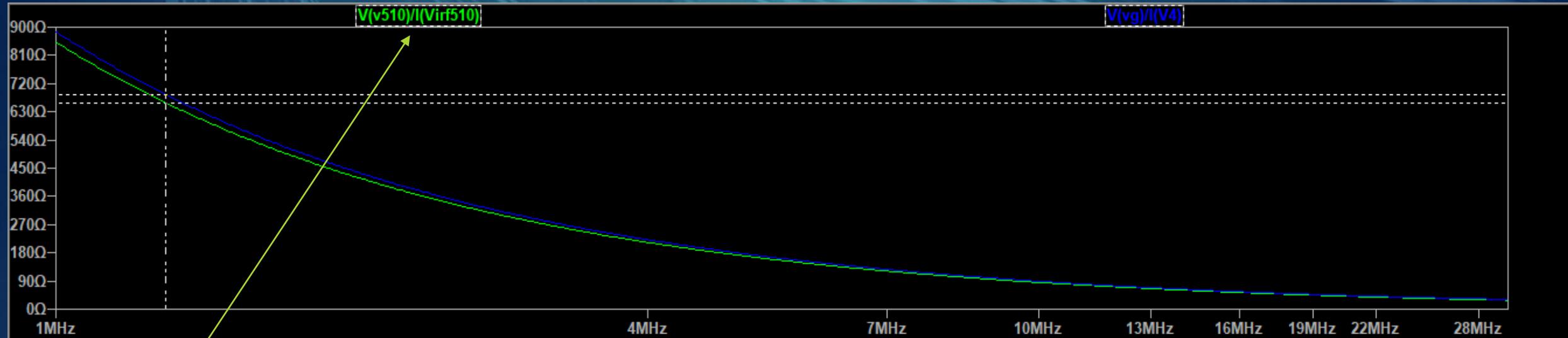



LTSpice Trick:

- ✓ right clk Select "Add Plot"
- ✓ select what you want to plot
- ✓ Can use \* / + - fun()

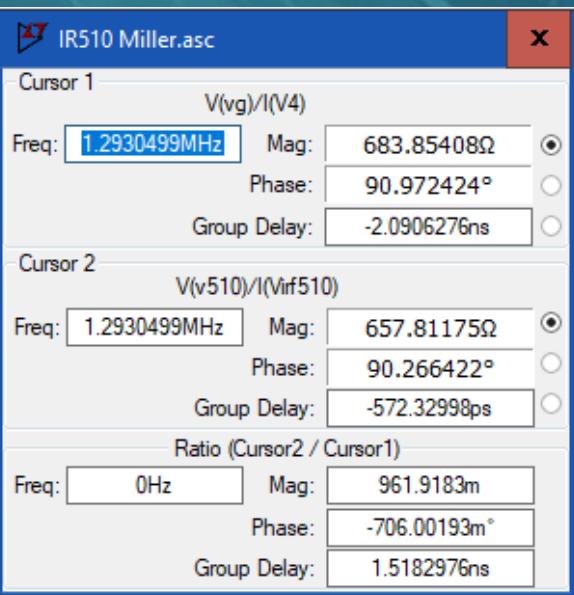[http://ltwiki.org/index.php?title=Waveform\\_Arithmetic](http://ltwiki.org/index.php?title=Waveform_Arithmetic)






# Back to the Buck...

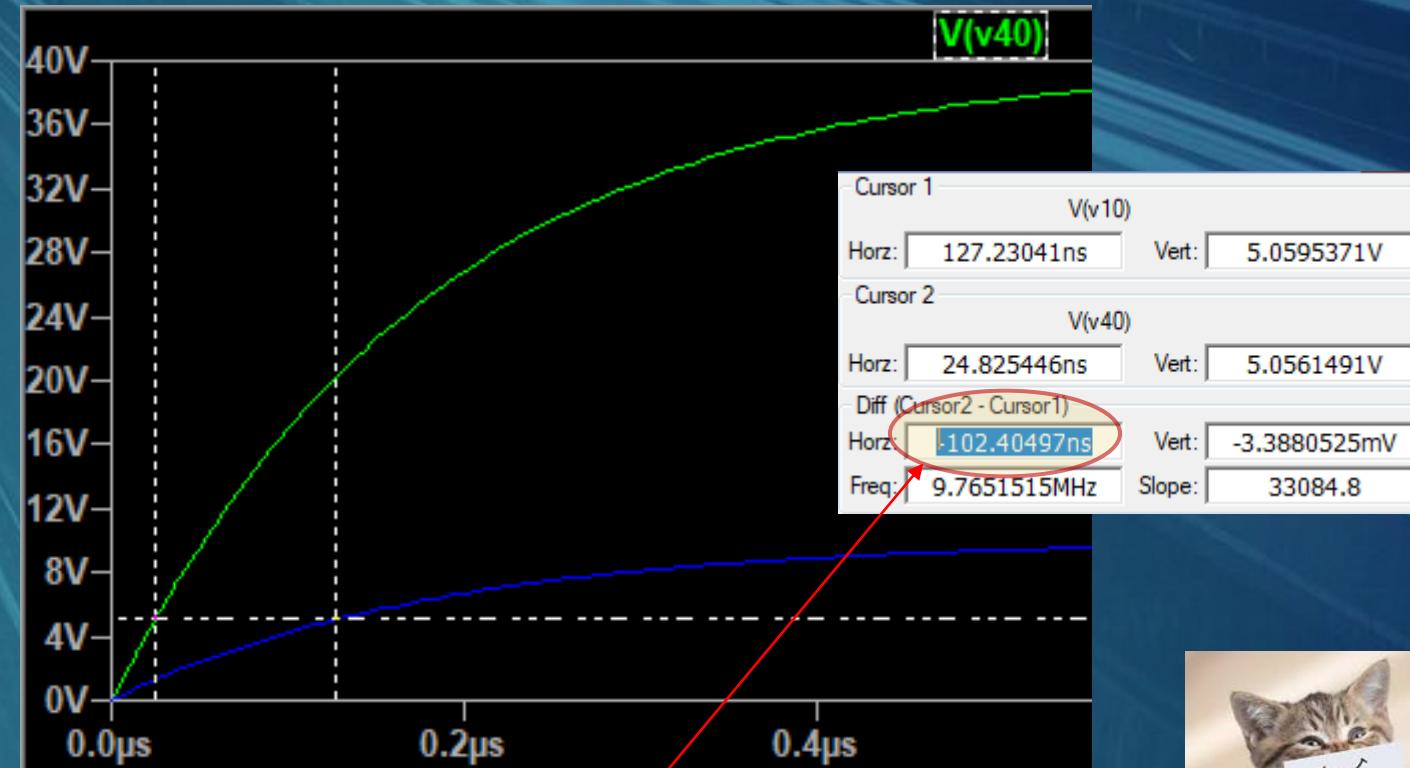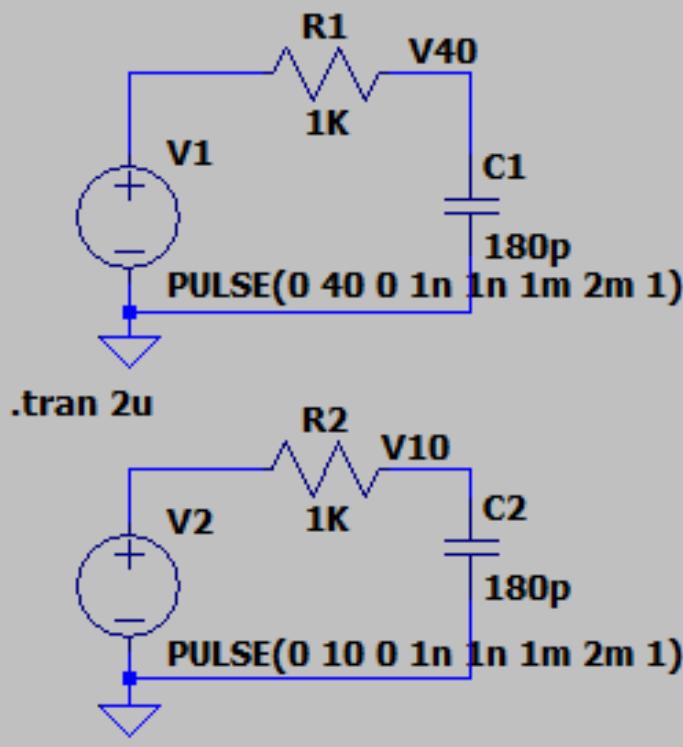

Lower voltage input takes longer to reach threshold


i.e. Higher  $V_{gs}$  causes Mosfet capacitor to charge faster and Mosfet to turn on faster

# What Does This Mean?!

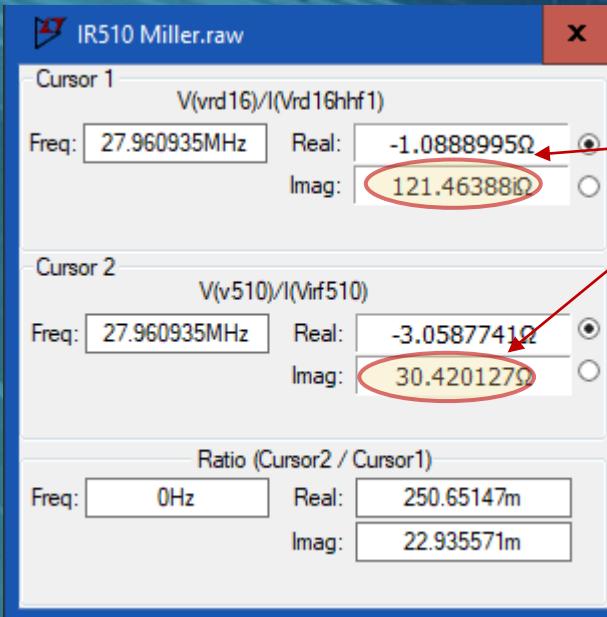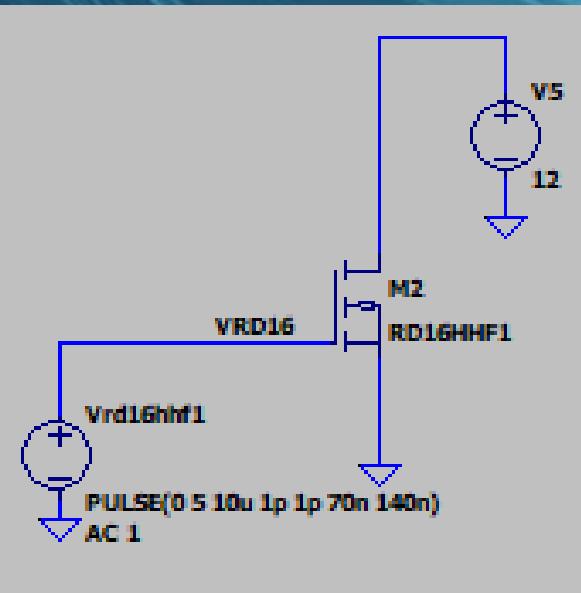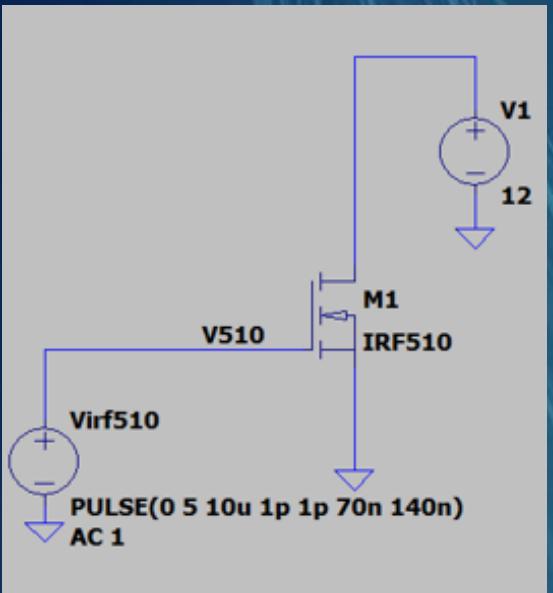


Dominated by **Imaginary** Impedance  
(at any frequency)

LTSpice Trick:

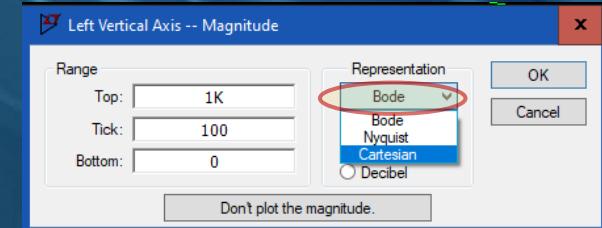
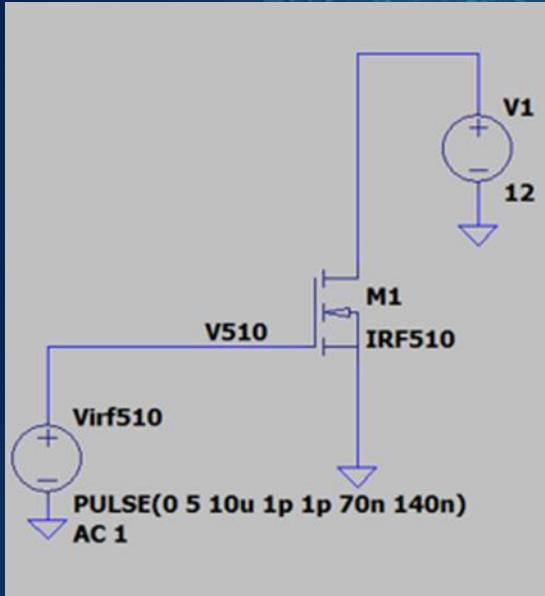
# In English...Please

Plot the impedance for several Mosfets at (say) 1.9 & 14.1 MHz





Mosfet	1.9 MHz			14.1 MHz		
	Magnitude	Real	Complex	Magnitude	Real	Complex
5010LLC	15.5	-3.2	15.2	3.5	-3.2	1.4
FQPF20N06	170.2	-1.0	170.2	22.8	-1.0	22.8
IRF530	173.0	-3.0	173.0	23.5	-3.0	23.3
IRFZ24N	212.5	-2.5	212.5	28.7	-2.5	28.6
IRF510	447.3	-3.1	447.3	60.4	-3.1	60.3
stp16nf06	113.1	-3.0	113.1	113.1	-3.0	113.1
SH8K25	950.9	-41.0	950.0	134.4	-41.0	128.0
RD16HHF1	1786.0	-1.1	1786.0	240.7	-1.1	240.7

## Notes:

1. Negative real impedance is typical for Mosfets (current direction? Phase? Capacitors?)
2. These measurements were done the hard way before I figured out how to make automated measurements



# Higher Frequencies....

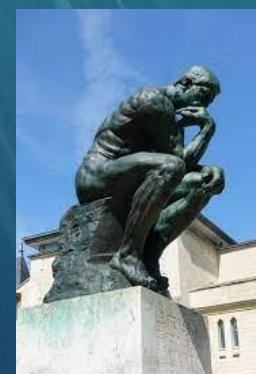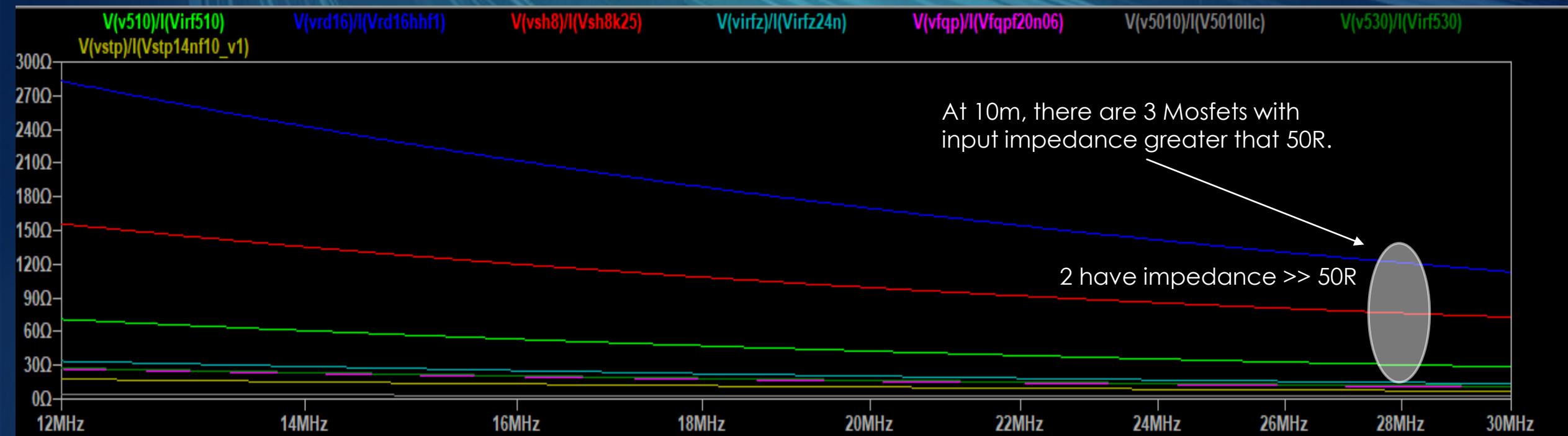

Hmmm...Maybe I can fix my D612 Power Amp.






# Rabbit Hole #3: Dueling SA612s MOSFET Power Amp Issues




More of a log and D612 background information


# In our last episode...

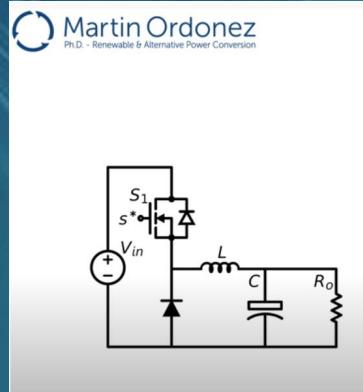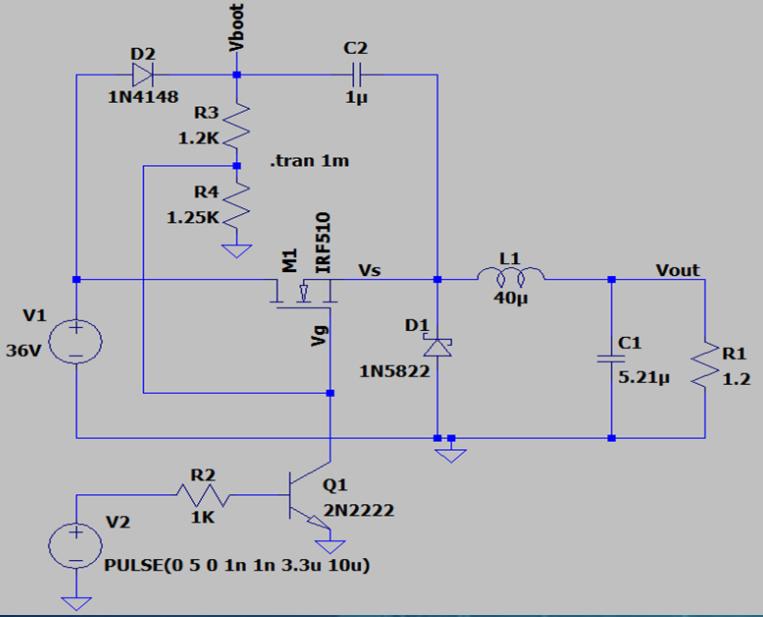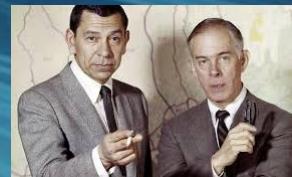





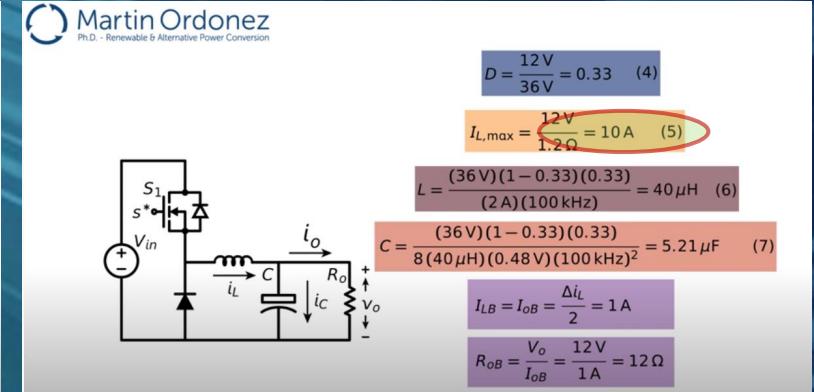
$V_{in} = 36\text{V}$   
 $V_o = 12\text{V}$   
 $f_{sw} = 100\text{kHz}$   
 $R_{o,min} = 1.2\Omega$   
 $\Delta i_L = 20\%$   
 $\Delta V_o = \pm 2\%$



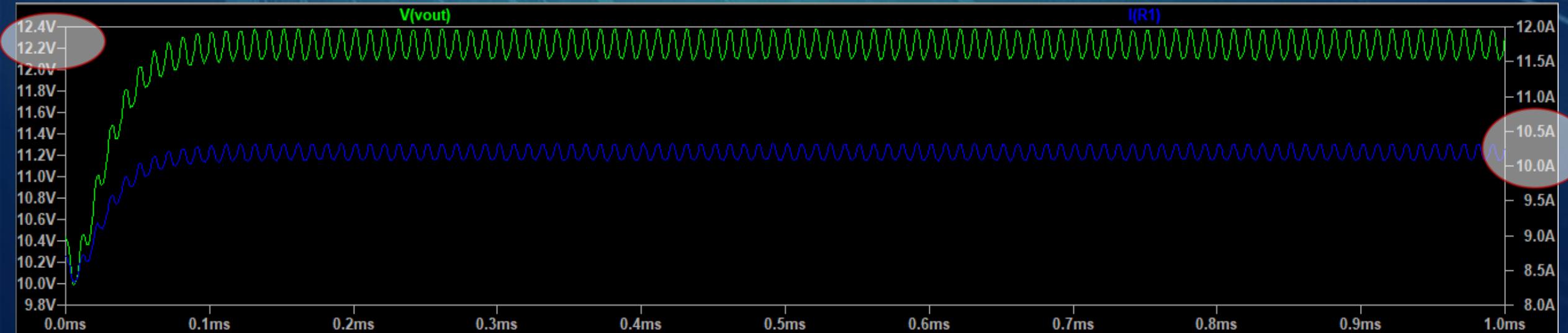Buck converter woes solved by high side bootstrap to turn on MOSFET properly









# In our last episode...

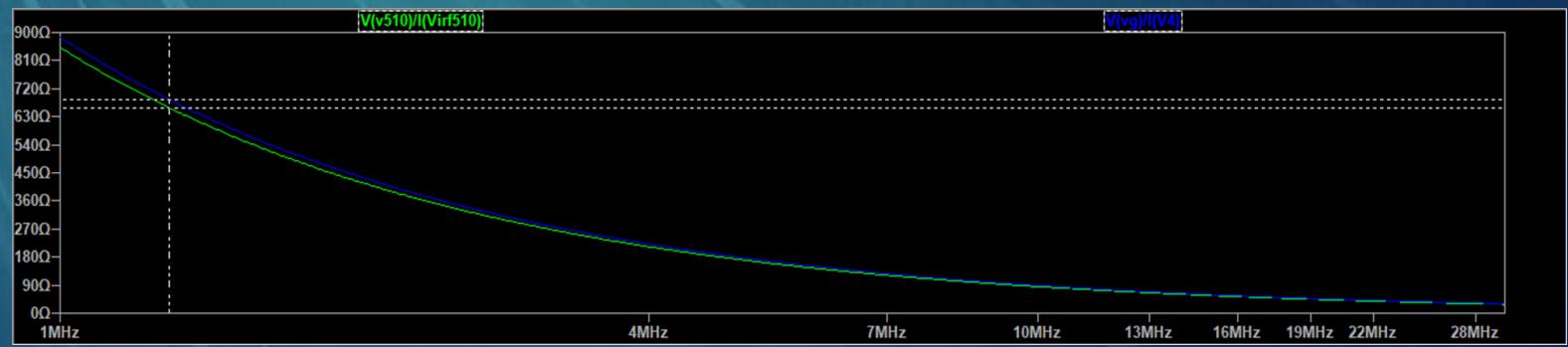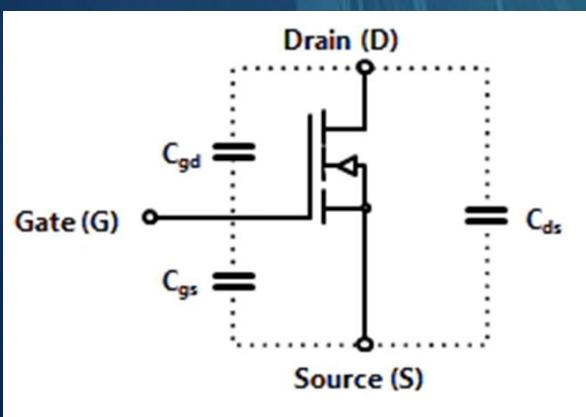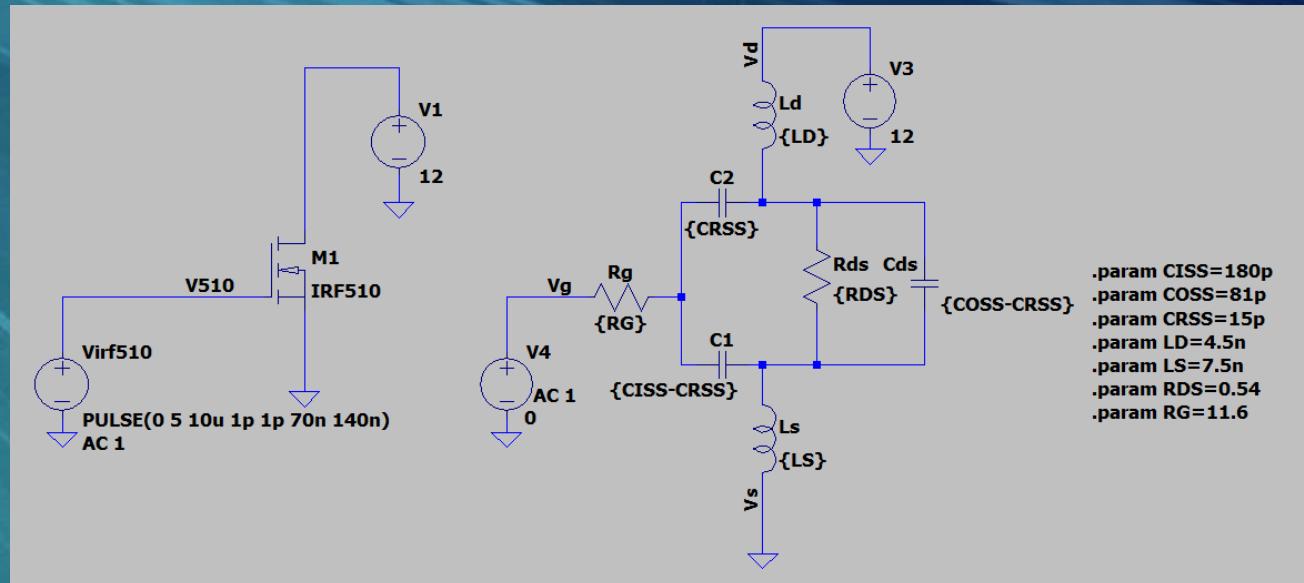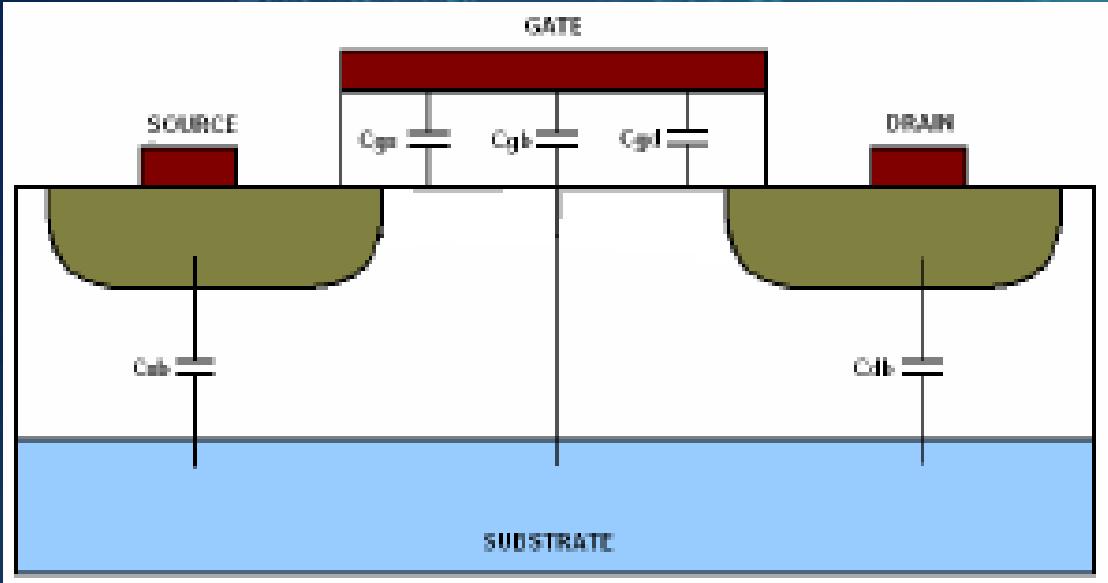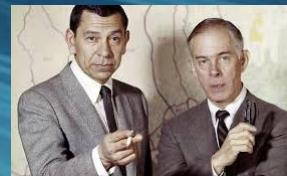

Dynamic			$f = 1.0 \text{ MHz}, \text{ see fig. 5}$	pF
Input capacitance	$C_{iss}$	-	$V_{GS} = 0 \text{ V},$	
Output capacitance	$C_{oss}$	-	$V_{DS} = 25 \text{ V},$	
Reverse transfer capacitance	$C_{rss}$	-	$f = 1.0 \text{ MHz}, \text{ see fig. 5}$	

# In our last episode...

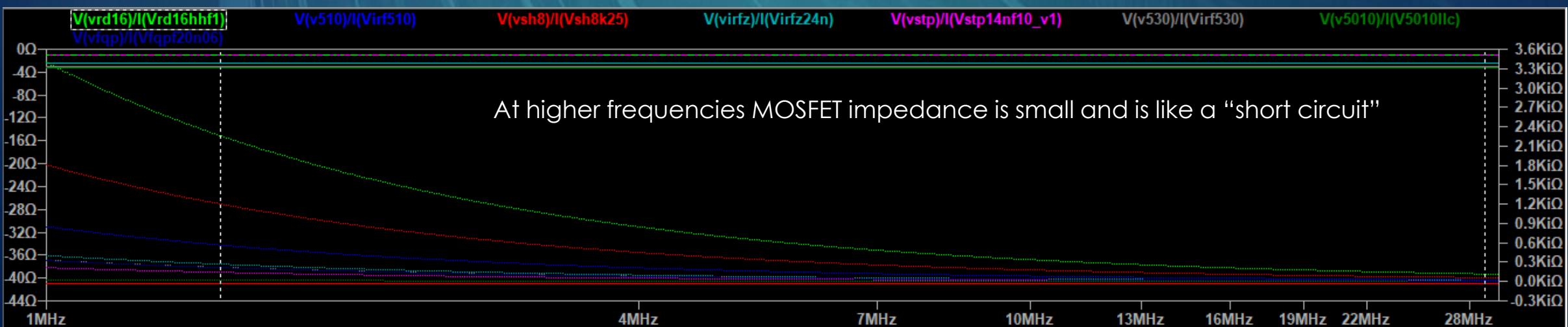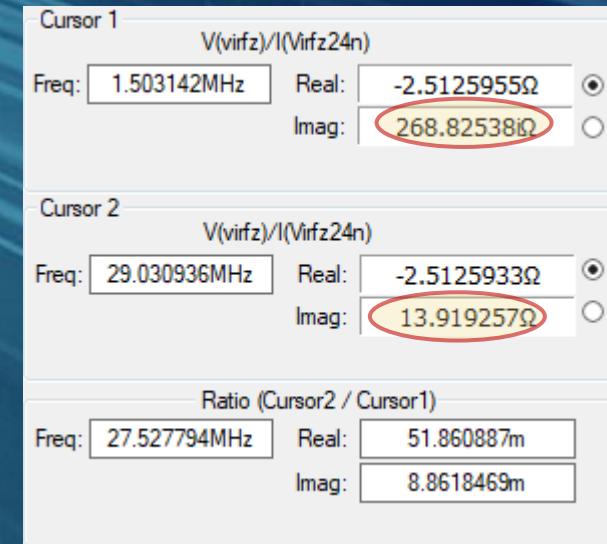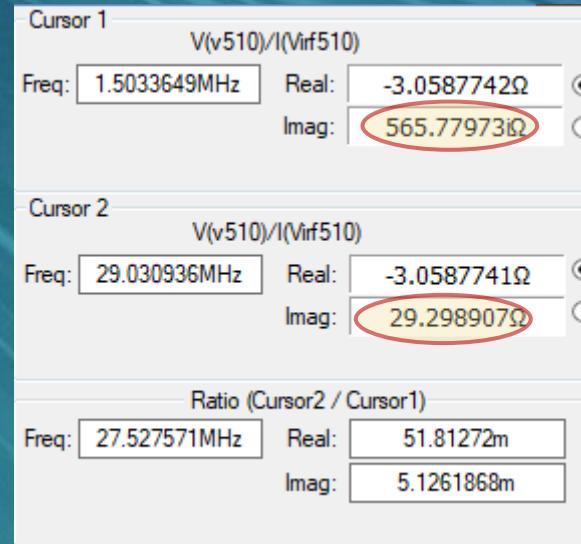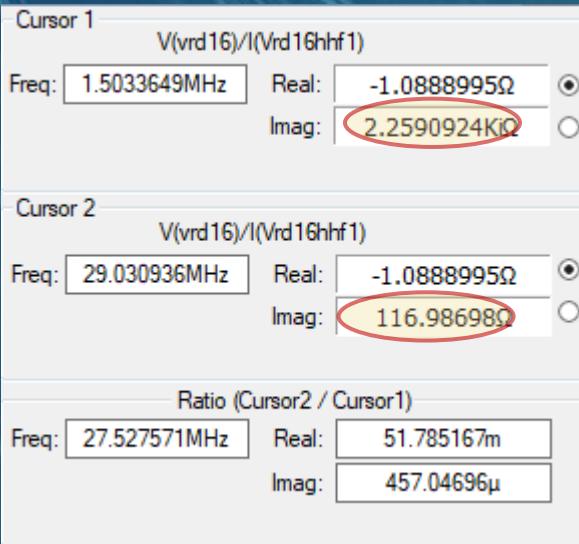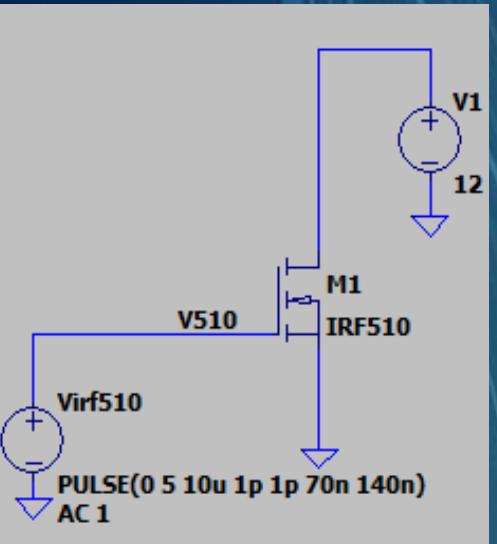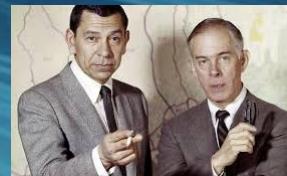

# Agenda

1. Background of Dueling SA612 Transceiver and Power Amp (PA)

2. The ugly rears its head



3. Select most popular/functional MOSFET PA for D612




4. Analyze and select best PA with best MOSFET

# Reinvent the Wheel


## Design Goals (BUMA)

1. Based on Pete Juliano (N6QW) Sudden 40 (circa 2018)
2. Multiband – original was 40m only
  - ✓ Use 12 MHz IF instead of 9 MHz (Bitx40)
  - ✓ Use pluggable BPF & LPF
3. Use opamps as much as possible to keep size down
  - ✓ Opamps can control gain
    - ✓ Control RF Pre Amp
    - ✓ Control Power output
  - ✓ Use LM386
4. Smeter, PWR, SWR
5. Use PARC Sig Gen
6. ~~Not use relays~~


Band	Orig Amp		New Amp (Typical)		New Amp (Max)	
	Power	Voltage Gain	Power	Voltage Gain	Power	Voltage Gain
160m	4	174	9	146	9	146
80m	5	173	8	145	10	147
40m	5	174	5	142	12	149
20m	1	165	2	129	11	149
10m	0.03	137	0.11	103	2.24	132

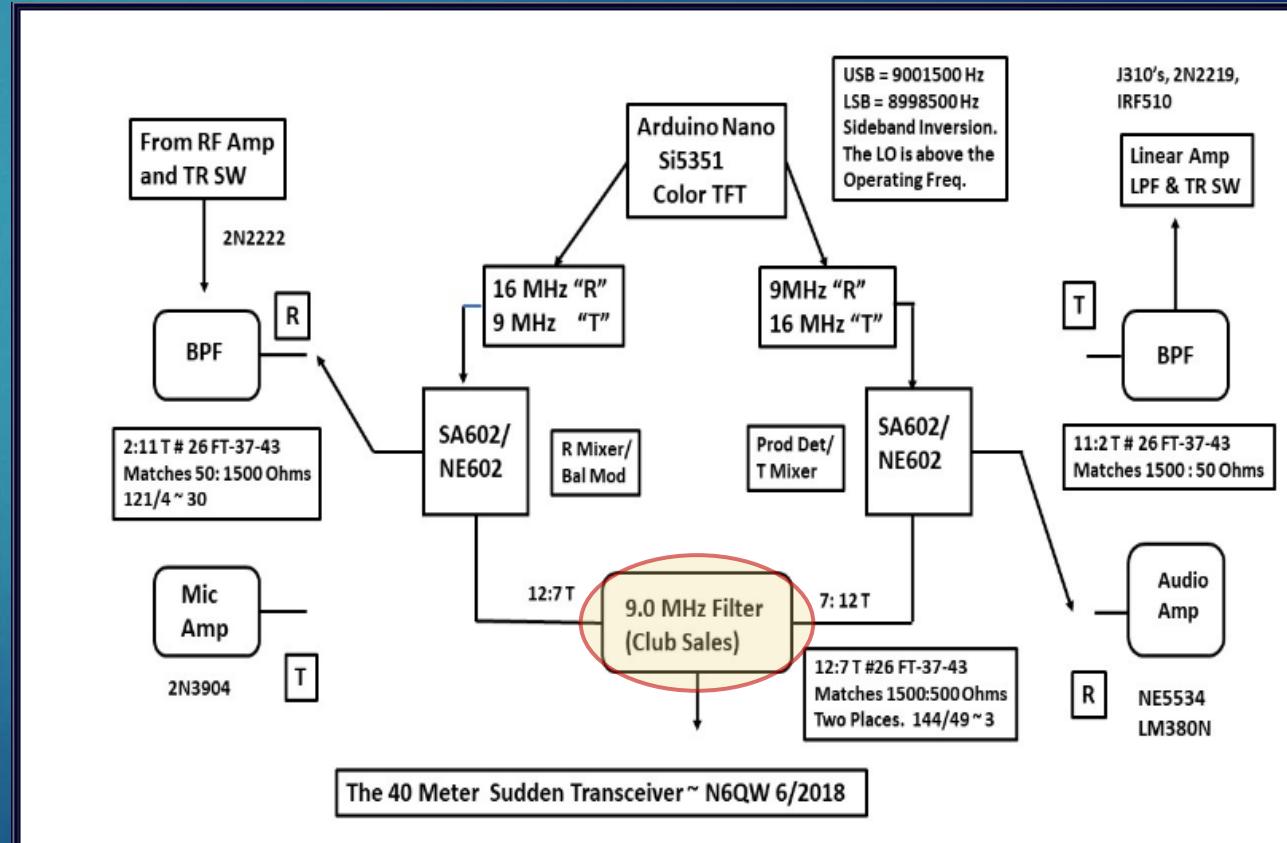

Based on Pete Juliano (N6QW)  
Sudden 40

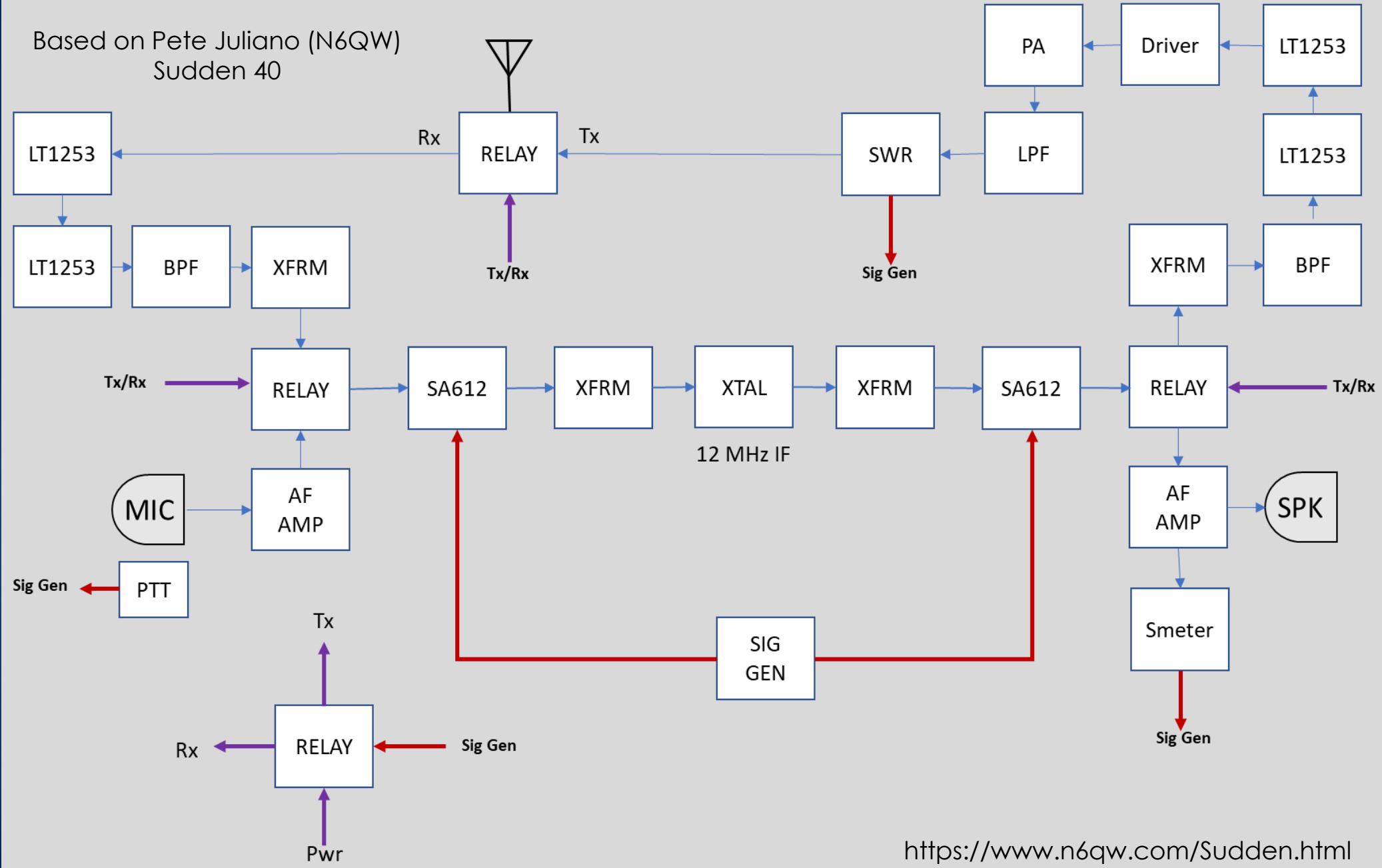

# Modified D612 PA

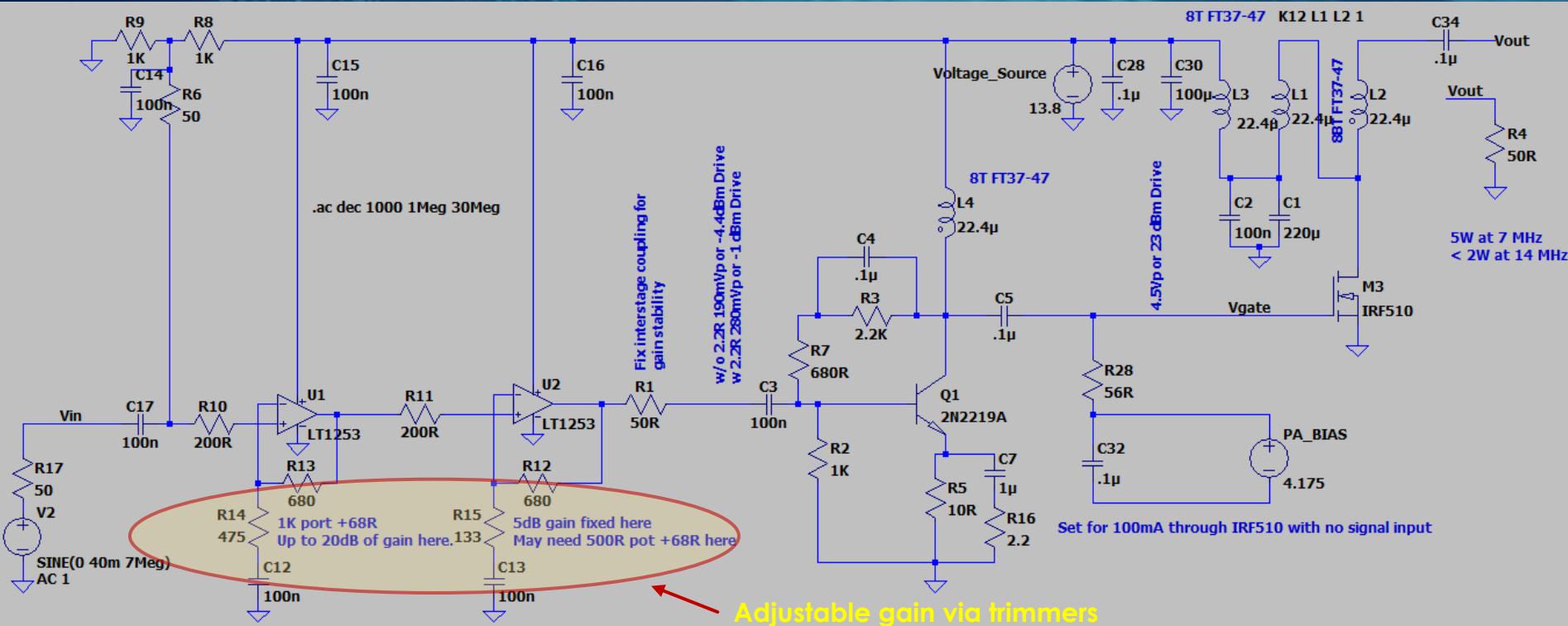


Cursor 1	V(vout)		
Freq:	1.9099371MHz	Mag:	61.356549dB
Phase:	-19.501823°		
Group Delay:	60.820056ns		
Cursor 2	V(vout)		
Freq:	28.028667MHz	Mag:	39.466293dB
Phase:	-243.47349°		
Group Delay:	12.30808ns		
Ratio (Cursor2 / Cursor1)			
Freq:	26.11873MHz	Mag:	-21.890256dB
Phase:	136.02834°		
Group Delay:	-48.511976ns		



Can adjust gain



# Dueling 612

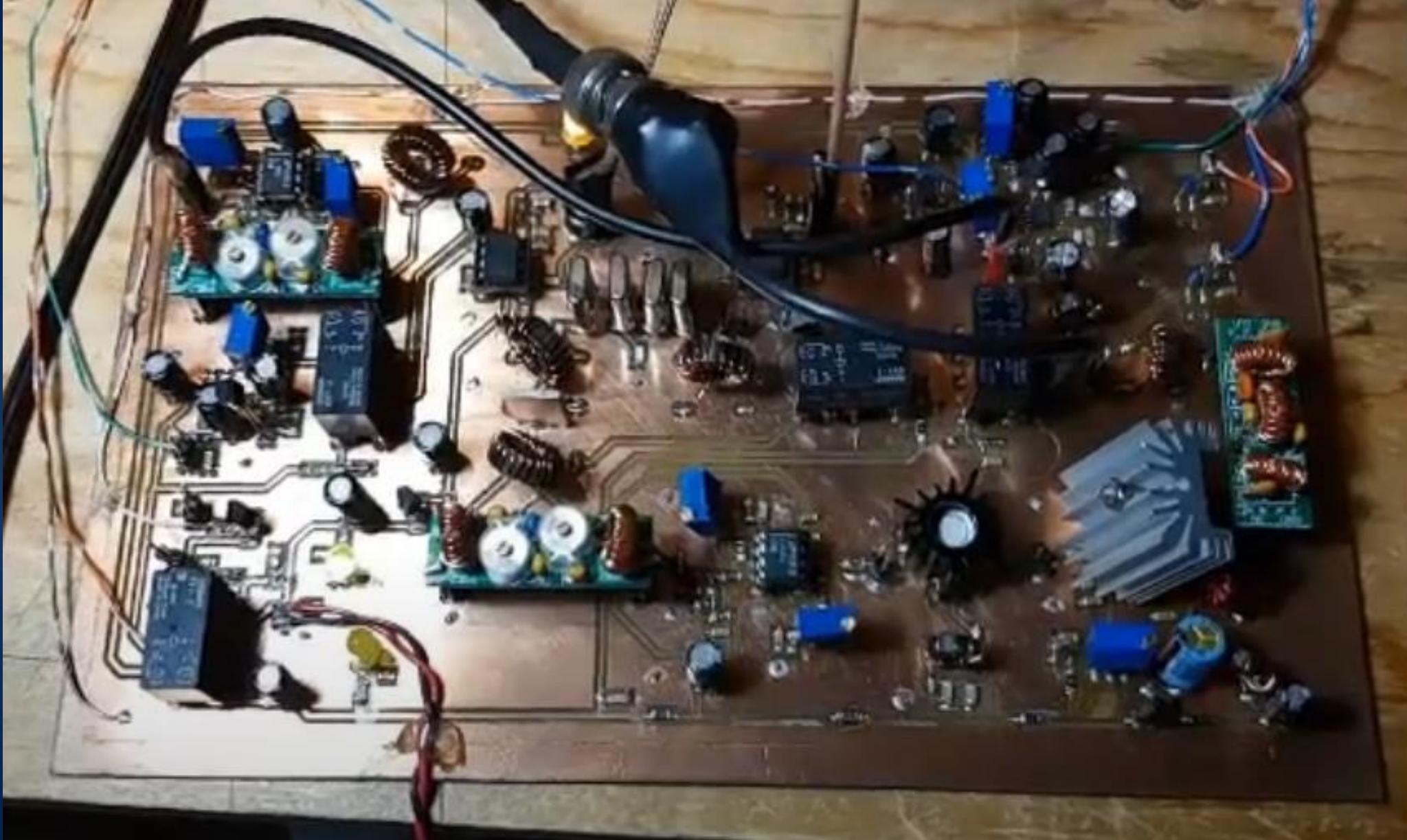

# 80m Contact

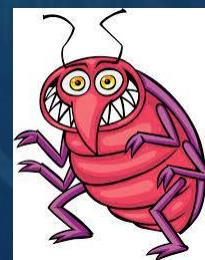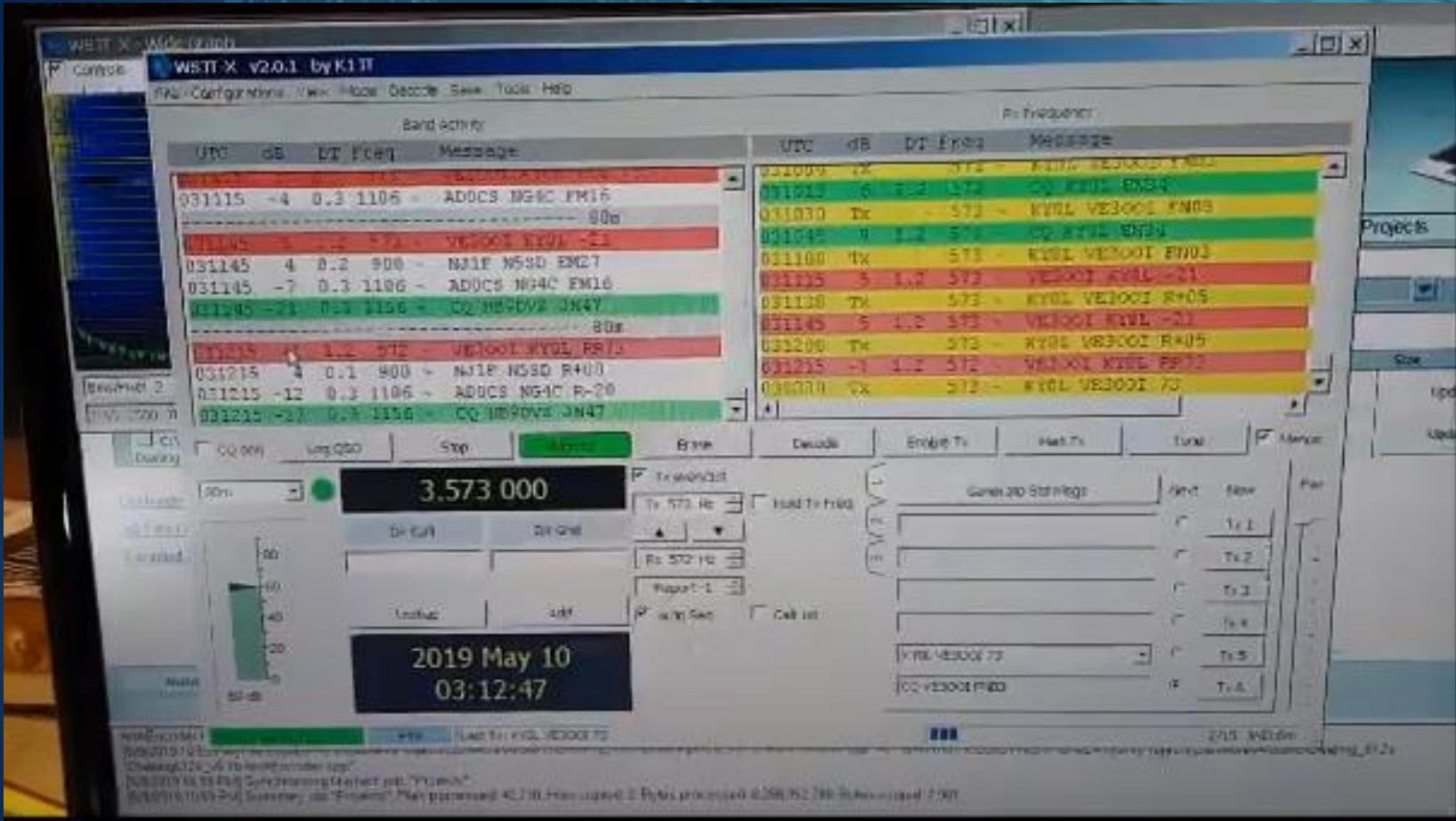

# 40m Contact

WSJT-X v2.0.1 by K1EL

File Configuration View Mode Decode Setup Tools Help

Band ACTIVE

UTC	DE	DT	Freq	Message
212245	-	0.1	760	VE3OJI VE3OOI FN03
212245	-4	0.2	879	AC2G WA4DWD R-08
				40m
212245	-3	0.1	1245	VE3OJI VE3OOI FN03
212245	-20	-0.4	221	CQ K2FPC FN34
212315	-17	-0.4	223	CQ K2FPC FN34
212315	-4	0.2	879	AC2G WA4DWD R-08
				40m
212345	5	0.1	1245	VE3OJI VE3OOI RR77
212345	0	0.2	489	VE3OJI VE3OOI FN46
212345	-4	0.1	660	K9JDI VE3OOI -20
212345	-1	0.2	879	AC2G WA4DWD R-08

R: Frequency

UTC	DE	DT	Freq	Message
212315	TX	1187	-	VE3OJI VE3OOI FN03
212315	-6	0.1	1245	CO K0622 EN95
212203	TX	1245	-	KQ622 VE3OOI FN03
212315	1	0.1	1245	CO K0622 EN95
212230	TX	1245	-	KQ622 VE3OOI FN03
212245	5	0.1	1245	CO K0622 EN95
212300	TX	1245	-	KQ622 VE3OOI FN03
212315	6	0.1	1245	VE3OOI VE3OOI FN03
212330	TX	1245	-	KQ622 VE3OOI FN03
212345	5	0.1	1245	VE3OOI VE3OOI RR77
212400	TX	1245	-	KQ622 VE3OOI 73

Copy Log QSO Stop **Transmit**  Transmit  Hold Trans

Transmit  Hold Trans



Generate Set Msgs  Tr 1  Tr 2  Tr 3  Tr 4  Tr 5  Tr 6

Tr 1  Tr 2  Tr 3  Tr 4  Tr 5  Tr 6


2019 May 09  
21:24:19



# 30m Contact

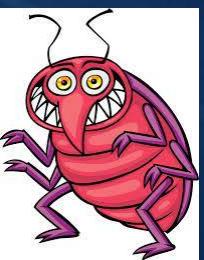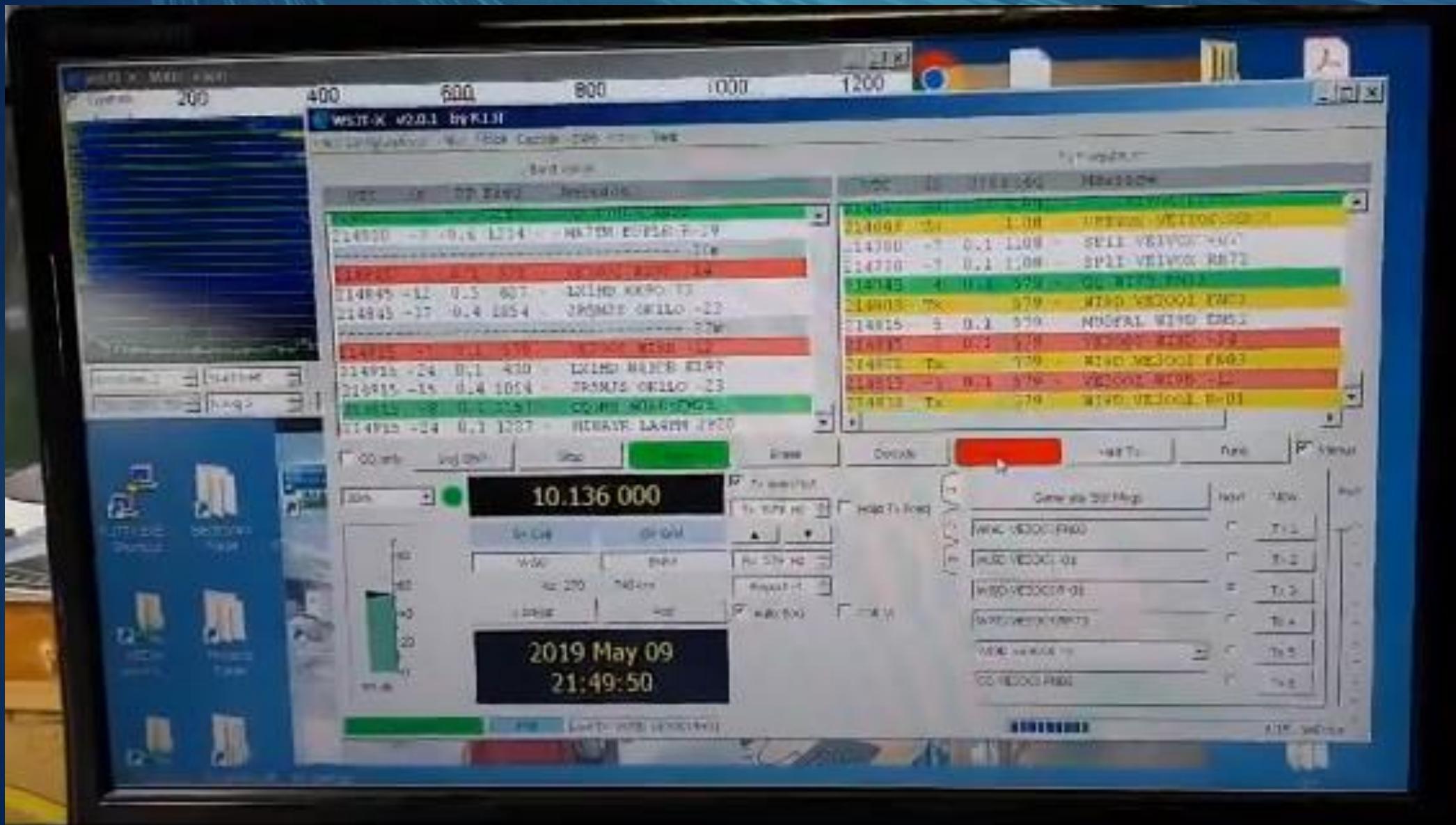

# 20m Contact

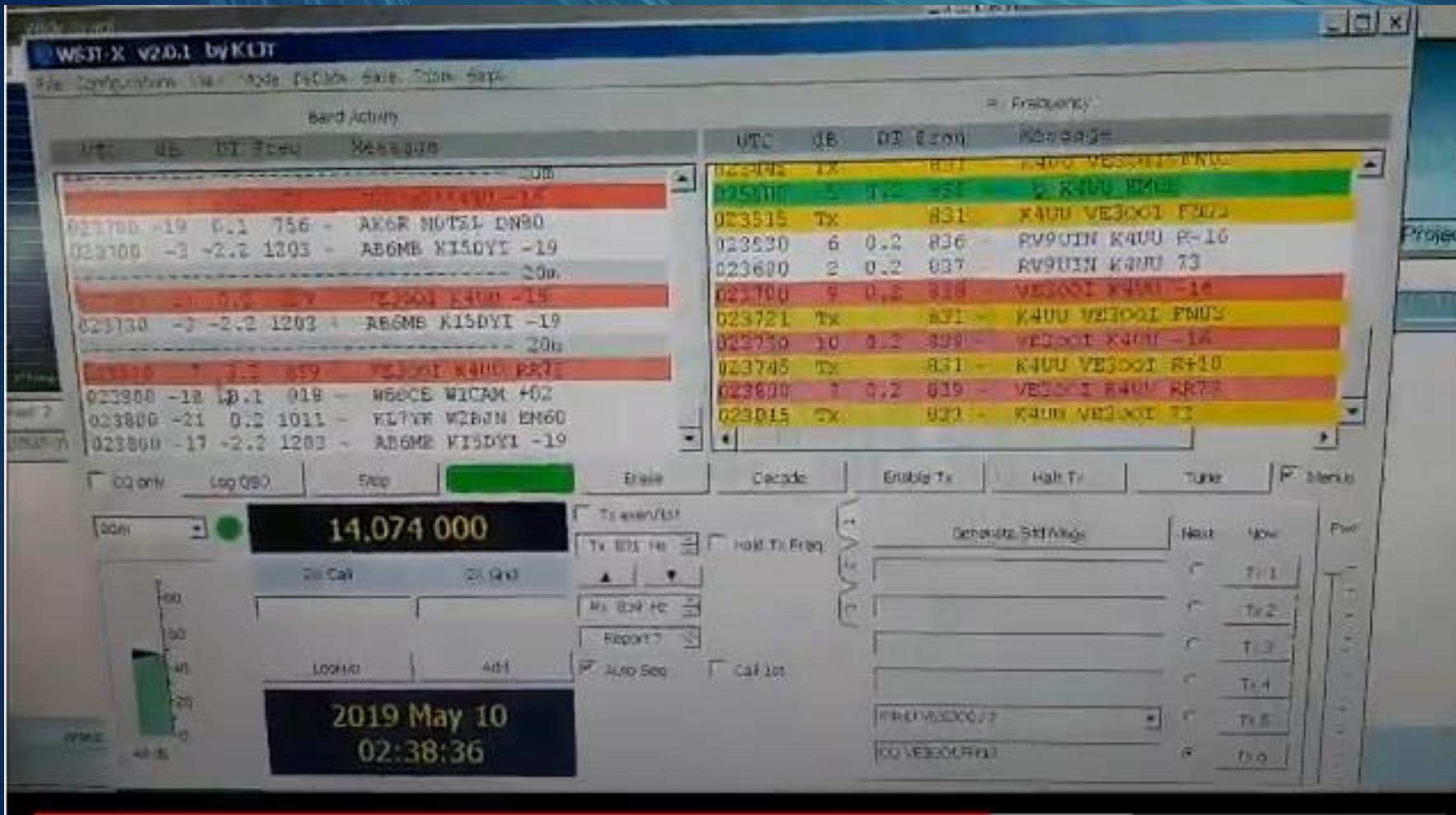

# Spurious Emission's Ugly Head



97.307 Emission standards.

(d) For transmitters installed after January 1, 2003, the mean power of any spurious emission from a station transmitter or external RF power amplifier transmitting on a frequency below 30 MHz must be at least 43 dB below the mean power of the fundamental emission.

For transmitters installed on or before January 1, 2003, the mean power of any spurious emission from a station transmitter or external RF power amplifier transmitting on a frequency below 30 MHz must not exceed 50 mW and must be at least 40 dB below the mean power of the fundamental emission. For a transmitter of mean power less than 5 W installed on or before January 1, 2003, the attenuation must be at least 30 dB. A transmitter built before April 15, 1977, or first marketed before January 1, 1978, is exempt from this requirement.

Category C

Category C limits are an example of more stringent spurious emission limits than Category A limits. They are based on limits defined and adopted in the United States of America and Canada and used by some other countries. These limits are given in § 4.4.

HF broadcasting

80 dBc

The power of unwanted emissions shall be attenuated below the transmitter's output power, P (dBW) as follows:

- a. 25 dB; on any frequency removed from the channel frequency by more than 50% and up to 100% of the authorized bandwidth measured with a resolution bandwidth of 300 Hz;
- b. 35 dB; on any frequency removed from the channel frequency by more than 100% up to 250% of the authorized bandwidth measured with a resolution bandwidth of 300 Hz;
- c.  $43 + 10 \log(p)$  or 70 dB, whichever is less stringent; in any 30 kHz bandwidth removed from the channel frequency by more than 250% of the authorized bandwidth.

Where:

p refers to the transmitter's output power expressed in watts.

<https://www.ic.gc.ca/eic/site/smt-gst.nsf/eng/sf01240.html>

In Canada:

- For 5W, emission: 43.7dBc
- For 10W, emission: 44.0 dBc
- ✓ 44 dBc



# The Issue (2019)...






- The D612 had harmonics stronger than -44 dBc limit (mid to high - 30 dBc)
- For 20m, had to adjust gain on PA pre-driver to get 4-5 Watts output. Harmonics got worst
  - With same Gain on Opamp: 5W@7MHz, 1.7W@14MHz
- Power Amp was too dirty. Hard to make contacts. Thrown against wall.



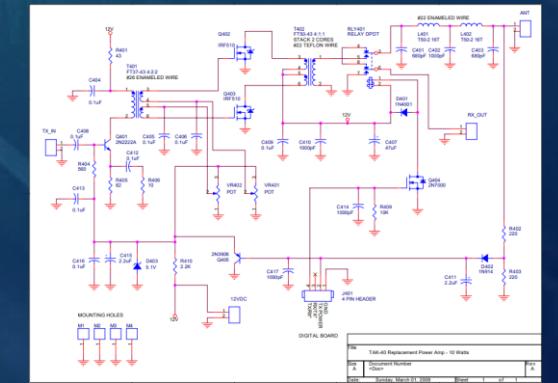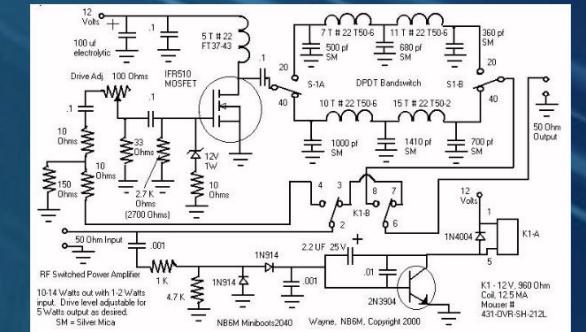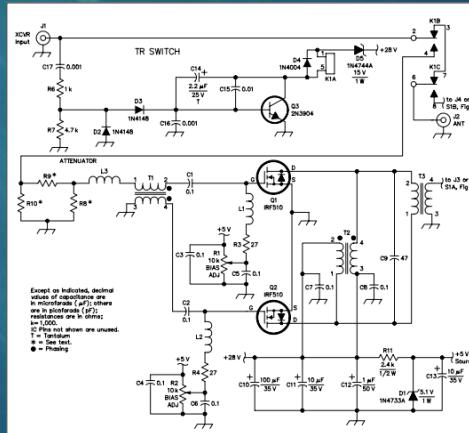
# Recently (2022)...After RH#3



- Abandon D612 PA to find a better alternative
- Searched and reviewed designs. Basically, the same
- Focused on BitX and Hans Summers Push Pull (Tony Parks - SK).



# Original BitX20 PA

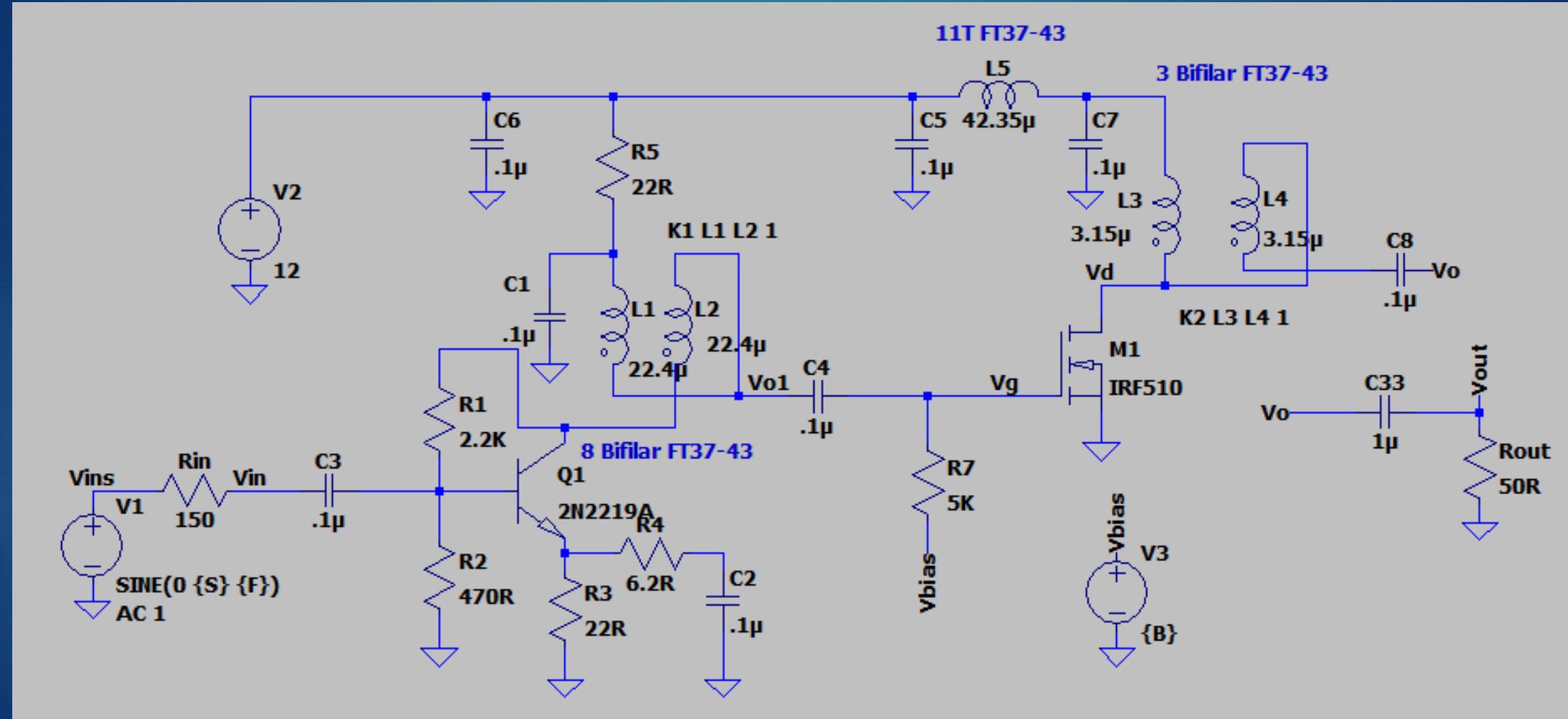

# Sweep of BITX20 Amp




Cursor 1	V(vout)
Freq:	1.9300966MHz
Mag:	46.568344dB
Phase:	-189.67584°
Group Delay:	49.506561ns
Cursor 2	V(vout)
Freq:	29.090598MHz
Mag:	30.95617dB
Phase:	-319.53171°
Group Delay:	6.3112131ns
Ratio (Cursor2 / Cursor1)	
Freq:	27.160502MHz
Mag:	-15.612174dB
Phase:	-129.85587°
Group Delay:	-43.195348ns

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	28	27	26	25	25	24	23	21

7 dB Roll Off

# Newer BitX40 PA

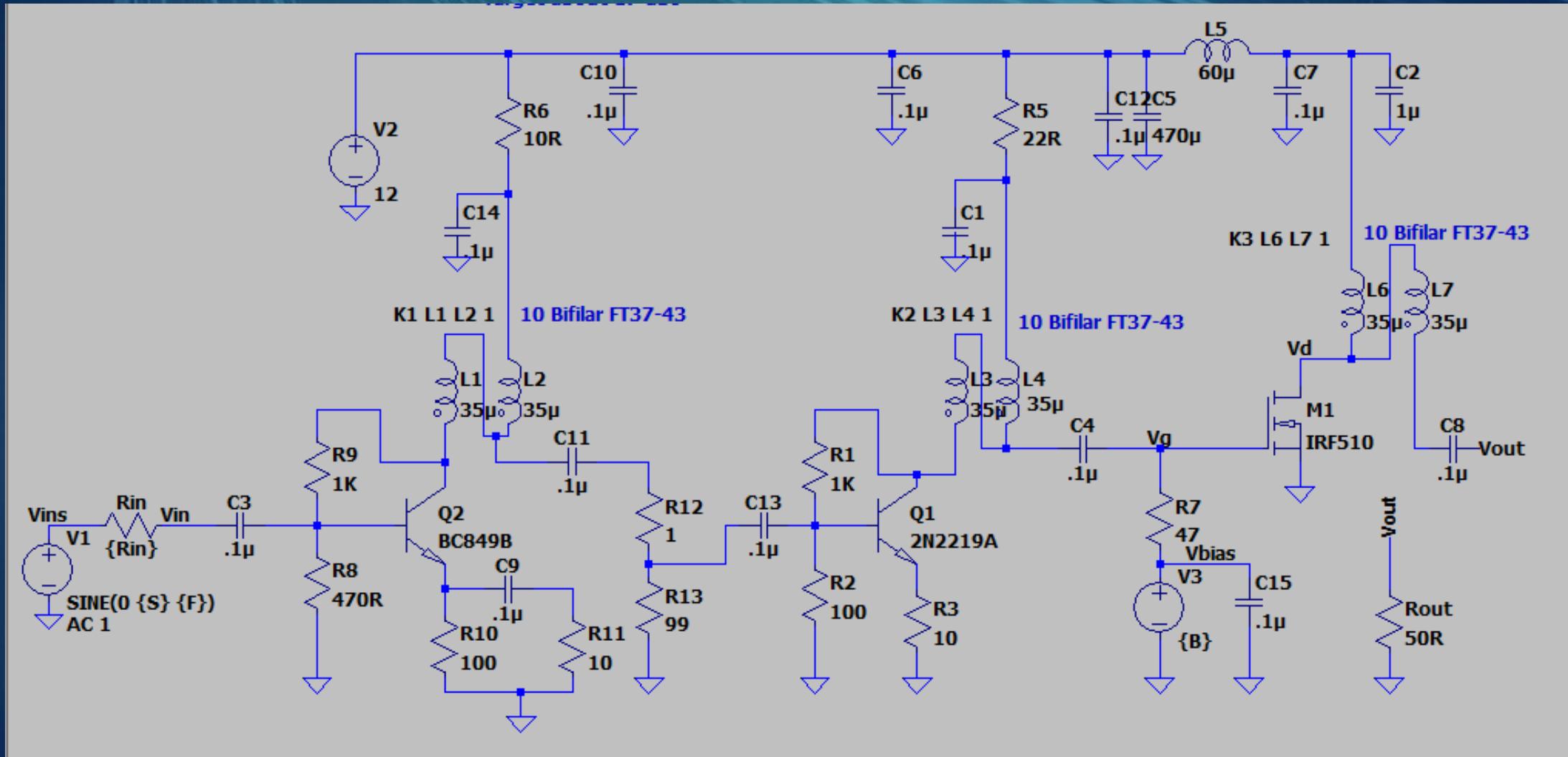

# Sweep of BitX40 Amp




Cursor 1	V(vout)
Freq:	1.9300966MHz
Mag:	46.473816dB
Phase:	-189.72452°
Group Delay:	49.64468ns
Cursor 2	V(vout)
Freq:	29.090598MHz
Mag:	30.825798dB
Phase:	-319.61914°
Group Delay:	6.3112536ns
Ratio (Cursor2 / Cursor1)	
Freq:	27.160502MHz
Mag:	-15.648018dB
Phase:	-129.89462°
Group Delay:	-43.333427ns

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	27	27	27	27	27	27	26	25

2 dB Roll Off  
(BitX 20 transformer issue?)

# uBitX Push Pull

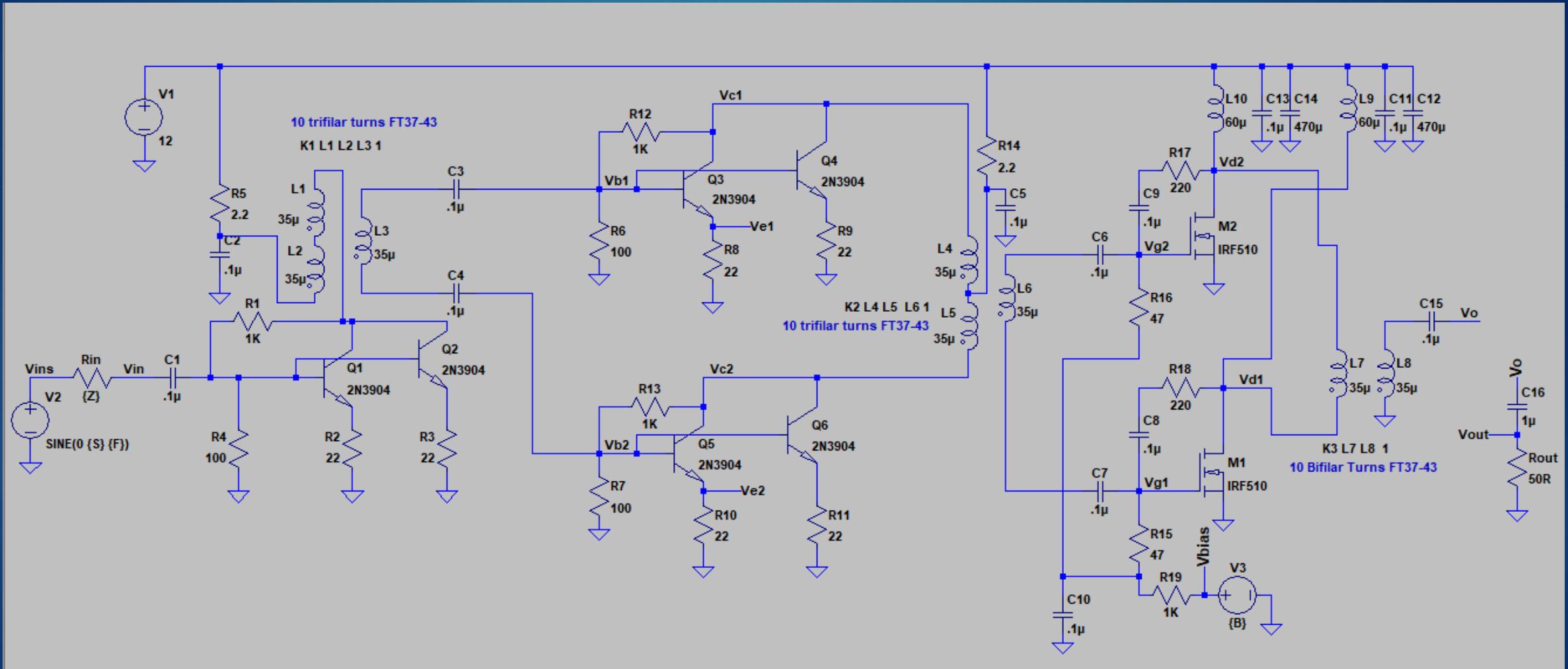

# Sweep of uBitx Amp




Cursor 1	
V(vo)	
Freq: 1.9035053MHz	Mag: 43.975638dB
Phase: -178.22166°	<input checked="" type="radio"/>
Group Delay: 45.532628ns	<input type="radio"/>
Cursor 2	
V(vo)	
Freq: 29.052195MHz	Mag: 32.333626dB
Phase: -306.46419°	<input checked="" type="radio"/>
Group Delay: 6.2547018ns	<input type="radio"/>
Ratio (Cursor2 / Cursor1)	
Freq: 27.14869MHz	Mag: -11.642012dB
Phase: -128.24253°	
Group Delay: -39.277926ns	

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	32	32	32	32	32	32	31	29

3 dB Roll Off

# WA2EBY Push Pull

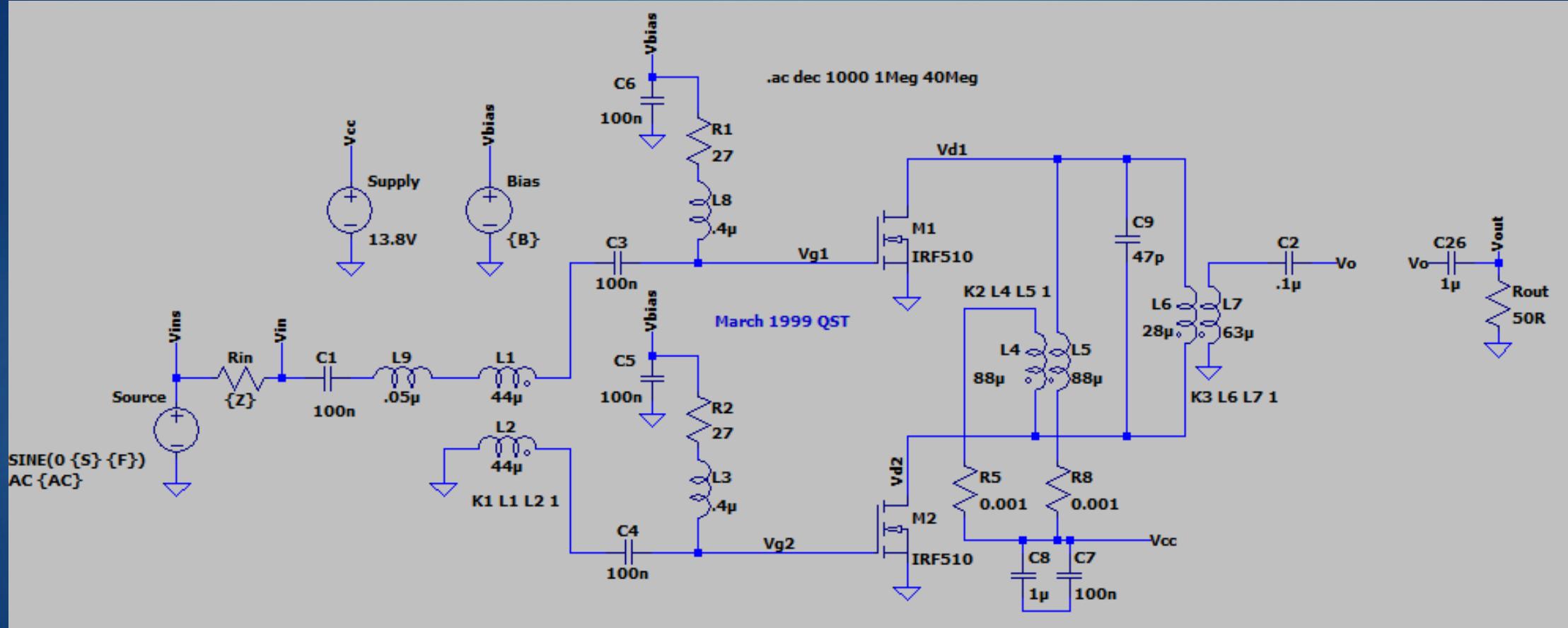

# Sweep of WA2EBY Amp




Cursor 1		
V(vout)		
Freq:	1.9013782MHz	Mag: 30.2823dB
Phase:	-178.47031°	<input checked="" type="radio"/>
Group Delay:	16.35912ns	<input type="radio"/>
Cursor 2		
V(vout)		
Freq:	29.094957MHz	Mag: 25.013247dB
Phase:	-263.30327°	<input type="radio"/>
Group Delay:	4.1707583ns	<input checked="" type="radio"/>
Ratio (Cursor2 / Cursor1)		
Freq:	27.193579MHz	Mag: -5.2690527dB
Phase:	-84.832955°	<input type="radio"/>
Group Delay:	-12.188362ns	<input checked="" type="radio"/>

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	20	20	19	18	18	18	20	20

About 2 dB variation

# Hans Summers (Tony Parks) Push Pull

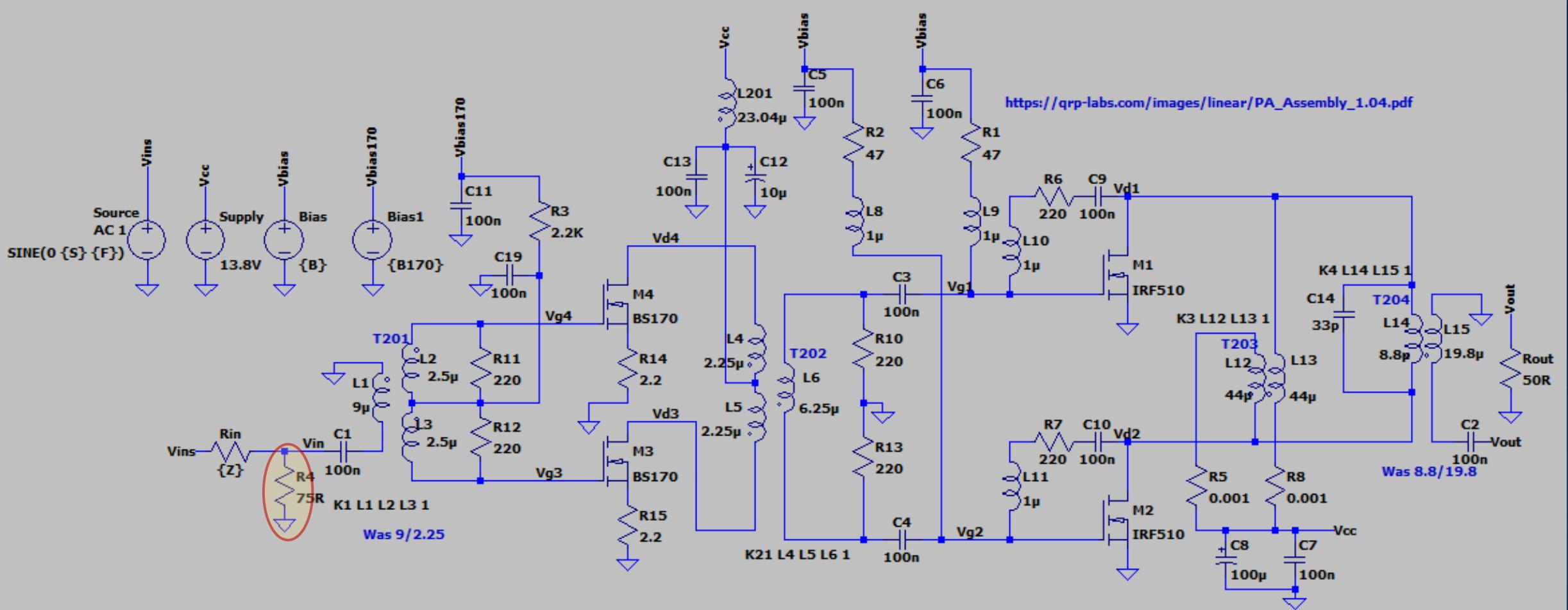


# Sweep of Hans Summers Amp



Cursor 1	
V(vout)	
Freq:	1.9012454MHz
Mag:	14.665251dB
Phase:	42.079529°
Group Delay:	86.018154ns
Cursor 2	
V(vout)	
Freq:	28.017949MHz
Mag:	4.3630493dB
Phase:	-133.70787°
Group Delay:	6.0636017ns
Ratio (Cursor2 / Cursor1)	
Freq:	26.116704MHz
Mag:	-10.302202dB
Phase:	-175.7874°
Group Delay:	-79.954552ns

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	20	19	18	18	17	16	12	8

16 dB?

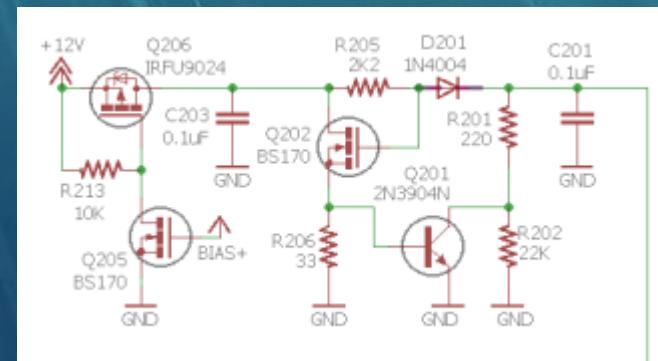

# Analysis


- Issues with N6QW, Bitx20 and Hans Summers Push Pull.
  - Significant roll off with frequency. uBitx a little flatter.
    - Transformer vs MOSFET Capacitance vs Other?
  - Independent testing of Hans Summers amp indicated broadband...shoot the rabbit
- WA2EBY, BitX40 and uBitX better response
  - WA2EBY needs 1W drive. Preamp may bandwidth limit amp.
- Don't boil the ocean: Focus on finding a MOSFET that is better than IRF510 with better high frequency response
  - Looked at other MOSFET amps and did a Digikey parameter search for lowest capacitance
  - Found several candidates. Needed to compare their performance

# Comparing Performance

- Difficult to make measurement from LTSpice waveforms
  - ✓ Select best MOSFET bias voltages (for Class A operation)
  - ✓ Select optimum input drive level for best and clean output
  - ✓ Measure purity using FFT for IC compliance.
  - ✓ Measure output power
  - ✓ Measure MOSFET power dissipation/temperature
  - ✓ Measure Input/output impedance
- Needed to learn about LTSpice **FFT** and making **automated measurements**.



# Fundamental Measurements

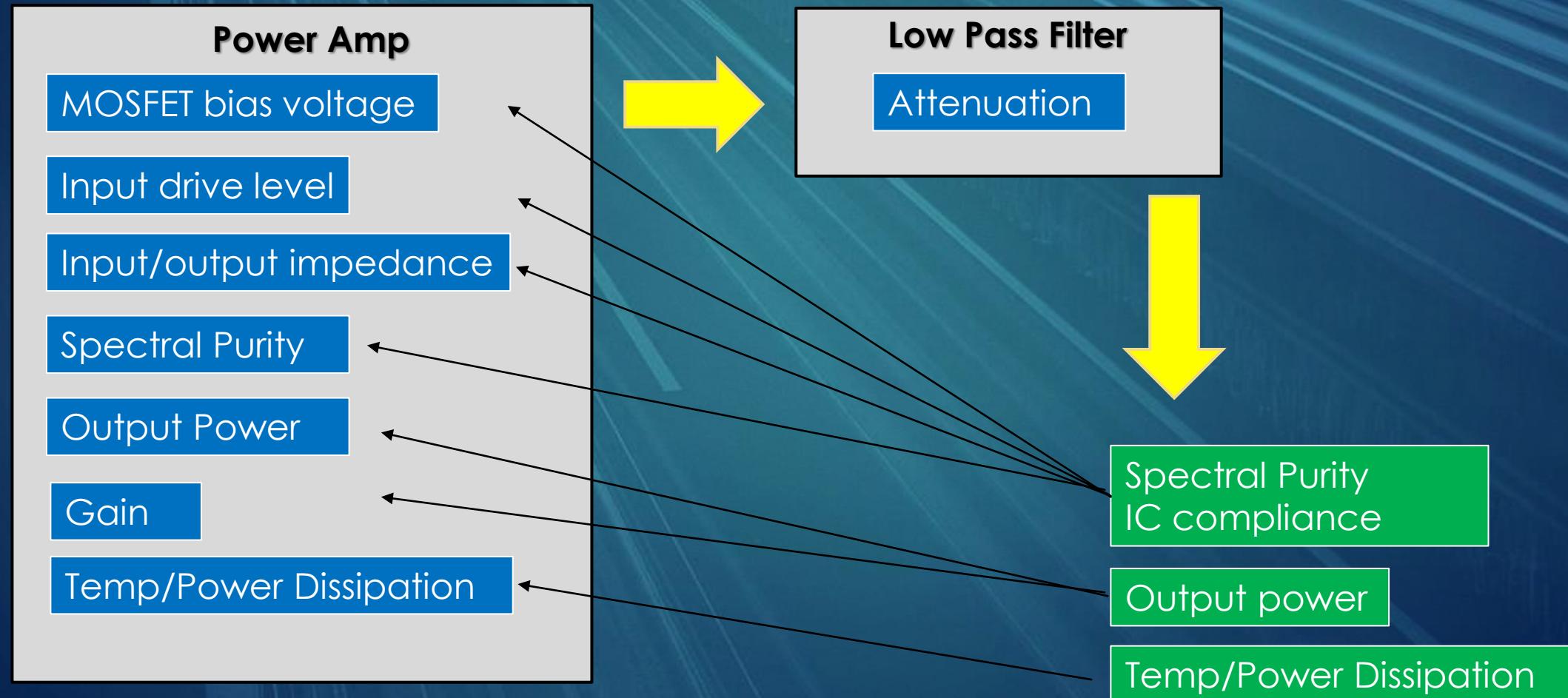

# Low Pass Filters

c.  $43 + 10 \log(p)$  or 70 dB, whichever is less stringent; in any 30 kHz bandwidth removed from the channel frequency by more than 250% of the authorized bandwidth.


- First, what is maximum output voltage for harmonic?
  - $-44 = 10 \log (P_h/P_f)$  or  $-44 = 20 \log (V_h/V_f)$
  - Solve  $V_h = 0.00631 * V_f$ 
    - Any harmonic is “at most” 0.63% of fundamental
- Second, what attenuation will LPF provide?

Harmonic	80m PA	40m PA	20m PA
2	-11	-14	-17
3	-15	-17	-19
4	-32	-30	-32

Harmonic	80m LPF	40m LPF	20m LPF
2	-47	-55	-66
3	-76	-82	-93
4	-98	-107	-114

~49dB

Ok if output from PA is < 0 dBc

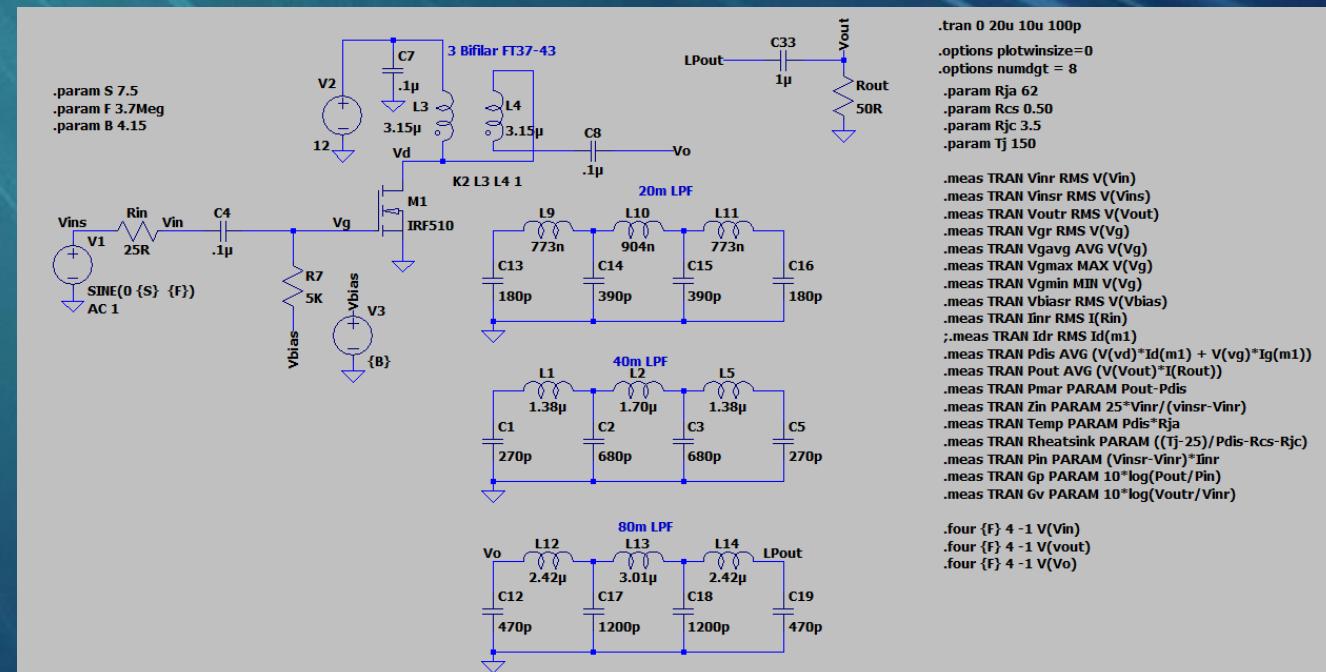



# Summary

- For Bitx and Hans Summers PAs
  - ✓ Assume component are all ok – only adjust bias
  - ✓ For several “potentially good” MOSFETs
  - ✓ Measure Spectral Purity, Power Output, Power Dissipated
    - ✓ Measure without LPF and keep harmonic dBc as low as possible. Pick arbitrary value
  - ✓ Select optimum bias and drive
  - ✓ Compare and select best MOSFET


# Rabbit Hole #3.1: LTSpice FFT




# In our last episode...

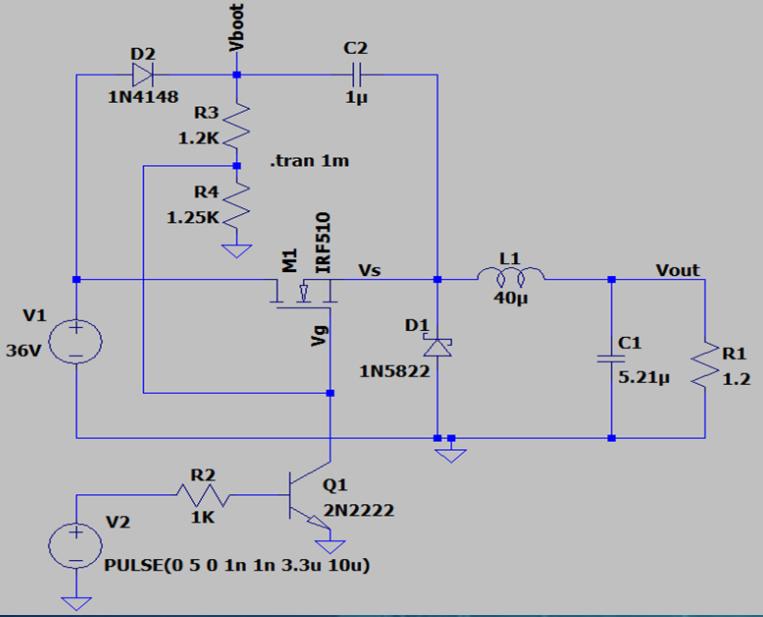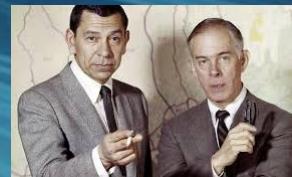




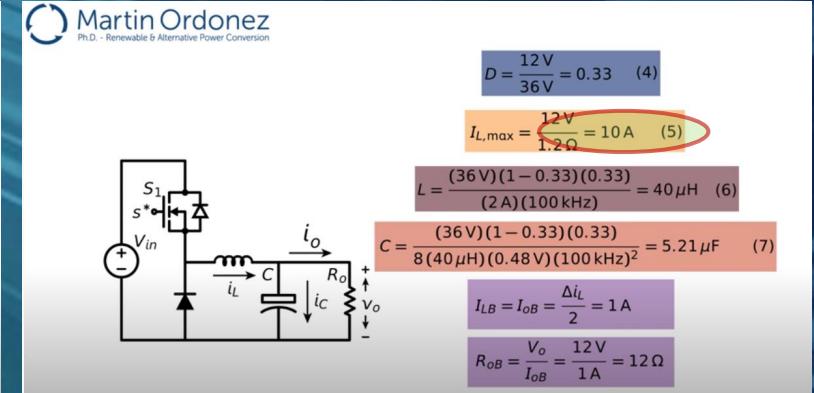
$V_{in} = 36\text{V}$   
 $V_o = 12\text{V}$   
 $f_{sw} = 100\text{kHz}$   
 $R_{o,min} = 1.2\Omega$   
 $\Delta i_L = 20\%$   
 $\Delta V_o = \pm 2\%$



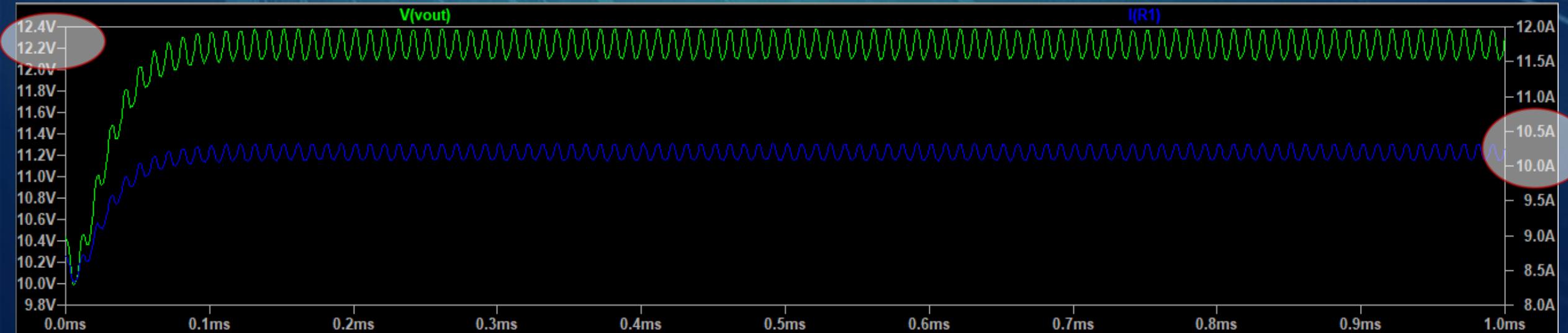Buck converter woes solved by high side bootstrap to turn on MOSFET properly



# In our last episode...

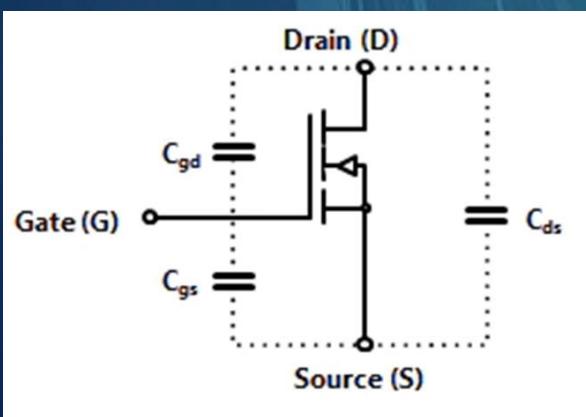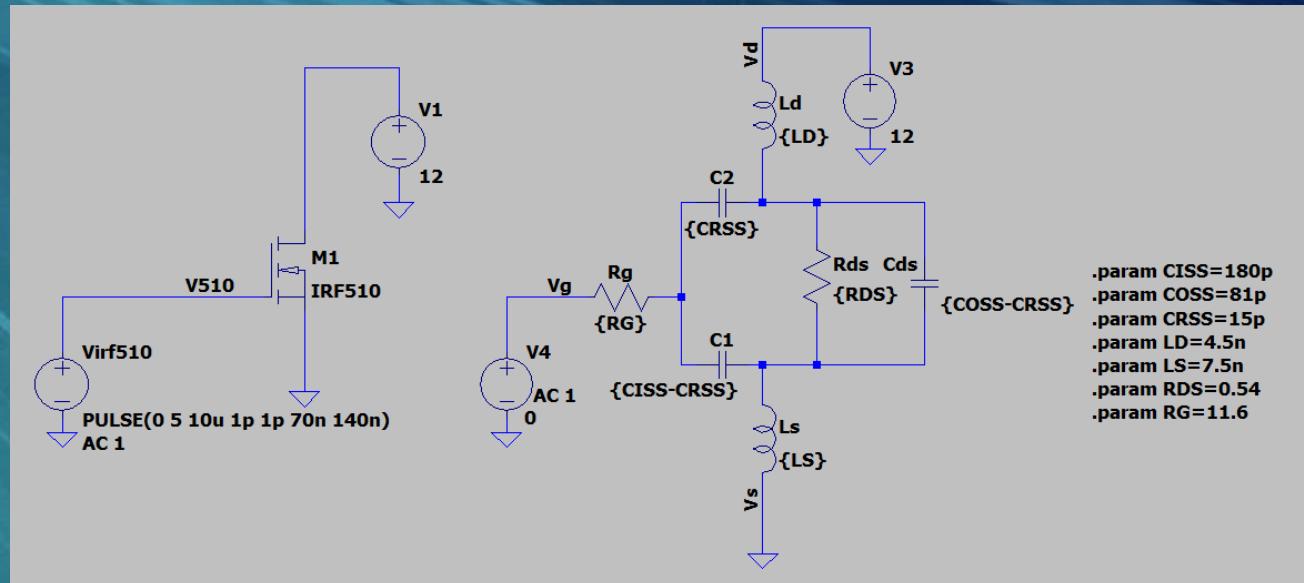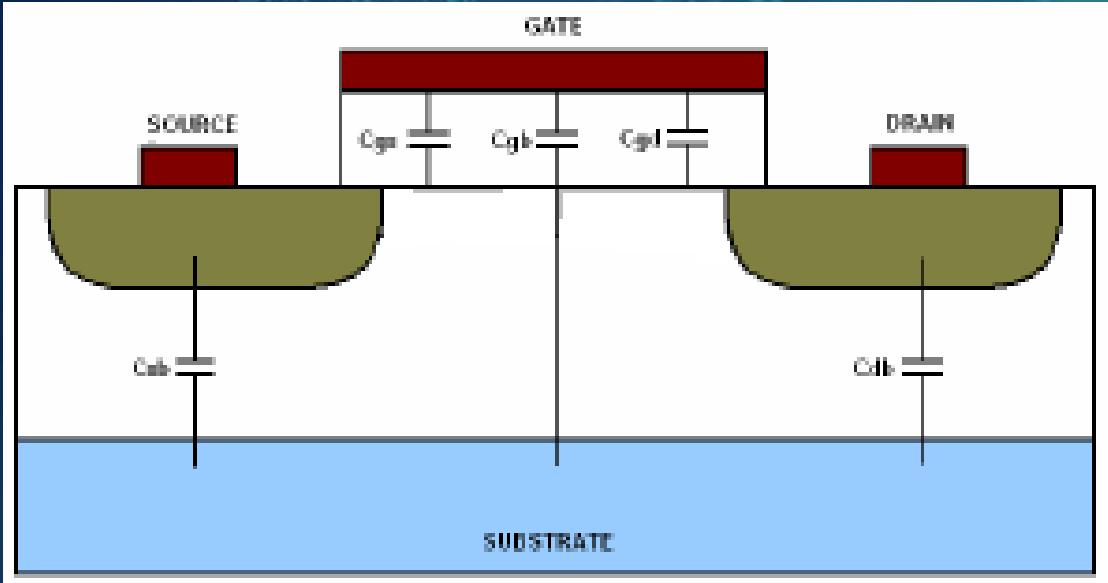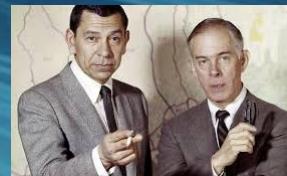

Dynamic			$f = 1.0 \text{ MHz}, \text{ see fig. 5}$	pF
Input capacitance	$C_{iss}$	-	$V_{GS} = 0 \text{ V},$	
Output capacitance	$C_{oss}$	-	$V_{DS} = 25 \text{ V},$	
Reverse transfer capacitance	$C_{rss}$	-	$f = 1.0 \text{ MHz}, \text{ see fig. 5}$	

# In our last episode...



## Errata

- ✗ All gains presented for various PA was incorrect
  - ✗ Use of Log vs Log10 in LTSpice
  - ✗ E.g.,  $\log_{10}(10) = 1$ ,  $\ln(10) = 2.3025\dots$
  - ✗  $\log_{10}$  is based on  $10^x$
  - ✗  $\log_e$  or  $\ln$  is based on  $e^x$
- ✗ No consideration for conduction angle
  - ✗ PA were not “linear”.

$\ln(x)$ log (x)	Natural logarithm of x.	LTspice	E, I, B
------------------	-------------------------	---------	---------

$\log_{10}(x)$	Base 10 logarithm. Generates a real valued output for all x.	LTspice	E, I, B
----------------	--	---------	---------

The natural logarithm of a number is its **logarithm to the base of the mathematical constant e**, which is an irrational and transcendental number approximately equal to 2.718281828459. The natural logarithm of x is generally written as  $\ln x$ ,  $\log_e x$ , or sometimes, if the base e is implicit, simply  $\log x$ .

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	46	46	44	42	41	42	45	46

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	20	20	19	18	18	18	20	20

Values are multiple of 2.3

Note:

- ✓  $\log_{10}(10)=1$ ,  $\ln(10)=2.3$
- ✓  $\log_{10}(3) = 0.48$ ,  $\ln(3)=1.1$

# In our last episode...



Bug in  
Dueling 612  
(D612)

The power of unwanted emissions shall be attenuated below the transmitter's output power, P (dBW) as follows:

- 25 dB; on any frequency removed from the channel frequency by more than 50% and up to 100% of the authorized bandwidth measured with a resolution bandwidth of 300 Hz;
- 35 dB; on any frequency removed from the channel frequency by more than 100% up to 250% of the authorized bandwidth measured with a resolution bandwidth of 300 Hz;
- $43 + 10 \log(p)$  or 70 dB, whichever is less stringent; in any 30 kHz bandwidth removed from the channel frequency by more than 250% of the authorized bandwidth.

Where:

p refers to the transmitter's output power expressed in watts.

<https://www.ic.gc.ca/eic/site/smt-gst.nsf/eng/sf01240.html>



In Canada:

- For 5W, emission: 43.7 dBc
- For 10W, emission: 44.0 dBc

✓ 44 dBc

⌚ D612 was less than 40dBc



\*\*Use Log10()

Orig. D612 PA

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	63	64	65	65	65	65	62	57
Pwr (W)	9	10	12	13	14	12	6	2

8 dB Roll Off

BITX20 Power Amp

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	28	27	26	25	25	24	23	21

7 dB Roll Off

BITX40 Power Amp

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	27	27	27	27	27	27	26	25

2 dB Roll Off

uBITX Power Amp

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	32	32	32	32	32	32	31	29

3 dB Roll Off

WA2EBY Power Amp

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	20	20	19	18	18	18	20	20

2 dB variation



Hans S. Power Amp

Freq (MHz)	1.5	3.7	5.37	7.1	10.1	14.1	21.1	28.7
Gain (dB)	20	19	18	18	17	16	12	8

12 dB?



# In our last episode...

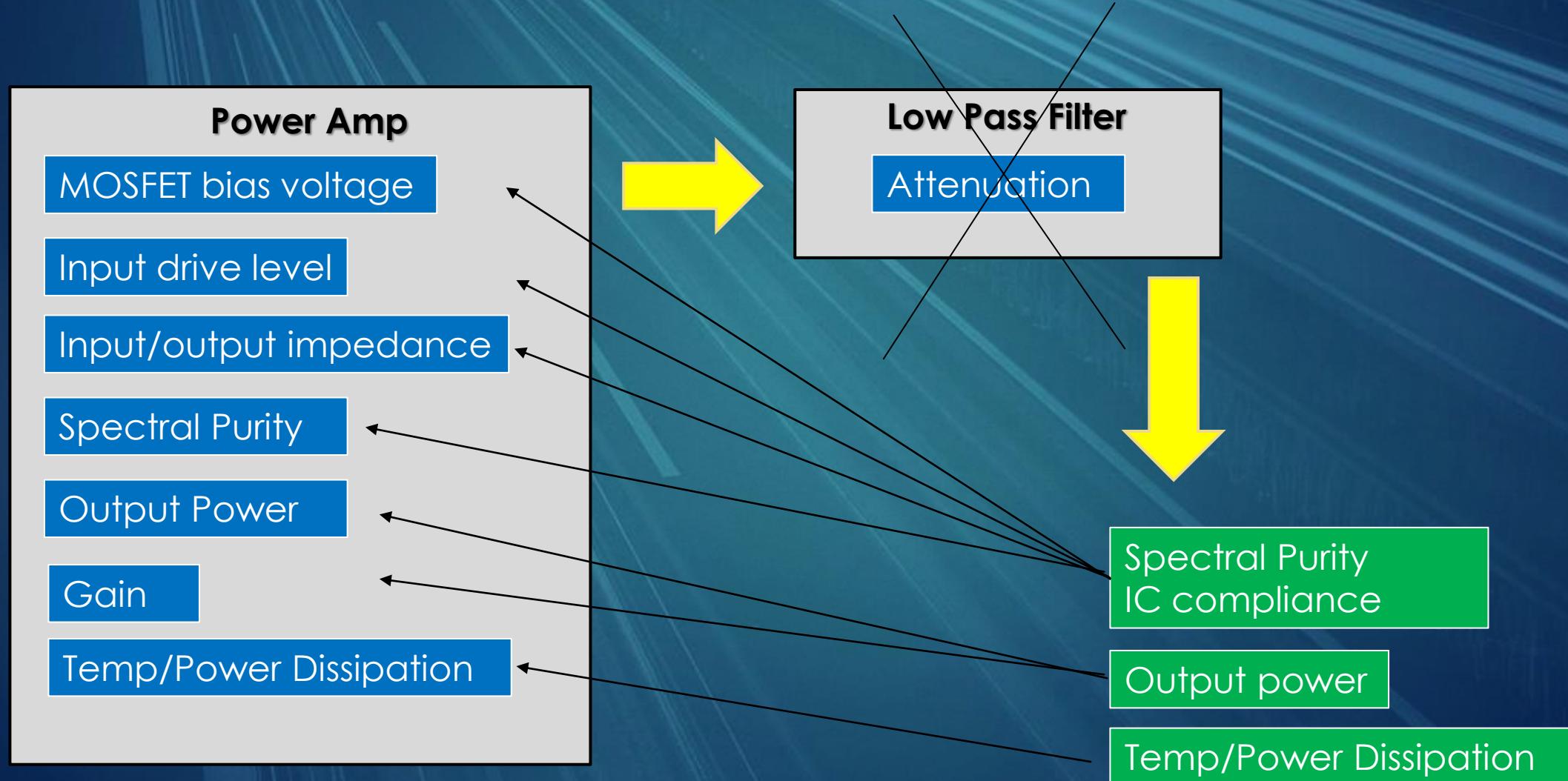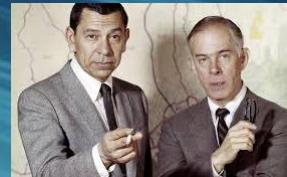


# Agenda

1. Fourier Transform Background
2. Fourier Transform vs Fast Fourier vs Discrete Fourier Transform
3. Important Parameters for FFT
4. LTSpice FFT


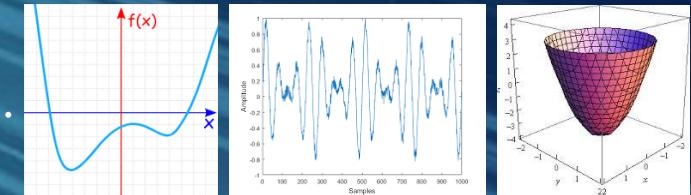
# Fourier Expansion

- A mathematical mechanism to break down any periodic function in terms of an infinite sum of sines and cosines.
- In mathematics, it's convenient to solve equations with sines and cosines.
- This was originally developed for “continuous functions”



Coefficients used to define a function

Coefficients (volume control) for Cosine Terms

$$f(t) = a_0 + a_1 \cos(t) + a_2 \cos(2t) + a_3 \cos(3t) + \dots$$
$$+ b_1 \sin(t) + b_2 \sin(2t) + b_3 \sin(3t) + \dots$$

Coefficients (volume controls) for Sine Terms

# Fourier Coefficients

With a bit of math can figure out:

$$f(x) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} a_n \cos(nx) + \sum_{n=1}^{\infty} b_n \sin(nx),$$

Notice summation is n=1 to infinity. This is the continuous Fourier Transform



$$a_0 = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) dx$$
$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos(nx) dx$$
$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(nx) dx$$

Unipolar Square Wave with DC Offset



As an example, what are the coefficients for a square wave? Turns out that cosine terms integrate to 0 and only sine terms ("a" coefficients apply).

$$\mathcal{A}_0 = Amp / 2$$

For n even:  $\mathcal{B}_n = 0$  ( $\mathcal{B}_2 = \mathcal{B}_4 = \mathcal{B}_6 = \mathcal{B}_8 = 0, \dots$ )

For n odd:  $\mathcal{B}_n = 2Amp/n\pi$  ( $Amp$  is amplitude)

For a 3Vp Square Wave:  $\mathcal{B}_0 = 1.5$ ,  $\mathcal{B}_1 = 1.9$ ,  $\mathcal{B}_3 = 0.63$ ,  $\mathcal{B}_5 = 0.38, \dots$

For a waveform (e.g., square wave), the coefficients are the amount (volume) of a particular frequency (i.e., the "nx" term in the sine terms)

# Correlation


$$a_0 = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) dx$$
$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos(nx) dx$$
$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(nx) dx$$




Performing a summation of a multiplication of two functions  $F(x)$  and  $\sin(nx)$  is used to determine if the two functions are similar. i.e., is there a correlation between the two functions.

Example 1


$F(x)$

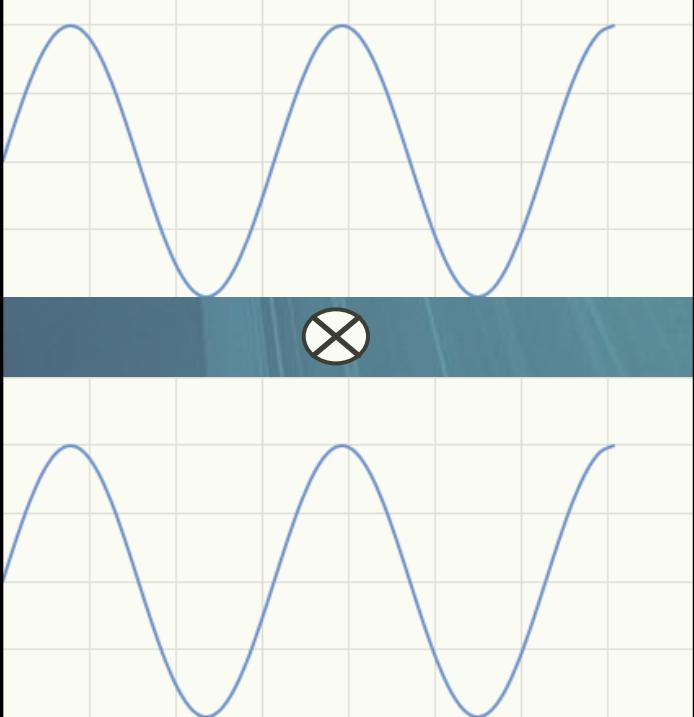

Example 2

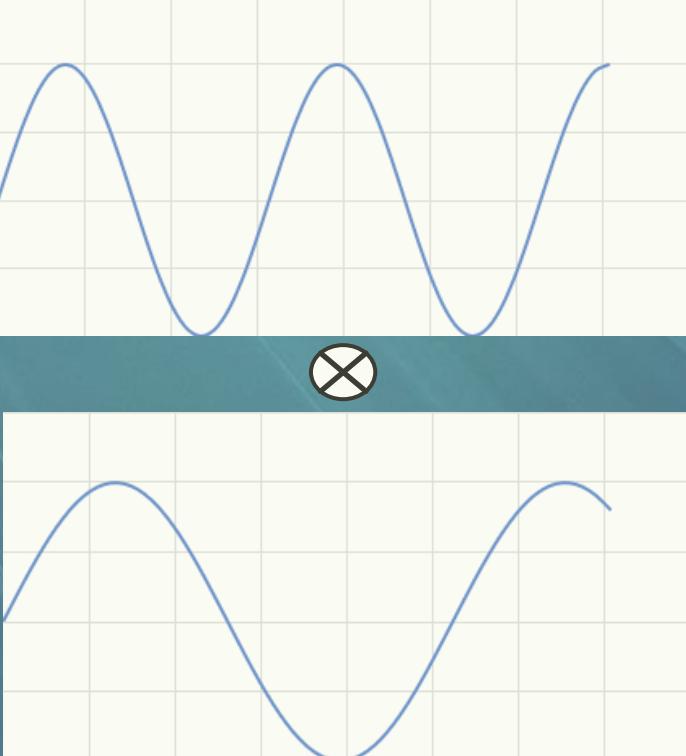

Example 3

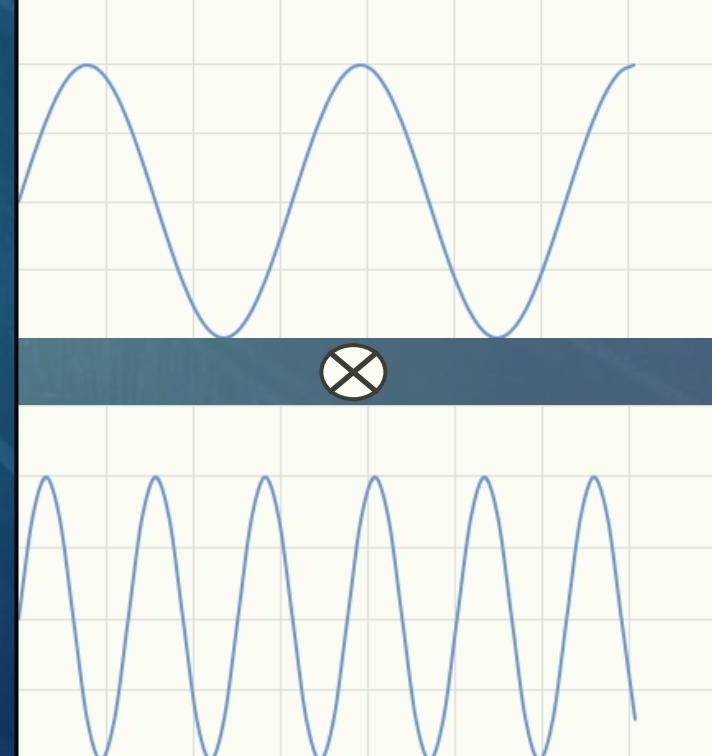

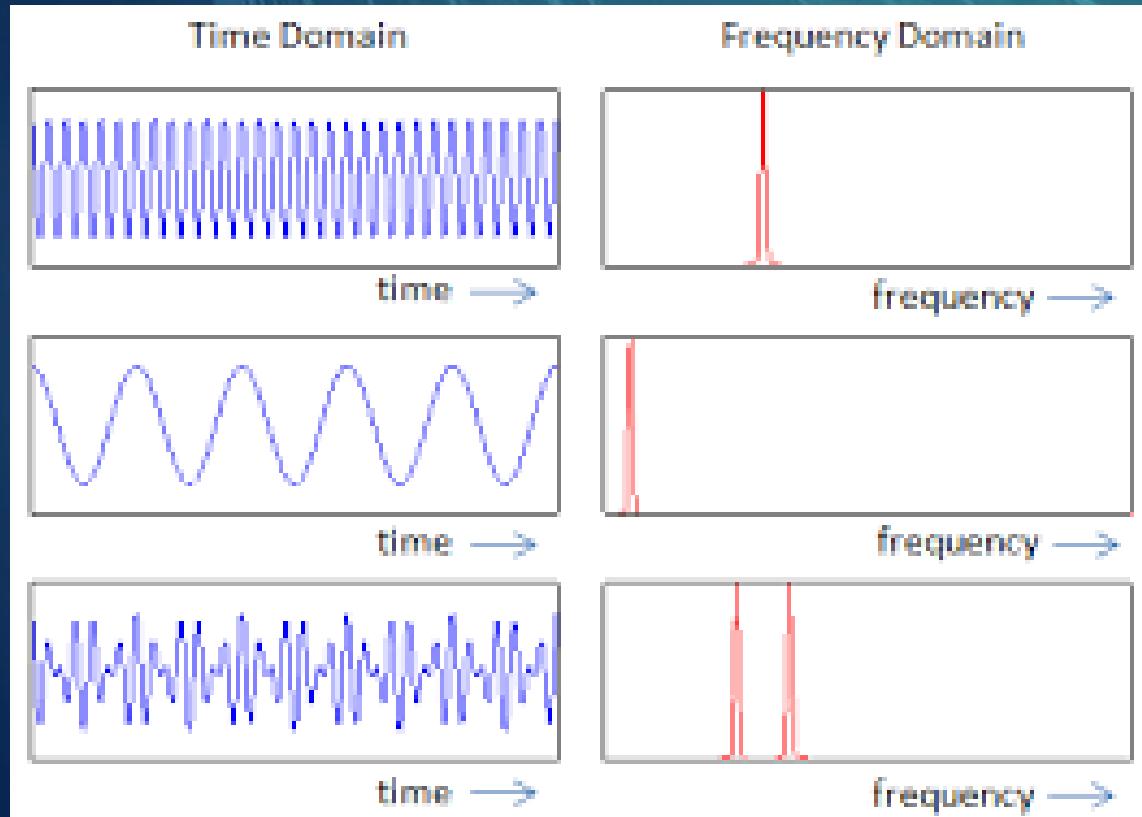
# Fourier Transform

$$a_0 = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) dx$$
$$a_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \cos(nx) dx$$
$$b_n = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(nx) dx$$



The Fourier coefficients  $a_0$ ,  $a_n$ ,  $b_n$  are telling us the strength (volume) of frequencies in a function or signal or waveform




What does this Fourier mumbo jumbo mean?

- ✓ We can use it to tell us the frequency components of an electronic waveform
- ✓ We need to figure out the coefficients for each frequency component
  - ❖ i.e., How much of 1MHz is there? How much of 13 MHz is there?
- ✓ Spectrum Analyzers do this in hardware (FPGA) at extremely fast speeds. Some scopes do this as well
- ✓ To do this using continuous “Fourier” expansion, this takes time and computing power


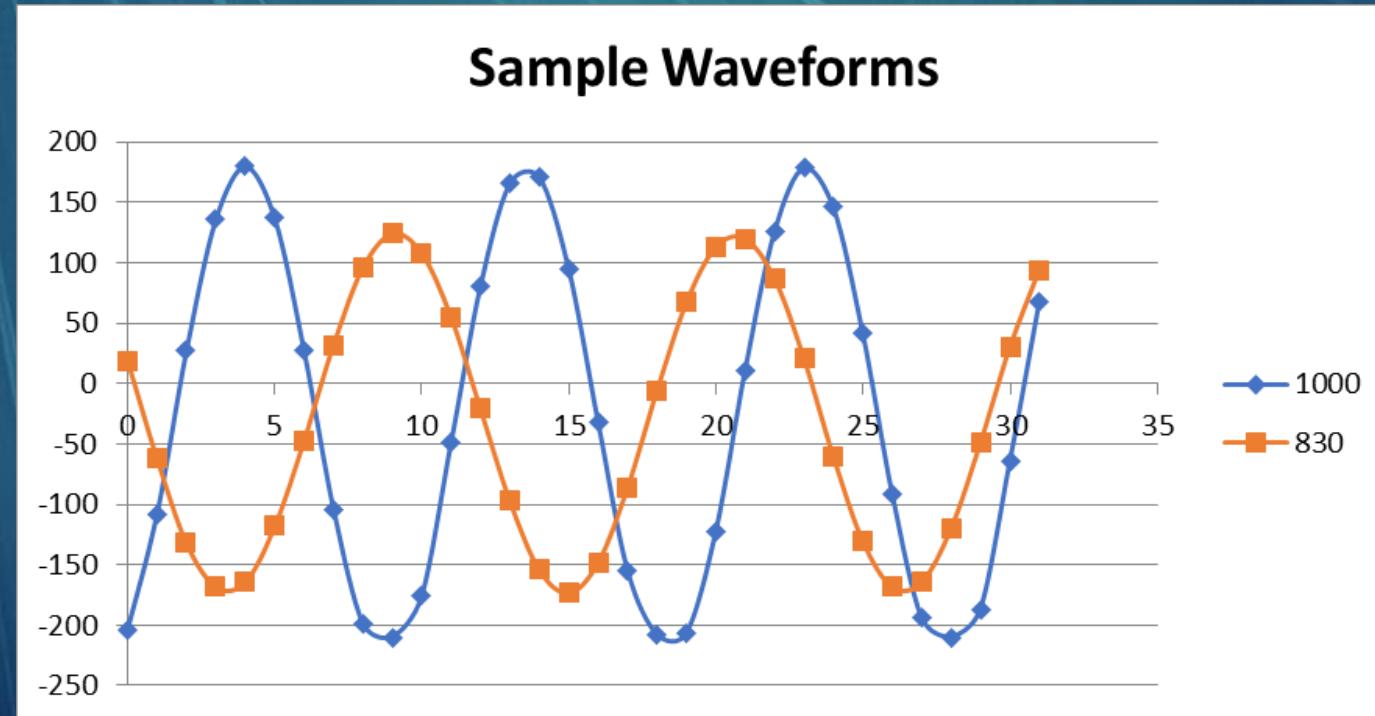
# Correlation Example

In 2017 Built a RTTY/PSK Transceiver based on an Arduino Mega

- Based conversation with Paul Darlington (M0XPD) “An 16bit Arduino Cannot Decode RTTY/PSK”
- Used M0XPD/KANGA “sudden” Rx and Tx modules
- Took audio signal and digitized at 9600 Hz for 10bit samples
- Used two tones for RTTY 830 & 1000 Hz
- Used correlation (not FFT)to detect presence of 830/1000 Hz in real time for a buffer of 30 samples



# Correlation Example

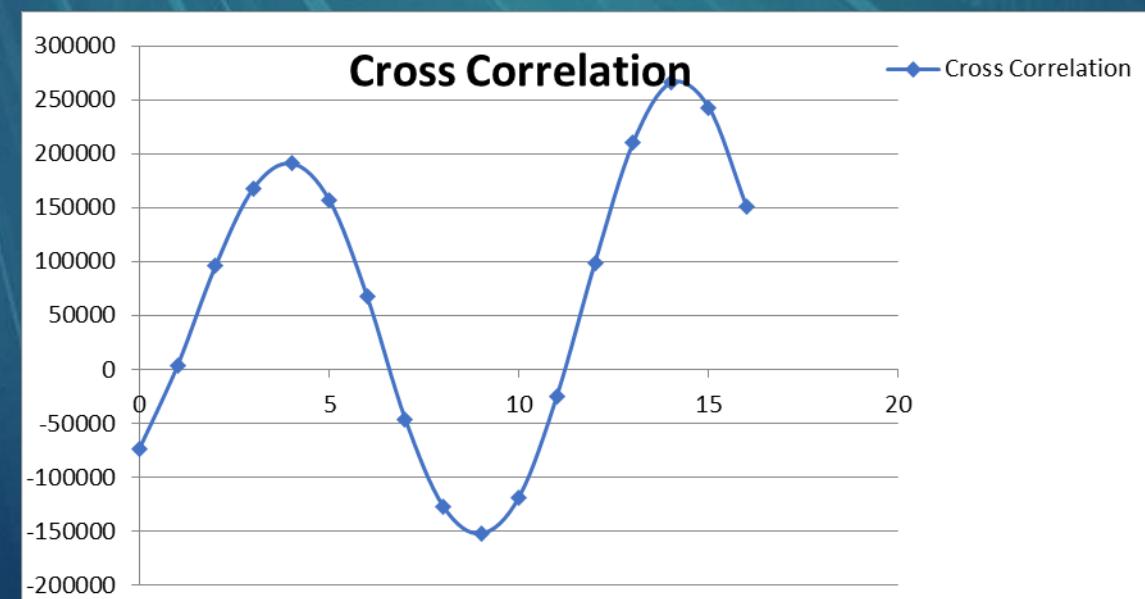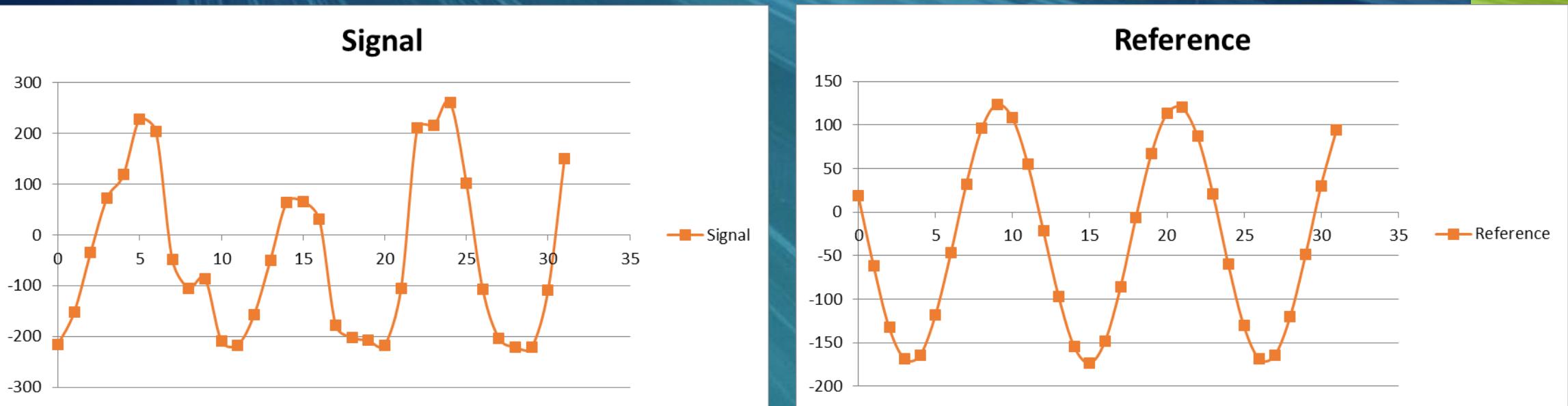


# Autocorrelation Demo




# Continuous vs Discrete

- Not practical to use continuous Fourier expansion
- In the real world we deal with digitized waveforms/signals. i.e., discrete numbers

Continuous

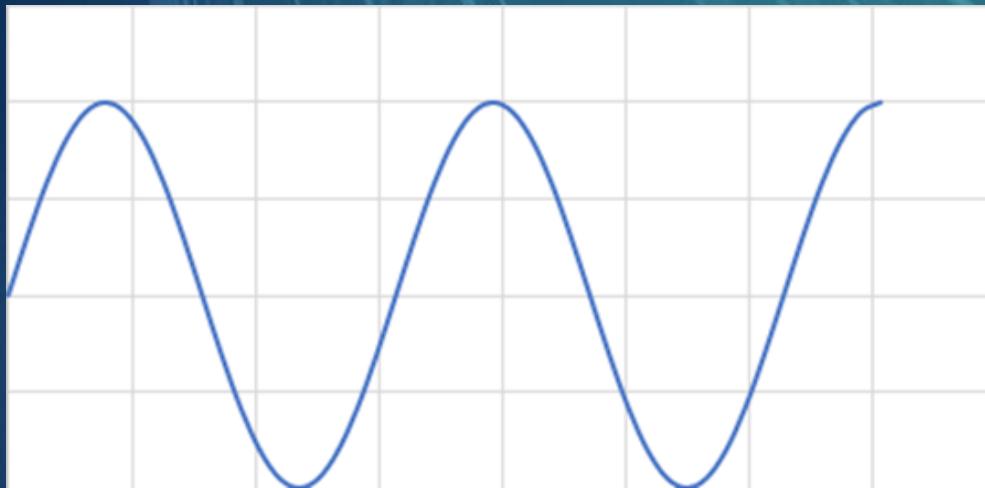


Discrete

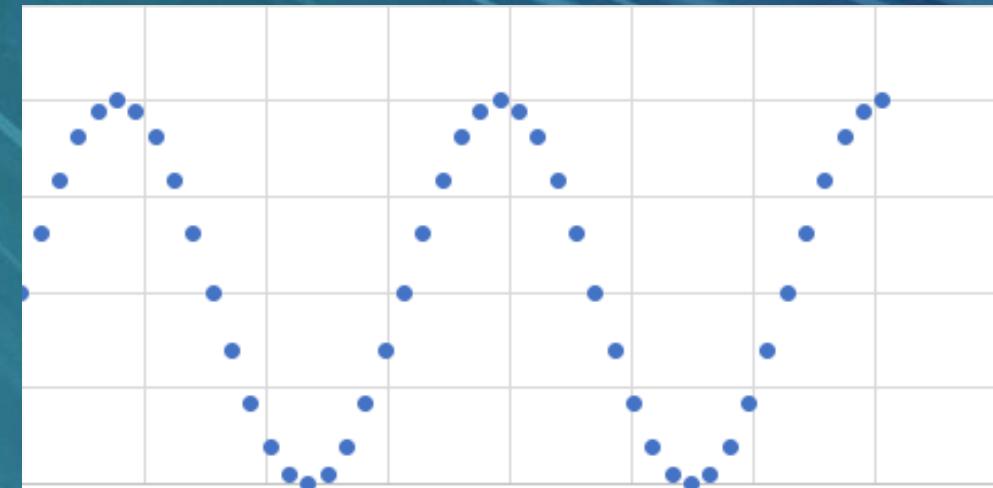
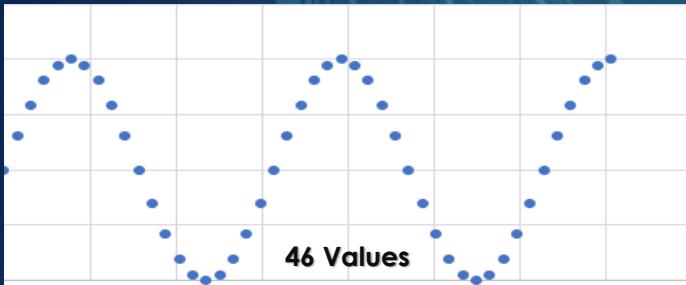
# The Discrete Fourier Transform

With some clever math, can use the Discrete Fourier Transform for data points



- Waveform is made of N values (e.g., 46)
- Values are denoted as  $x_n$   $x_1, x_2, x_3, \dots, x_n$   
e.g., 1, 1.3, 1.5, 1.8, 1.9, ...

$$X_k = \sum_{n=0}^{N-1} x_n e^{\frac{-j2\pi}{N} kn}$$



$$X_k = \sum_{n=0}^{N-1} x_n \left[ \cos \left( \frac{2\pi}{N} kn \right) - j \sin \left( \frac{2\pi}{N} kn \right) \right]$$

e is Euler's number 2.71828

"e" term is simply sine and cosine

N is total number of samples (e.g., 46)


n is the values (index) in the waveform

k is "bin" number...wait for it



$X_k$  is the strength of frequency component for the k<sup>th</sup> bin
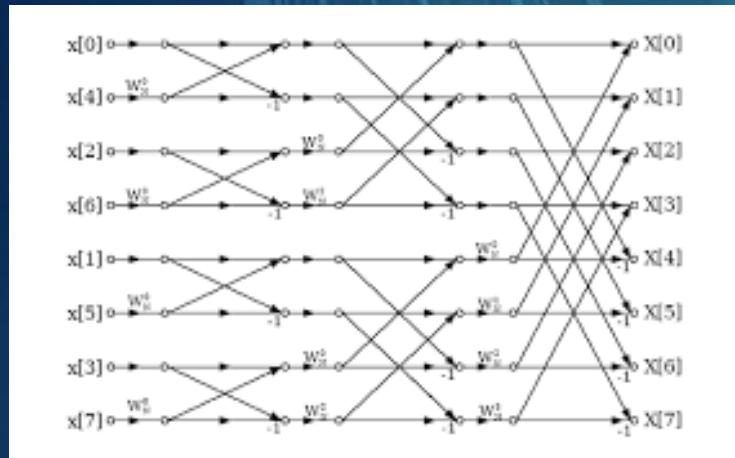
# The Fast Fourier Transform (FFT)

- With some more clever math, can optimize the calculations to complete FFT on computers and microcontrollers.



- For the FFT to work you need the number of samples to be an exponent of 2 (e.g., 4, 8, 16, 32, 64, 128... $2^y$ ). Let's assume 32 samples
- The sample Frequency determines the resolution.
- Let's assume we sample at 128 KHz, then maximum frequency we can resolve is 64 KHz (Nyquist–Shannon sampling theorem)
- The bins ( $k$ ) are the frequency resolution. For N samples, frequency resolution for each bin is  $64 \text{ KHz}/32$  or 2 KHz
- Maximum Frequency we can “detect” is Nyquist Frequency or 32 KHz

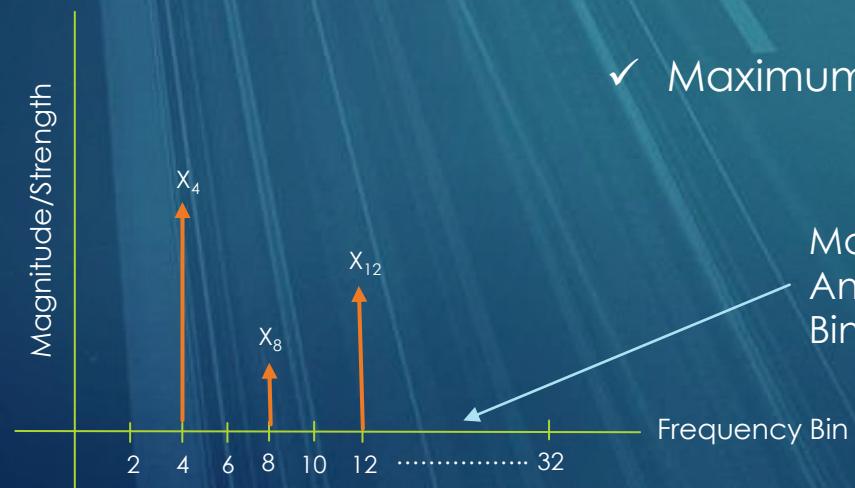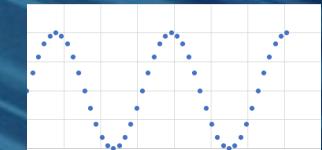



Max Frequency is 32 KHz. Which bin is for 32 KHz?  
Answer:  $2\text{ KHz} \times \text{Bin } 16 = 32 \text{ KHz}$ .  
Bins higher than 16 is a mirror image of bins 0-16 (Aliased...wraps around)

# FFT Demo


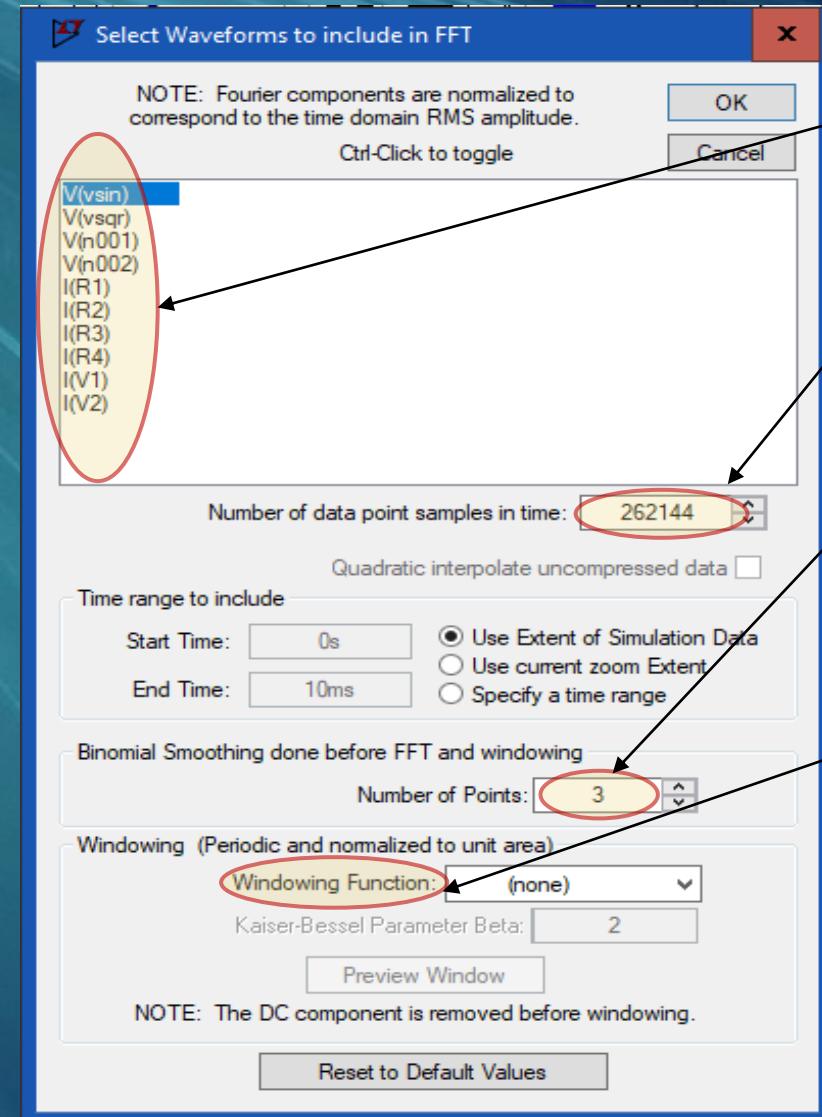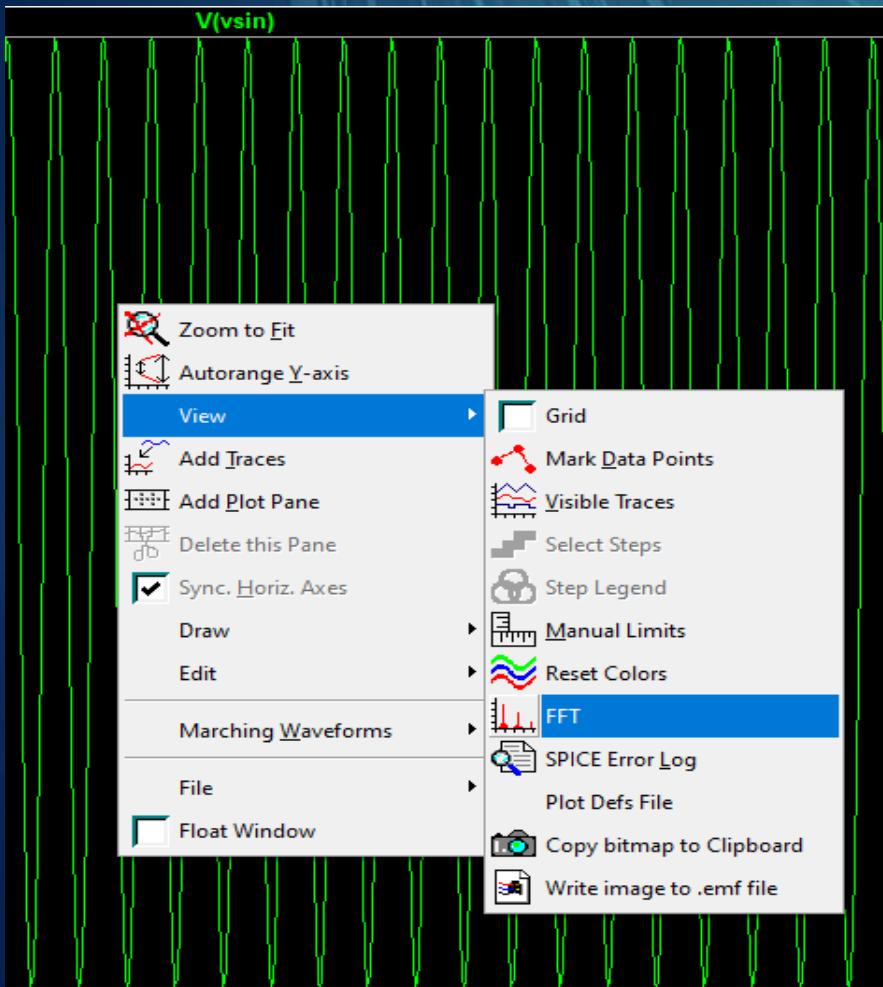
# LTSpice FFT

Can plot FFT for any signal plotted. Right Click on plot area. Select View, FFT





Select Signal

Select "N"  
 $(2^{18} = 262144)$


Average Samples. Smooth noise

For discontinuity in stream. More for real time data.

# LTSpice FFT Issues

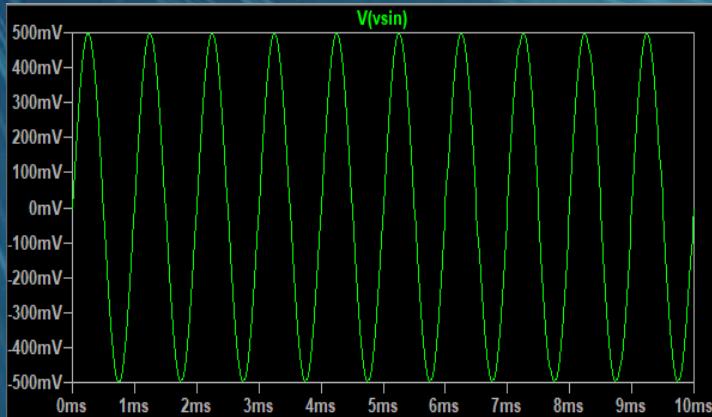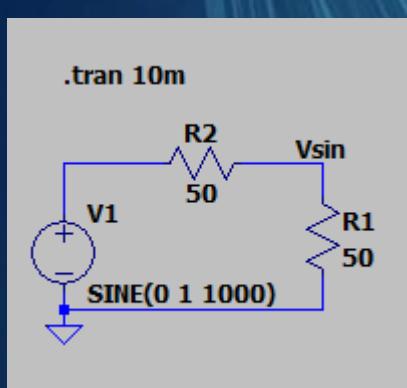


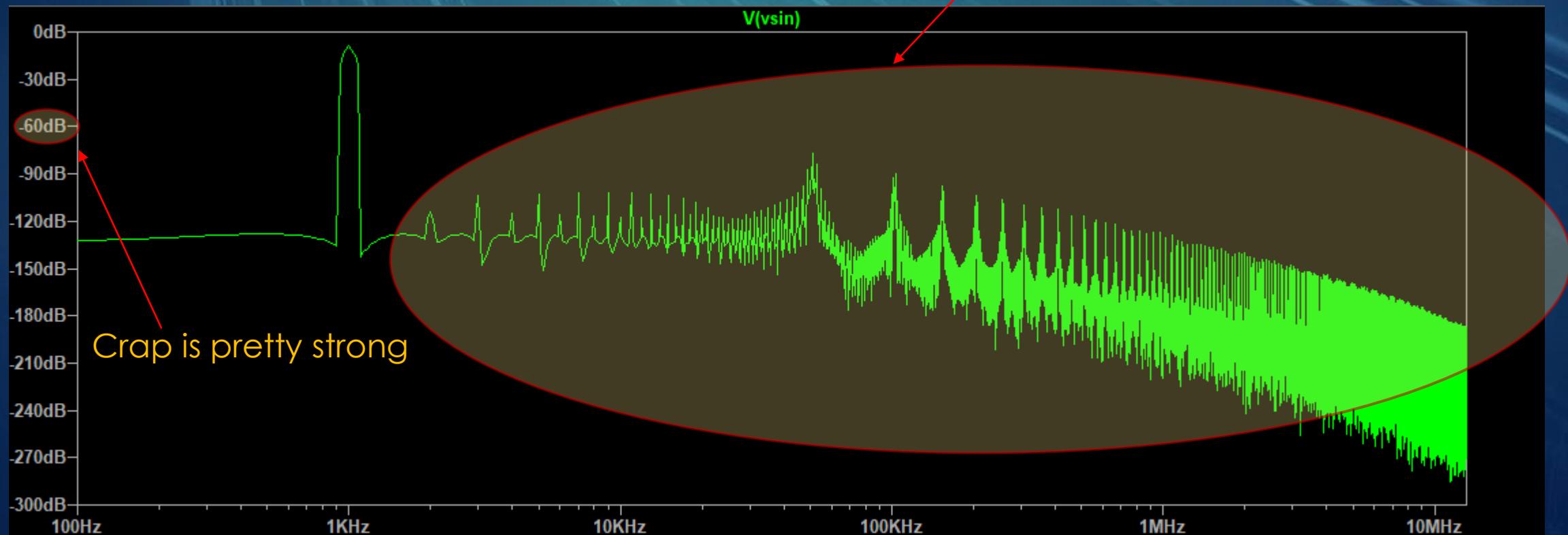
WTF?! This is a pure sine wave.  
Should only be one frequency component



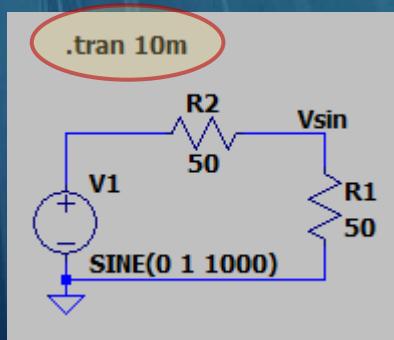
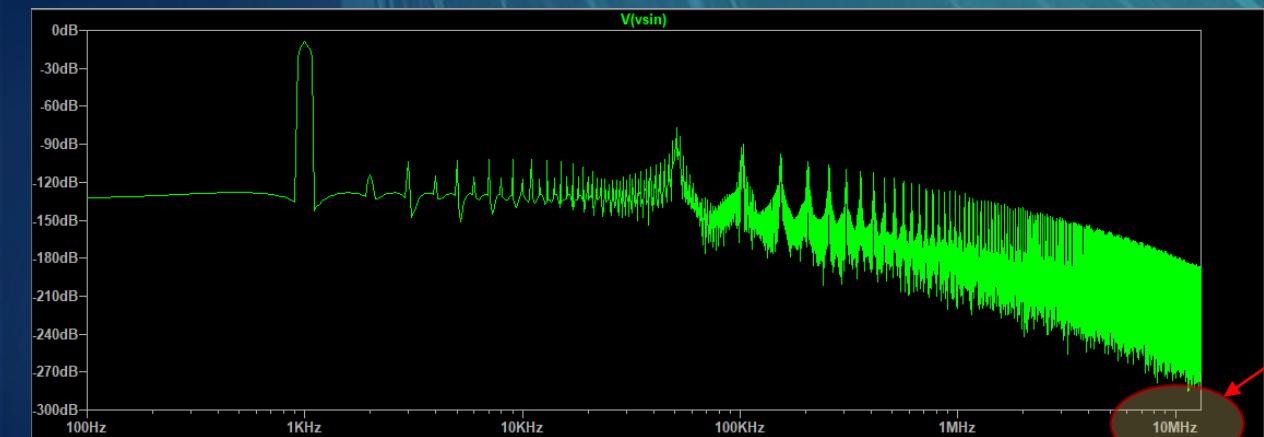
# LTSpice FFT: Issue #1 - Resolution

- The number of samples taken N determines resolution. More points the more resolution. E.g. 1024 samples will have smaller “bin” size than 262144.
- LTSpice takes the timespan & number of samples to calculate the maximum frequency to resolve

Same horizontal bandwidth, 10 MHz really?






Narrower peaks. Better resolution

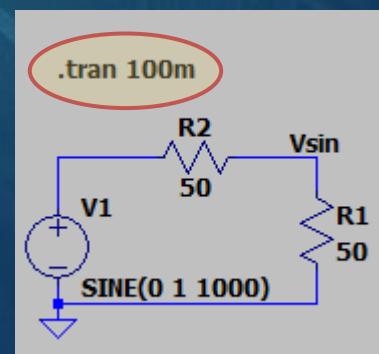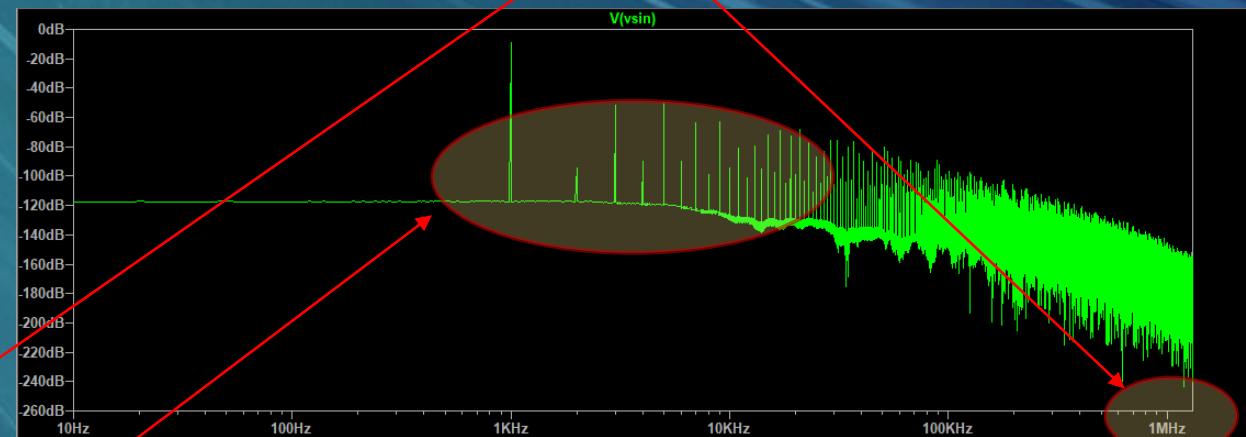

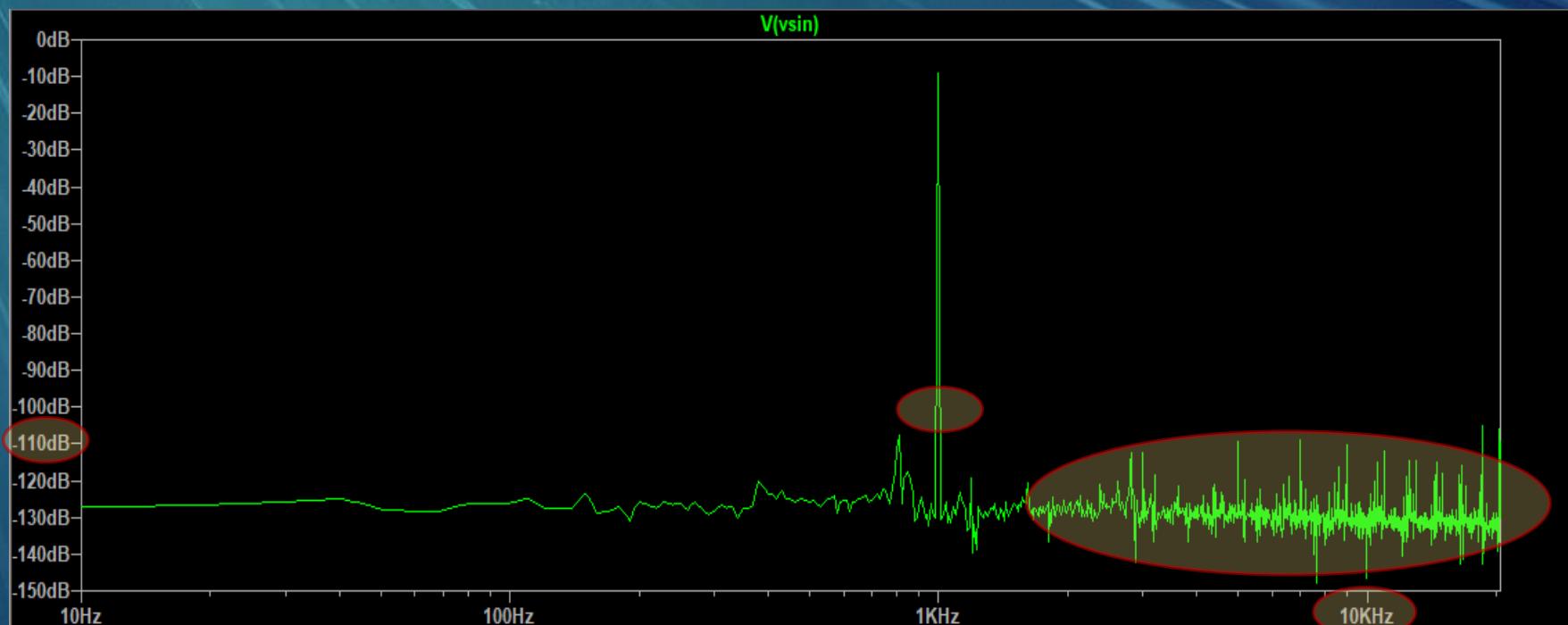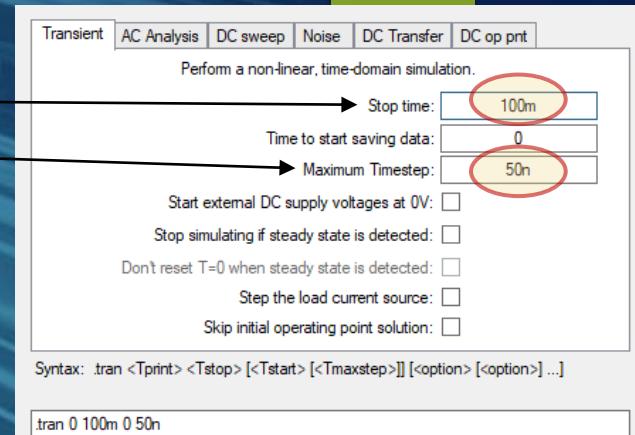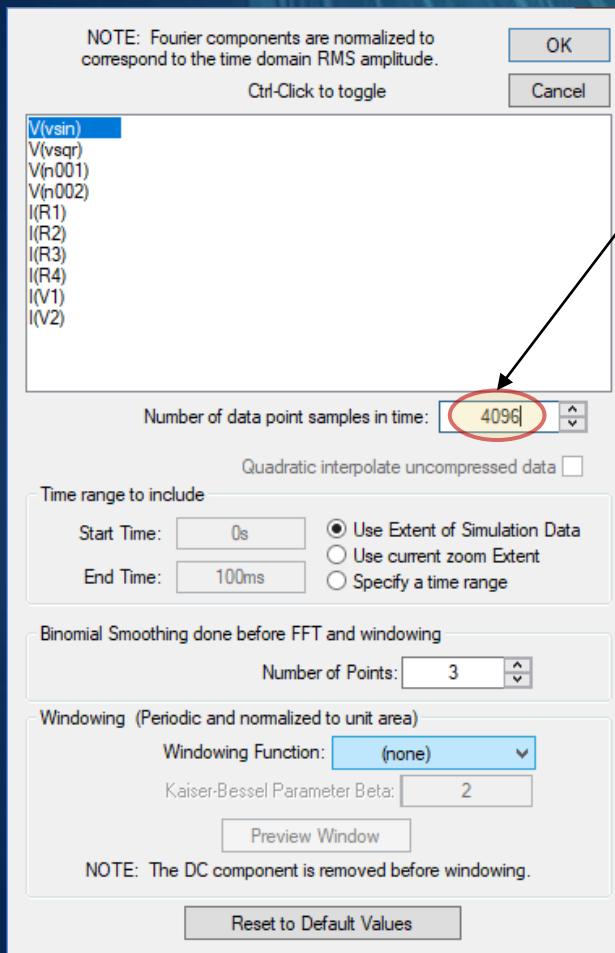
# LTSpice FFT: Issue #1 – Resolution Fixes

- ✓ Need to increase timespan for more resolution
- ✓ Need to decrease time step (sample frequency)
- ✓ Need to reduce the number of samples to process to reduce horizontal bandwidth




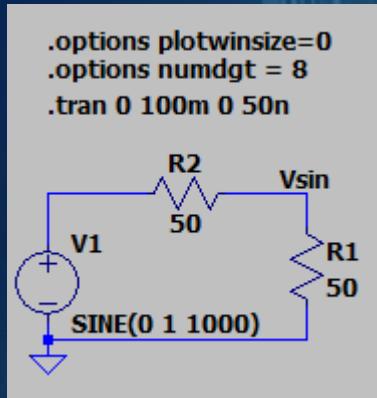
# LTSpice FFT: Issue #2 - Defaults

LTSpice samples calculated are compressed and with limited number of decimal digits



plotwinspace	Num.	300	Number of data points to compress in one window. Set to zero to disable compression.
numdgt	Num.	6	Historically "numdgt" was used to set the number of significant figures used for output data. In LTspice, if "numdgt" is set to be > 6, double precision is used for dependent variable data.

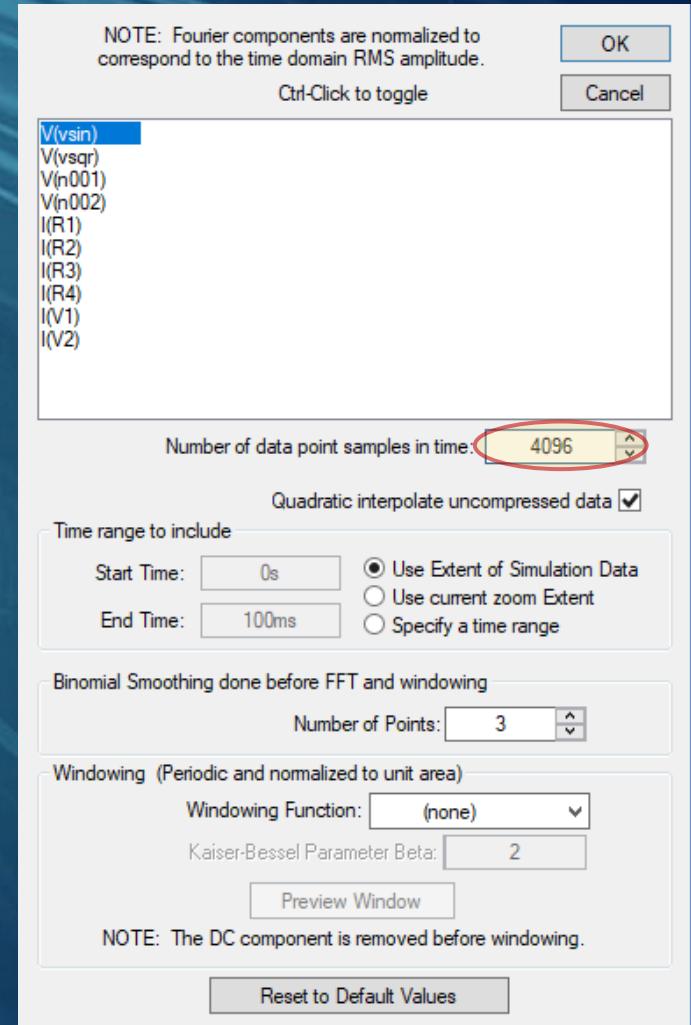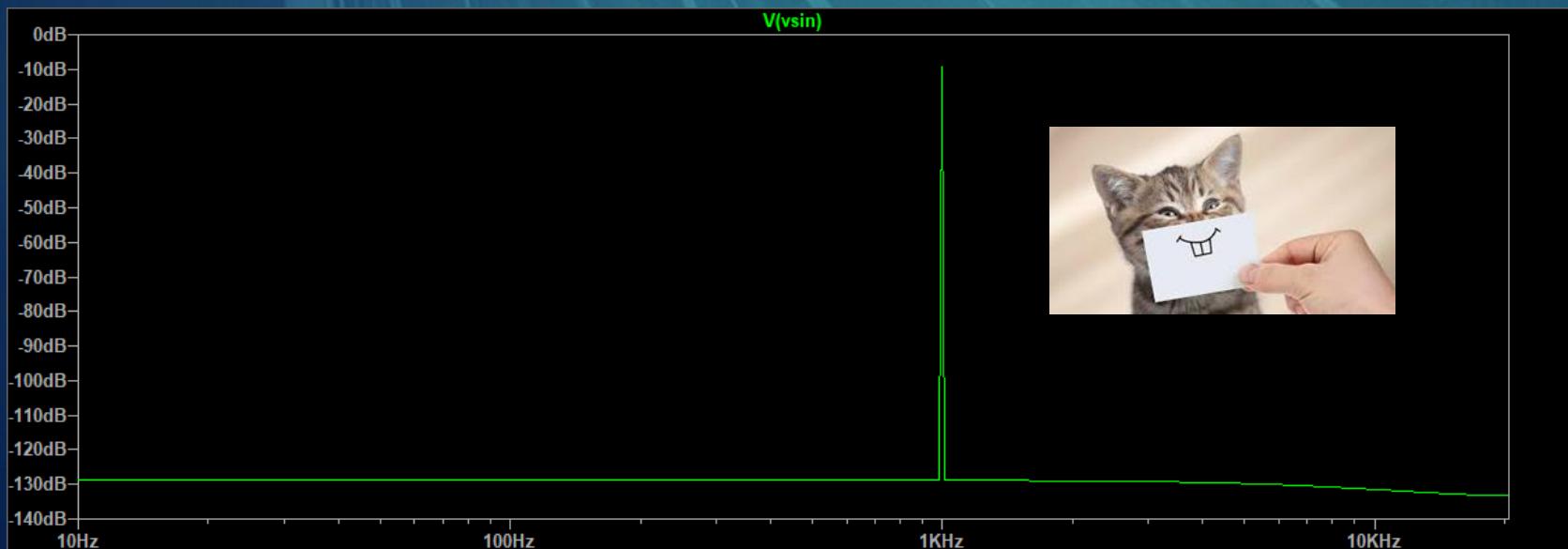[http://ltwiki.org/LTspiceHelp/LTspiceHelp/\\_OPTIONS\\_Set\\_simulator\\_options.htm](http://ltwiki.org/LTspiceHelp/LTspiceHelp/_OPTIONS_Set_simulator_options.htm)



# Please don't shoot me...

There is a **FAR** easier way to get the FFT data that we typically need

## SIMULATE TOTAL HARMONIC DISTORTION USING LTSPICE

1. Setup a transient analysis with the analysis time a multiple of your signal generator's period
2. Add `.four` command using the "SPICE directive" button. 

Syntax: `.four <frequency> [Nharmonics] [Nperiods] <datatrace1> [<data trace2> ...]`

**Note:** The frequency in `.four` command is the same as the frequency of an input source. For example, if your signal generator is set to 1kHz and you want to watch the node named "out." The command would be:

Example: `.four 1kHz V(out)`

3. After running the simulation, you can see the results of THD using *View >> SPICE error log*

<https://eecs.oregonstate.edu/education/docs/ece323/Appendix.pdf>

`.four 1000 4 -1 V(Vsin)`

```
Fourier components of V(vsin)
DC component:-0.000156885

Harmonic      Frequency      Fourier      Normalized
  Number        [Hz]          Component   Component
    1           1.000e+03     2.500e-01   1.000e+00
    2           2.000e+03     1.248e-07   4.994e-07
    3           3.000e+03     1.575e-03   6.300e-03
    4           4.000e+03     6.242e-08   2.497e-07

Total Harmonic Distortion: 0.629967% (0.630096%)
```

For harmonic distortion, we can identify how strong are the harmonics

# Total Harmonic Distortion


The **total harmonic distortion (THD or THDi)** is a measurement of the **harmonic distortion** present in a signal and is defined as the ratio of the sum of the powers of all harmonic components to the power of the **fundamental frequency**. **Distortion factor**, a closely related term, is sometimes used as a synonym.

In radio communications, devices with lower THD tend to produce less unintentional interference with other electronic devices. Since harmonic distortion tends to widen the frequency spectrum of the output emissions from a device by adding signals at multiples of the input frequency, devices with high THD are less suitable in applications such as **spectrum sharing and spectrum sensing**.<sup>[1]</sup>

$$\text{THD}_F = \frac{\sqrt{V_2^2 + V_3^2 + V_4^2 + \dots}}{V_1}$$

where  $V_n$  is the RMS value of the  $n$ th harmonic voltage and  $V_1$  is the RMS value of the fundamental component.

## Total Harmonic Distortion (THD)

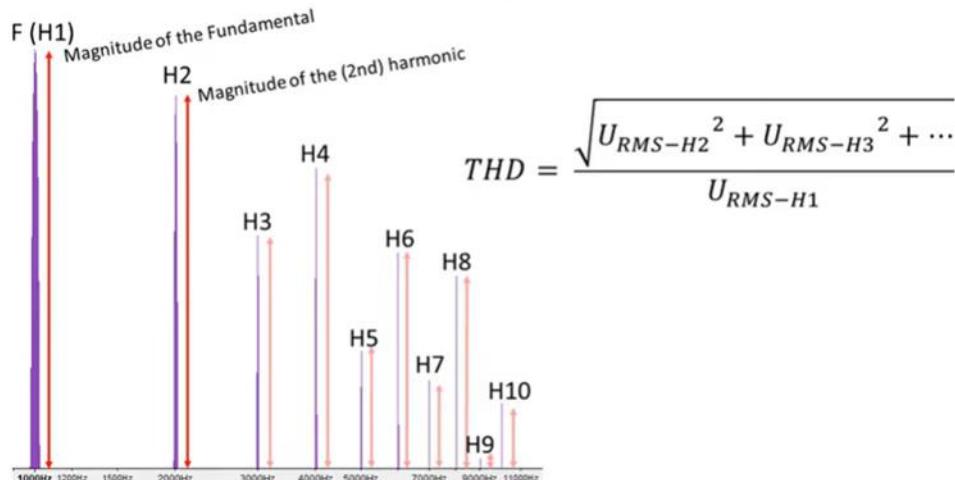

Take the square root of the sums of the squares for the harmonic strength and divide by the strength of the fundamental

# What does this mean...

- ✓ Use THD to check purity of output when I compare power amps, MOSFETS, etc


c.  $43 + 10 \log(p)$  or 70 dB, whichever is less stringent; in any 30 kHz bandwidth removed from the channel frequency by more than 250% of the authorized bandwidth.

In Canada:

- For 5W, emission: 43.7 dBc
- For 10W, emission: 44 dBc
- ✓ Assume 44 dBc


Some math....

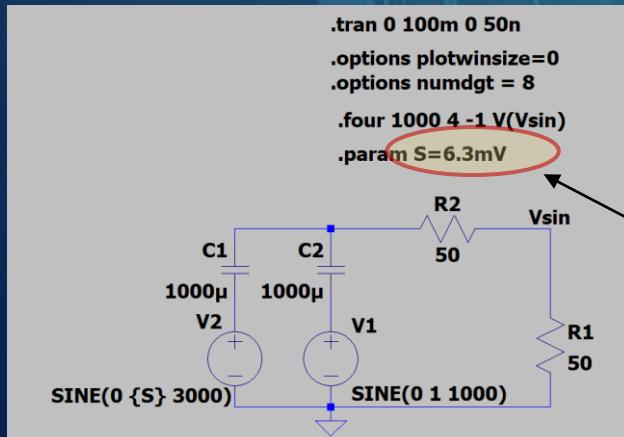- $-44 = 10 \log (P_h/P_f)$  or  $-44 = 20 \log (V_h/V_f)$
- Solve  $V_h = 0.00631 * V_f$ 
  - ✓ Any harmonic is "at most" 0.63% of fundamental



$$\begin{aligned}dB &= 20 \log (0.0063/1) \\dB &= 20 \log(6.3mV) \\dB &= -44\end{aligned}$$

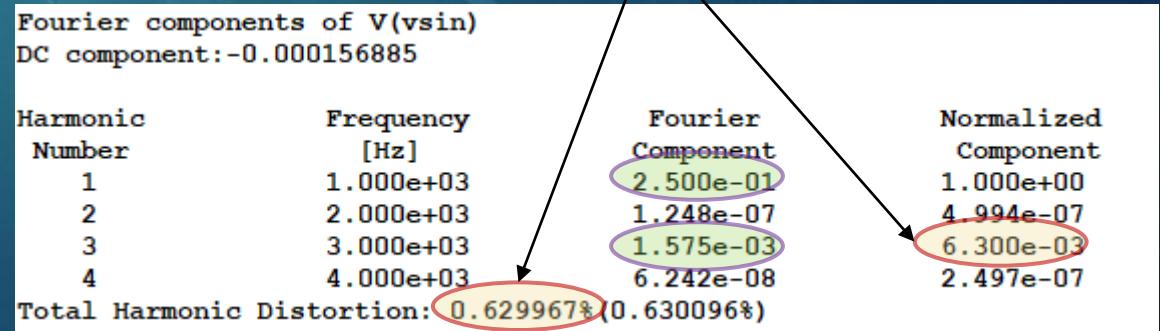
Largest harmonic must be 0.63% to meet IC



# Summary

- Use Fourier Transform to decompose a frequency into fundamental components
- Use Discrete Fourier Transform to decomposes sampled waveform (e.g. Spectrum Analyzer, Scope with FFT)
- Use Fast Fourier Transform to optimize Discrete Fourier Transform
- There are rules when using FFT
  - ✓ e.g.,  $2n$  data points, Sample Frequency, bin size, etc.)
- LTSpice by default does a crappy job of doing FFT.
  - ✓ Disable compression
  - ✓ Change decimal precision
  - ✓ Increase number of data points (longer simulation time, faster computation interval)
  - ✓ Reduce the number of data points in FFT to match resolution
- For Harmonic Analysis use the .four directive
  - ✓ Gives strength of harmonics
  - ✓ Provides DC level
  - ✓ Provides Total Harmonic Distortion (THD)

# Rabbit Hole #3.2: LTSpice Measurements

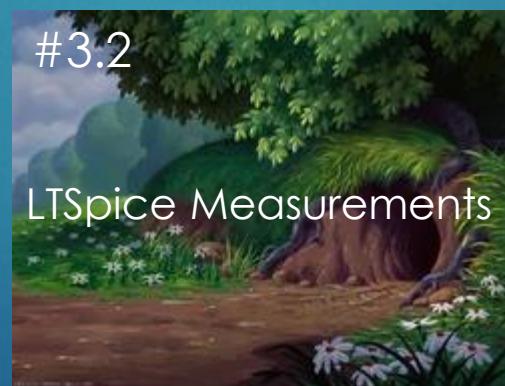

# Measure Command


- Spice Directive
- Details at:

[http://ltwiki.org/LTspiceHelp/LTspiceHelp\\_MEASURE\\_Evaluate\\_User Defined Electrical Quantities.htm](http://ltwiki.org/LTspiceHelp/LTspiceHelp_MEASURE_Evaluate_User Defined Electrical Quantities.htm)



[http://km2000.us/franklinduan/articles/hspice/hspice\\_2001\\_2-48.html](http://km2000.us/franklinduan/articles/hspice/hspice_2001_2-48.html)

- Walkthrough at: <https://www.youtube.com/watch?v=DqLXW4qn6j0>

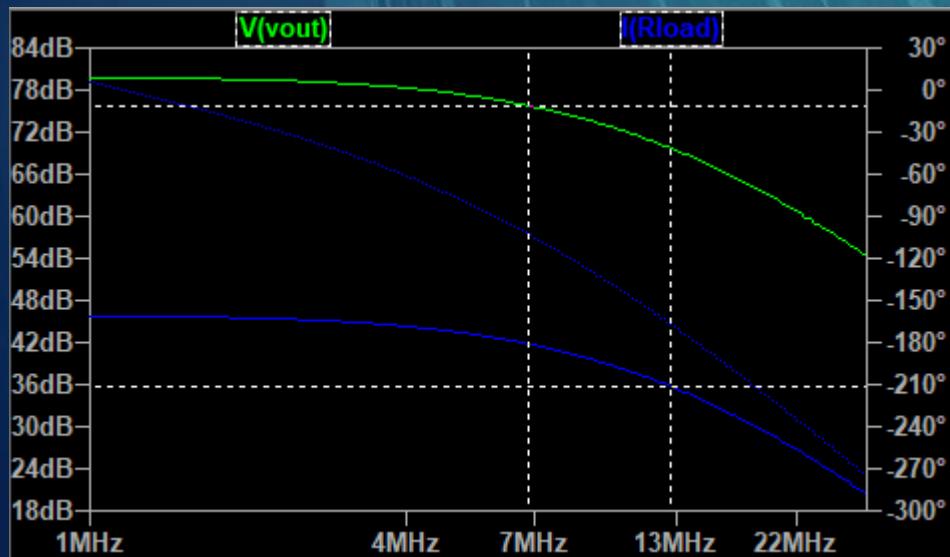- Mechanism to make measurements without using Graph and Cursors




- Values given in “Error Log”

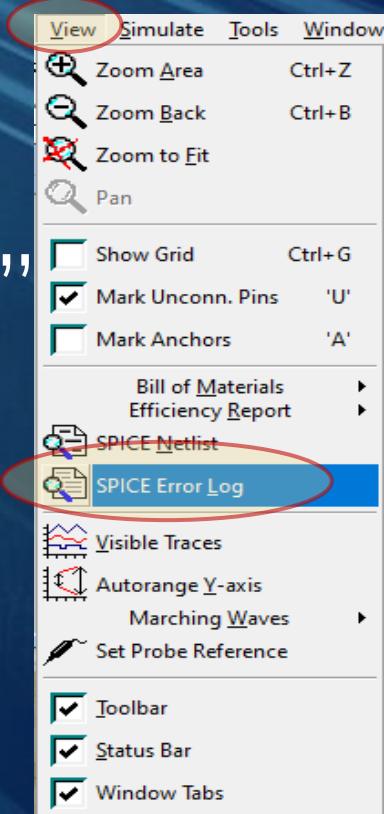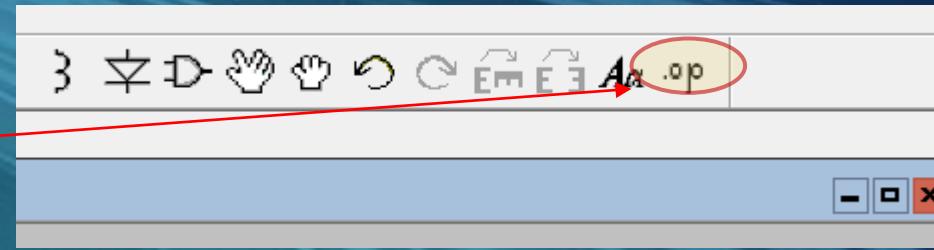

# LTS spice Measurements

## Measure a point

```
Syntax: .MEAS [SURE] [AC|DC|OP|TRAN|TF|NOISE] <name>
+ [<FIND|DERIV|PARAM> <expr>]
+ [WHEN <expr> | AT=<expr>]
+ [TD=<val1>] [<RISE|FALL|CROSS>=<count1>|LAST]
```

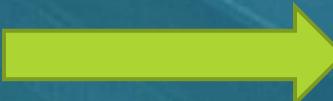

```
.meas AC Irl FIND I(Rload) WHEN Freq=1.5Meg
.meas AC V1 FIND V(Vout) WHEN Freq=1.5Meg
.meas AC X1 PARAM V1/Irl
```

## Measure over a range

```
Syntax: .MEAS [AC|DC|OP|TRAN|TF|NOISE] <name>
+ [<AVG|MAX|MIN|PP|RMS|INTEG> <expr>]
+ [<TRIG> <lhs1> [[VAL]=]<rhs1>] [TD=<val1>]
+ [<RISE|FALL|CROSS>=<count1>]
+ [<TARG> <lhs2> [[VAL]=]<rhs2>] [TD=<val2>]
+ [<RISE|FALL|CROSS>=<count2>]
```



```
.meas TRAN Vi RMS V(Vin)
.meas TRAN Vo RMS V(Vout)
.meas TRAN Io RMS I(Rload)
.meas TRAN P PARAM Vo*Io
.meas TRAN Gv PARAM 20*log(Vo/Vi)
```

Keyword	Operation perform over interval
AVG	Compute the average of <expr>
MAX	Find the maximum value of <expr>
MIN	Find the minimum value of <expr>
PP	Find the peak-to-peak of <expr>
RMS	Compute the root mean square of <expr>
INTEG	Integrate <expr>

# Example Measurements

## Measure sometime at a specific time/frequency:

- ✓ .meas AC Irl FIND I(Rload) WHEN Freq=1.5Meg //This is at a specific frequency
- ✓ .meas TRAN Vx FIND V(Vout) WHEN time=37us //This is at a specific time

```
vx: v(vout)=29.6018 at 3.7e-005
```

```
irl: i(rload)=(-54.1277dB,-10.5573°) at 1.5e+006
```

```
v1: v(vout)=(79.6417dB,-10.496°) at 1.5e+006  
v3: v(vout)=(78.4865dB,-56.2326°) at 3.7e+006  
v7: v(vout)=(75.4355dB,-106.72°) at 7.1e+006  
v14: v(vout)=(68.1973dB,-179.061°) at 1.41e+007  
v18: v(vout)=(64.2513dB,150.597°) at 1.81e+007  
v21: v(vout)=(61.4771dB,131.176°) at 2.11e+007  
v29: v(vout)=(54.9895dB,89.0891°) at 2.9e+007
```

## Measure sometime over a range

- ✓ .meas TRAN P0 RMS (V(Vin)\*I(Rload))
- ✓ .meas TRAN P1 RMS (V(Vin)\*I(Rload)) trig at 50us //This is from 53us to end)
- ✓ .meas TRAN P2 RMS (V(Vin)\*I(Rload)) from 10us to 55us

```
p0: RMS (v(vout)*i(rload))=12.8336 FROM 0 TO 0.0001  
p1: RMS (v(vout)*i(rload))=13.0288 FROM 5e-005 TO 0.0001  
p2: RMS (v(vout)*i(rload))=13.1959 FROM 1e-005 TO 5.5e-005  
vx: v(vout)=29.6018 at 3.7e-005  
vi: RMS (v(vin))=0.0140959 FROM 0 TO 0.0001  
vo: RMS (v(vout))=24.5653 FROM 0 TO 0.0001  
io: RMS (i(rload))=0.491307 FROM 0 TO 0.0001  
p: vo*io=12.0691  
gv: 20*log(vo/vi)=149.264
```

```
Syntax: .MEAS [SURE] [AC|DC|OP|TRAN|TF|NOISE] <name>  
+ [<FIND|DERIV|PARAM> <expr>]  
+ [WHEN <expr> | AT=<expr>]]  
+ [TD=<val1>] [<RISE|FALL|CROSS>=[<count1>|LAST]]
```

```
Syntax: .MEAS [AC|DC|OP|TRAN|TF|NOISE] <name>  
+ [<AVG|MAX|MIN|PP|RMS|INTEG> <expr>]  
+ [TRIG <lhs1> [<VAL>=<rhs1>] [TD=<val1>]  
+ [<RISE|FALL|CROSS>=<count1>]  
+ [TARG <lhs2> [<VAL>=<rhs2>] [TD=<val2>]  
+ [<RISE|FALL|CROSS>=<count2>]
```

Keyword	Operation perform over interval
AVG	Compute the average of <expr>
MAX	Find the maximum value of <expr>
MIN	Find the minimum value of <expr>
PP	Find the peak-to-peak of <expr>
RMS	Compute the root mean square of <expr>
INTEG	Integrate <expr>

# Example Measurements

Measure sometime at a specific time/frequency:

- ✓ .meas AC Irl FIND I(Rload) WHEN Freq=1.5Meg //This is at a specific point

```
irl: i(rload)=(-54.1277dB,-10.5573°) at 1.5e+006
```

```
Syntax: .MEAS [SURE] [AC|DC|OP|TRAN|TF|NOISE] <name>
+ [<FIND|DERIV|PARAM> <expr>]
+ [WHEN <expr> | AT=<expr>]]
+ [TD=<val1>] [<RISE|FALL|CROSS>=<count1>|LAST]]
```

Measure sometime over a range

- ✓ .meas TRAN P0 RMS (V(Vin)\*I(Rload))
- ✓ .meas TRAN P1 RMS (V(Vin)\*I(Rload)) trig at 50us //This is from 50us to end)
- ✓ .meas TRAN P2 RMS (V(Vin)\*I(Rload)) from 10us to 55us

```
p0: RMS(v(vin)*i(rload))=0.00649814 FROM 0 TO 0.0001
p1: RMS(v(vin)*i(rload))=0.0065611 FROM 5e-005 TO 0.0001
p2: RMS(v(vin)*i(rload))=0.00661577 FROM 1e-005 TO 5.5e-005
vi: RMS(v(vin))=0.014096 FROM 0 TO 0.0001
vo: RMS(v(vout))=24.5654 FROM 0 TO 0.0001
io: RMS(i(rload))=0.491308 FROM 0 TO 0.0001
p: vo*io=12.0692
gv: 20*log(vo/vi)=149.264
```

```
Syntax: .MEAS [AC|DC|OP|TRAN|TF|NOISE] <name>
+ [<AVG|MAX|MIN|PP|RMS|INTEG> <expr>]
+ [TRIG <lhs1> [[VAL]=]<rhs1>] [TD=<val1>]
+ [<RISE|FALL|CROSS>=<count1>]
+ [TARG <lhs2> [[VAL]=]<rhs2>] [TD=<val2>]
+ [<RISE|FALL|CROSS>=<count2>]
```

Keyword	Operation perform over interval
AVG	Compute the average of <expr>
MAX	Find the maximum value of <expr>
MIN	Find the minimum value of <expr>
PP	Find the peak-to-peak of <expr>
RMS	Compute the root mean square of <expr>
INTEG	Integrate <expr>

# Power Amp Measurements

What to measure when comparing power amps?

1. Power Output
2. Power Dissipated (temperature)
3. Power Margin (difference in above)
4. Gain
5. Input impedance
6. Output Impedance
7. Gate characteristics (Voltage, Bias)
8. Drain characteristics
9. Harmonics (THD)
10. Troubleshooting voltages

```
.tran 0 100u 95u 100p
.options plotwinspace=0
.options numdgt = 8

.param Rja 62
.param Rcs 0.50
.param Rjc 3.5
.param Tj 150

.meas TRAN Vinr RMS V(Vin)
.meas TRAN Vo1r RMS V(Vo1)
.meas TRAN Vinsr RMS V(Vins)
.meas TRAN Voutr RMS V(Vout)
.meas TRAN Vgr RMS V(Vg)
.meas TRAN Vgavg AVG V(Vg)
.meas TRAN Vgmax MAX V(Vg)
.meas TRAN Vgmin MIN V(Vg)
.meas TRAN Vbiasr RMS V(Vbias)
.meas TRAN Iinr RMS I(Rin)
.meas TRAN Pdis AVG (V(vd)*Id(m1) + V(vg)*Ig(m1))
;.meas TRAN Pdis AVG (V(vd)*Ix(m1:d) + V(vg)*Ix(m1:g))
.meas TRAN Pq1 AVG ( (V(vc)-V(ve))*Ic(Q1) + (V(Vb)-V(ve))*Ib(Q1)
.meas TRAN Po AVG (V(Vo)*V(Vo)/50)
.meas TRAN Pout AVG (V(Vout)*I(Rout))
.meas TRAN Pmar PARAM Pout-Pdis
.meas TRAN Zin PARAM 150*Vinr/(vinsr-Vinr)
.meas TRAN Temp PARAM Pdis*Rja
.meas TRAN Rheatsink PARAM ((Tj-25)/Pdis-Rcs-Rjc)
.meas TRAN Pin PARAM (Vinsr-Vinr)*Iinr
.meas TRAN Gp PARAM 10*log(Pout/Pin)
.meas TRAN Gv PARAM 10*log(Voutr/Vinr)
.meas TRAN Gv1 PARAM 10*log(Vo1r/Vinr)

.four {F} 4 -1 V(vout)
```

# Sample Measurements

- 1) Set bias to sweep between range in data sheet. Set Input to be initially 1.5-2 times bias voltage
- 2) Select best power margin. Increase/decrease bias to Vgate min is slightly above 0
- 3) Select base bias and find idle current. Select resonable temperature
- 3) Select best output Vout harmonics must be smaller than (or equal) 7.08E-3
- 4) Sweep input to get best power output and power margin and output harmonics


```
;step param S 1 10 1
.param S 7.5
.param F 14.1Meg
.param B 4.15
.param Z 17
.step param F list 1.5Meg 3.7Meg 5.37Meg 7.1Meg 10.1Meg 14.1Meg 21.1Meg 28.7Meg
.param S 3
.param B 4.375
.step param B 4.0 4.3 0.15
.param F 14.1Meg
.param S 10
.step param B 4.0 4.3 0.15
.param F 14.1Meg
.param S 0
```

Set bias and input to set 28Mhz harmonic about 44dBc

Bias: 4.15V@88mA

Input 7.5 Vp

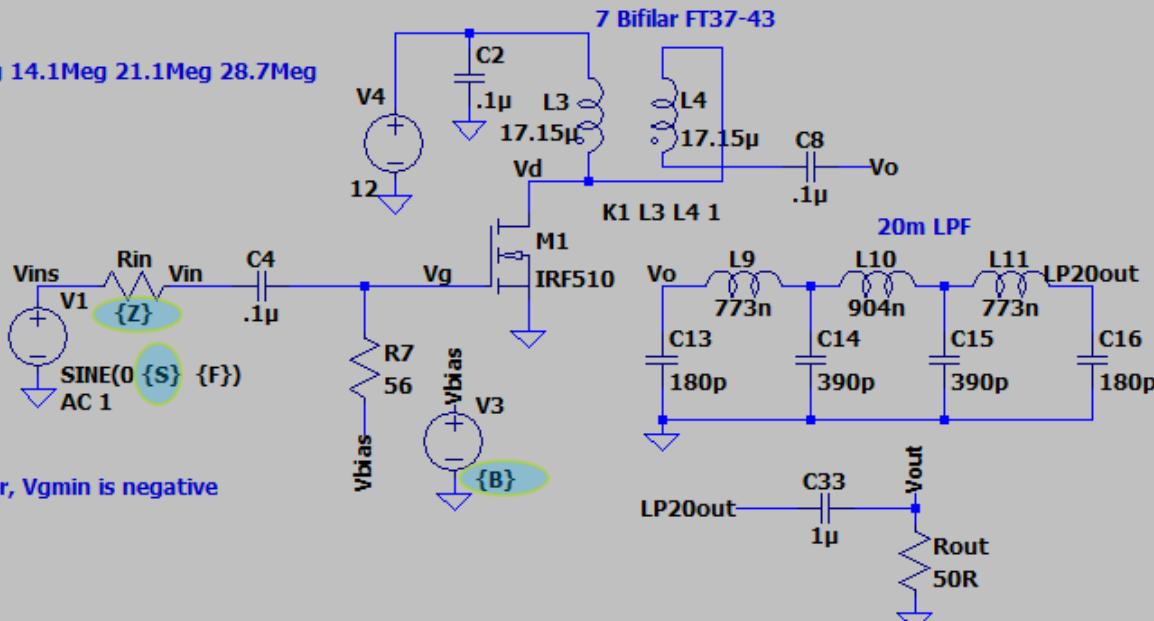
seems to be 4.15 bias and about 10 to 12V input. However, Vgmin is negative



```
.tran 0 20u 10u 100p
.options plotwintsize=0
.options numdgt = 8
.param Rja 62
.param Rcs 0.50
.param Rjc 3.5
.param Tj 150
.meas TRAN Vinr RMS V(Vin)
.meas TRAN Vinsr RMS V(Vins)
.meas TRAN Voutr RMS V(Vout)
.meas TRAN Vgr RMS V(Vg)
.meas TRAN Vgavg AVG V(Vg)
.meas TRAN Vgmax MAX V(Vg)
.meas TRAN Vgmin MIN V(Vg)
.meas TRAN Vbiasr RMS V(Vbias)
.meas TRAN Iinr RMS I(Rin)
.meas TRAN Idr RMS Id(m1)
.meas TRAN Pdis RMS (V(vd)*Id(m1) + V(vg)*Ig(m1))
.meas TRAN Pout RMS (V(Vout)*I(Rout))
.meas TRAN Pmar PARAM Pout-Pdis
.meas TRAN Zin PARAM Z*Vinr/(vinsr-Vinr)
.meas TRAN Temp PARAM Pdis*Rja
.meas TRAN Rheatshink PARAM ((Tj-25)/Pdis-Rcs-Rjc)
.meas TRAN Pin PARAM (Vinsr-Vinr)*Iinr
.meas TRAN Gp PARAM 10*log10(Pout/Pin)
.meas TRAN Gv PARAM 20*log10(Voutr/Vinr)

.four {F} 4 -1 V(vout)
.four {F} 4 -1 V(Vo)
.four {F} 4 -1 V(Vin)
```

# Harmonic Content Drives the Bus

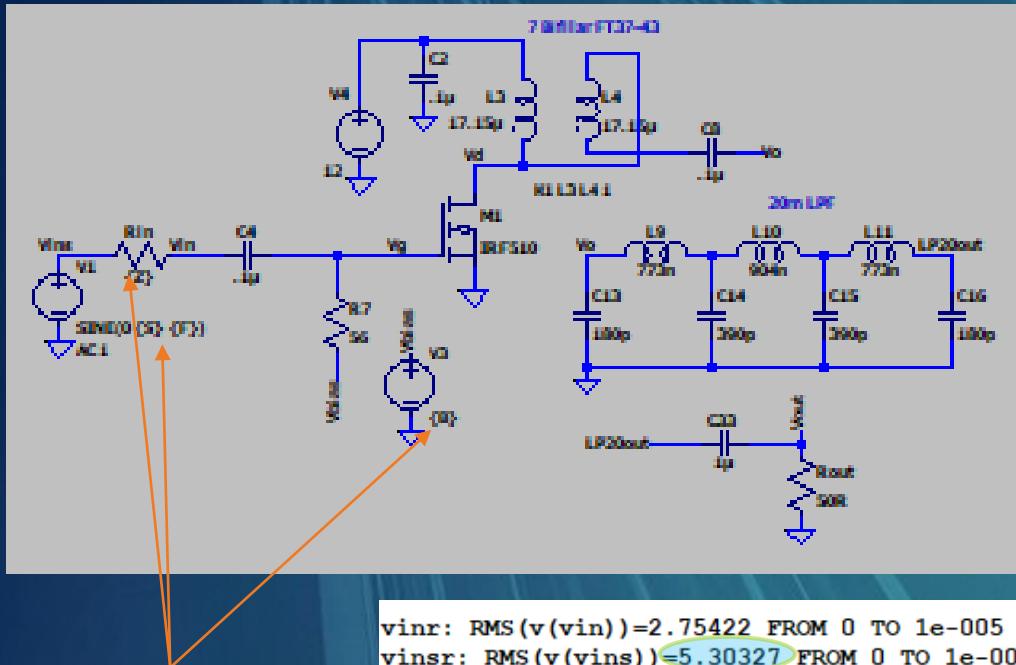

Adjust Mosfet bias  
and Input Drive for  
“optimum” results

Fourier components of V(vout)			
DC component: 0.605396			
Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.410e+07	2.830e+01	1.000e+00
2	2.820e+07	1.302e-02	4.599e-04
3	4.230e+07	3.903e-04	1.379e-05
4	5.640e+07	8.220e-04	2.904e-05

Total Harmonic Distortion: 0.046102% (2.194441%)

N-Period=all Fourier components of V(vo)			
DC component: 0.562705			
Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.410e+07	2.813e+01	1.000e+00
2	2.820e+07	3.257e+00	1.158e-01
3	4.230e+07	3.561e+00	1.266e-01
4	5.640e+07	4.828e-01	1.716e-02

Total Harmonic Distortion: 17.239882% (17.664440%)

Below 0.63% for IC & FCC

17% Seems to produce reasonable power

```

vinr: RMS(v(vin))=2.75422 FROM 0 TO 1e-005
vinsr: RMS(v(vins))=5.30327 FROM 0 TO 1e-005
voutr: RMS(v(vout))=20.026 FROM 0 TO 1e-005
vgr: RMS(v(vg))=4.96978 FROM 0 TO 1e-005
vgavg: AVG(v(vg))=4.1486 FROM 0 TO 1e-005
vgmax: MAX(v(vg))=7.99737 FROM 0 TO 1e-005
vgmin: MIN(v(vg))=-0.265911 FROM 0 TO 1e-005
vbiasr: RMS(v(vbias))=4.15 FROM 0 TO 1e-005
iinr: RMS(i(rin))=0.196356 FROM 0 TO 1e-005
idr: RMS(id(m1))=1.26583 FROM 0 TO 1e-005
pdis: RMS(v(vd)*id(m1) + v(vg)*ig(m1))=5.83671 FROM 0 TO 1e-005
pout: RMS(v(vout)*i(rout))=9.83714 FROM 0 TO 1e-005
pmar: pout-pdis=4.00043
zin: z*vindr/(vinsr-vinr)=18.3683
temp: pdis*rja=361.876
rheatsink: ((tj-25)/pdis-rcs-rjc)=17.4162
pin: (vinsr-vinr)*iinr=0.500521
gp: 10*log10(pout/pin)=12.9345
gv: 20*log10(voutr/vinr)=17.2319

```

“Linear-ish. However, dipping below Vgs will produce nasties  
This may be ok for CW but may not be good for Phone

More power dissipated in Load than Mosfet  
Assume this is good

Gain of about 17 dB (based on voltage gain)

# Rinse and Repeat for each Mosfet

```
.step param F list 1.5Meg 3.7Meg 5.37Meg 7.1Meg 10.1Meg 14.1Meg 21.1Meg 28.7Meg
.param S 3
.param B 4.375
.step param B 4.3 4.6 0.05
.param F 14.1Meg
.param S 6
.param Z 53
.step param S 4 10 1
.param F 14.1Meg
.param B=4.375
.param Z 53
;step param B 4.3 4.4 0.025
;step param B 4.5 4.75 0.05
.param B 4.6
.param F 14.1Meg
.param S 0
.param Z 53
.param B 4.375
.param F 14.1Meg
.param S 0
.param Z 178
```

Direct Newton iteration for .op point succeeded.

N-Period=all  
Fourier components of V(vout)  
DC component: 0.0248644


Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.410e+07	2.388e+01	1.000e+00
2	2.820e+07	1.112e-02	4.656e-04
3	4.230e+07	5.771e-04	2.417e-05
4	5.640e+07	4.009e-05	1.679e-06

Total Harmonic Distortion: 0.046621% (0.106267%)

N-Period=all  
Fourier components of V(vo)  
DC component: 0.0224581

Harmonic Number	Frequency [Hz]	Fourier Component	Normalized Component
1	1.410e+07	2.373e+01	1.000e+00
2	2.820e+07	3.163e+00	1.333e-01
3	4.230e+07	2.601e+00	1.096e-01
4	5.640e+07	8.732e-01	3.679e-02

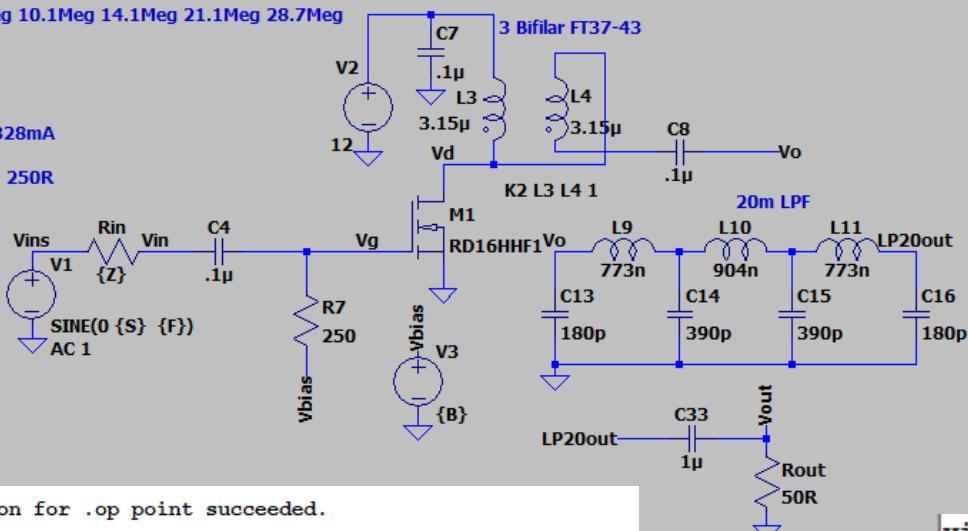Total Harmonic Distortion: 17.643436% (17.727908%)



```
.tran 0 20u 10u 100p
.options plotwintsize=0
.options numdgts = 8
.param Rja 62
.param Rcs 0.50
.param Rjc 2.2
.param Tj 150

.meas TRAN Vinr RMS V(Vin)
.meas TRAN Vinsr RMS V(Vins)
.meas TRAN Voutr RMS V(Vout)
.meas TRAN Vgr RMS V(Vg)
.meas TRAN Vgavg AVG V(Vg)
.meas TRAN Vgmax MAXV(Vg)
.meas TRAN Vgmin MIN V(Vg)
.meas TRAN Vbiasr RMS V(Vbias)
.meas TRAN Innr RMS I(Rin)
.meas TRAN Idr RMS Id(m1)
.meas TRAN Pdis RMS (V(vd)*Id(m1) + V(vg)*Ig(m1))
.meas TRAN Pout RMS (V(Vout)*I(Rout))
.meas TRAN Pmar PARAM Pout-Pdis
.meas TRAN Zin PARAM Z*Vinr/(vinsr-Vinr)
.meas TRAN Temp PARAM Pdis*Rja
.meas TRAN Rheatshink PARAM ((Tj-25)/Pdis-Rcs-Rjc)
.meas TRAN Pin PARAM (Vinsr-Vinr)*Innr

vinr: RMS(v(vin))=1.76134 FROM 0 TO 1e-005
vinsr: RMS(v(vins))=3.533551 FROM 0 TO 1e-005
voutr: RMS(v(vout))=16.8829 FROM 0 TO 1e-005
vgr: RMS(v(vg))=4.71529 FROM 0 TO 1e-005
vgavg: AVG(v(vg))=4.37442 FROM 0 TO 1e-005
vgmax=1e-005 FROM 0 TO 1e-005
vgmin: MIN(v(vg))=1.76624 FROM 0 TO 1e-005
vbiasr: RMS(v(vbias))=4.375 FROM 0 TO 1e-005
iinr: RMS(i(rin))=0.0124584 FROM 0 TO 1e-005
idr: RMS(id(m1))=1.00682 FROM 0 TO 1e-005
pdis: RMS(v(vd)*id(m1) + v(vg)*ig(m1))=4.10395 FROM 0 TO 1e-005
pout: RMS(v(vout)*i(rout))=6.98176 FROM 0 TO 1e-005
pmar: pout-pdis=2.87782
zin: z*vinr/(vinsr-vinr)=176.713
temp: pdis*rja=254.445
rheatshink: ((tj-25)/pdis-rcs-rjc)=27.7585
pin: (vinsr-vinr)*iinr=0.0221033
gp: 10*log10(pout/pin)=24.9951
gv: 20*log10(voutr/vinr)=19.6321
```

# Rinse and Repeat for Power Amp



# MOSFET Results

This is from a “Theoretical” simulation. The MOSFT model could not be accurate.

Mosfet	Parameters				Basic Amp @ 14.1 MHz						
	Power	Cioss	Rin		Input	Bias	Zin	Pout	Pmar	Har Dist	Idle mA
FQPF20N06	30	590p	10		3.0	3.7	7.0	10.8	5.8	17%	0.83uA
IRF510	43	180p	25		7.5	4.2	18.0	9.6	4.2	17%	88
IRFZ24N	45	370p	10		5.0	3.1	10.0	9.6	3.6	17%	5.4uA
RD16HHF1	57	50p	320		5.0	4.4	168.0	7.0	2.9	17%	328
stp16nf06	40	315p	12		3.2	4.0	10.0	8.8	3.9	16%	135
IRF530	88	670p	5		6.0	4.2	5.0	10.6	1.5	17%	125
SH8K25	3	100p	54		2.5	2.3		5.9	1.7	18%	4.7
5010LLC	520	4360p	4		3.8	4.1		3.3	-6.1	17%	113

Based on input impedance only,  
the RD16HHF1 appears to be a  
better choice than IRF510

RD16HHF1 appears to have a  
“reasonable” power output

FIN



Stay Safe