

SOAREX GROUP

Miller Effect (MOSFETS)

Dave VE3OOI

August 2023

Another riveting VE3OOI presentation....



AGENDA

1. Fundamentals:

- ✓ MOSFET Construction
- ✓ Observations

2. Miller Effect, Capacitance and Theorem.

3. Addressing Miller Effect

- ✓ CASCODE/HYCAS
- ✓ “Scotty” Approach

4. BONUS: Feedback Amplifiers

- ✓ What's not explained in EMRFD et. al.



Captain, we need to kick
Miller in the bag pipes

Danger Will Robinson...




Quote Charlie Morris, ZL2CTM:

This NOT a tutorial.

It's a log of my journey. Right or wrong.

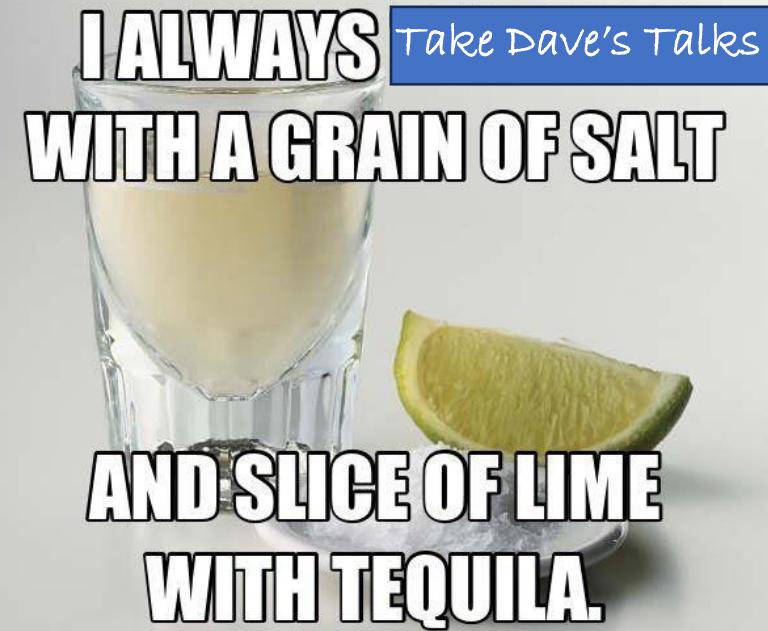I ALWAYS Take Dave's Talks
WITH A GRAIN OF SALT



**AND SLICE OF LIME
WITH TEQUILA.**



REFERENCES

#207: Basics of a Cascode Amplifier and the Miller Effect

https://youtu.be/Op_I3Ke7px0

The thumbnail shows a hand holding a blue pen over a handwritten note on lined paper. The note is titled 'BASICS OF THE CASCODE AMPLIFIER & THE MILLER EFFECT'. It includes a list of points and a schematic diagram of a cascode amplifier circuit.

- COMBINATION OF CE AMPLIFIER AND CB AMPLIFIER
- GAIN \approx CE AMPLIFIER
- USED MAINLY TO REDUCE THE MILLER EFFECT

Schematic Diagram:

```
graph LR; Input((INPUT)) --> Vbe((Vbe)); Vbe --> Q1((Q1)); Q1 --> Vce((Vcc)); Vce --> Rc((Rc)); Rc --> Output((OUTPUT));
```

w2aew 193K subscribers

Power Electronics with Dr. K 8.37K subscribers

EE-444/544 Power Electronics

Week 3-2

MOSFET Gate Charge and Turn-On Characteristics

Week 3-2 EE444/544 – Power Electronics

Power Electronics WK3_2 MOSFET Turn On Characteristics

<https://youtu.be/f1yt0s3gpcE>

Semiconductor Devices: Miller's Theorem

<https://youtu.be/yM9xlbAf43Q>

The thumbnail shows a screenshot of a simulation software interface. It displays a circuit diagram of a voltage-controlled voltage source (operating point analysis) and its corresponding Miller equivalent circuit. The circuit consists of a dependent voltage source $-A_v$ in series with a load Z , followed by a Miller feedback network with input impedance $Z_{in-Miller} = Z/A+1$ and output impedance $Z_{out-Miller} = Z A/(A+1)$.

Electronics with Professor Fiore 7.24K subscribers

Mateo Aboy 14.2K subscribers

MOSFET Amplifiers

MOSFET High Frequency Model

MOSFET High Frequency Model

<https://youtu.be/19kXfUPdF9I>

Dr. Cristina Crespo


High Frequency Model of MOSFET

<https://youtu.be/19kXfUPdF9I>

The thumbnail shows a screenshot of a presentation slide. It features a high-frequency model of a MOSFET circuit with nodes labeled C_{gs} , C_{gd} , C_{ds} , V_{gs} , V_{ds} , and V_{sd} . Below the diagram, there is a video frame showing a woman speaking.




This won't hurt at all...

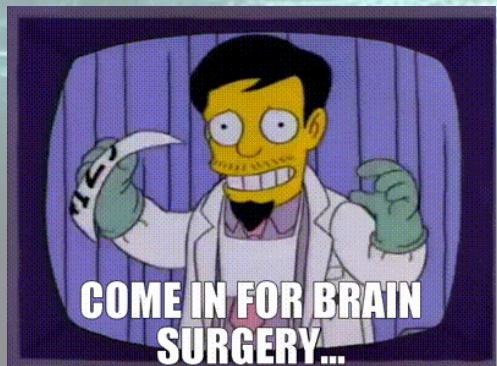


MOSFET CONSTRUCTION

N Channel
Enhancement Mode


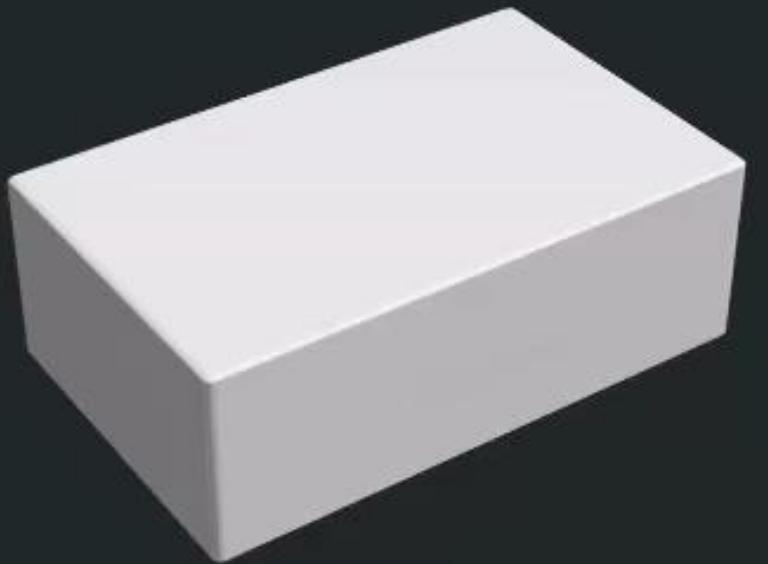


1. Created by applying two “N” doped semiconductors to a based on “P” doped semiconductor
2. N-Doped has impurity added with excess electrons and P-Doped has impurity added with more holes (missing electrons)
3. The N doped semiconductors are source and drain (Collector/Emitter)
4. A metal plate with an insulator is added to the P-doped base to create a capacitor.
5. When a voltage is applied to the gate with **respect to the source**, electrons are attracted to the gate, and a channel is formed.
6. Once a threshold gate voltage is applied, current flows between drain and source

Capacitors


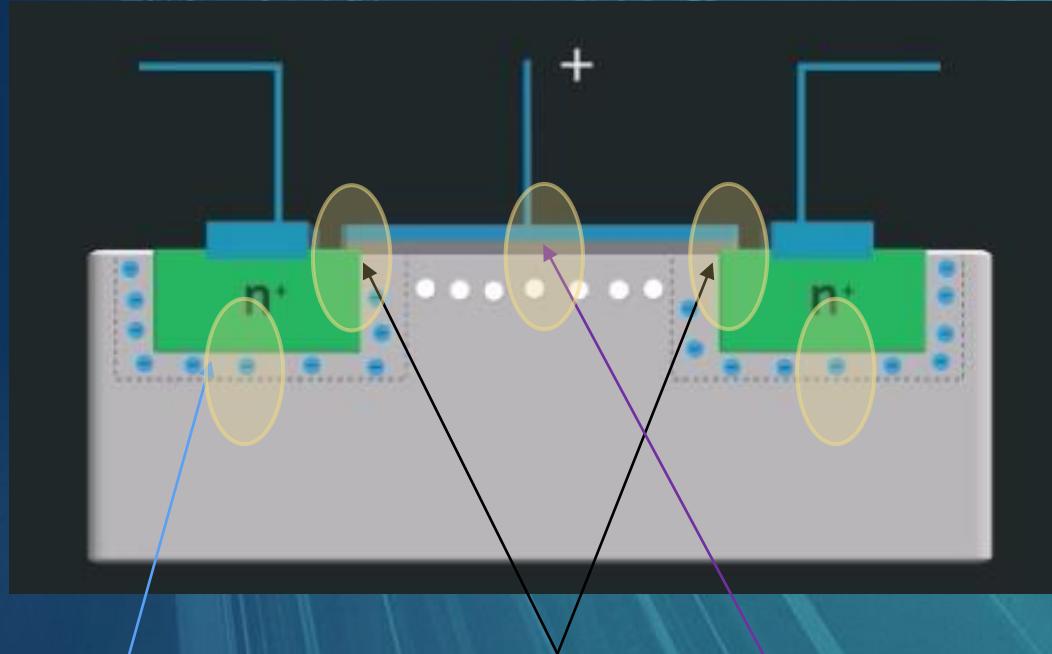


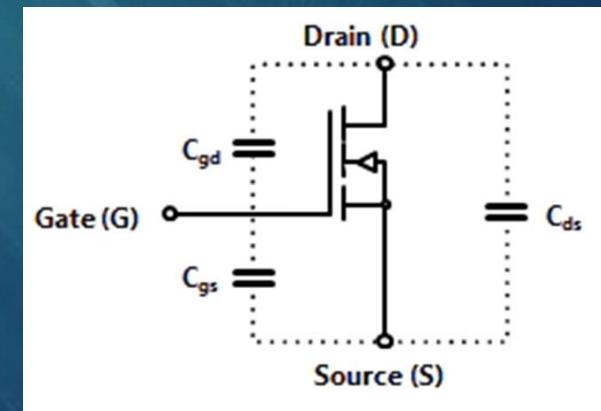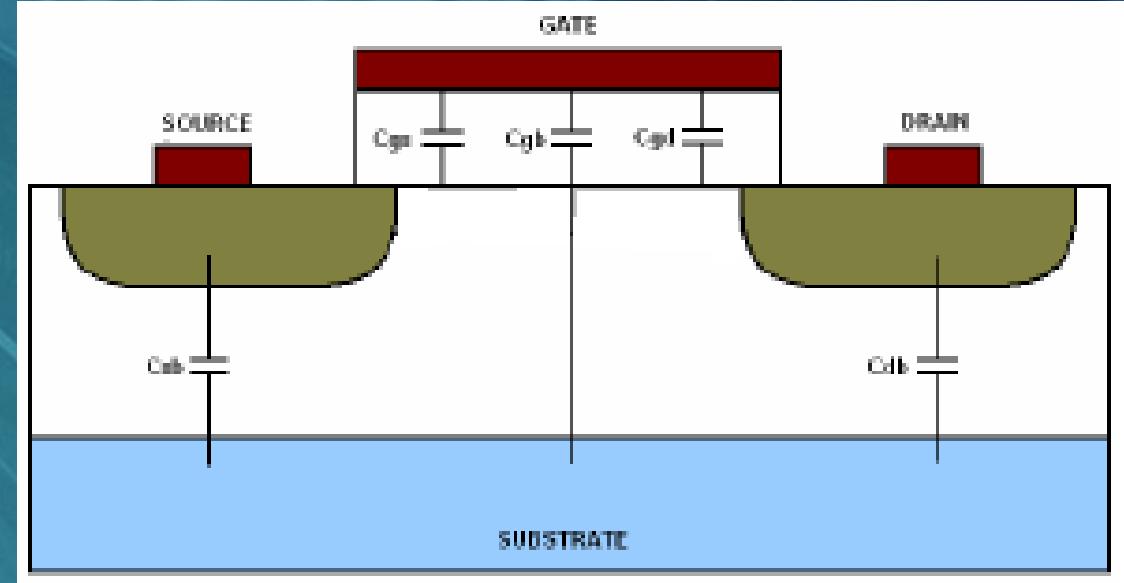Depletion region Overlap Oxide/dielectric





MOSFET CAPACITANCE DEFINED

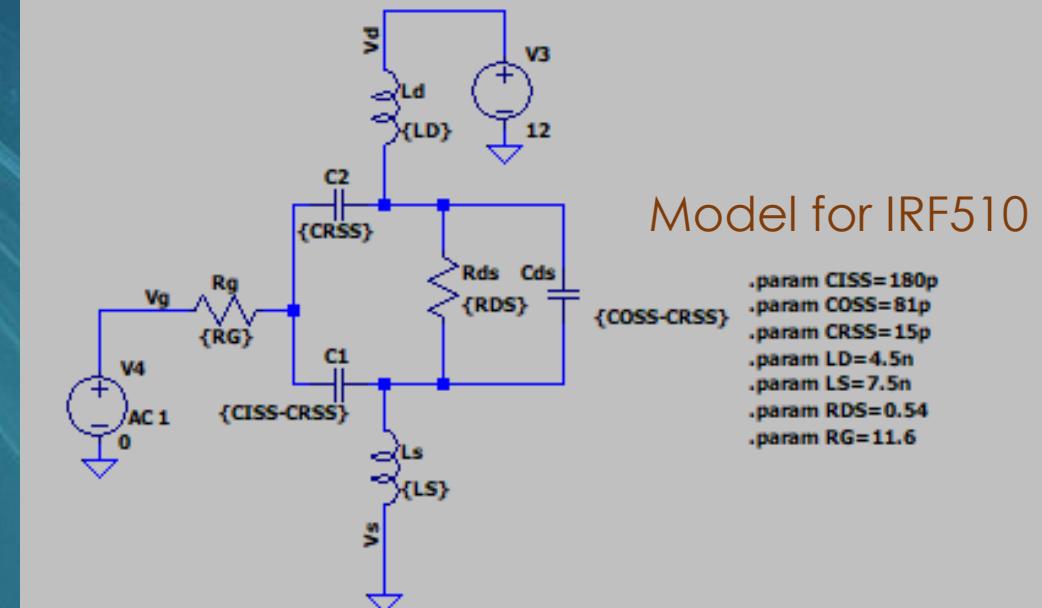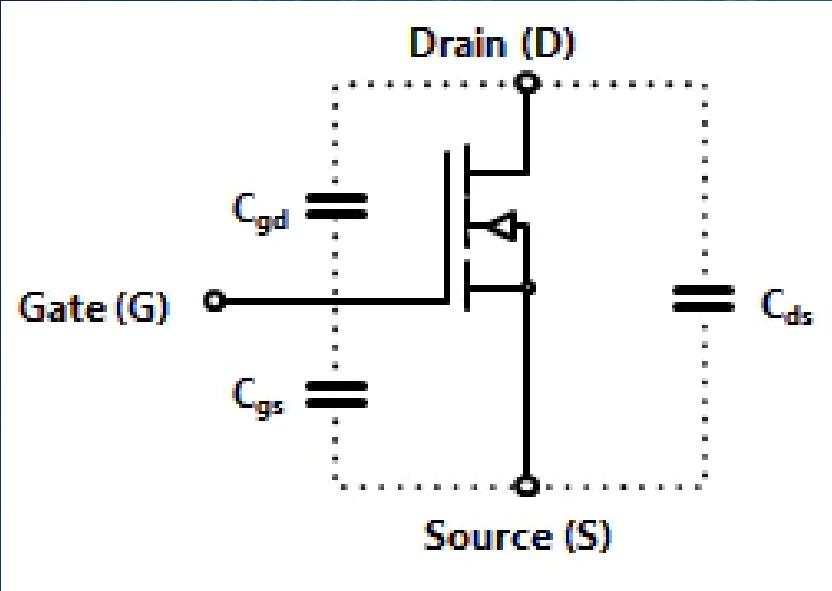

Dynamic							
Input capacitance	C_{iss}	$V_{GS} = 0 \text{ V},$ $V_{DS} = 25 \text{ V},$ $f = 1.0 \text{ MHz, see fig. 5}$	-	180	-	pF	
Output capacitance	C_{oss}		-	81	-		
Reverse transfer capacitance	C_{rss}		-	15	-		
Gate input resistance	R_g		$f = 1 \text{ MHz, open drain}$	2.5	-	11.6	Ω
Internal drain inductance	L_d	Between lead, 6 mm (0.25") from package and center of die contact		-	4.5	-	nH
Internal source inductance	L_s			-	7.5	-	

IRF510



Dr. Cristina Crespo
<https://youtu.be/19kXfUPdF9I>

Typical datasheet values:

Equivalent input capacitance: C_{iss}


Forward / Reverse Transfer Capacitance: C_{rss}

Equivalent output capacitance: C_{oss}


$$C_{iss} = C_{gs} + C_{gd}$$

$$C_{rss} = C_{gd}$$


$$C_{oss} = C_{gd} + C_{ds}$$

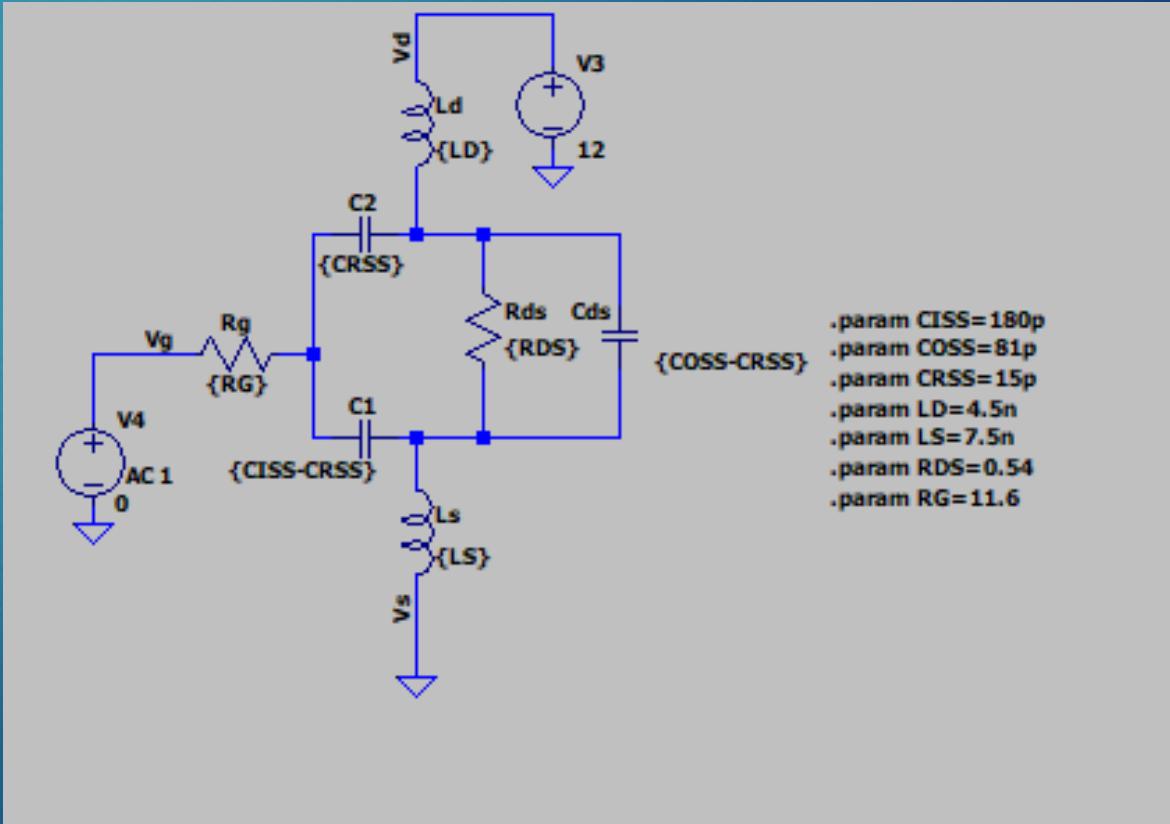

Model Comparison

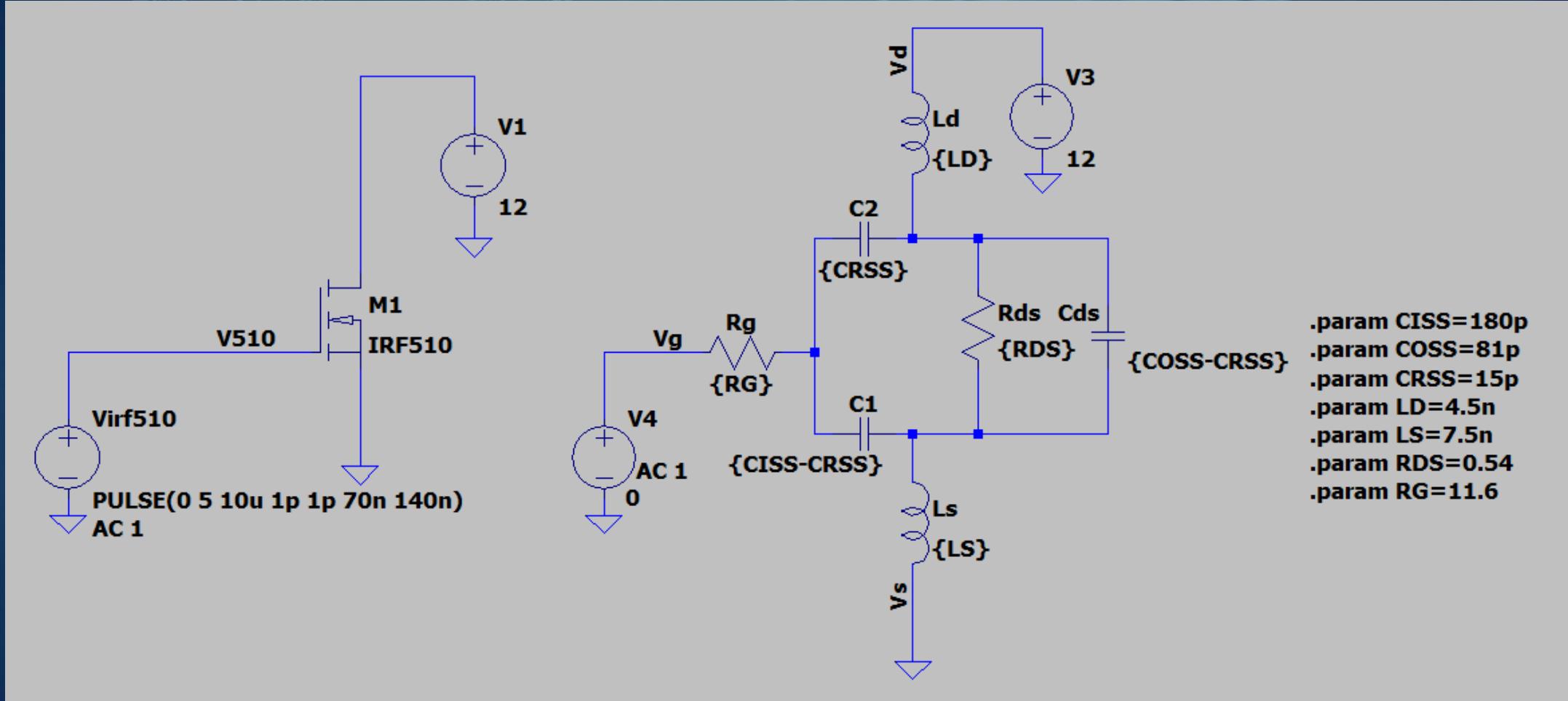


Winner... Winner...

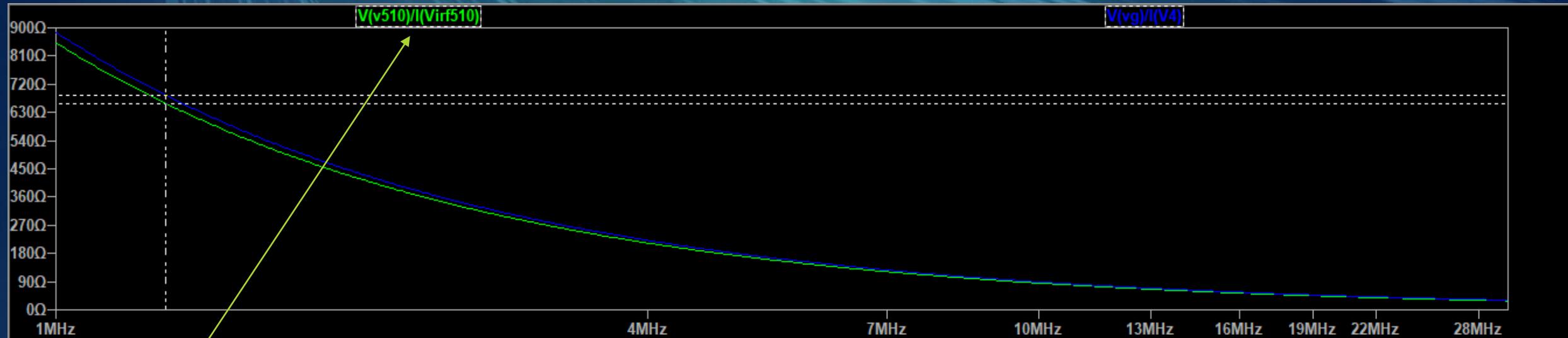

LTSpice Trick:

- ✓ right clk Select "Add Plot"
- ✓ select what you want to plot
- ✓ Can use * / + - fun()

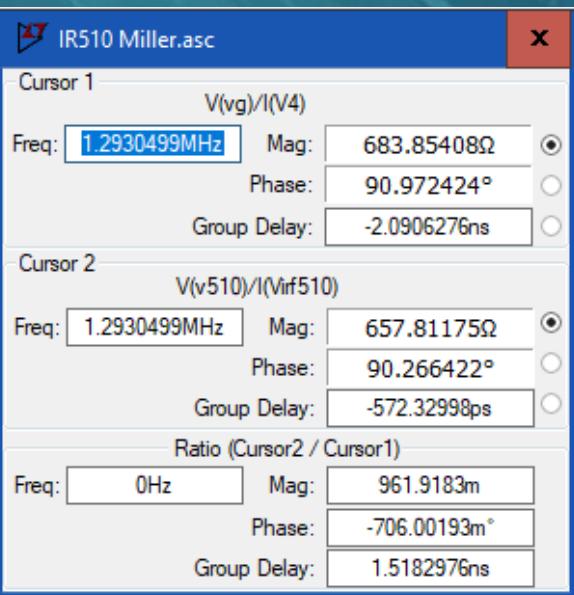http://ltwiki.org/index.php?title=Waveform_Arithmetic




SUMMARY: THE ISSUE

Due to the internal capacitors, the MOSFET is frequency dependant




- The MOSFET internal capacitors acts as a short circuit from gate to source
- Input impedance is very small

...but it gets worst!

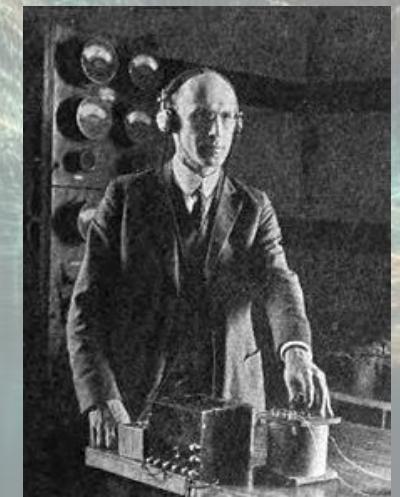


John Milton Miller



TRANSISTOR MODELS

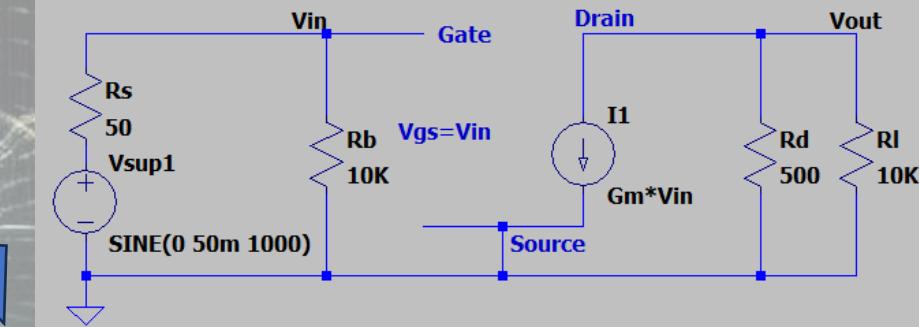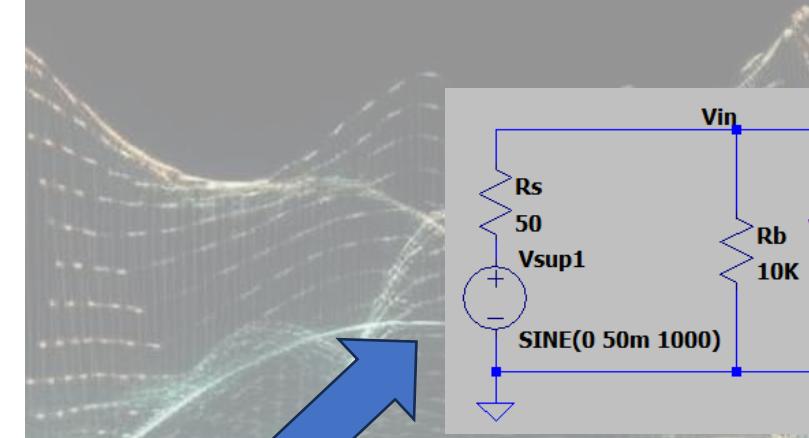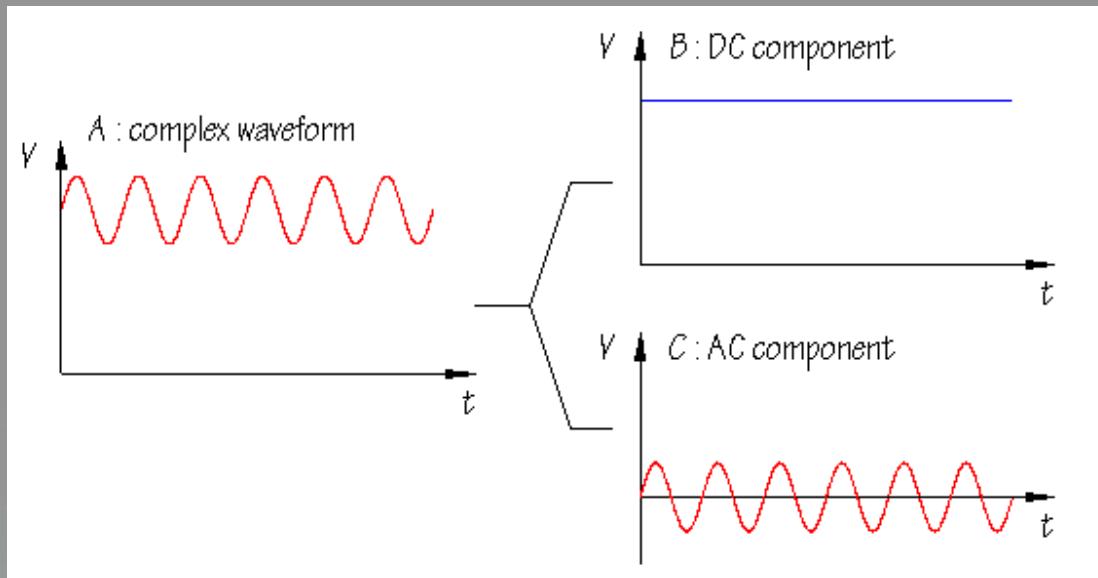

AC (Small Signal) Model

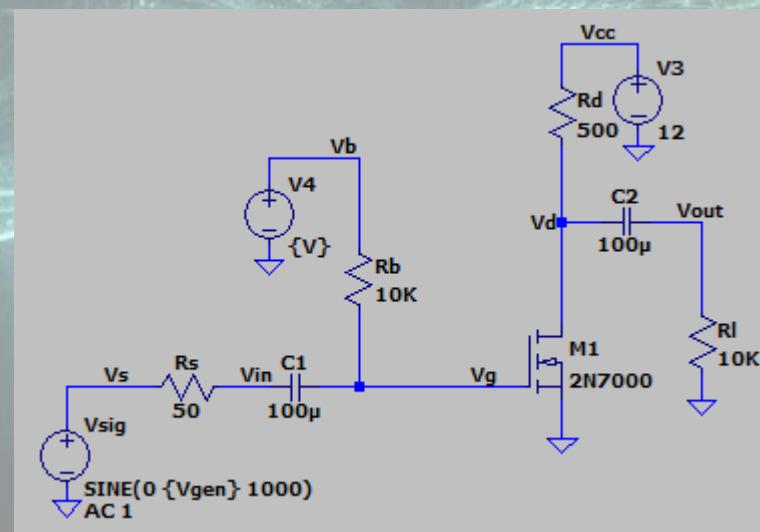



Common Source Amplifier

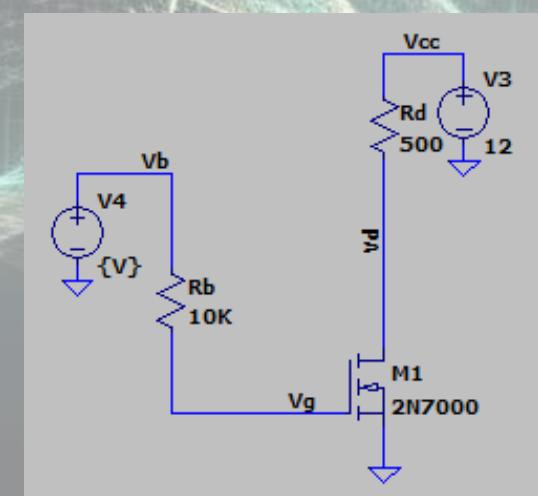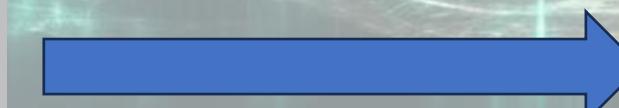

DC Model


FUNDAMENTALS

MOSFET Model

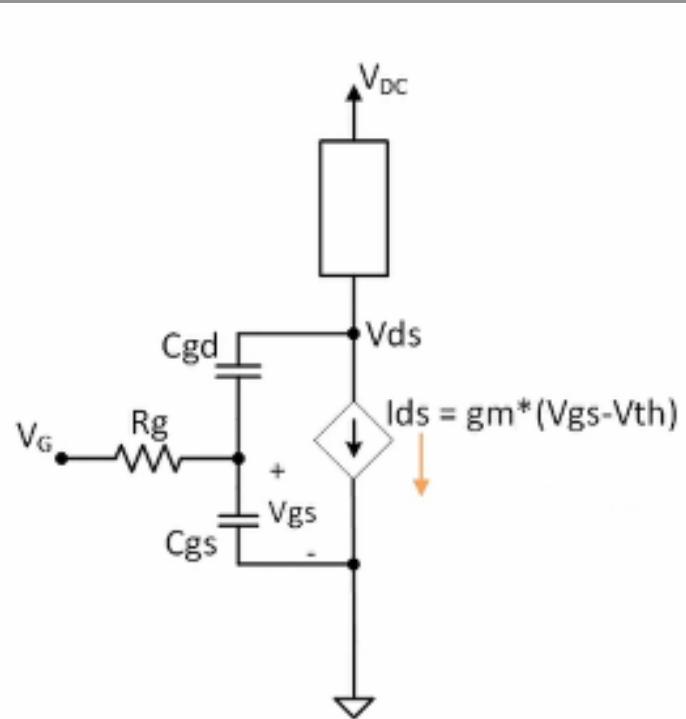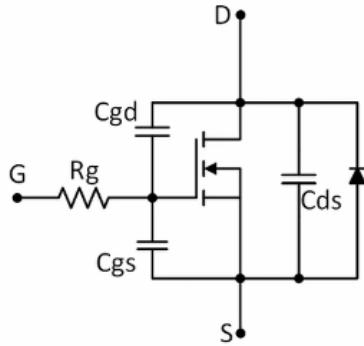

MOSFETs

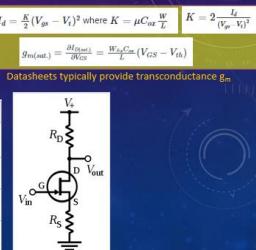- Similar Input and Output charts to BJT:
 - However, the input curve will show saturation if V_{gs} is high enough
- No concept of Beta (current amplification). MOSFET is a voltage device. Voltage controls current.
- The gain depends on g_m (transconductance) and K
- K is based on channel parameters inside MOSFET



- The model of a MOSFET is basically an ideal current source that is driven by the gate to source voltage**
- When gate voltage is zero, MOSFET is off and C_{gd} is charged with respect to V_{dc} .**
- When gate voltage starts to rise (small voltage), all current flows to C_{gs} and that starts to charge.**
- Once V_{gs} threshold reached, I_{ds} begins to increase and V_{ds} starts to drop. C_{gd} starts to discharge.**
- Once I_{ds} reaches maximum, then V_{ds} is close to zero and C_{gd} is discharged. As V_{gs} increases, C_{gd} now charges with opposite polarity. Once C_{gd} is fully charged, the MOSFET is on.**
- The time for the MOSFET to turn on is from charge time of BOTH C_{gs} and C_{gd} . This is critical for MOSFET as a switch (e.g. buck converter)**

IRF510

DATASHEET

One ampere is equal to 1 coulomb moving past a point in 1 second, or $6.241509074 \times 10^{18}$ electrons' worth of charge moving past a point in 1 second.

PARAMETER	SYMBOL	TEST CONDITIONS	MIN.	TYP.	MAX.	UNIT	
Static							
Drain-source breakdown voltage	V_{DS}	$V_{GS} = 0 \text{ V}, I_D = 250 \mu\text{A}$	100	-	-	V	
V_{OS} temperature coefficient	$\Delta V_{DS}/T_J$	Reference to 25 °C, $I_D = 1 \text{ mA}$	-	0.12	-	V/°C	
Gate-source threshold voltage	$V_{GS(\text{th})}$	$V_{DS} = V_{GS}, I_D = 250 \mu\text{A}$	2.0	-	4.0	V	
Gate-source leakage	I_{GSS}	$V_{GS} = \pm 20 \text{ V}$	-	-	± 100	nA	
Zero gate voltage drain current	I_{GSS}	$V_{DS} = 100 \text{ V}, V_{GS} = 0 \text{ V}$	-	-	25	μA	
		$V_{DS} = 80 \text{ V}, V_{GS} = 0 \text{ V}, T_J = 150 \text{ °C}$	-	-	250		
Drain-source on-state resistance	$R_{DS(on)}$	$V_{GS} = 10 \text{ V}$	$I_D = 3.4 \text{ A}^b$	-	-	0.54	Ω
Forward transconductance	g_{fs}	$V_{DS} = 50 \text{ V}, I_D = 3.4 \text{ A}^b$	1.3	-	-	S	
Dynamic							
Input capacitance	C_{iss}	$V_{GS} = 0 \text{ V},$ $V_{DS} = 25 \text{ V},$ $f = 1.0 \text{ MHz, see fig. 5}$	-	180	-	pF	
Output capacitance	C_{oss}		-	81	-		
Reverse transfer capacitance	C_{rss}		-	15	-		
Total gate charge	Q_g	$V_{GS} = 10 \text{ V}$	$I_D = 5.6 \text{ A}, V_{DS} = 80 \text{ V}$ $V_{DS} = 10 \text{ V},$ see fig. 6 and fig. 13 ^b	-	-	nC	
Gate-source charge	Q_{gs}			-	-		
Gate-drain charge	Q_{gd}			-	-		
Turn-on delay time	$t_{d(on)}$	$V_{DD} = 50 \text{ V}, I_D = 5.6 \text{ A}$ $R_g = 24 \Omega, R_D = 8.4 \Omega, \text{ see fig. 10}^b$	-	6.9	-	ns	
Rise time	t_r		-	16	-		
Turn-off delay time	$t_{d(off)}$		-	15	-		
Fall time	t_f		-	9.4	-		
Gate input resistance	R_g	$f = 1 \text{ MHz, open drain}$		2.5	-	11.6	Ω
Internal drain inductance	L_D	Between lead, 6 mm (0.25") from package and center of die contact	-	4.5	-	nH	
Internal source inductance	L_S		-	7.5	-		



SCOPING A MOSFET



Input capacitance	C_{iss}	$V_{GS} = 0 \text{ V},$ $V_{DS} = 25 \text{ V},$ $f = 1.0 \text{ MHz, see fig. 5}$	-	180	-	pF
Output capacitance	C_{oss}		-	81	-	
Reverse transfer capacitance	C_{rss}		-	15	-	

MILLER CAPACITANCE: THEORY

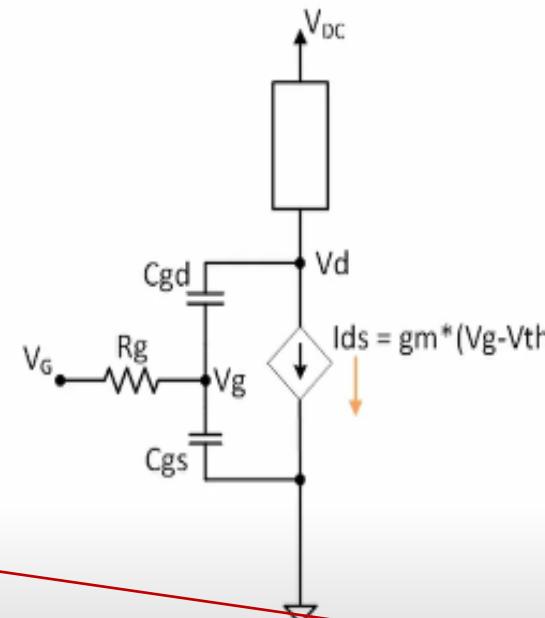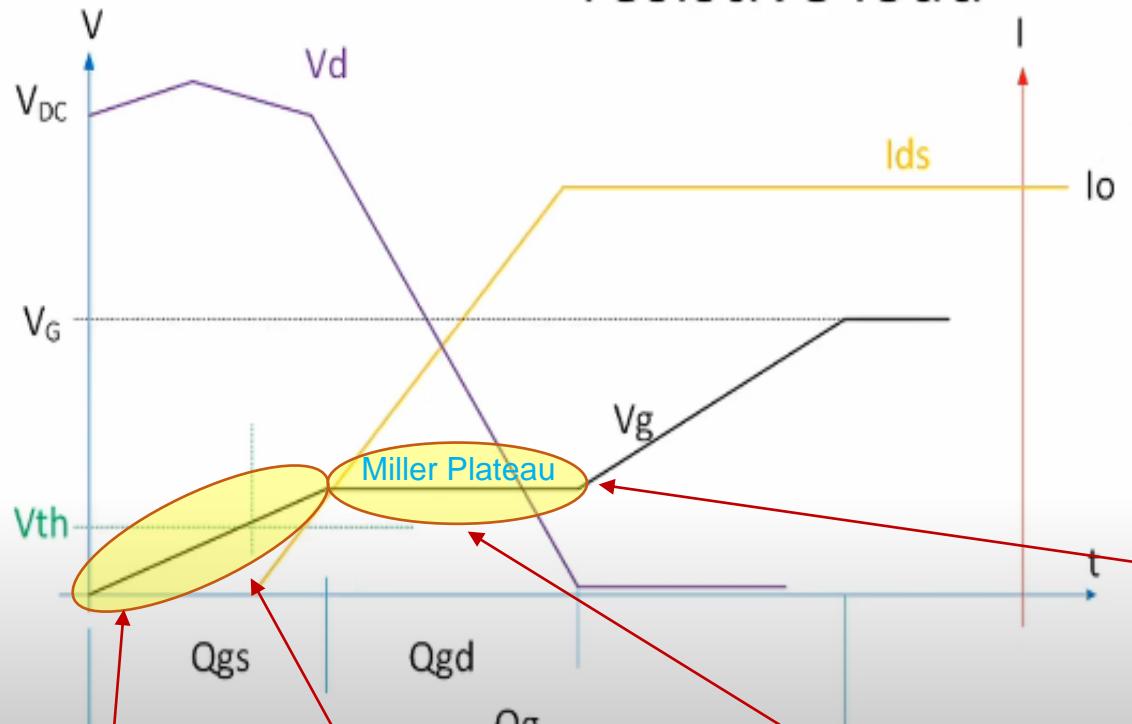MOSFET turn-on characteristics
resistive load



$C_{gd} \& C_{gs}$ Almost Fully Charged



Max Current and Zero Voltage drop

C_{gs} Charging

MOSFET Threshold Voltage

C_{gd} Discharging (After V_d Drops)

MILLER CAPACITANCE: 2N7000

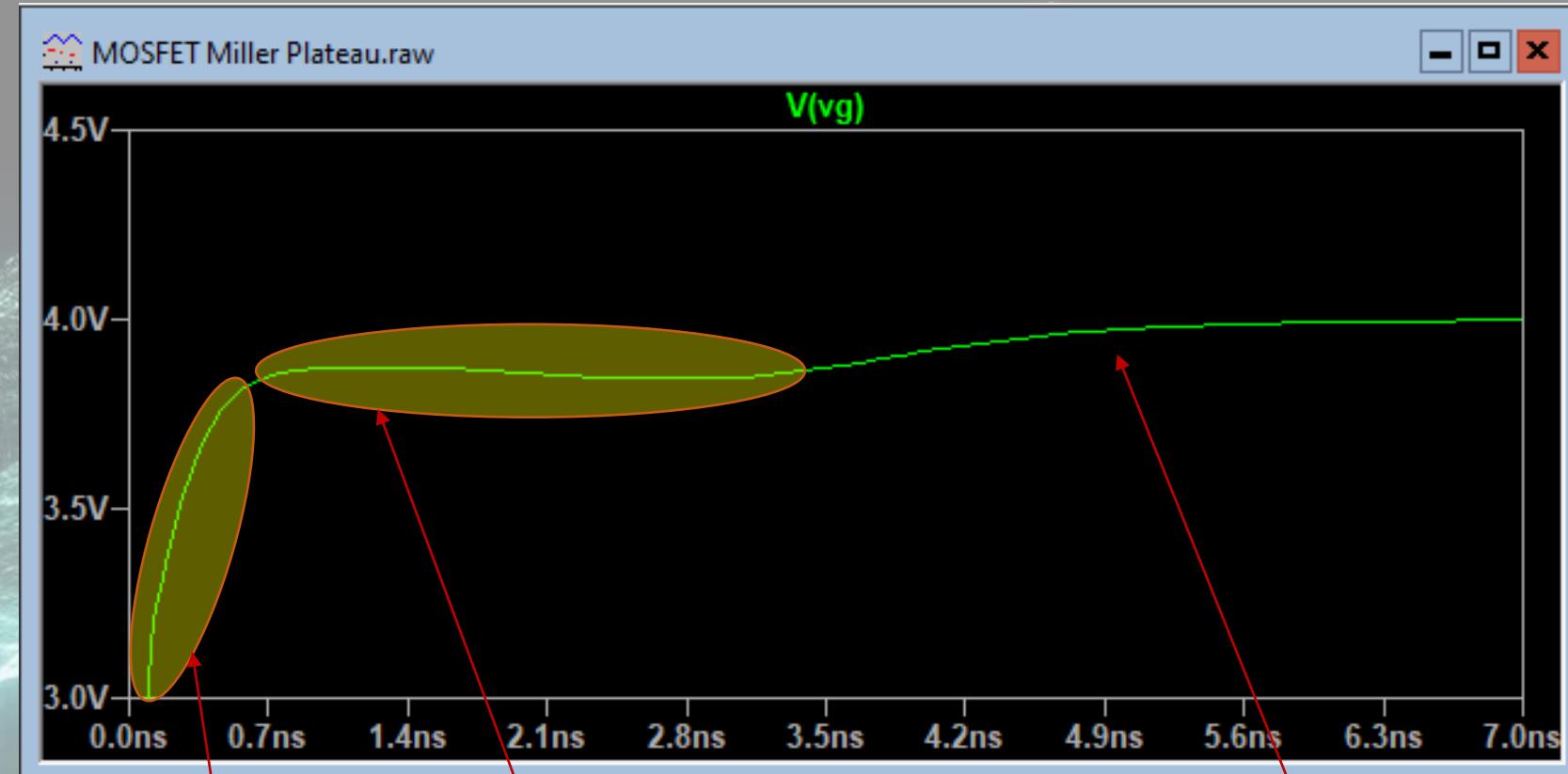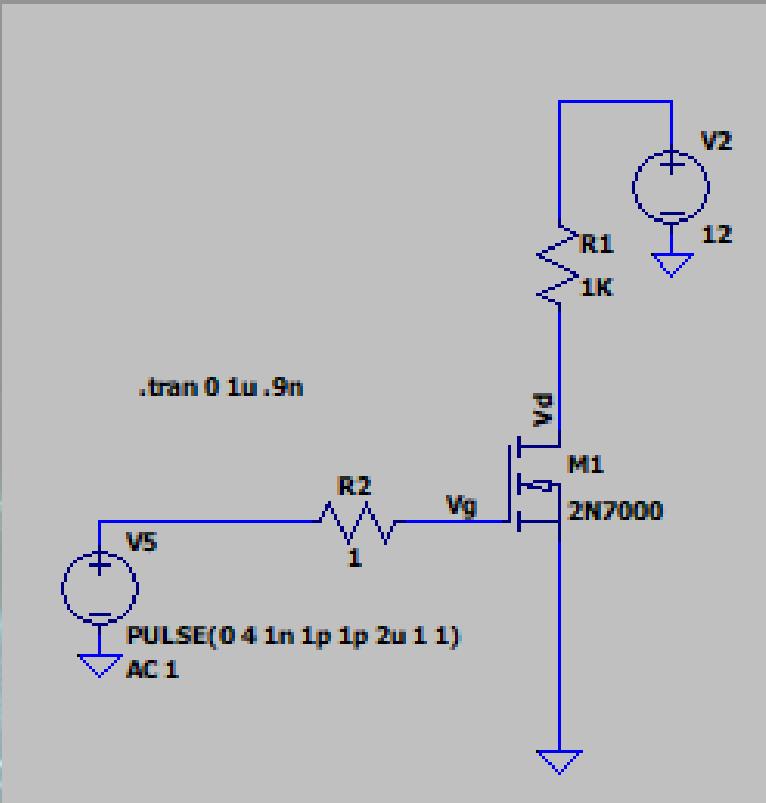

Cgs Charging

**Cgd Discharging
(After V_d drops)**


**All Capacitors
Fully Charged**

The plot thickens....

- 1. Due to the internal capacitors, the MOSFET is frequency dependant. At high frequencies, the input impedance is reduced (almost short circuit)**
- 2. The time for the MOSFET to turn on completely is dependent on the C_{gs} and C_{gd} capacitors charging**

Total gate charge	Q_g	V _{GS} = 10 V	I _D = 5.6 A, V _{DS} = 80 V V _{DS} = 10 V, see fig. 6 and fig. 13 ^b	-	-	8.3	nC
Gate-source charge	Q_{gs}			-	-	2.3	
Gate-drain charge	Q_{gd}			-	-	3.8	

MILLER EFFECT, CAPACITANCE & THEOREM

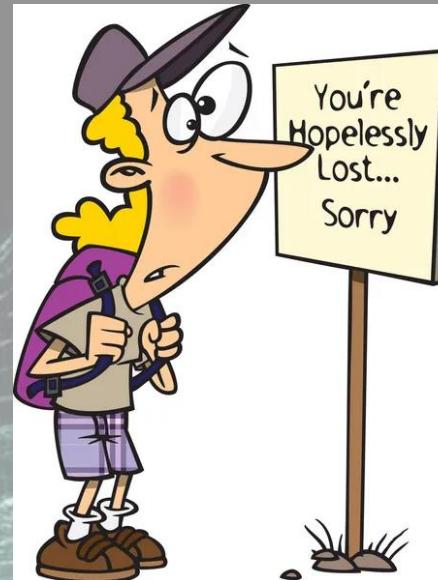

This is a cycle of resistance and capacitance occurring between the input and output of an amplifier circuit, which can create a primitive low-pass filter that is signal dependant. The effective input impedance of an amplifier depends on the impedance connected from input to output of the amplifier. The apparent scaling of this impedance often dominates the input impedance and frequency response of the amplifier. This effect was first reported by John Miller in 1919 and is now commonly known as the Miller Effect or Miller Capacitance.

Although the term *Miller effect* normally refers to capacitance, any impedance connected between the input and another node exhibiting gain can modify the amplifier input impedance via this effect. These properties of the Miller effect are generalized in the Miller theorem. The Miller capacitance due to parasitic capacitance between the output and input of active devices like transistors and vacuum tubes is a major factor limiting their gain at high frequencies. Miller capacitance was identified in 1920 in triode vacuum tubes by John Milton Miller.

MILLER EFFECT/THEOREM




In electronics, the **Miller effect** accounts for the increase in the equivalent input capacitance of an inverting voltage amplifier due to amplification of the effect of capacitance between the input and output terminals. The virtually increased input capacitance due to the Miller effect is given by

$$C_M = C(1 + A_v)$$



where $-A_v$ is the voltage gain of the inverting amplifier (A_v positive) and C is the feedback capacitance.

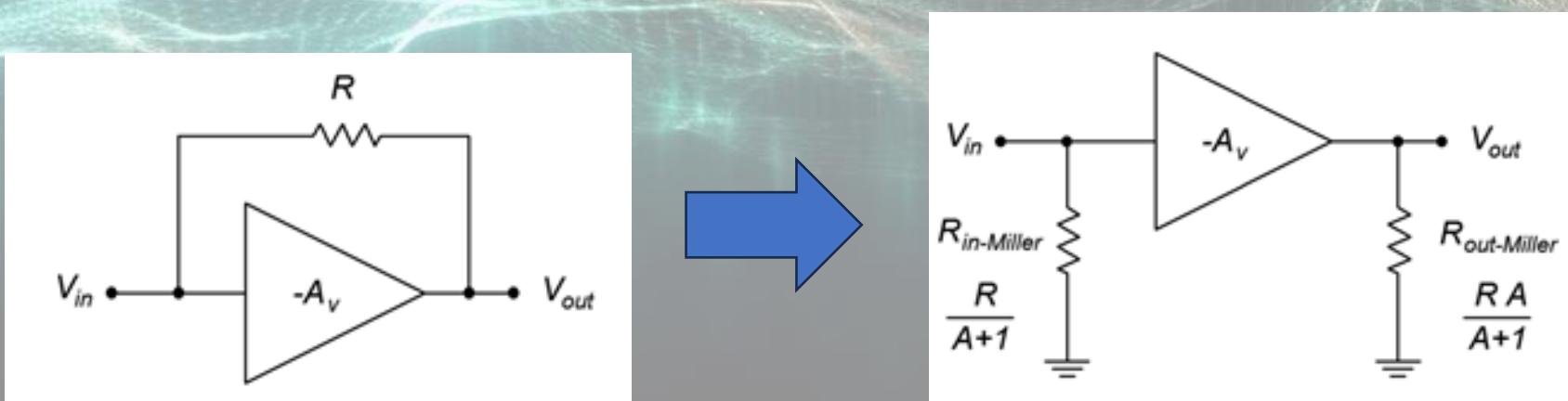Although the term *Miller effect* normally refers to capacitance, any impedance connected between the input and another node exhibiting gain can modify the amplifier input impedance via this effect. These properties of the Miller effect are generalized in the *Miller theorem*.




MILLER CAPACITANCE

MOSFET Model


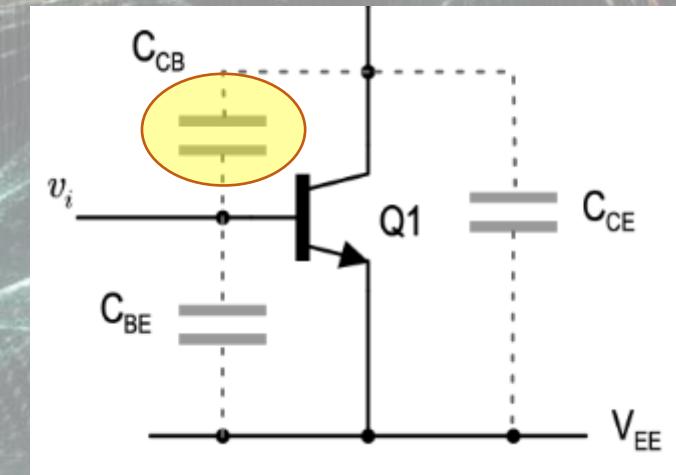
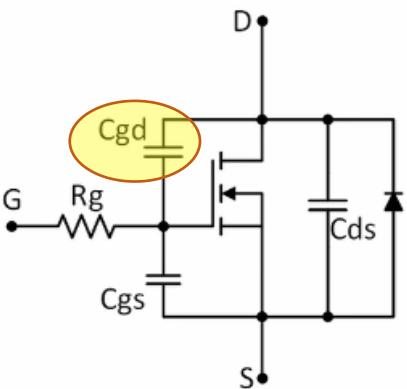


Miller Impedance Calculations

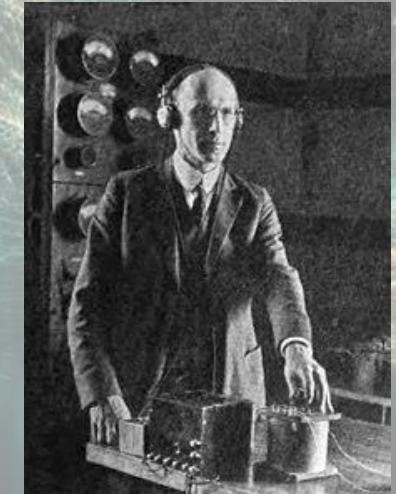

John Milton Miller


NO MILLER EFFECT: 2N3904

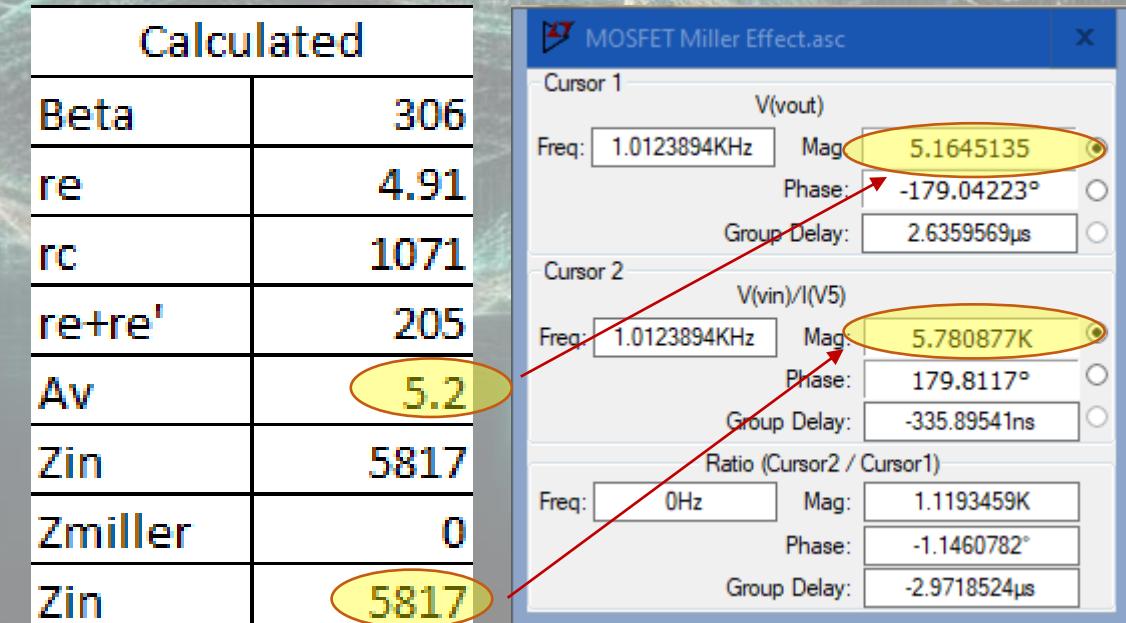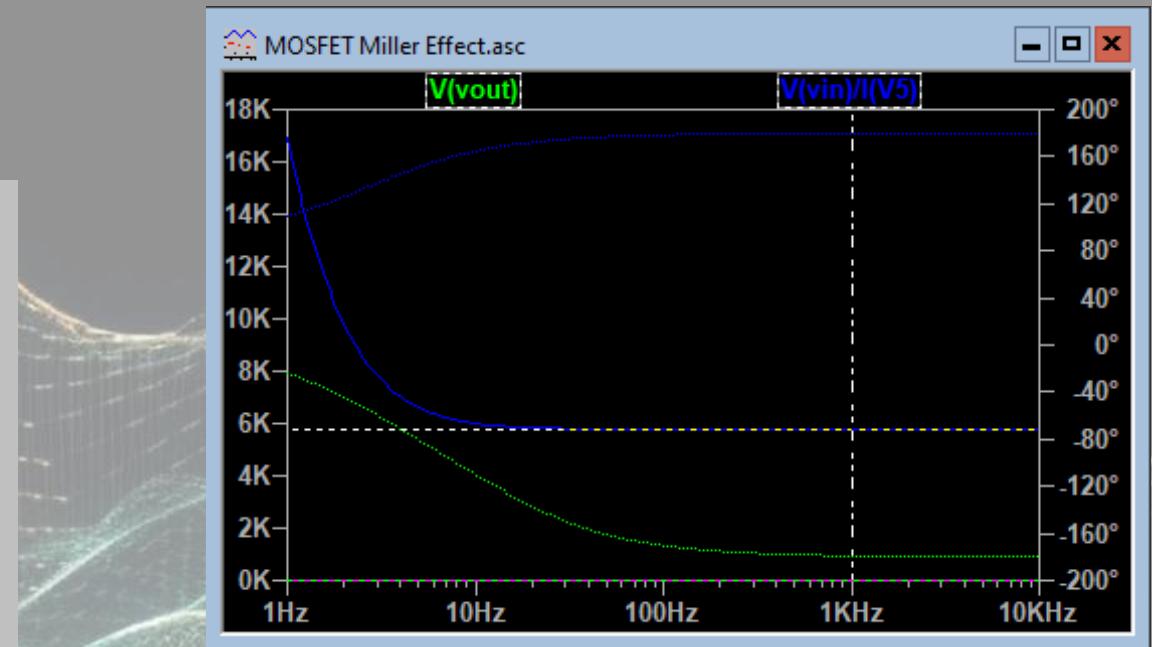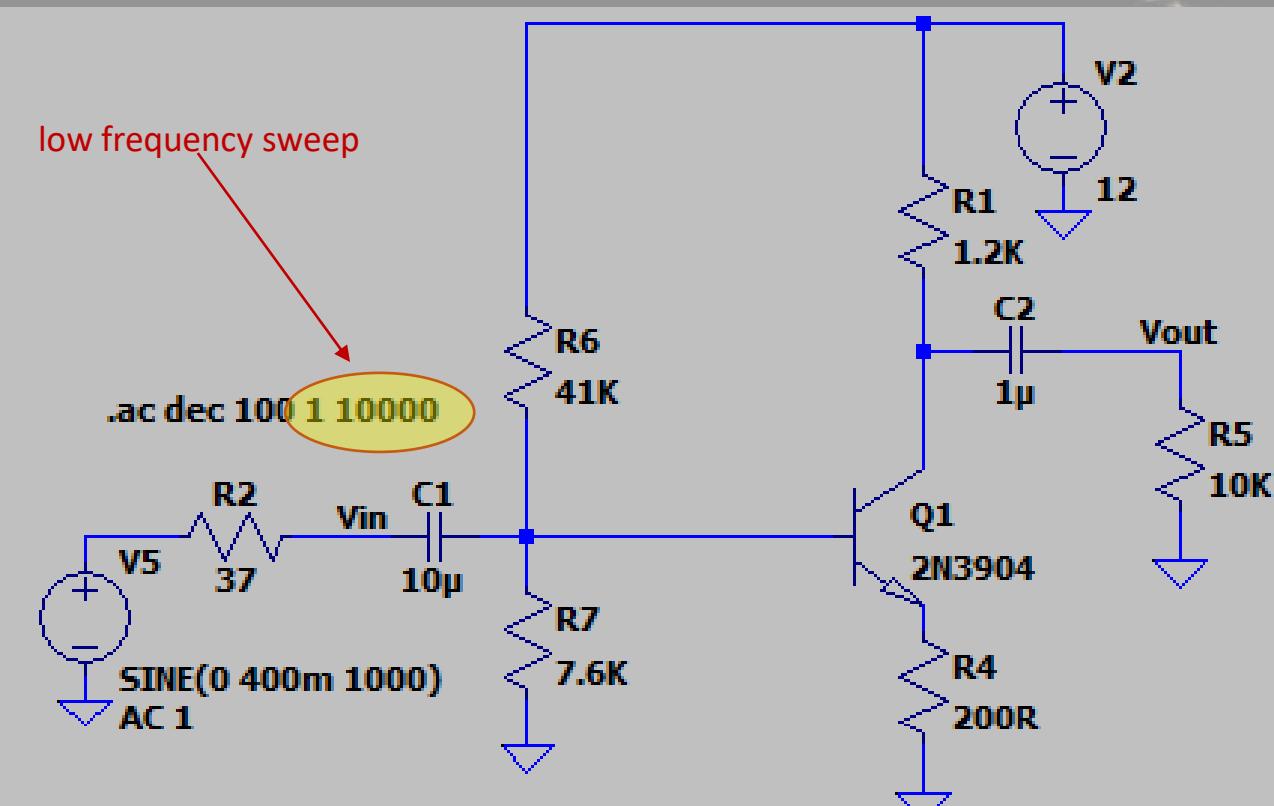

NO MILLER EFFECT: MATH

For low frequency, input impedance:

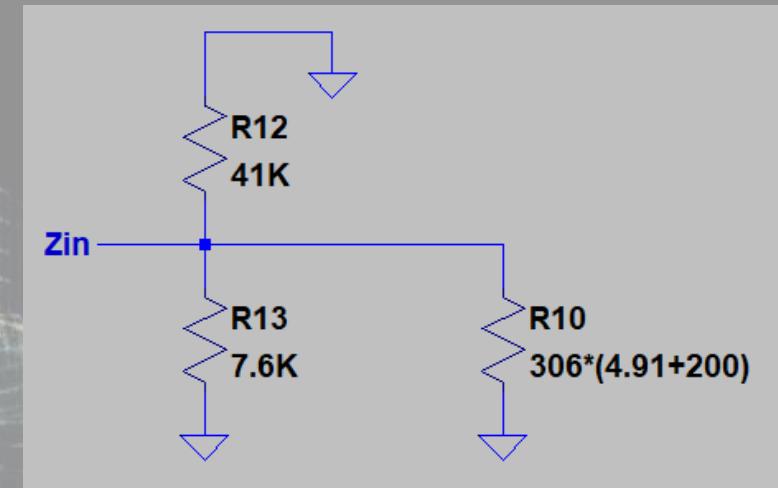
1. Ground all DC sources
 - For BJT, $r_e = V_t/I_c$ (intrinsic resistance from base to emitter)
 - For BJT we calculate $R_{in} = \text{Beta} * (r_e + R_e)$ which is grounded
 - For MOSFET@Saturation, its removed due to high input impedance
2. Short all DC blocking capacitors (i.e., large value caps)
3. We take a parallel combination of all resistors
 - At low frequencies, we can ignore Miller Capacitance to ground. At RF frequencies we need to account for Miller Capacitance




$$1/Z_{in} = 1/41K + 1/7.6K + 1/62744 = 0.00172$$

$$Z_{in} = 5817$$

MILLER EFFECT: Z 2N3904

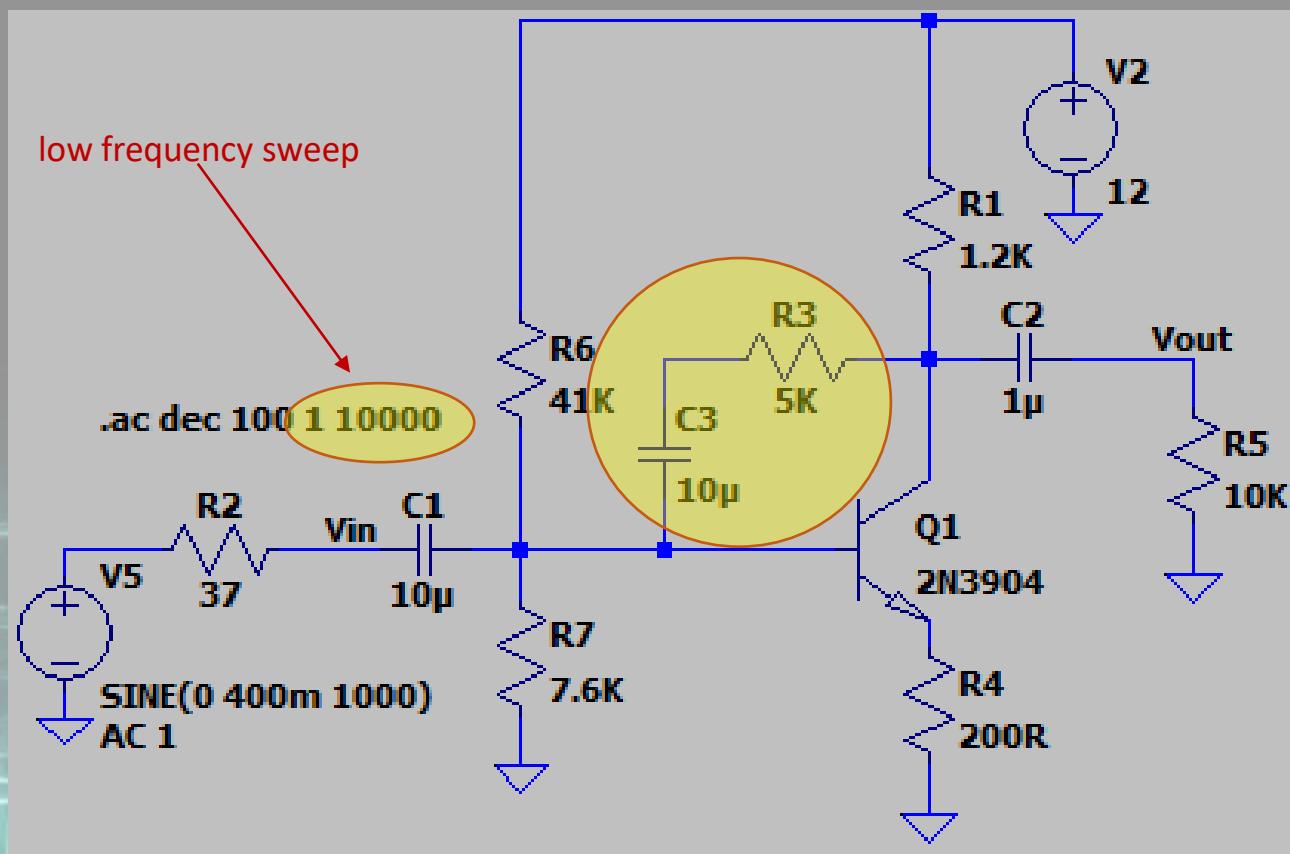

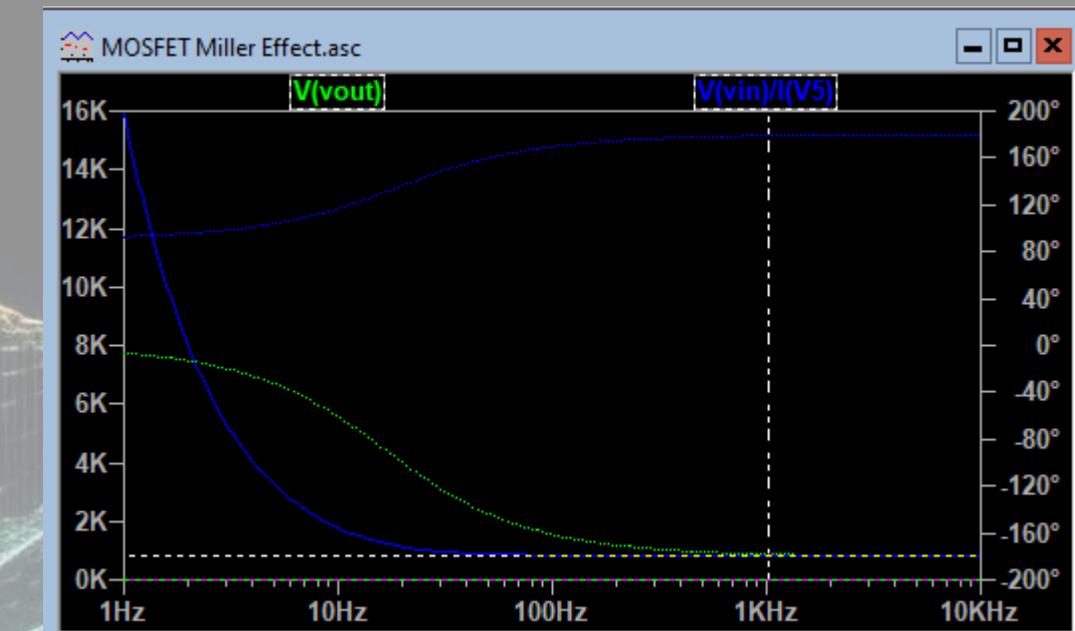At low frequencies,
“Intrinsic” Capacitance is negligible.
C3 is DC Blocker




Calculated	
Beta	306
r _e	4.91
r _c	882
r _e +r _{e'}	205
A _v	4.3
Z _{in}	5817
Z _{miller}	942
Z _{in}	811

Cursor 1	V(vout)		
Freq:	1kHz	Mag:	3.9308282
Phase:	-178.1703°		
Group Delay:	5.0911252 μ s		
Cursor 2	V(vin)/I(V5)		
Freq:	1kHz	Mag:	837.72507
Phase:	178.83502°		
Group Delay:	-3.2191284 μ s		
Ratio (Cursor2 / Cursor1)			
Freq:	0Hz	Mag:	213.11669
Phase:	-2.9946825°		
Group Delay:	-8.3102536 μ s		

MILLER EFFECT: Z MATH

For low frequency, input impedance:

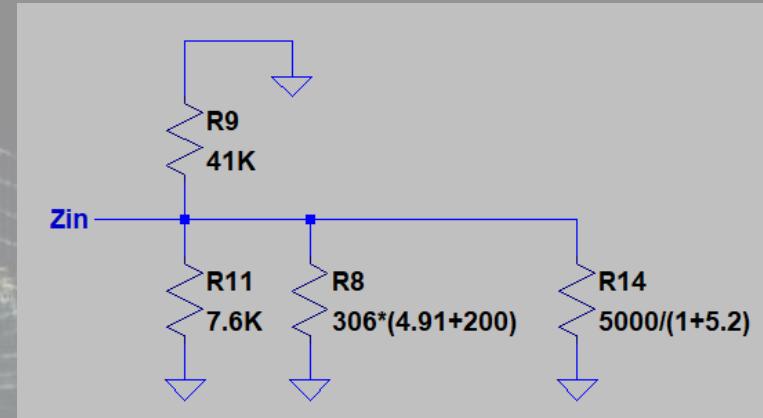
1. Ground all DC sources
 - For BJT, $r_e = V_t/I_c$ (intrinsic resistance from base to emitter)
 - For BJT we calculate $R_{in} = \beta * (r_e + R_e)$ which is grounded
 - For MOSFET, it's removed because it has very high input impedance
2. Short all DC blocking capacitors (i.e., large value caps)
3. Need to add Miller Impedance to ground $R_{Miller} = Z_{feedback}/(1+A)$
4. We take a parallel combination of all resistors
 - At low frequencies, we can ignore Miller Capacitance to ground. At RF frequencies we need to account for Miller Capacitance



$$1/Z_{in} = 1/41K + 1/7.6K + 1/62744 + 1/942 = 0.001233$$

$$Z_{in} = 811$$


Miller Capacitance Calculations

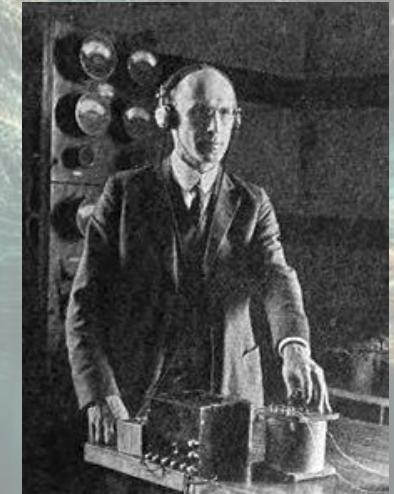


John Milton Miller

MILLER CAPACITANCE

MOSFET Model

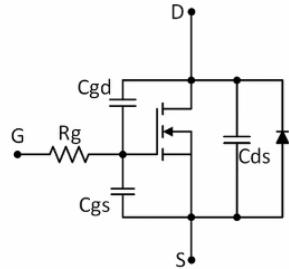

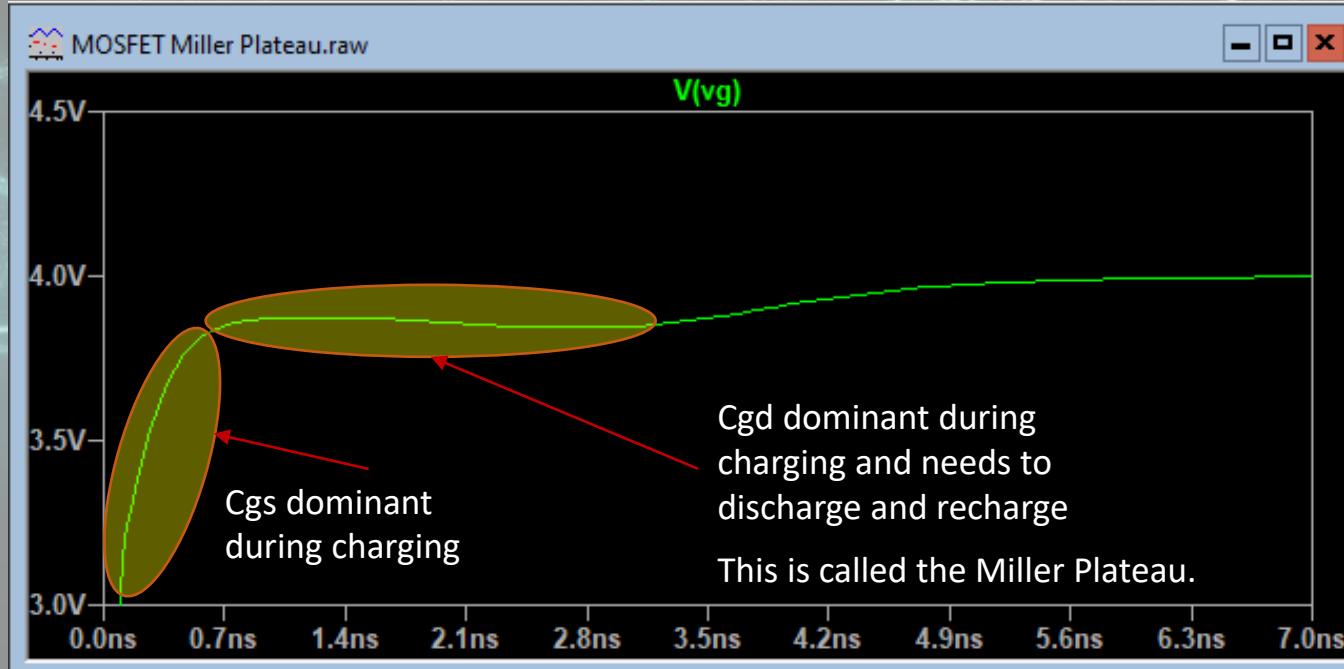
1. Without any feedback network, internal MOSFET capacitors take time to charge especially if current is limited (i.e., the R in RC time constant)
2. C_{gs} charges, C_{gd} needs to discharge, then C_{gd} needs to recharge.



1. C_{gd} is dominant and charges much slowly. This is called the Miller Plateau.
2. Once C_{gd} is discharged, V_{ds} can continue to rise as C_{gs} recharge. V_{ds} is allowed to reach full voltage.



Need time or current for capacitors to charge!

MILLER EFFECT: C IR510

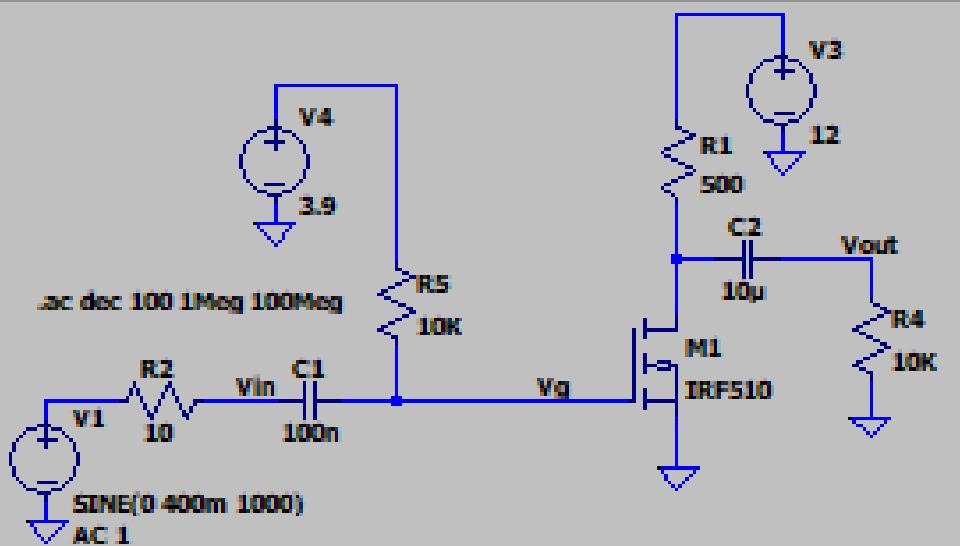

IRF510 Datasheet


Circuit (DataSheet)		Calculated	
Rbias	10000		
Rd	500		
Rs	10		
Rout	10000		
Cgd	15 pF	Cmiller	615
Cgs	165 pF	Cin	780
Cfb	0 pF	Rin	10
Measured		Fc	
Av	40.0	20.833	
Zin	25.0		

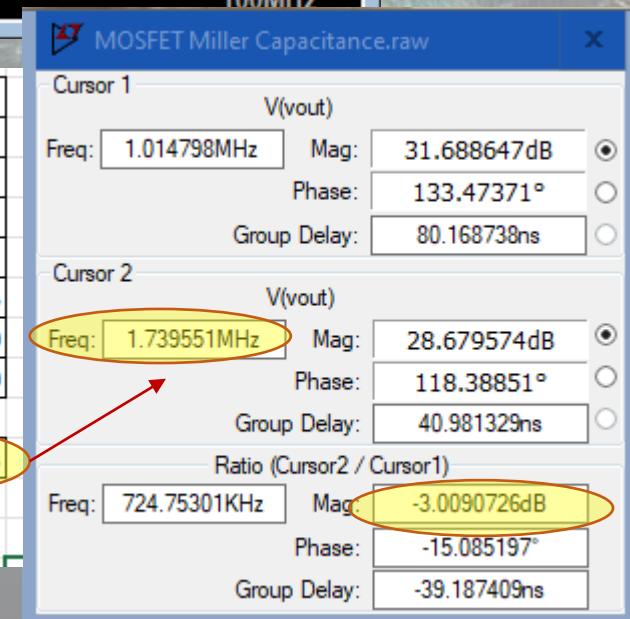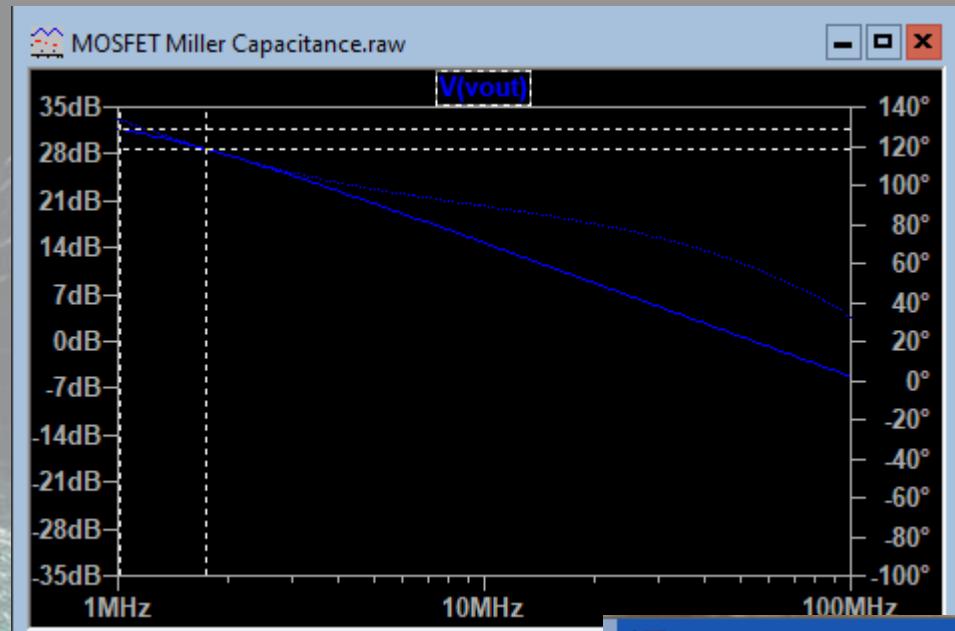

WTF?!



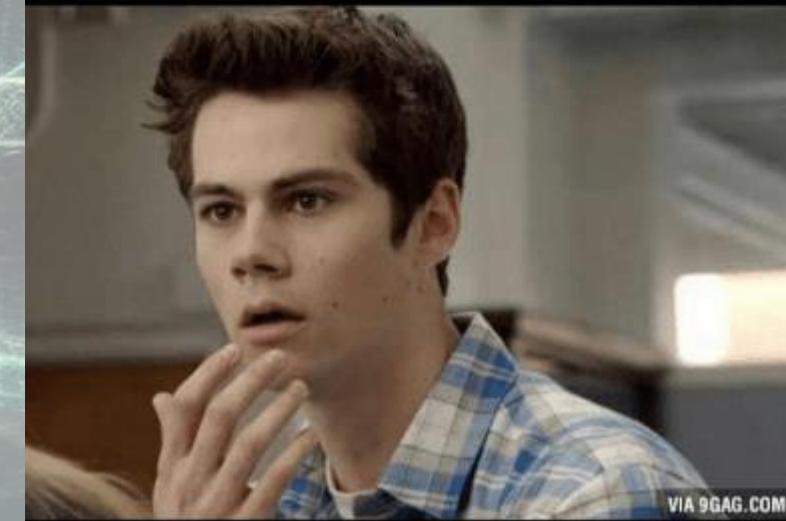**When the whole class is fighting
over whether the answer is 17 or 18
but you got 157**



VIA 9GAG.COM

LTSPICE MODELS: Trustworthy?

Datasheet

Dynamic		V _{GS} = 0 V, V _{DS} = 25 V, f = 1.0 MHz, see fig. 5	-	180	-	pF
Input capacitance	C _{iss}		-	81	-	
Output capacitance	C _{oss}		-	15	-	
Reverse transfer capacitance	C _{rss}	V _{GS} = 10 V R _g = 24 Ω, R _D = 8.4 Ω, see fig. 10 ^b	-	8.3		nC
Total gate charge	Q _g		-	-	2.3	
Gate-source charge	Q _{gs}		-	-	3.8	
Gate-drain charge	Q _{gd}		-	6.9	-	
Turn-on delay time	t _{d(on)}		-	16	-	
Rise time	t _r		-	15	-	
Turn-off delay time	t _{d(off)}		-	9.4	-	
Fall time	t _f		2.5	-	11.6	Ω
Gate input resistance	R _g					
Internal drain inductance	L _D		-	4.5	-	nH
Internal source inductance	L _S	Between lead, 6 mm (0.25") from package and center of die contact	-	7.5	-	


C _{gd}	15	pF
C _{gs}	165	pF

LTSpice (.op Analysis)

Name:	m1
Model:	irf510
Id:	1.18e-02
Vgs:	3.90e+00
Vds:	6.10e+00
Vth:	3.80e+00
Gm:	1.32e-01
Gds:	1.11e-04
Cgs:	1.00e-10
Cgd:	1.17e-10
Cbody:	6.38e-11

```
.model mosfet NMOS (VTO=1.899 RS=0.15519 KP=3.91 RD=0.1943 TC1RD=0.0231 RG=45.199 IS=1e-36
+ CGDMAX=7.40E-10 CGDMIN=1.00E-11 XG2CGD=1.6 XG1CGD=0.1 CBD=6.92E-11 VT CGD=0.2)
.model diode D( IS=2.61e-13 RS=0.0407 TT=1.614e-07)
```

MILLER EFFECT: C IR510

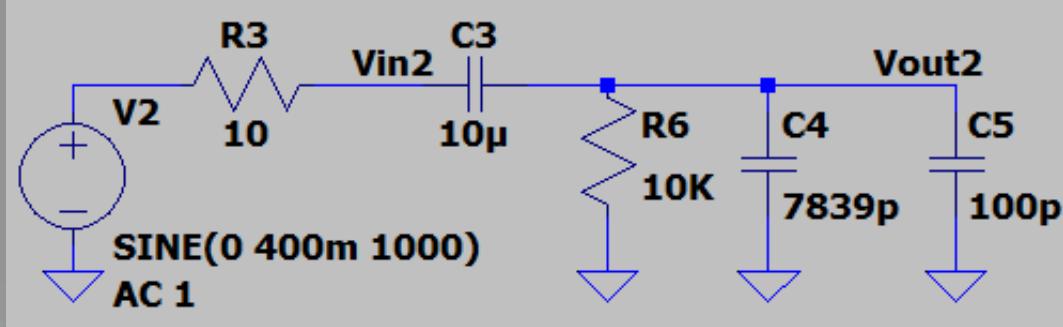


Simplified AC Model






LTSpice Model

Circuit (LTSpice)		Calculated	
R_{bias}	10000		
R_d	500		
R_s	10		
R_{out}	10000		
C_{gd}	117 pF		
C_{gs}	100 pF		
C_{fb}	0 pF		
		G_m	0.132
		A_v	66
		C_{miller}	7839
		C_{in}	7939
		R_{in}	10
		F_c	2.047

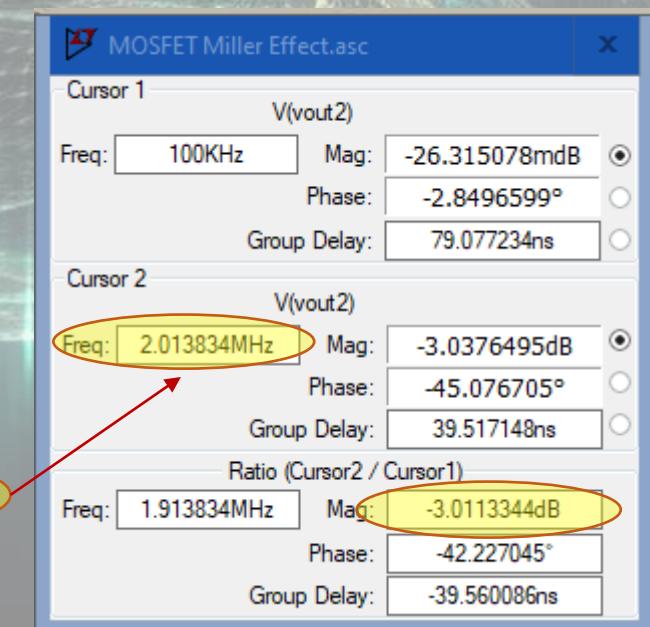

MILLER EFFECT: C IRF510

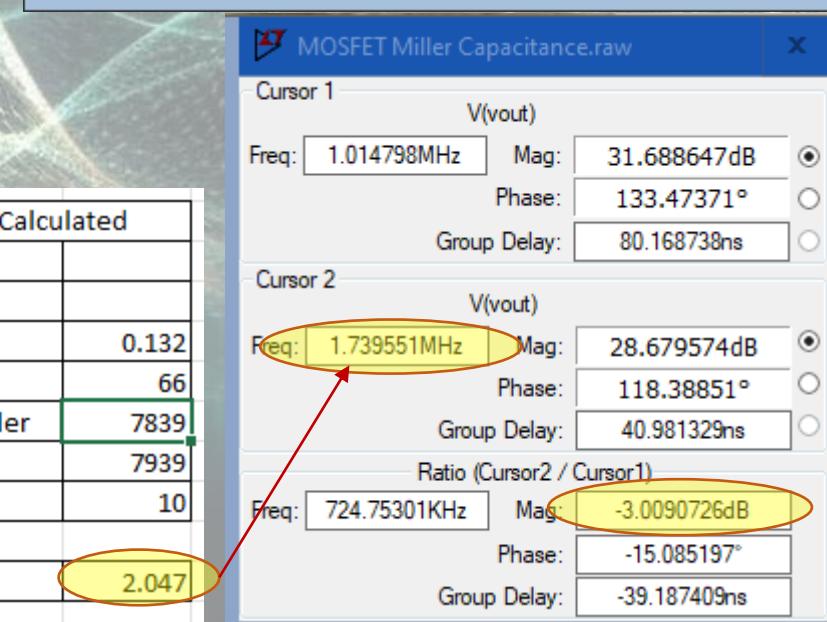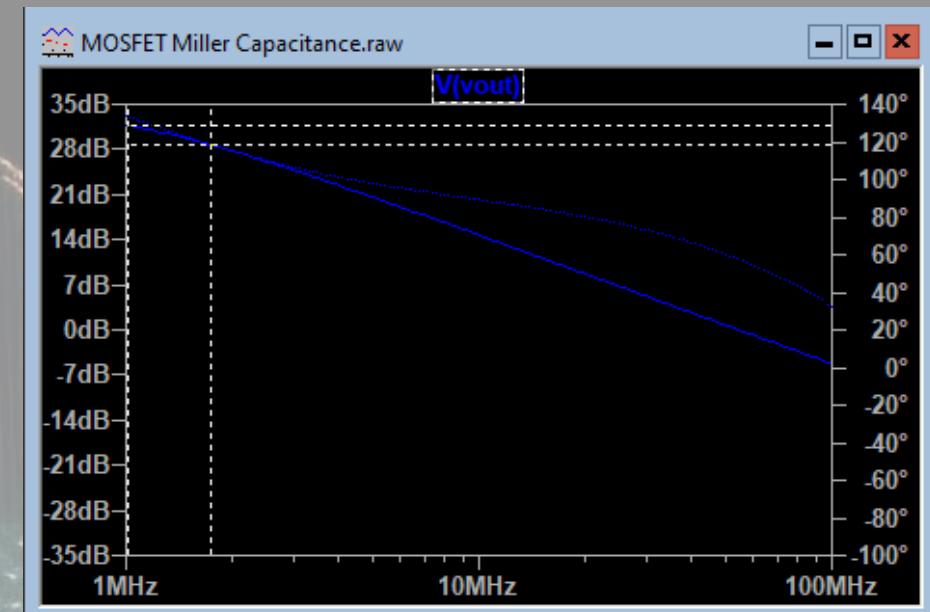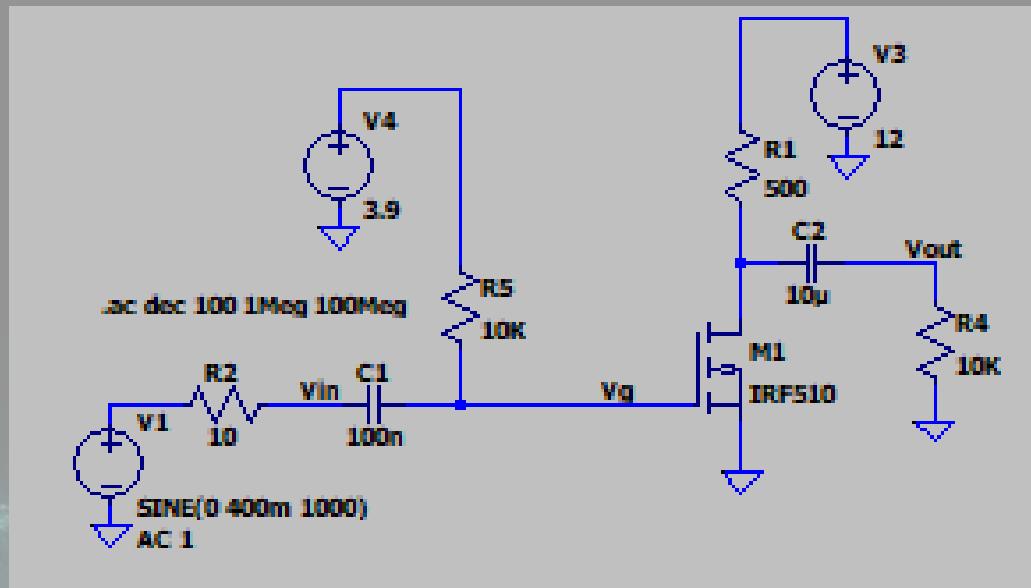


Circuit (LTSpice)	Calculated
R_{bias}	10000
R_d	500
R_s	10
R_{out}	10000
C_{gd}	117 pF
C_{gs}	100 pF
C_{fb}	0 pF
G_m	0.132
A_v	66
C_{miller}	7839
C_{in}	7939
R_{in}	10
F_c	2.047

MILLER EFFECT: C MATH

For RF frequency, high 3dB cutoff:

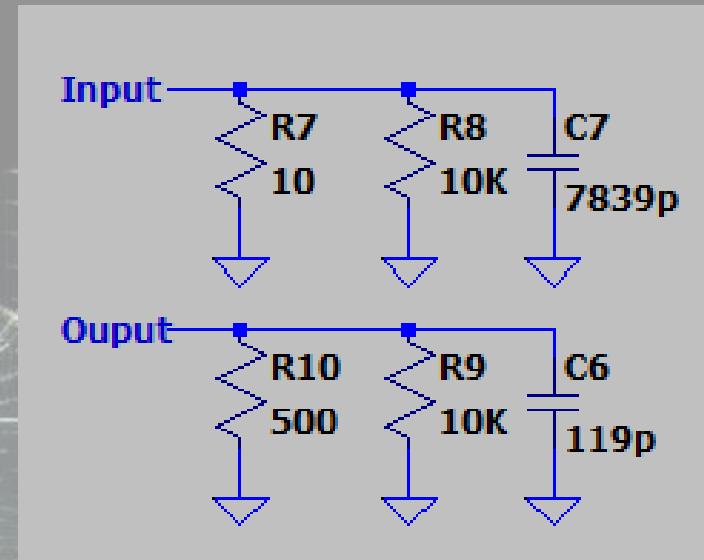
1. Ground all DC sources
 - For BJT, $r_e = V_t/I_c$ (intrinsic resistance from base to emitter)
 - For BJT we calculate $R_{in} = \beta * (r_e + R_e)$ which is grounded
 - For MOSFET, it's removed because it has very high input impedance
2. Short all DC blocking capacitors (i.e., large value caps)
3. Need to add Miller Capacitance to ground
 - Input: $C_{Miller_in} = C_{gd} * (1+A)$ *where A is gain without feedback
 - Output: $C_{Miller_out} = C_{gd} * (1+A) / A$
4. Calculate input resistance including source resistance
 - For MOSFET $R_{in} = 1/(1/R_b + 1/R_s)$
 - For BJT $R_{in} = 1/[1/R_{b1} + 1/R_{b2} + 1/R_s + 1/(\beta * (R_e + r_e))]$
5. Calculate Output resistance including load resistance
 - For MOSFET $R_{out} = 1/(1/R_d + 1/R_l)$
 - For BJT $R_{in} = 1/[1/R_c + 1/R_c + 1/R_e]$
6. Calculate 3dB Frequency at input and output using
 - R_{in} and C_{Miller_in} for input $F_c = 1/(2\pi R_{in} C_{Miller_in})$
 - R_{out} and C_{Miller_out} for output $F_c = 1/(2\pi R_{out} C_{Miller_out})$





$$F_{c1} = 1/(2\pi 3.14 * 10 * 7839 \text{ pF}) = 2.047 \text{ MHz}$$

$$F_{c2} = 1/(2\pi 3.14 * 476 * 119 \text{ pF}) = 2.814 \text{ MHz}$$


Wrap your head around this....

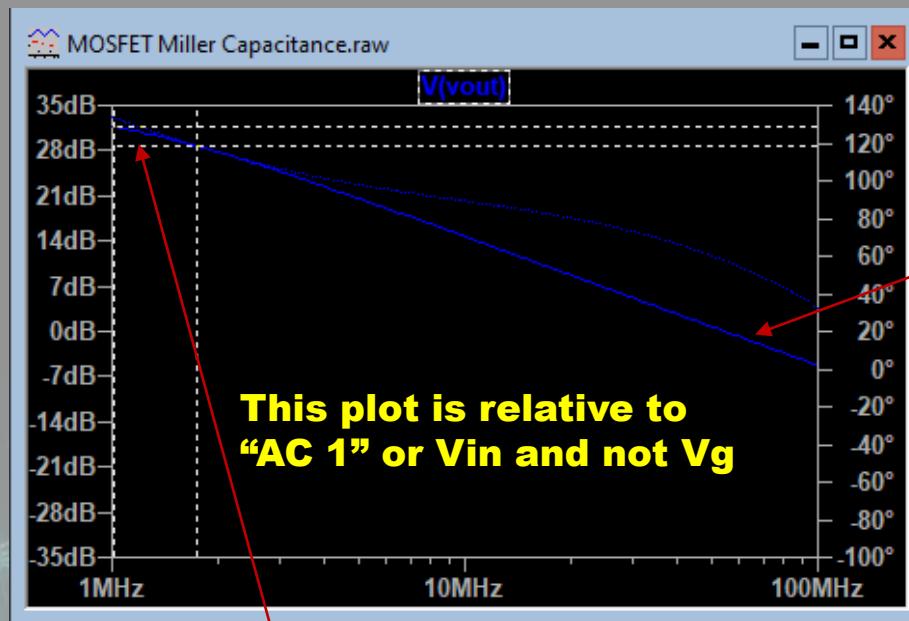

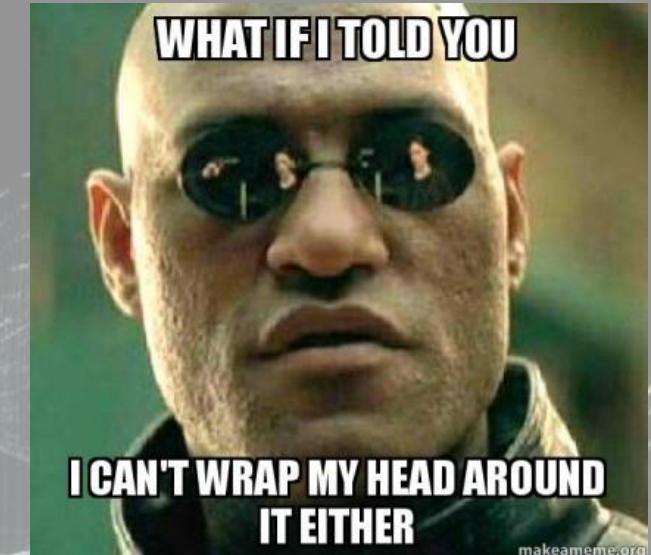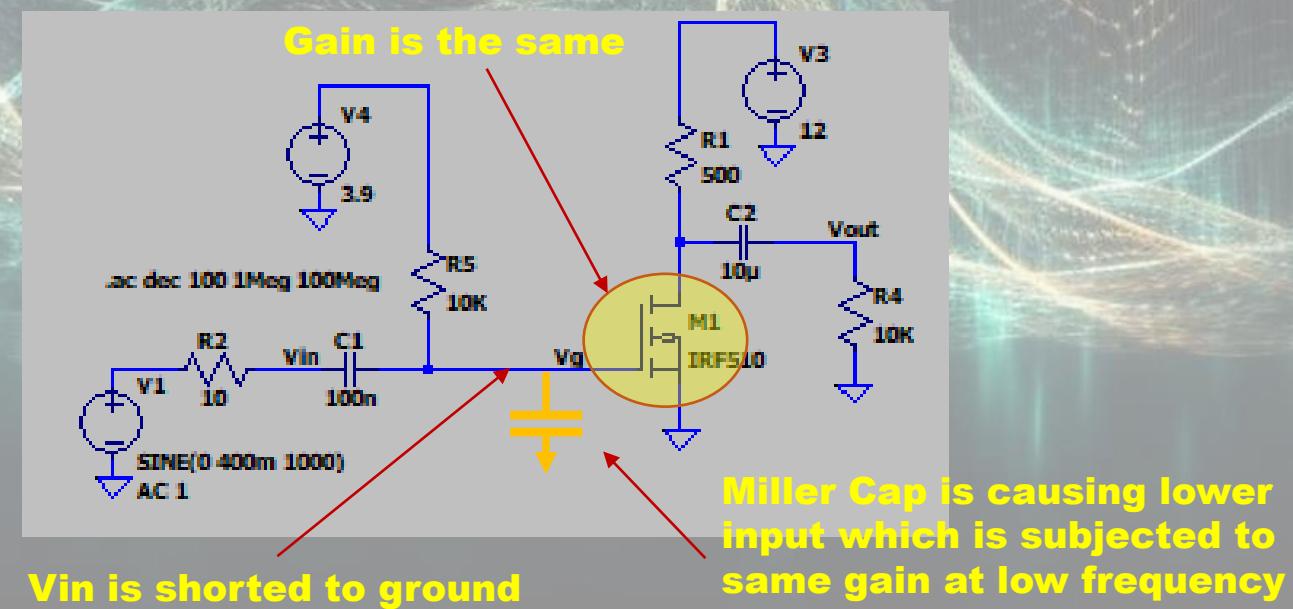This is and **ALWAYS** will be the gain (maybe larger at lower frequencies)




MILLER EFFECT: C 2N7000

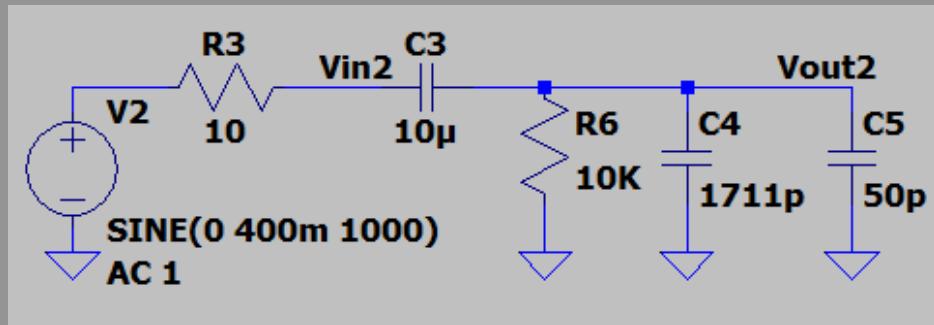

Simplified AC Model

Input -3dB Frequency!!!

LTSpice Model

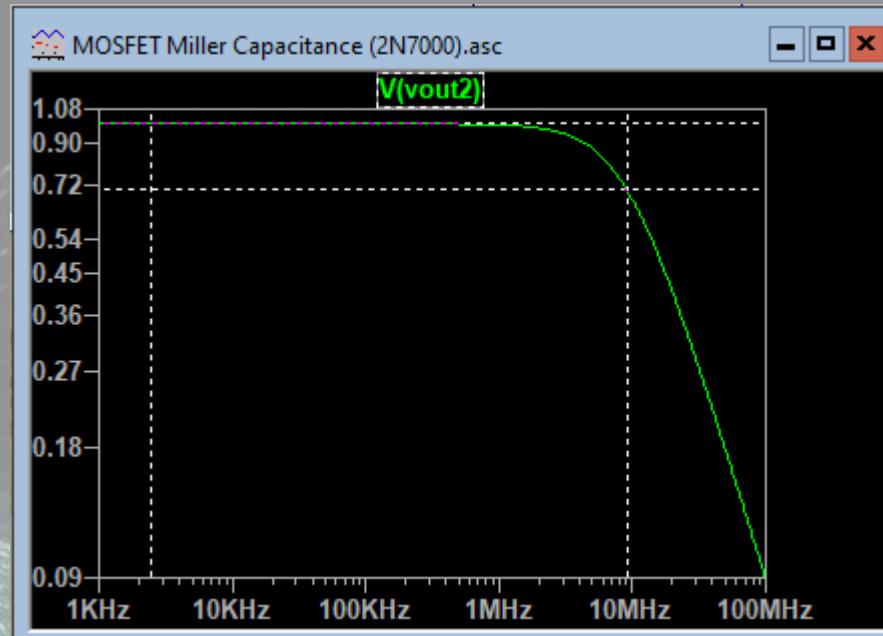

Circuit (LTSpice)	Calculated
Rbias	10000
Rd	500
Rs	10
RI	10000
Rout	10000 pF
Cin	1000000 pF
Cout	1000000 pF
Cgd	56.1 pF
Cgs	50 pF
Cfb	0

Cursor 1

V(vout2)

Freq: 2.446516KHz Mag: 998.82521m Phase: 21.740001m° Group Delay: 59.880297ns

Cursor 2


V(vout2)

Freq: 9.0764461MHz Mag: 705.18973m Phase: -45.087435° Group Delay: 8.7681108ns


Ratio (Cursor2 / Cursor1)

Freq: 9.0739996MHz Mag: -3.0236703dB Phase: -45.109175° Group Delay: -51.112186ns

MILLER EFFECT: C 2N7000

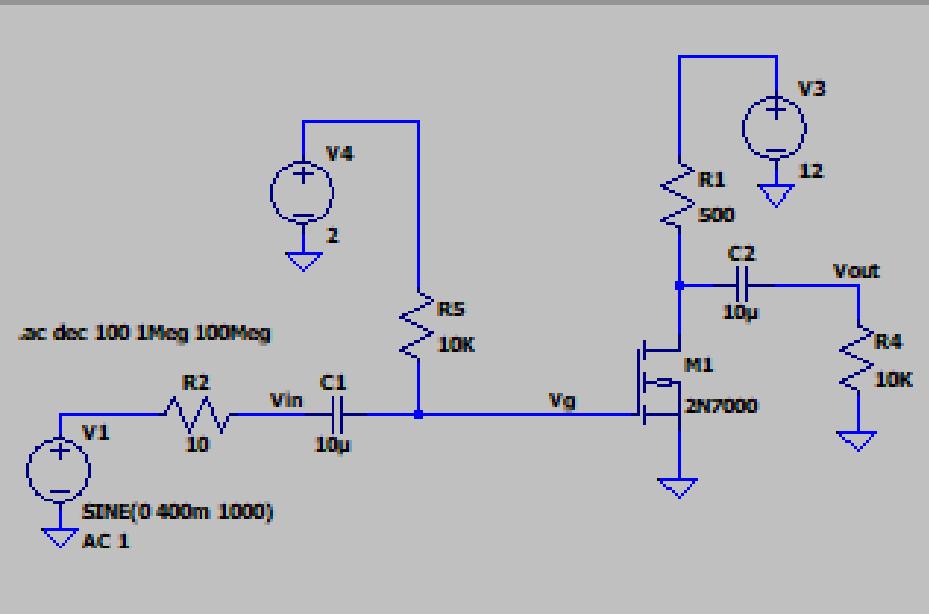

LTSpice Model

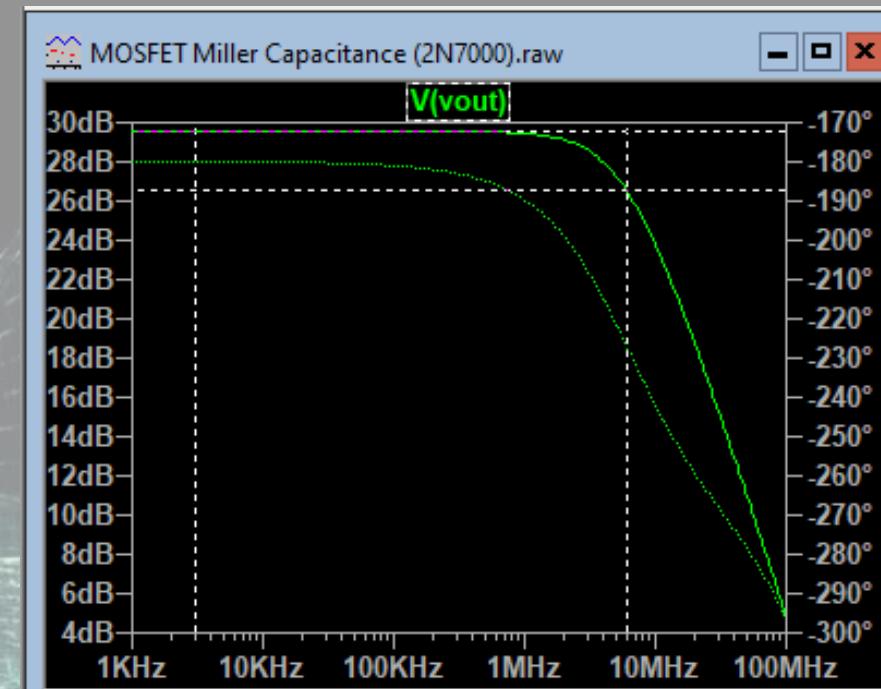


Circuit (LTSpice)		Calculated	
Rbias	10000		
Rd	500		
Rs	10	Gm	0.083
Rl	10000	Av	30
Rout	10000	CmillerIn	1711
Cin	1000000	Cin	1761
Cout	1000000	Rin	10
Cgd	56.1 pF	CmillerOut	58
Cgs	50 pF	Rout	476
Cfb	0	Fhi	9.047
		Fho	5.762

Cursor 1	V(out)		
Freq:	2.9896442KHz	Mag:	29.561261dB
Phase:	-179.96983°		
Group Delay:	82.586196ns		
Cursor 2	V(out)		
Req:	6.0391417MHz	Mag:	26.538735dB
Phase:	-226.92462°		
Group Delay:	14.029613ns		
Ratio (Cursor2 / Cursor1)			
Freq:	6.0361521MHz	Mag:	-3.0225265dB
Phase:	-46.95479°		
Group Delay:	-68.556583ns		

The universe makes more sense now....

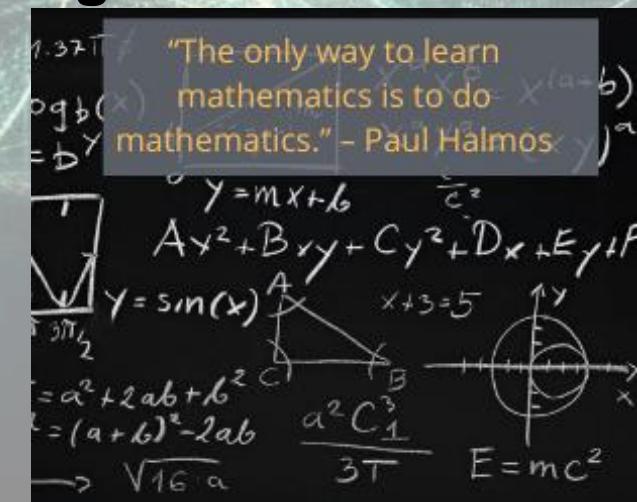1. Observed: Due to the internal capacitors, the MOSFET is frequency dependant. At high frequencies, the input impedance is reduced (almost short circuit)
2. The time for the MOSFET to turn on completely is dependent on the C_{gs} and C_{gd} capacitors to charge
3. The Miller Effect causes any **Feedback Impedance** of an Inverting Amplifier to be shorted to ground and reduced by a factor of the gain
$$Z_{\text{Miller}} = R / (1+A)$$
4. The Miller Effect caused any **Feedback Capacitance** of an Inverting Amplifier to be shorted to ground and increased by a factor of the gain
$$C_{\text{Miller}} = C * (1+A)$$
5. High gain RF amplifiers **will be** problematic!
 - ✓ Impedance will decrease. Input is shorted.
 - ✓ Internal Capacitance will increase. 3dB bandwidth decreases
 - ✓ High gain RF amplifiers **will be** problematic!



DON'T TRUST “NON-NATIVE” LTSPICE MODELS!!



"Trust but Verify."

- Ronald Wilson Reagan




..to be continued

SOAREX GROUP

Addressing the Miller Effect (MOSFETS)

Dave VE3OOI

December 2023

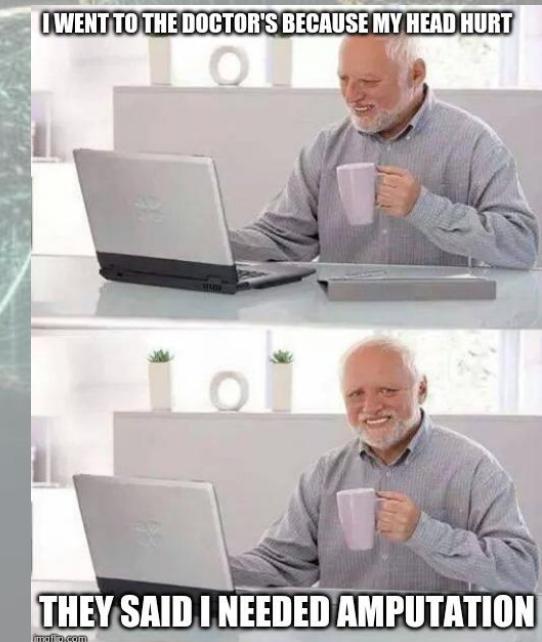

AGENDA

Addressing Miller Effect using the “Scotty Approach”

1. Recap

2. Approaches to neutralize Miller Effect

- ✓ **Change amplifier type**
- ✓ **Reduce Gain**
- ✓ **Change RC Time Constant**



**Captain, we need to kick
Miller in the bag pipes**

Danger Will Robinson...




Quote Charlie Morris, ZL2CTM:

This NOT a tutorial.

It's a log of my journey. Right or wrong.

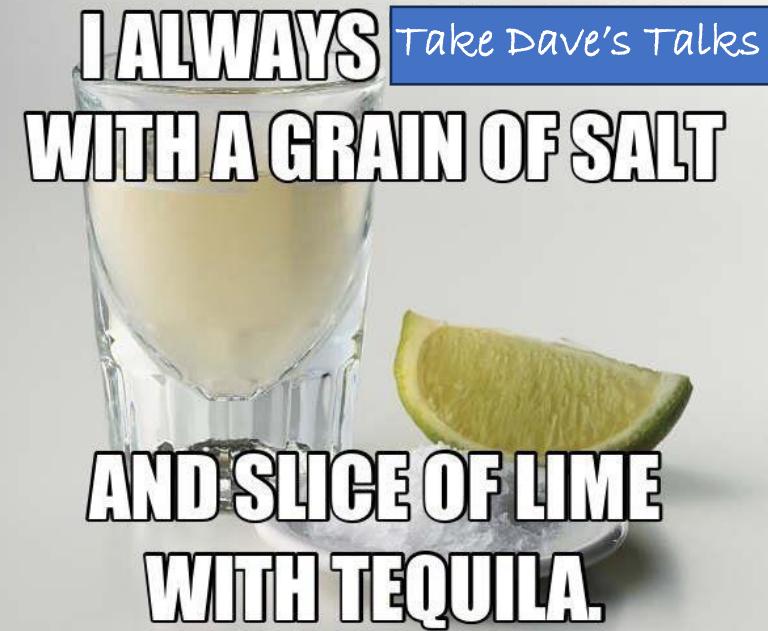I ALWAYS Take Dave's Talks
WITH A GRAIN OF SALT



**AND SLICE OF LIME
WITH TEQUILA.**



REFERENCES

#207: Basics of a Cascode Amplifier and the Miller Effect

https://youtu.be/Op_I3Ke7px0

The thumbnail shows a hand holding a blue pen over a handwritten note on lined paper. The note is titled 'BASICS OF THE CASCODE AMPLIFIER & THE MILLER EFFECT'. It includes a list of points and a schematic diagram of a cascode amplifier circuit.

- COMBINATION OF CE AMPLIFIER AND CB AMPLIFIER
- GAIN \approx CE AMPLIFIER
- USED MAINLY TO REDUCE THE MILLER EFFECT

Schematic Diagram:

```
graph LR; Input((INPUT)) --> Vbe((Vbe)); Vbe --> Q1((Q1)); Q1 --> Vce((Vcc)); Vce --> Rc((Rc)); Rc --> Output((OUTPUT));
```

w2aew 193K subscribers

Power Electronics with Dr. K 8.37K subscribers

EE-444/544 Power Electronics

Week 3-2

MOSFET Gate Charge and Turn-On Characteristics

Week 3-2 EE444/544 – Power Electronics

Power Electronics WK3_2 MOSFET Turn On Characteristics

<https://youtu.be/f1yt0s3gpcE>

Semiconductor Devices: Miller's Theorem

<https://youtu.be/yM9xlbAf43Q>

The thumbnail shows a screenshot of a simulation software interface. It displays a circuit diagram of a voltage-controlled voltage source (operating point analysis) and its corresponding Miller equivalent circuit. The circuit consists of a dependent voltage source $-A_v$ in series with a load Z , followed by a Miller feedback network with input impedance $Z_{in-Miller} = Z/A+1$ and output impedance $Z_{out-Miller} = Z A/(A+1)$.

Electronics with Professor Fiore 7.24K subscribers

Mateo Aboy 14.2K subscribers

MOSFET Amplifiers

MOSFET High Frequency Model

MOSFET High Frequency Model

<https://youtu.be/19kXfUPdF9I>


Dr. Cristina Crespo

High Frequency Model of MOSFET

<https://youtu.be/19kXfUPdF9I>

The thumbnail shows a screenshot of a presentation slide. It features a high-frequency model of a MOSFET circuit diagram with nodes labeled C_{gs} , C_{gd} , C_{ds} , V_{gs} , V_{ds} , and V_{sd} .



FUNDAMENTALS

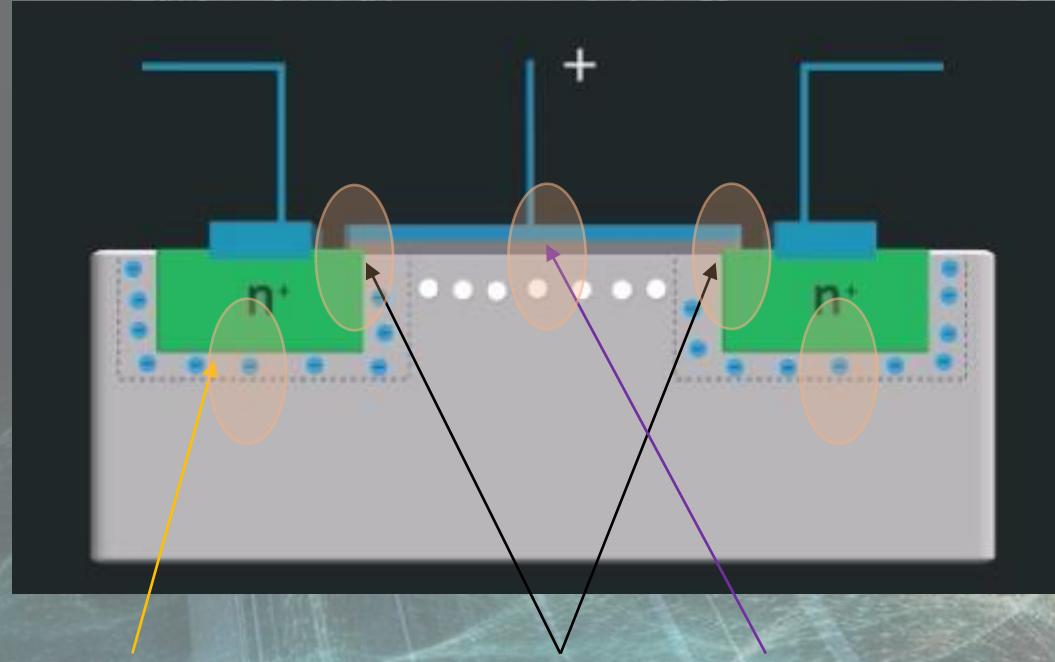

Depletion region



Overlap

Oxide/dielectric

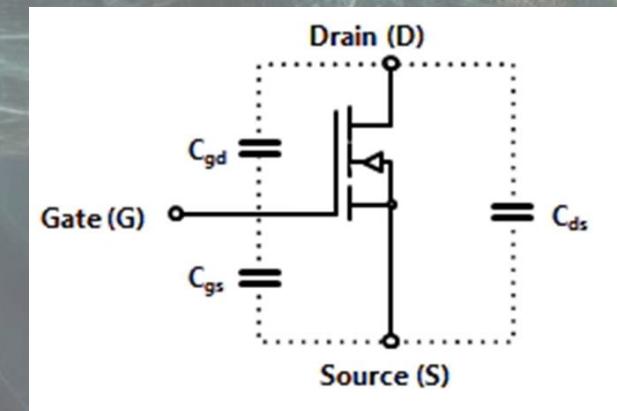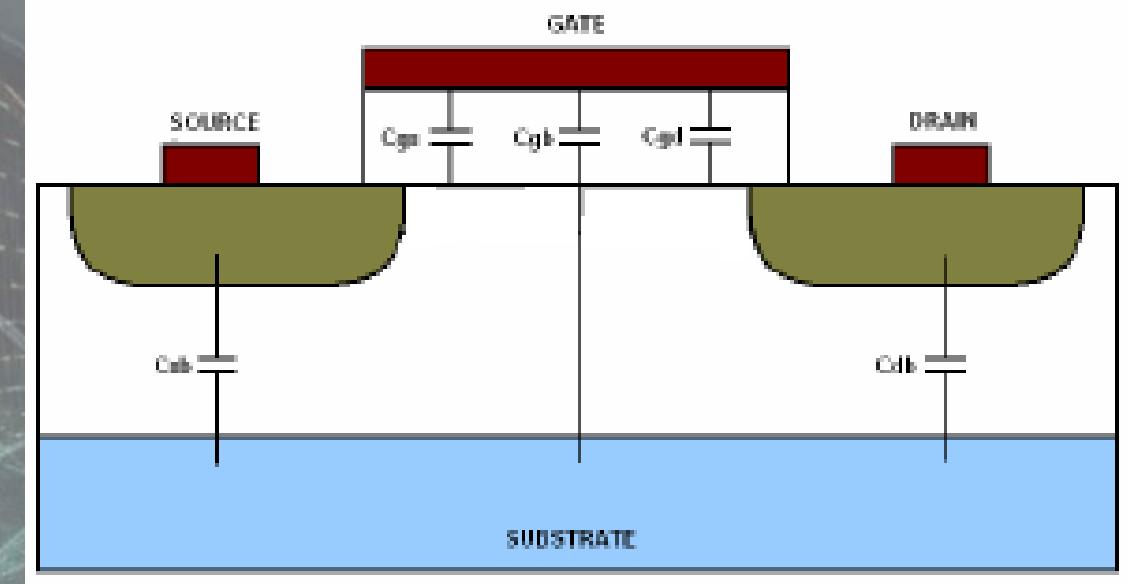


FUNDAMENTALS

MOSFET Model

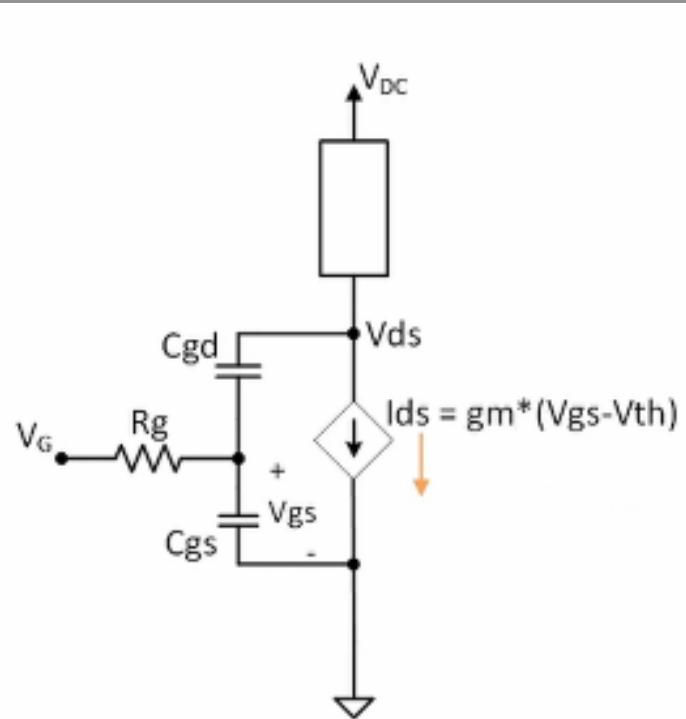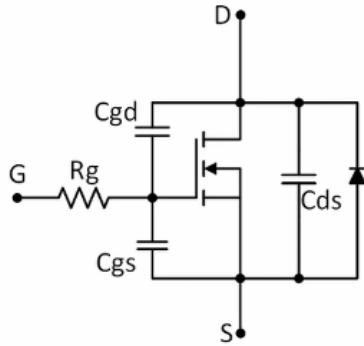

MOSFETs

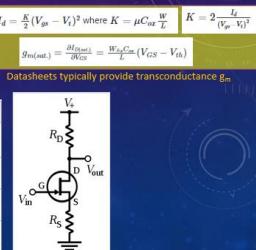- Similar Input and Output charts to BJT:
 - However, the input curve will show saturation if V_{gs} is high enough
- No concept of Beta (current amplification). MOSFET is a voltage device. Voltage controls current.
- The gain depends on g_m (transconductance) and K
- K is based on channel parameters inside MOSFET



$$I_d = \frac{K}{2} (V_{ds} - V_t)^2 \text{ where } K = \mu C_{ox} \frac{W}{L} \quad K = 2 \frac{I_d}{(V_{gs} - V_t)^2}$$



$$g_{m(sat)} = \frac{\partial I_{ds}}{\partial V_{gs}} = \frac{W C_{ox}}{L} (V_{gs} - V_{th})$$

Datasheets typically provide transconductance g_m

- The model of a MOSFET is basically an ideal current source that is driven by the gate to source voltage**
- When gate voltage is zero, MOSFET is off and C_{gd} is charged with respect to V_{dc} .**
- When gate voltage starts to rise (small voltage), all current flows to C_{gs} and that starts to charge.**
- Once V_{gs} threshold reached, I_{ds} begins to increase and V_{ds} starts to drop. C_{gd} starts to discharge.**
- Once I_{ds} reaches maximum, then V_{ds} is close to zero and C_{gd} is discharged. As V_{gs} increases, C_{gd} now charges with opposite polarity. Once C_{gd} is fully charged, the MOSFET is on.**
- The time for the MOSFET to turn on is from charge time of BOTH C_{gs} and C_{gd} . This is critical for MOSFET as a switch (e.g. buck converter)**

MILLER CAPACITANCE: THEORY

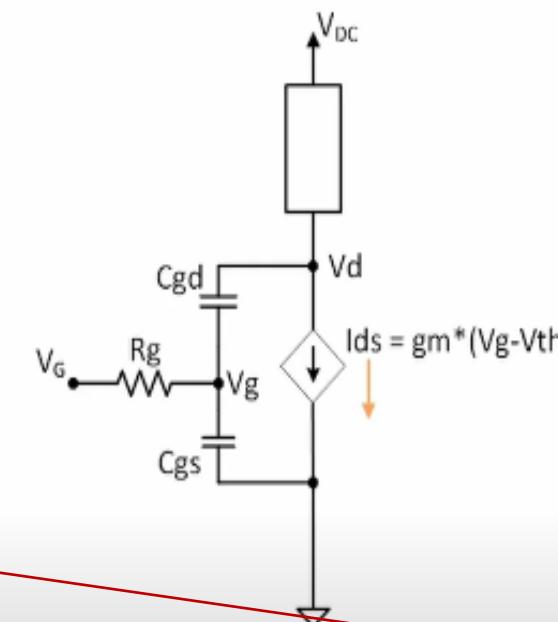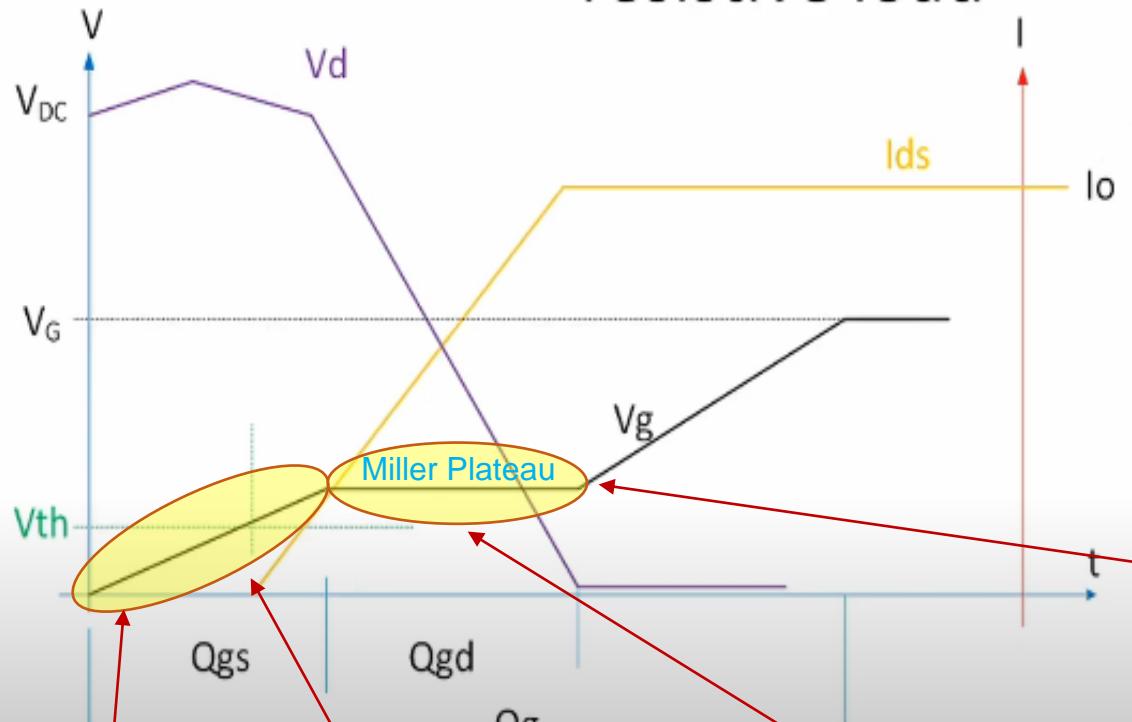MOSFET turn-on characteristics
resistive load



C_{gd} & C_{gs} Almost Fully Charged


Max Current and Zero Voltage drop

C_{gs} Charging

MOSFET Threshold Voltage

C_{gd} Discharging (After V_d Drops)

MILLER “DISTORTION”

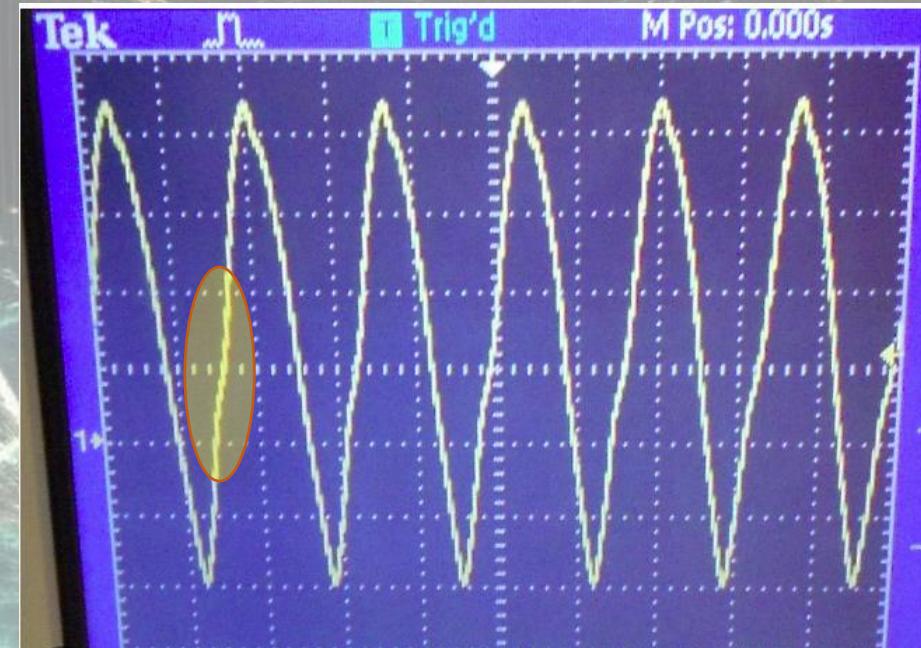

This has been exaggerated for illustration purposes

MILLER EFFECT/THEOREM




In electronics, the **Miller effect** accounts for the increase in the equivalent input capacitance of an inverting voltage amplifier due to amplification of the effect of capacitance between the input and output terminals. The virtually increased input capacitance due to the Miller effect is given by

$$C_M = C(1 + A_v)$$

where $-A_v$ is the voltage gain of the inverting amplifier (A_v positive) and C is the feedback capacitance.

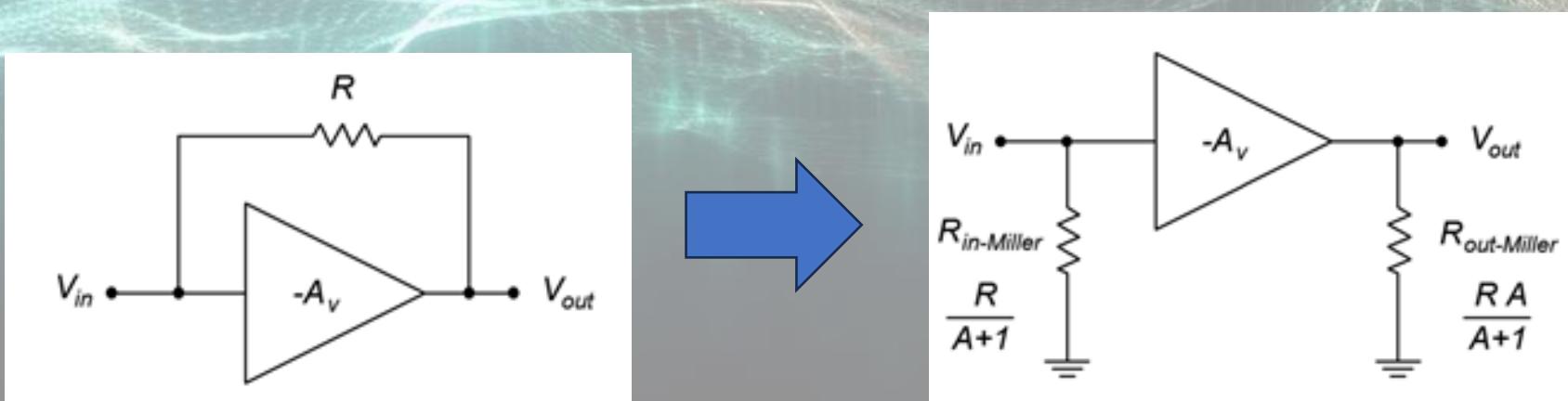Although the term *Miller effect* normally refers to capacitance, any impedance connected between the input and another node exhibiting gain can modify the amplifier input impedance via this effect. These properties of the Miller effect are generalized in the *Miller theorem*.



Miller Neutralization: Kick in Bag Pipes



1. Reduce the gain hence reduce Miller Capacitance

- ✓ Use HYCAS or **CASCODE** amplifiers. Add common base, common gate stage 😊
- ✓ **Negative feedback** 😊

2. Increase the input drive to compensate for the low input impedance

- ✓ Use lower source impedance (transformer?) to compensate for voltage divider

3. Change the RC time constant for the internal capacitors (faster turn on)

- ✓ Use **lower source impedance** (transformer?) 😊
- ✓ Reduce internal capacitance (different MOSFET)




4. Increase the current to reduce the charge time of the capacitors (faster turn on)

- ✓ Use lower source impedance (transformer?)
- ✓ Use a high current source (opamp)
- ✓ Use **positive feedback** 😊


SAME

CASCODE AMPLIFIER


MILLER EFFECT ON TRANSISTOR AMPLIFIERS

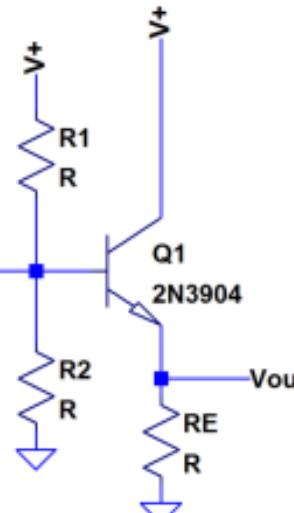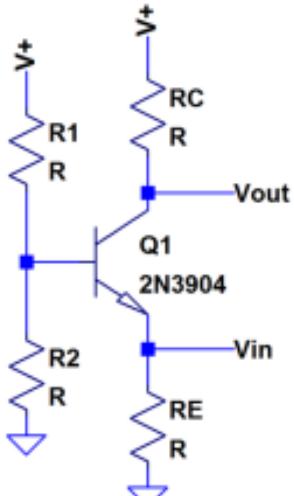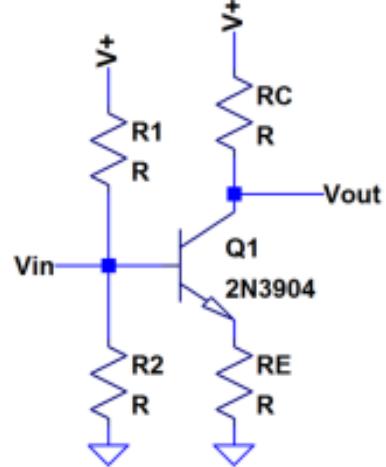


Circuit Types

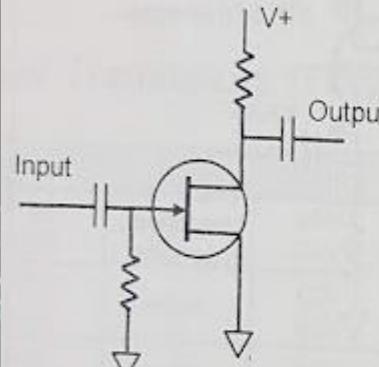

Common
Source

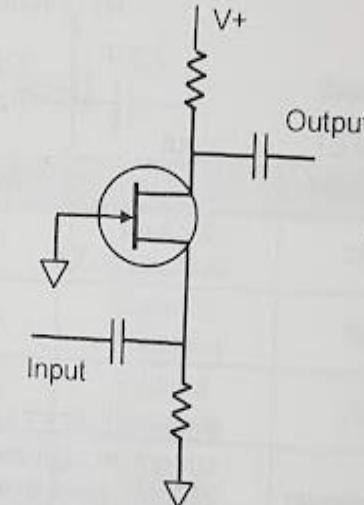

Common
Ground

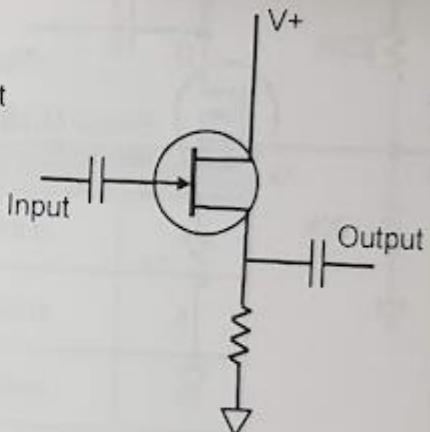

Common
Drain

NPN BJT

N-Channel FET/MOSFET

MILLER EFFECT ON TRANSISTOR AMPLIFIERS


Susceptible to
Miller Effect

Amplifier type	Characteristics ^a				
	R_{in}	A_{vo}	R_o	A_v	G_v
Common source (Fig. 7.35)	∞	$-\frac{g_m R_D}{R_D}$	R_D	$-\frac{g_m (R_D \parallel R_L)}{R_D}$	$-\frac{g_m (R_D \parallel R_L)}{R_D}$
Common source with R_s (Fig. 7.37)	∞	$-\frac{g_m R_D}{1 + g_m R_s}$	R_D	$\frac{-g_m (R_D \parallel R_L)}{1 + g_m R_s}$	$-\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$
Common gate (Fig. 7.39)	$\frac{1}{g_m}$	$g_m R_D$	R_D	$g_m (R_D \parallel R_L)$	$\frac{R_D \parallel R_L}{R_{sig} + 1/g_m}$
Source follower (Fig. 7.42)	∞	1	$\frac{1}{g_m}$	$\frac{R_L}{R_L + 1/g_m}$	$\frac{R_L}{R_L + 1/g_m}$

^a For the interpretation of R_{in} , A_{vo} , and R_o , refer to Fig. 7.34(b).

N-Channel FET/MOSFET

NPN BJT

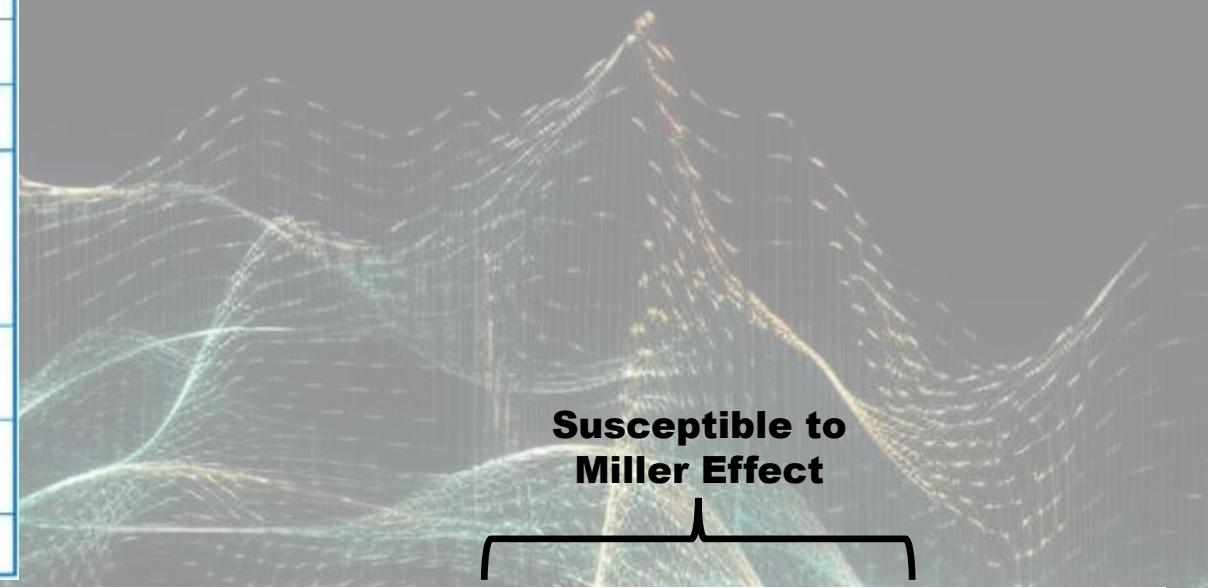


AMPLIFIER TYPE	COMMON BASE	COMMON Emitter	COMMON Emitter (Emitter Resistor)	COMMON COLLECTOR (Emitter Follower)
INPUT/OUTPUT PHASE RELATIONSHIP	0°	180°	180°	0°
VOLTAGE GAIN	HIGH $\frac{\alpha R_c}{R_s + r_e}$	MEDIUM $\frac{\beta (R_c \parallel r_o)}{R_s + r_e}$	MEDIUM $\frac{\beta R_c}{R_s + (\beta + 1)(r_e + R_L)}$	LOW $\frac{(\beta + 1)(R_c \parallel r_o)}{R_s + (\beta + 1)[r_e + (R_L \parallel R_o)]}$
CURRENT GAIN	LOW α	MEDIUM $\beta \frac{r_o}{R_c + r_o}$	MEDIUM β	HIGH $(\beta + 1) \frac{r_o}{r_o + R_L}$
POWER GAIN	LOW	HIGH	HIGH	MEDIUM
INPUT RESISTANCE	LOW r_e	MEDIUM $r_e = (\beta + 1) r_e$	MEDIUM $(\beta + 1)(r_e + R_E)$	HIGH $(\beta + 1)[r_e + (r_e + R_L \parallel R_o)]$
OUTPUT RESISTANCE	HIGH R_c	MEDIUM $R_c \parallel r_o$	MEDIUM R_c	LOW $r_o \parallel \left[r_o + \frac{R_o}{(\beta + 1)} \right]$

MILLER NEUTRALIZATION: CASCODE

**Miller Effect
Negatable for
common Gate**

Amplifier Type	R_{in}	R_{out}	A_V	A_i
Common-source/emitter	High	High	High	High
Common-gate/base	Low	High	High	-1
Common-drain/collector	High	Low	< 1	High

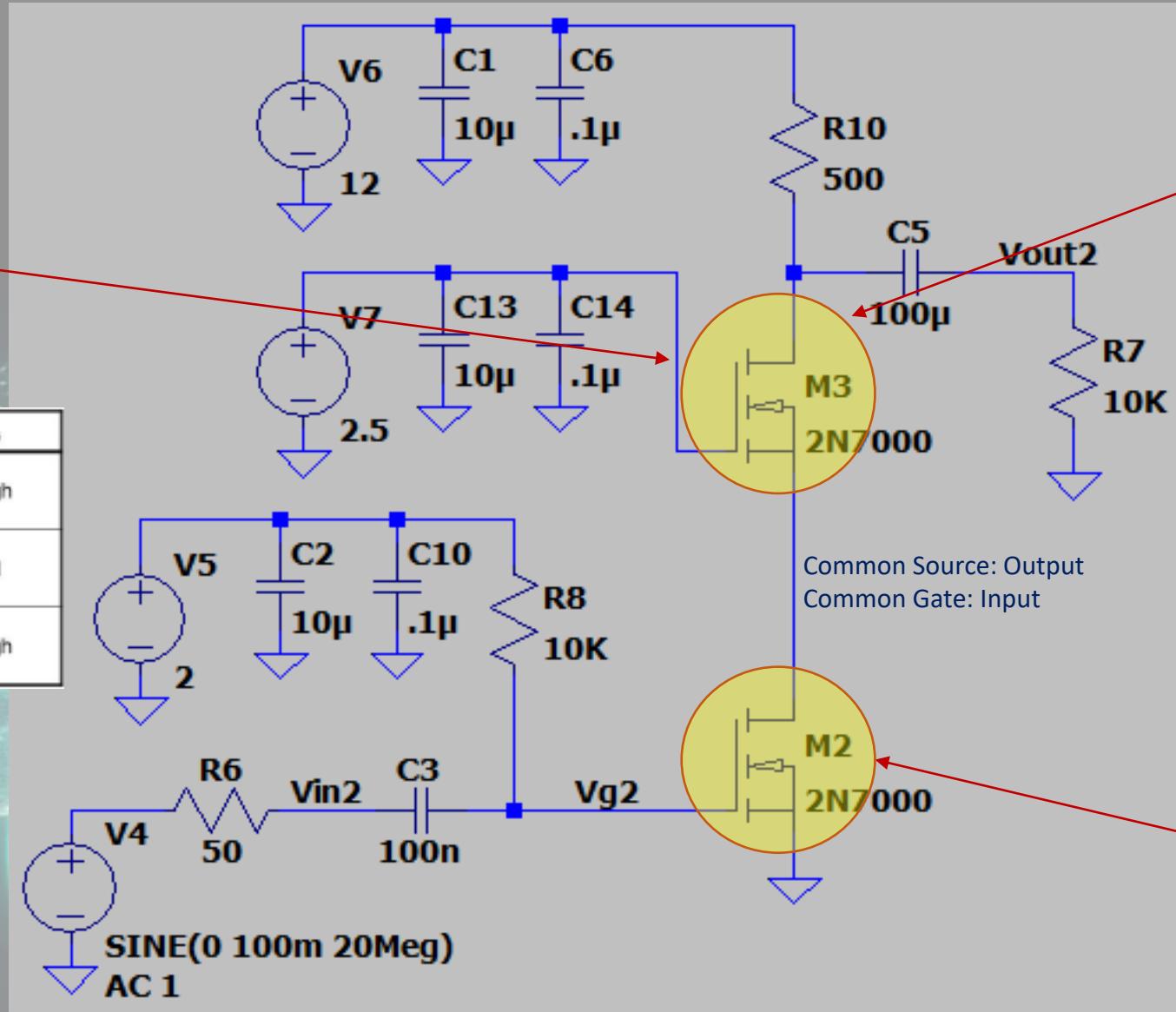


**COMMON GATE
(All Gain Here)**

**COMMON SOURCE
(Unity Gain Here)**



WARNING!


MILLER NEUTRALIZATION: CASCODE

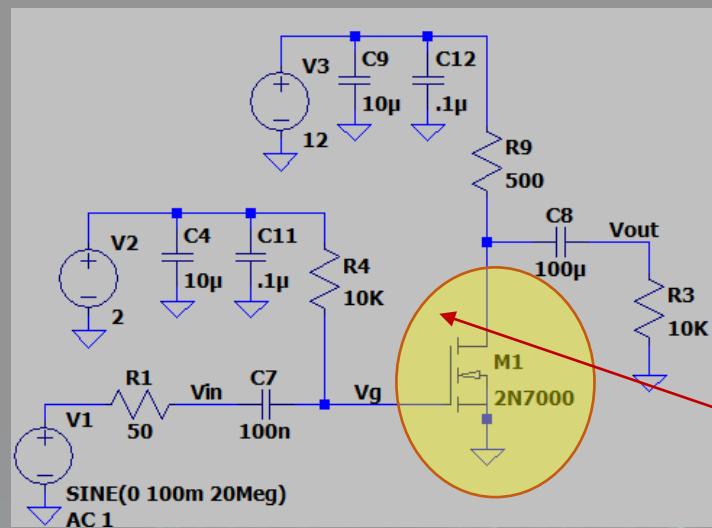

Miller Effect
Negatable

Miller Effect
Substantial


CONTROL AMP

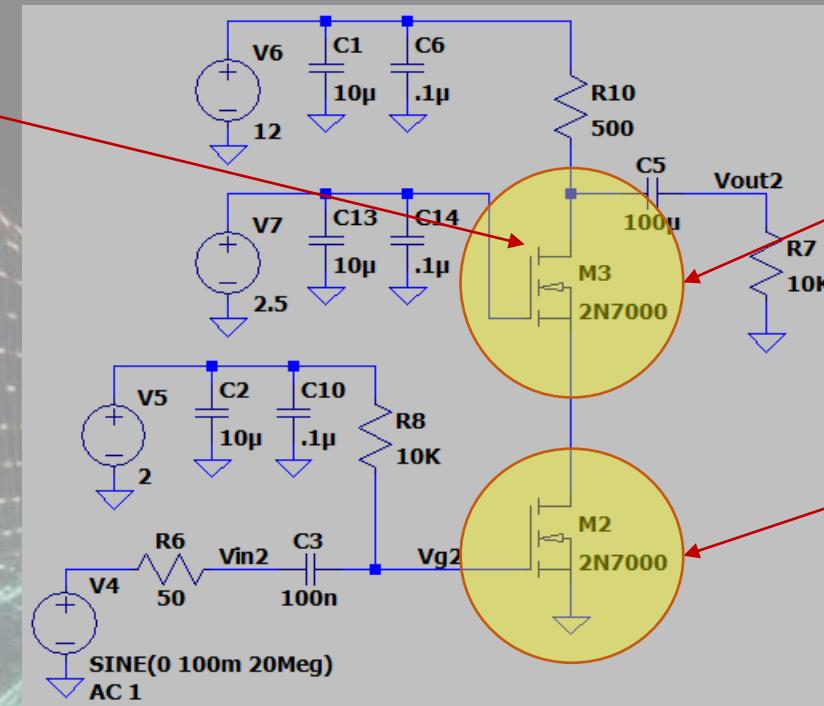

COMMON GATE
(All Gain Here)

COMMON SOURCE
(Unity Gain Here)

CASCODE AMP

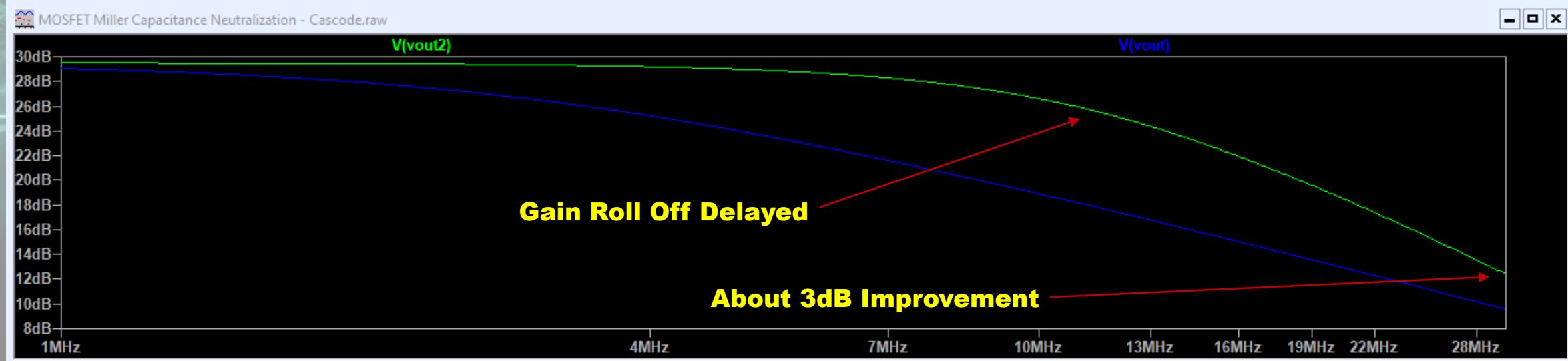

MILLER NEUTRALIZATION: HYCAS


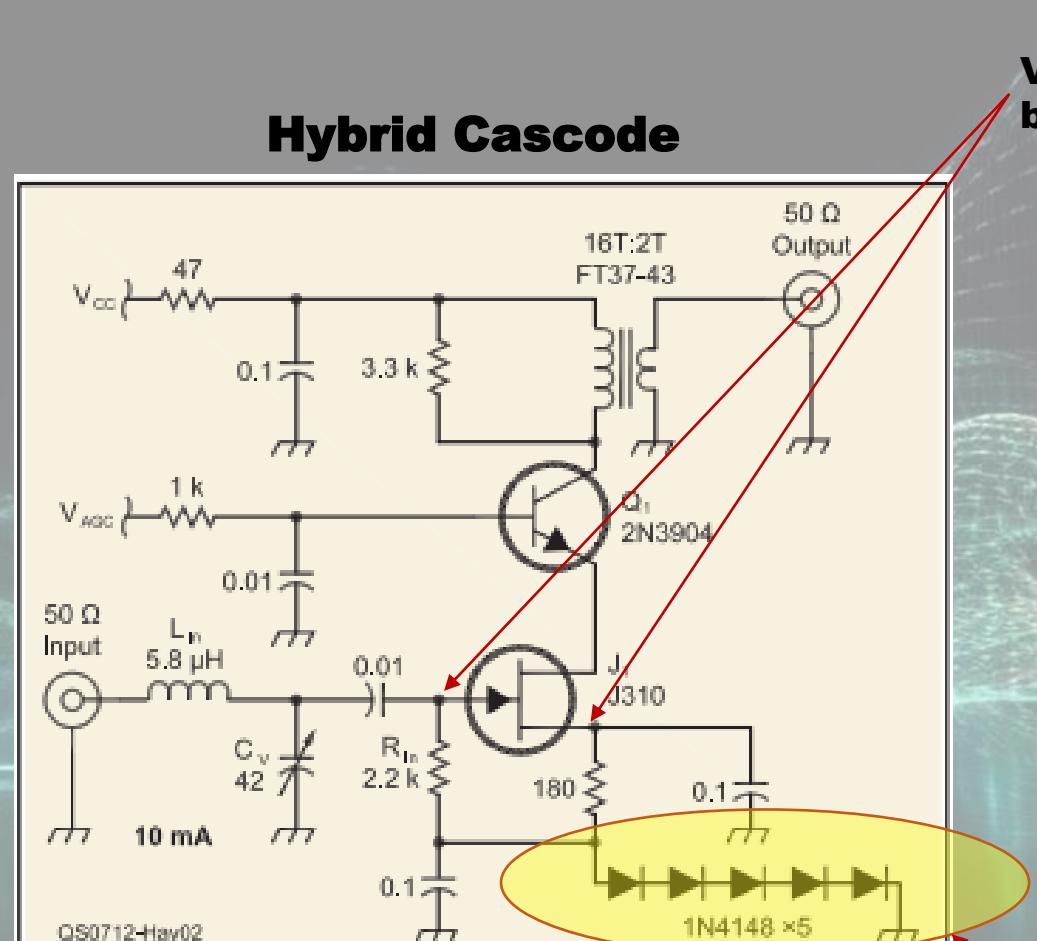



Figure 2 — Hybrid cascode. 9 MHz G_{MAX} of 23.9 dB when V_{AGC} is 8.5 V. Same tuning as Figure 1.

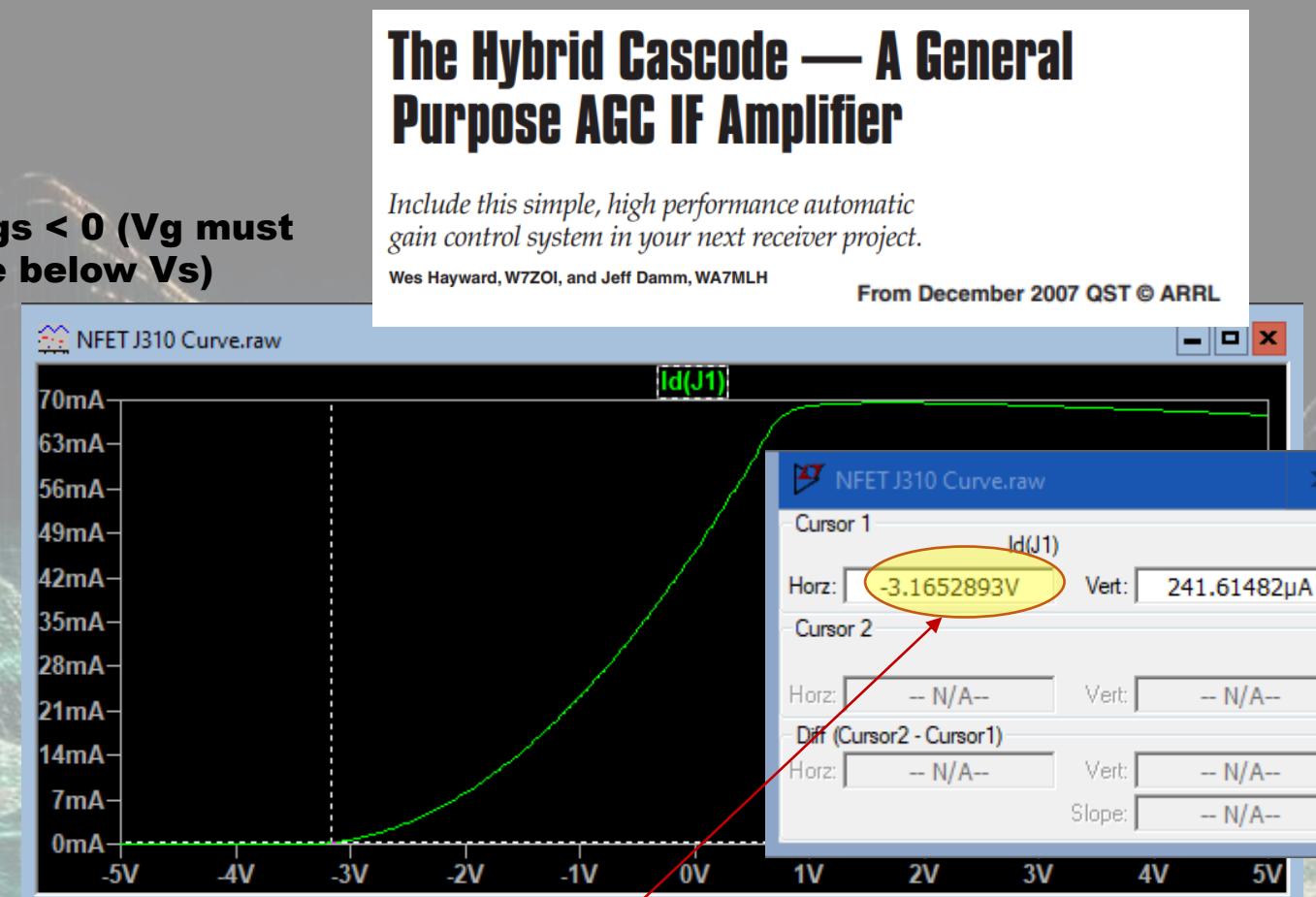


Diode drops raised Vs to a positive voltage...Say 3.5V. V_g must be 3.2V below Vs for JFET to turn on. If V_g is below 0.3V (relative to ground) JFET will turn on

NEGATIVE FEEDBACK AMPLIFIER

MILLER NEUTRALIZATION: -FEEDBACK


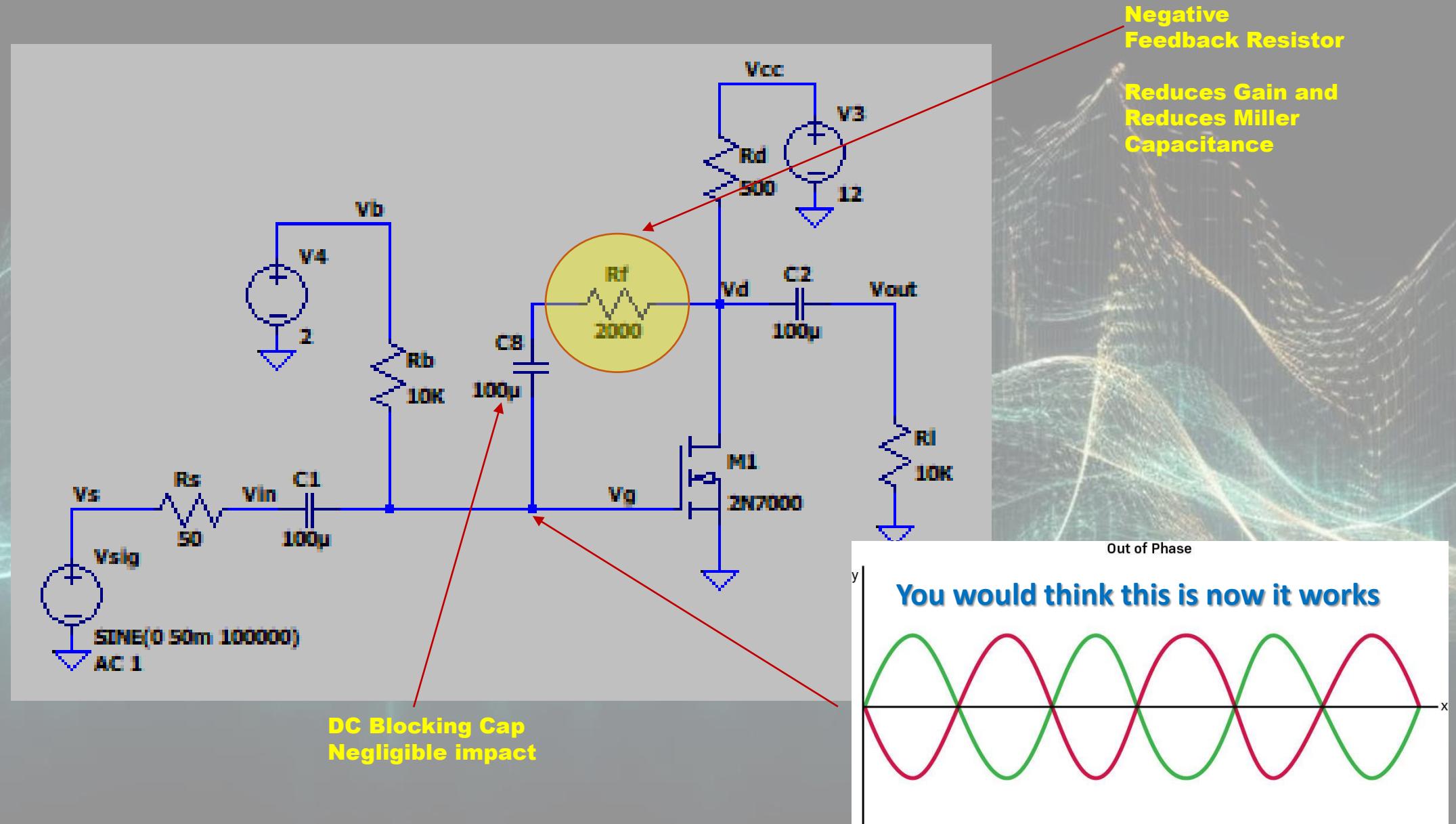


MILLER NEUTRALIZATION: -FEEDBACK

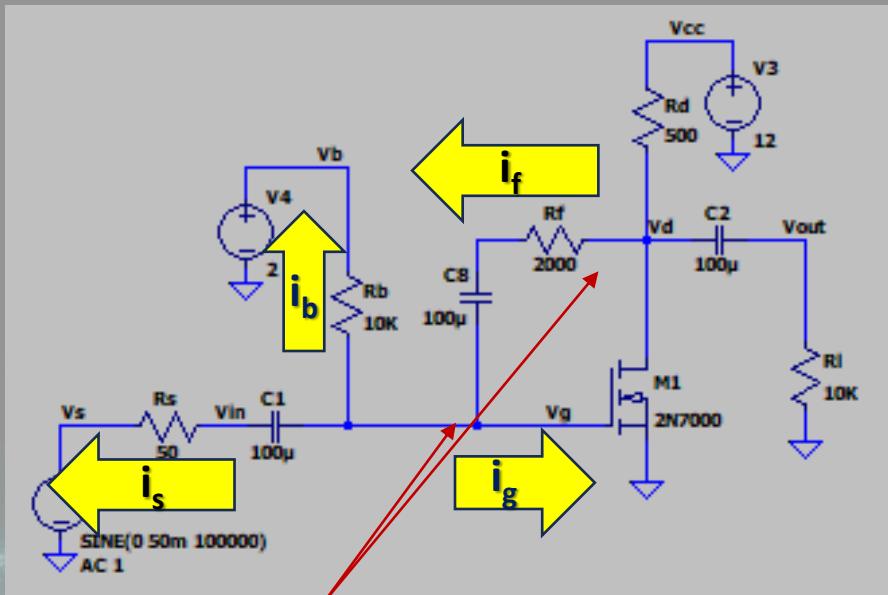

Voltage at output
is larger than
voltage at input
(there is gain)
Current flows to
lower voltage

v_g : 61mV (pp)

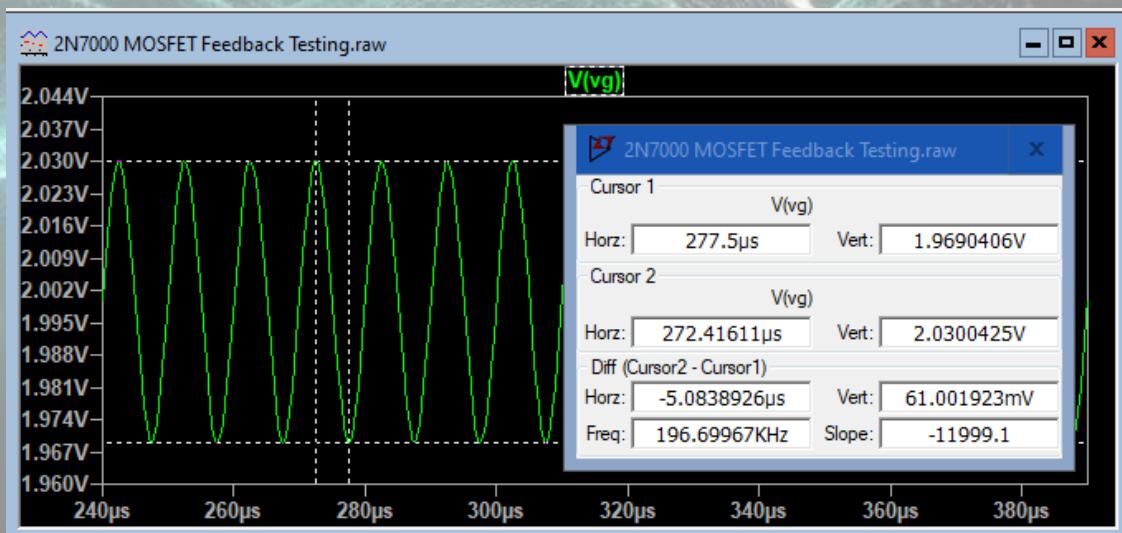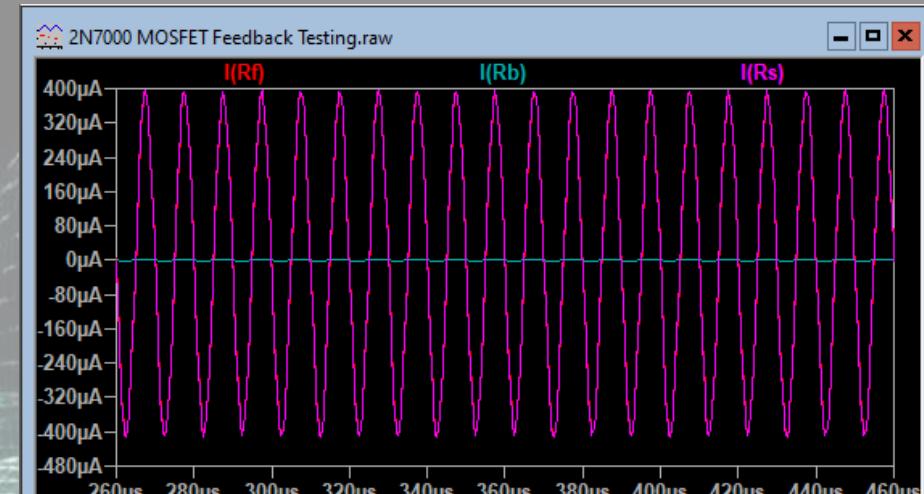

v_d : 5.5V
 v_g : 2V
 i_f : 271uA
 i_s : 273uA
 i_g : 7uA
 i_b : 2uA


This is a current feedback
amplifier.

Takes a voltage and feeds back
a current


(At least at 100 KHz)

MILLER NEUTRALIZATION: -FEEDBACK

100 KHz

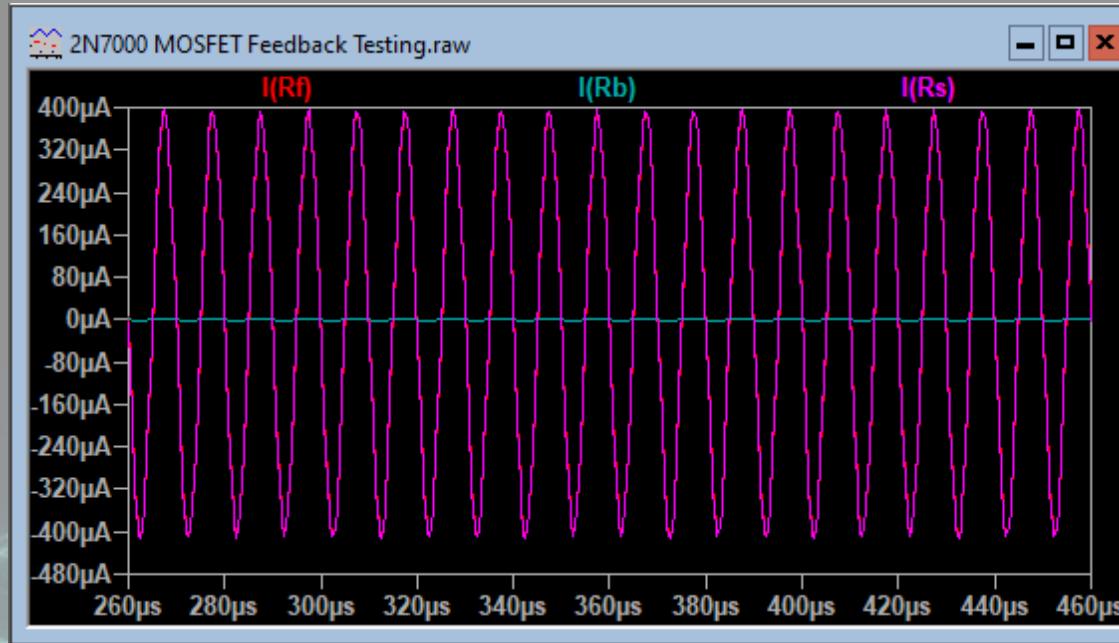



10 MHz

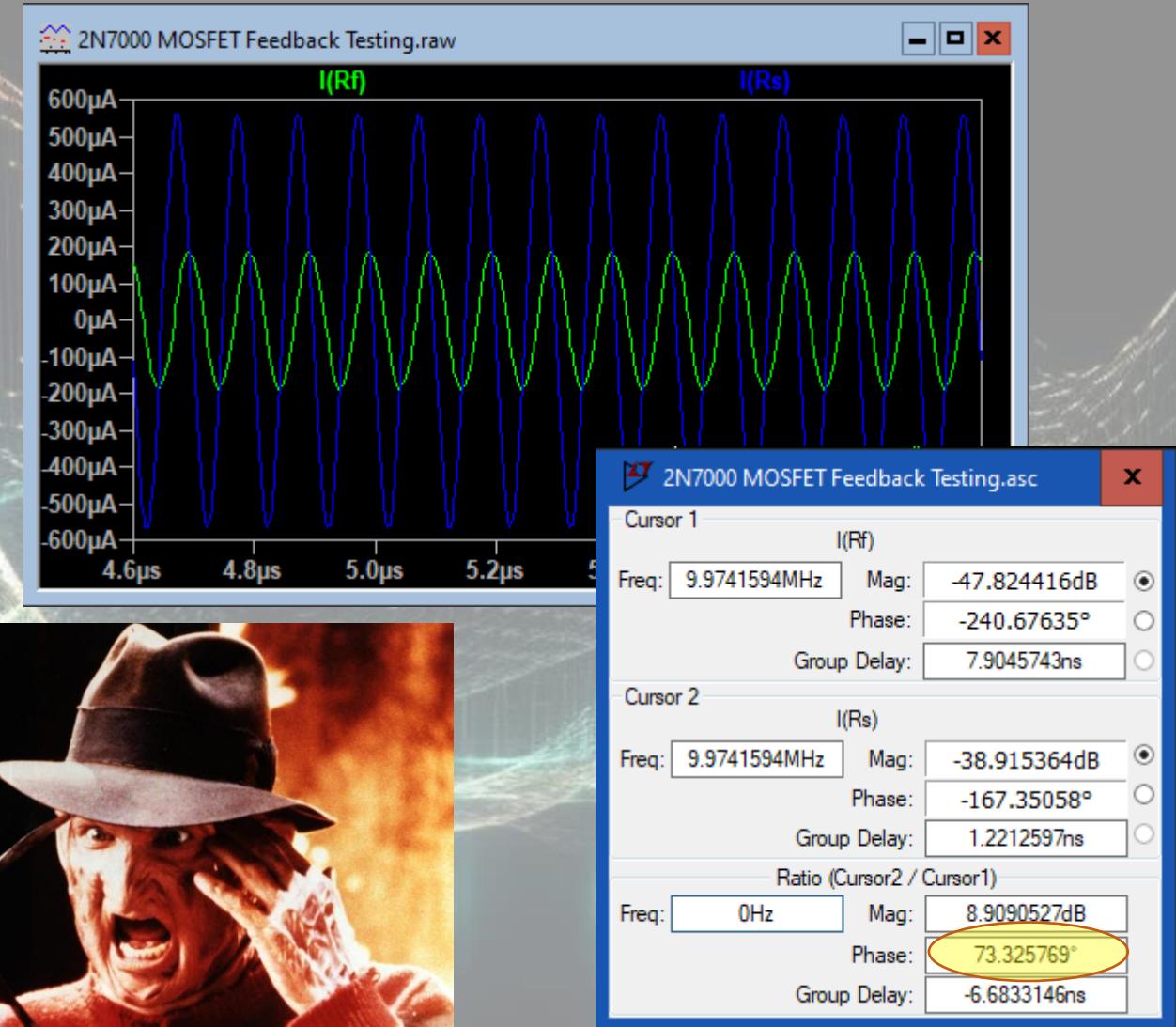

Welcome to my nightmare




MILLER NEUTRALIZATION: PHASE

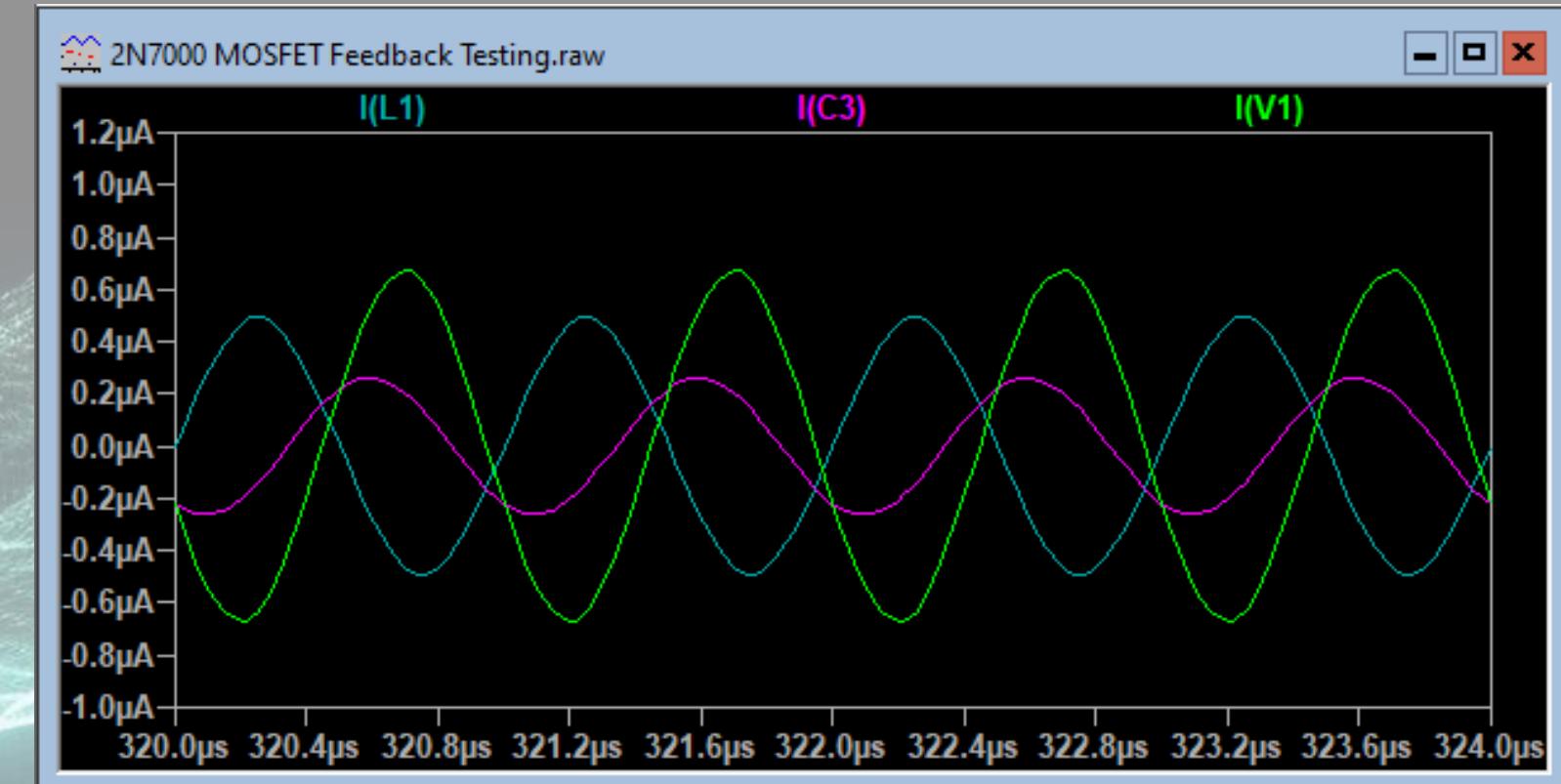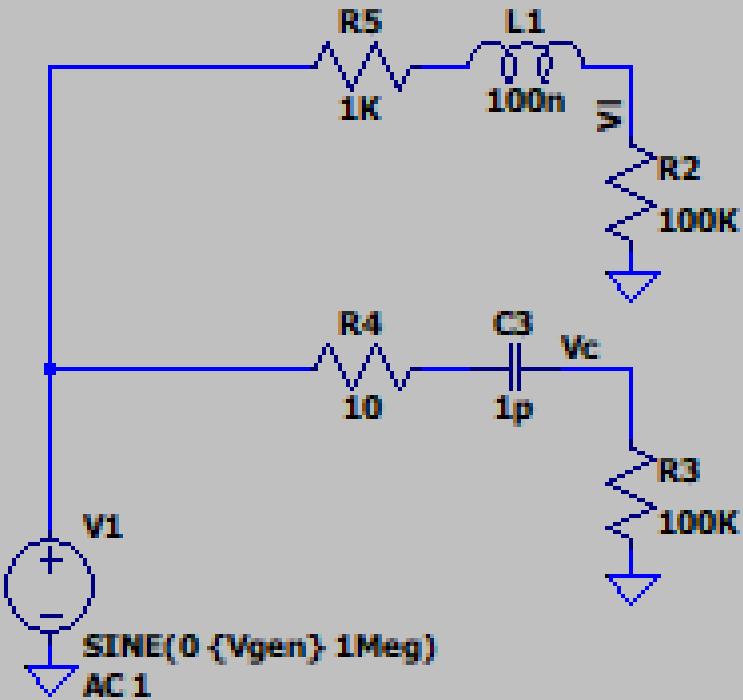


Analysis needs complex numbers that represents magnitude and phase


MILLER NEUTRALIZATION: -FEEDBACK

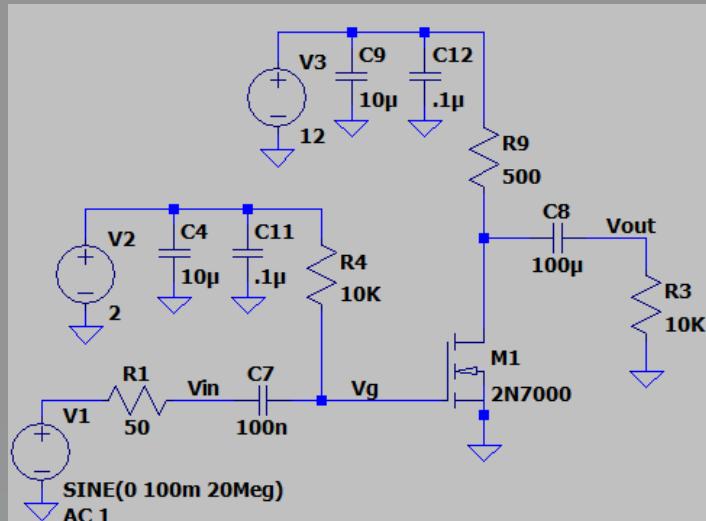


CONTROL AMP

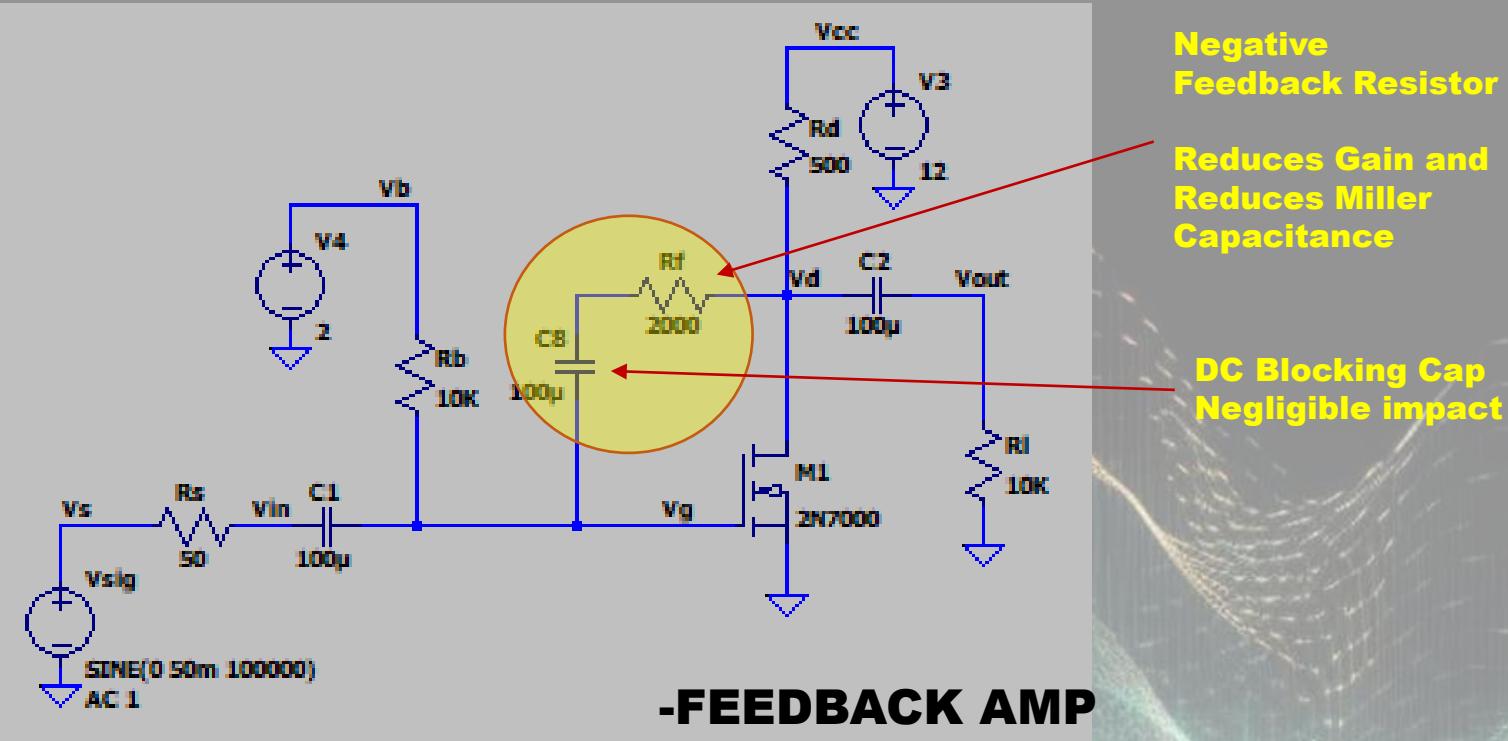

-FEEDBACK AMP

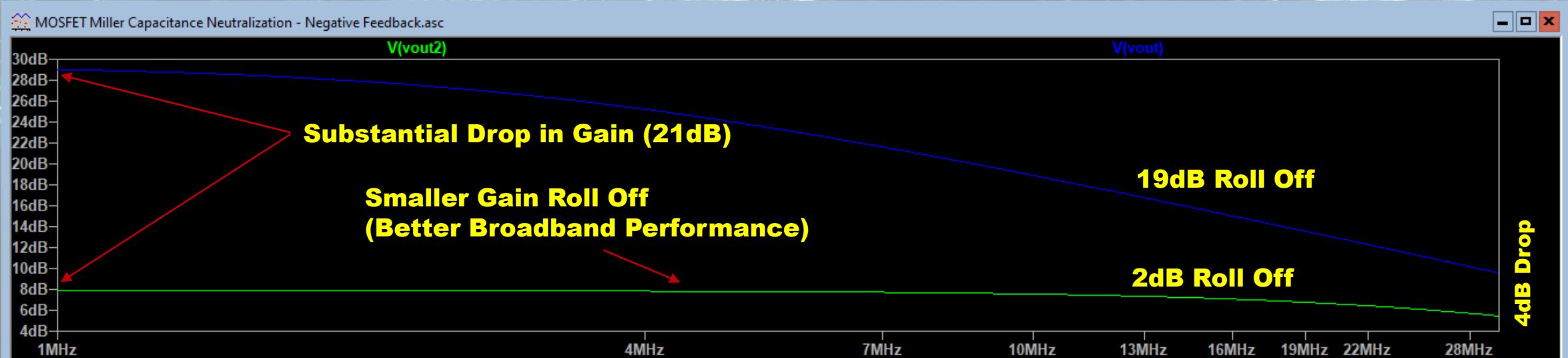

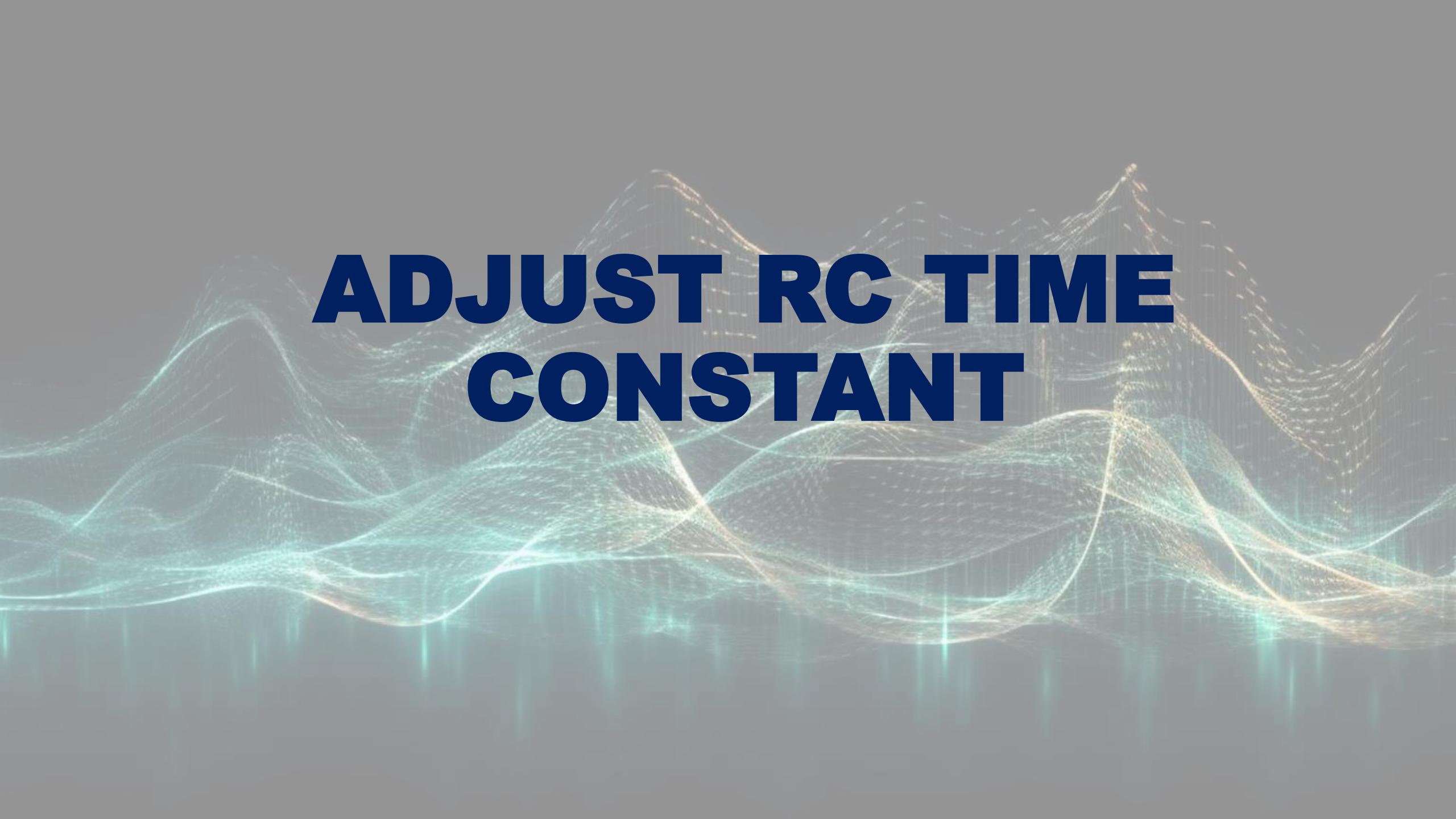
The background of the slide features a complex, abstract design composed of numerous thin, glowing lines in shades of blue, green, and yellow. These lines are arranged in a way that creates a sense of depth and motion, resembling a digital or quantum landscape. They form various wave-like patterns and intersecting lines across the entire frame.

ADJUST RC TIME CONSTANT

MILLER EFFECT: C TIME CONSTANT

Simplified AC 2N7000 Model

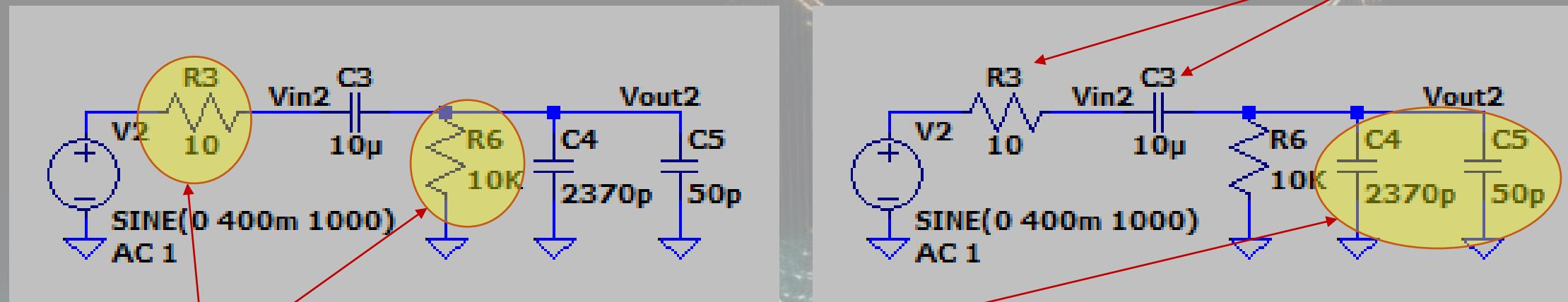**Note: C3 and R3 form
a “High Pass Filter”
with F 10 KHz**






“R” term in “RC” Time Constant


“C” term in “RC” Time Constant

Circuit (LTSpice)		Calculated	
Rbias	10000		
Rd	500		
Rs	10	Gm	0.083
RI	10000	Av	41
Rout	10000 pF	Cmiller	2370
Cin	1000000 pF	Cin	2420
Cout	1000000 pF	Rin	10
Cgd	56.1 pF		
Cgs	50 pF		
Cfb	0		
		Fc	6.714

MILLER NEUTRALIZATION: RC Constant

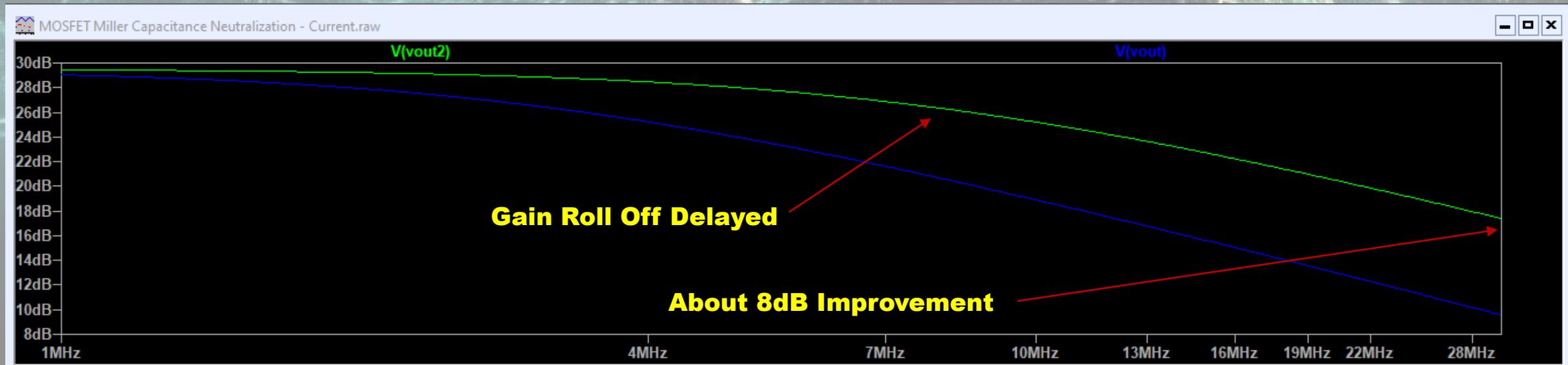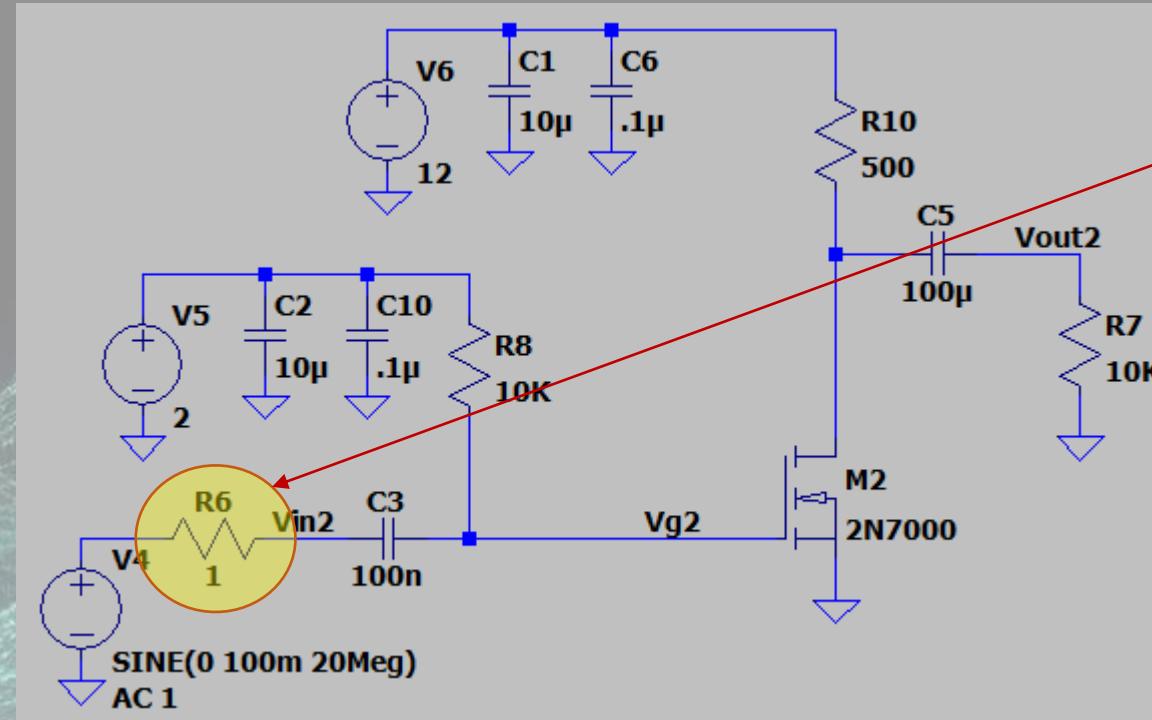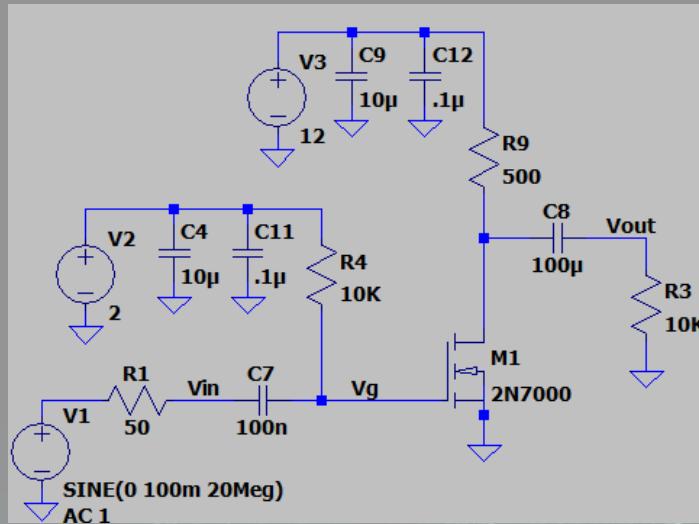


MILLER NEUTRALIZATION: RC Constant

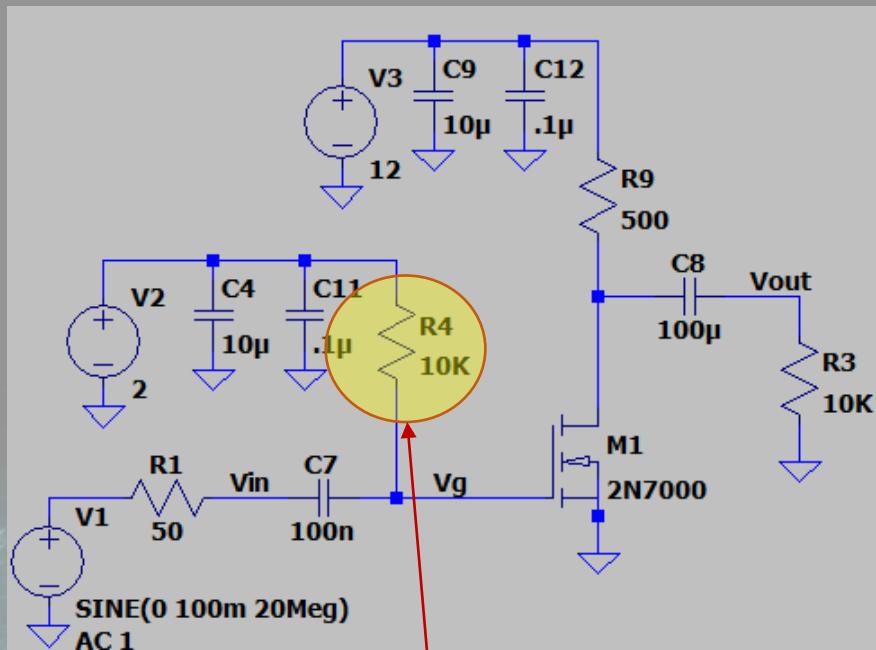

If bias resistors are same as or lower than source impedance, RC time constant is reduced


Simplified AC 2N7000 Model

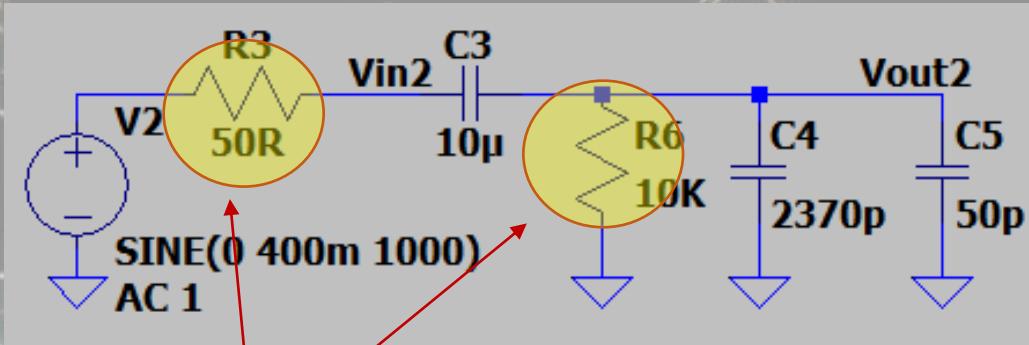

"R" term in "RC" Time Constant

Circuit (LTSpice)	Calculated
Rbias	10000
Rd	500
Rs	50
RI	10000
Rout	10000 pF
Cin	1000000 pF
Cout	1000000 pF
Cgd	56.1 pF
Cgs	50 pF
Cfb	0


MILLER EFFECT: INCREASE CURRENT

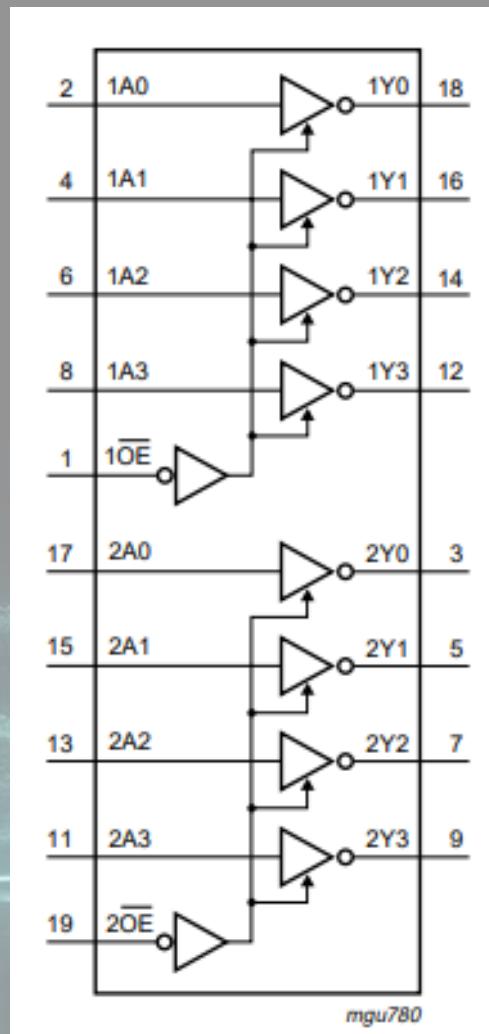

74HC240; 74HCT240

Octal buffer/line driver; 3-state; inverting

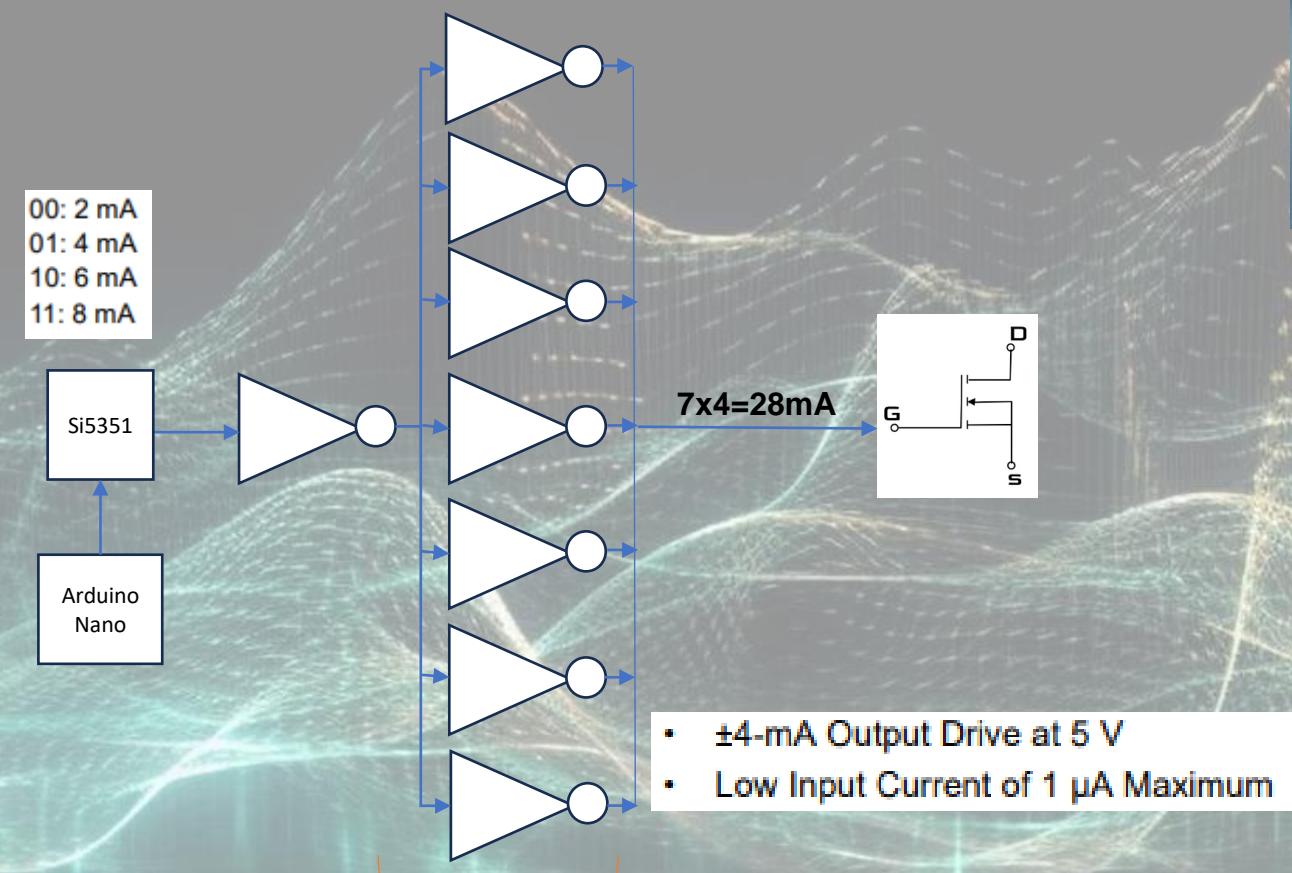The **74HC** family has High-speed CMOS circuitry, combining the speed of TTL with the very low power consumption of the




Buffer driver in parallel for greater current output.
Used for TTL Transmitters



Captain, we need more current...

The Si5351A/B/C features various output current drives ranging from 2 to 8 mA (default). It is recommended to configure the trace characteristics as shown in Figure 18 when an output drive setting of 8 mA is used.

MILLER EFFECT: INCREASE CURRENT

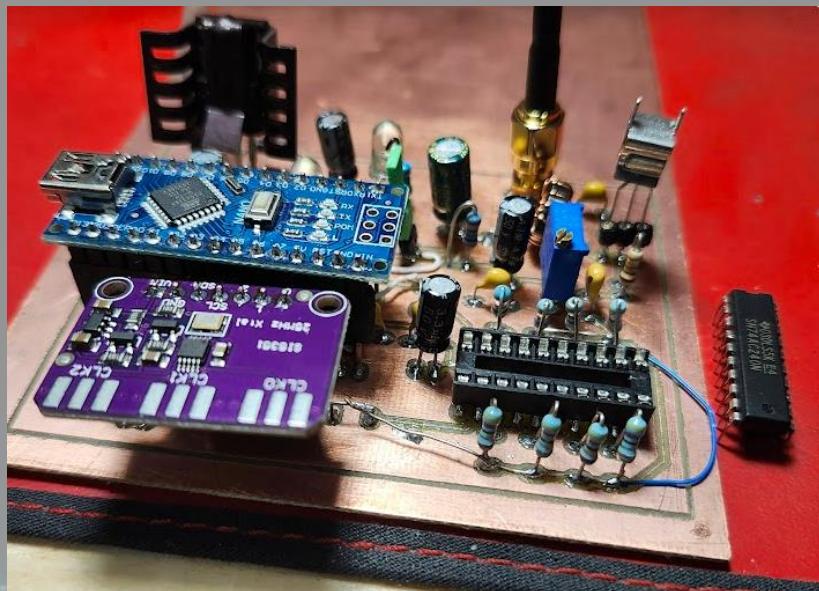


Si5351 driving BS170 MOSFET

Without 74HC240 Drivers				
Frequency (MHz)	Output (dBm)	Output (Watts)	Highest Harmonic (dBm)	Harmonic Attenuation
7	30.6	1.1	-21	-51.6
14	29.4	0.87	-21	-50.4
20	26.9	0.49	-24	-50.9
30	26.6	0.45	-24	-50.6

~8mA drive into 50R load

At least 3x
Current increase

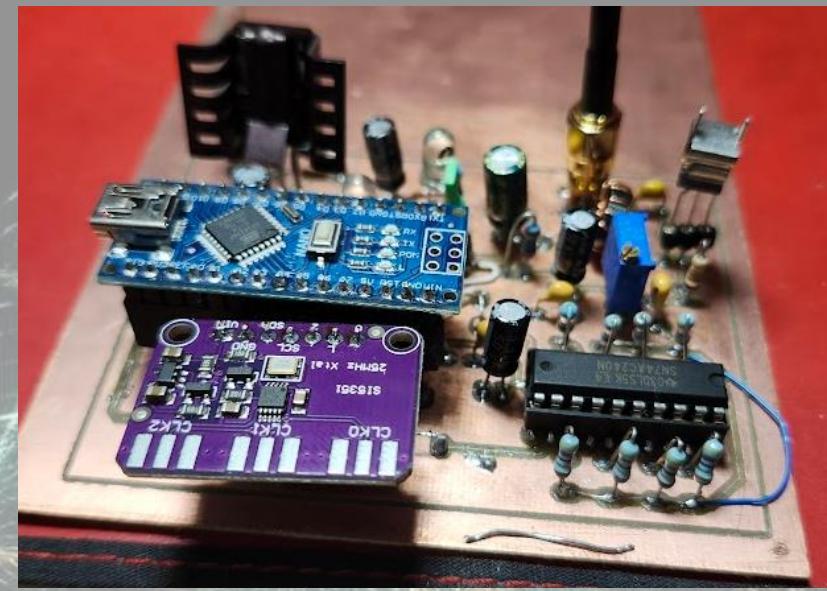Getting over 1W across HF
band with more current
from 74HC240 driver



Si5351 & 74HC140 driving BS170 MOSFET

With 74HC240 Drivers				
Frequency (MHz)	Output (dBm)	Output (Watts)	Highest Harmonic (dBm)	Harmonic Attenuation
7	32.8	1.9	-20	-52.8
14	31.8	1.5	-20	-51.8
20	31.2	1.3	-21	-52.2
30	30.5	1.1	-21	-51.5

~28mA drive into ?? load

POSITIVE FEEDBACK



MILLER NEUTRALIZATION: +FEEDBACK

A 1-V Transformer-Feedback Low-Noise Amplifier for 5-GHz Wireless LAN in 0.18- μ m CMOS

David J. Cassan, *Member, IEEE*, and John R. Long, *Member, IEEE*

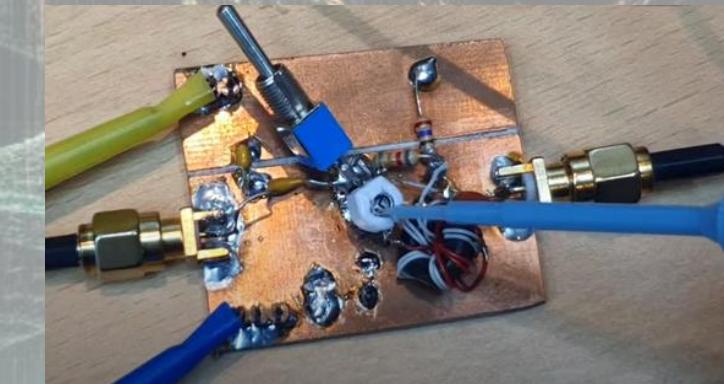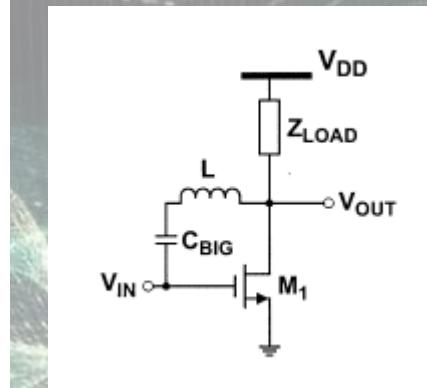III. TRANSFORMER-FEEDBACK LNA

An alternative approach to neutralization uses transformer feedback, which introduces magnetic coupling between drain and source inductors of a common-source transistor, as shown in Fig. 2(c). Feeding back a portion of the output signal via the transformer can effectively cancel the feedback from output to input through the Miller capacitance (C_{gd}) and neutralize the amplifier. The circuit parameters that define this condition are derived in Sections III-A and B.




All Electronics Channel
10.3K subscribers


https://youtu.be/czk0I3ga3LQ?si=BfAECM6Ak_sQOEQT

Transistor Miller Effect Neutralization

MILLER NEUTRALIZATION: +FEEDBACK

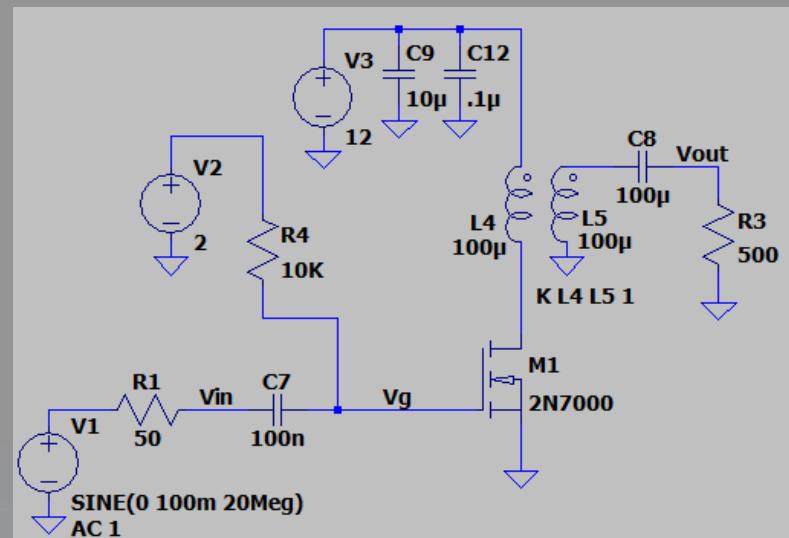

CONTROL AMP

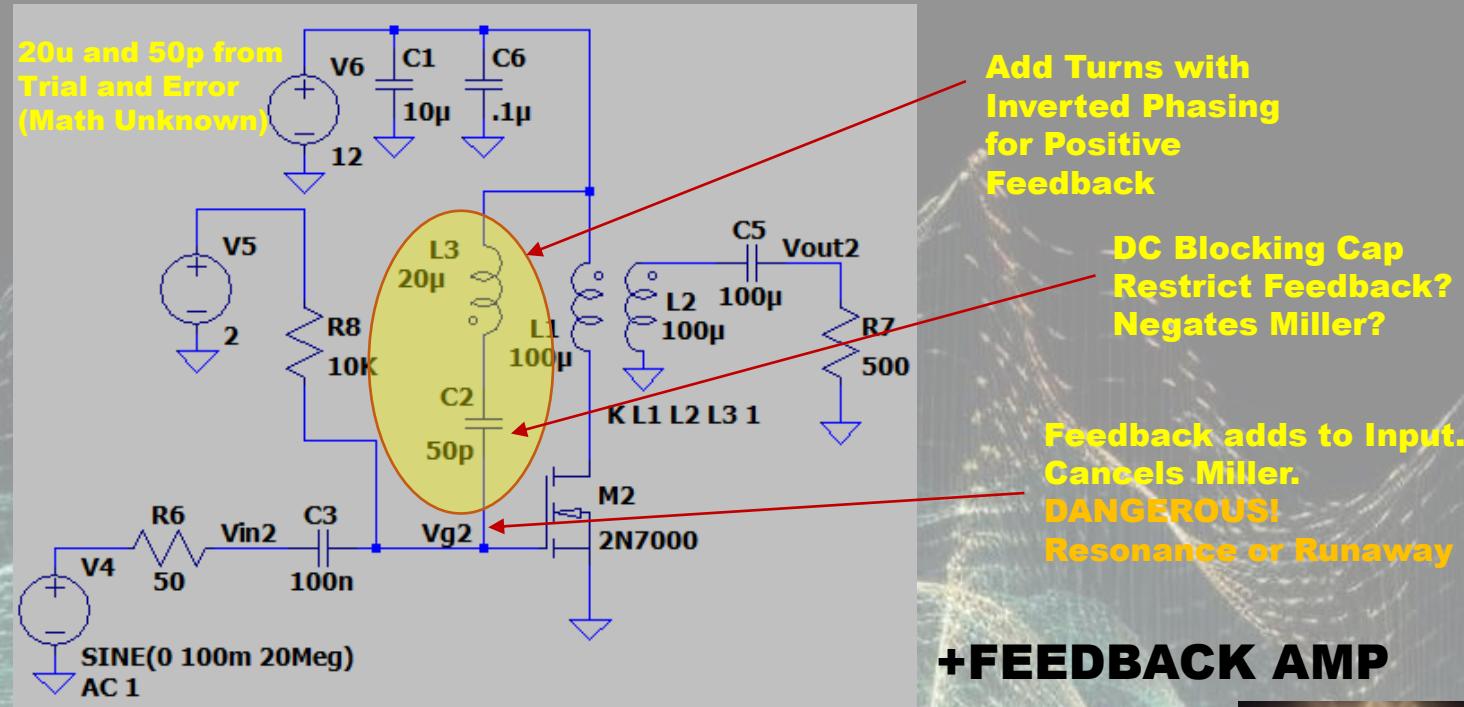

+FEEDBACK AMP

MOSFET Miller Capacitance Neutralization - Positive Feedback.asc



Don't take my word...



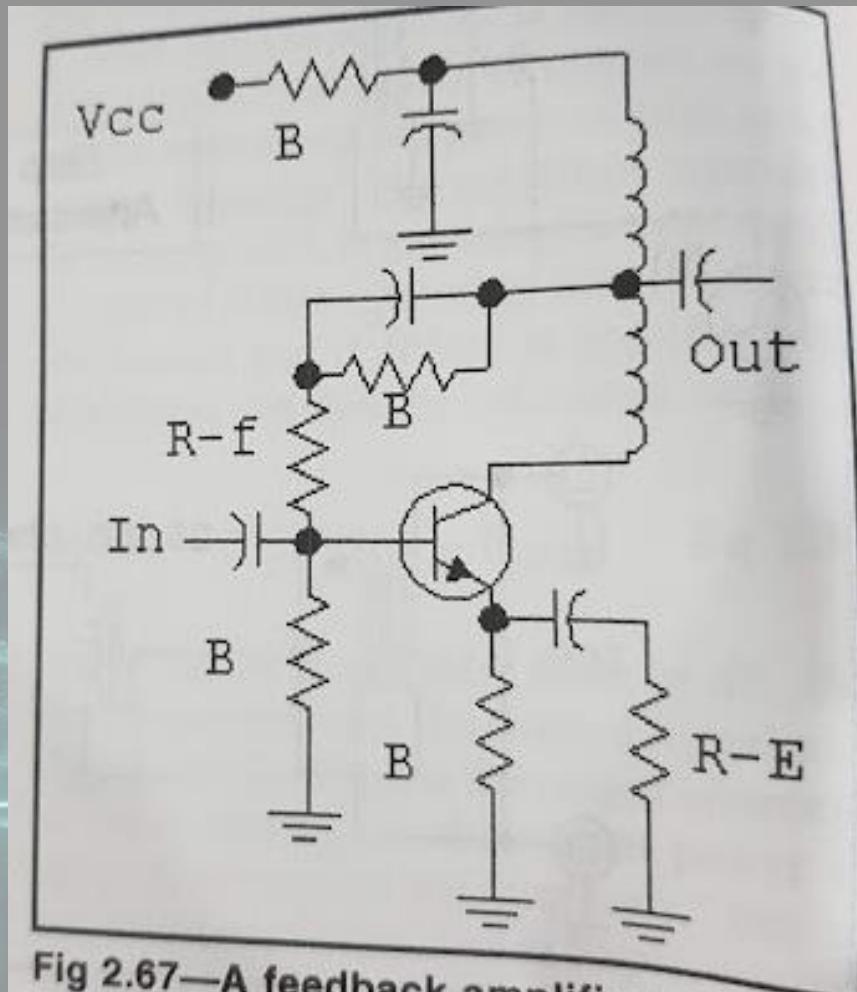
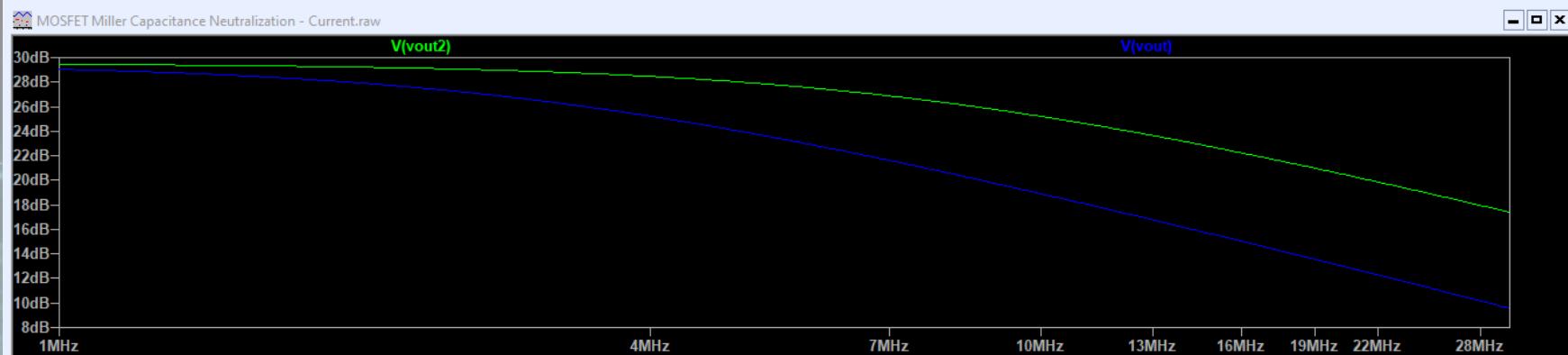


Fig 2.67—A feedback amplifier with feedback from the output transformer tap. This is common, but can produce unstable results.

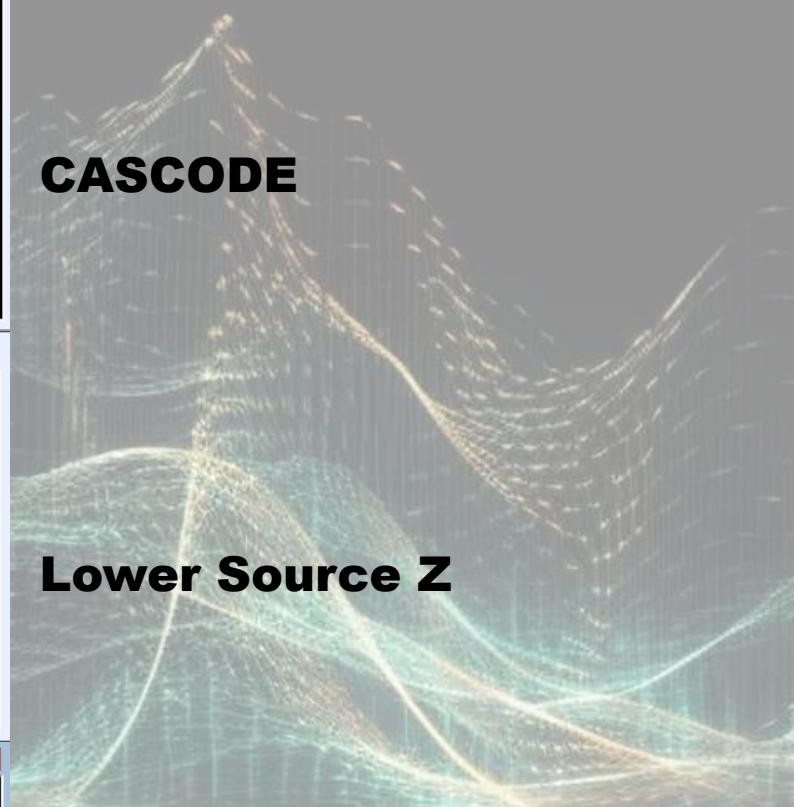


EMRFD “Feedback Amplifiers”

MILLER NEUTRALIZATION: COMPARISON

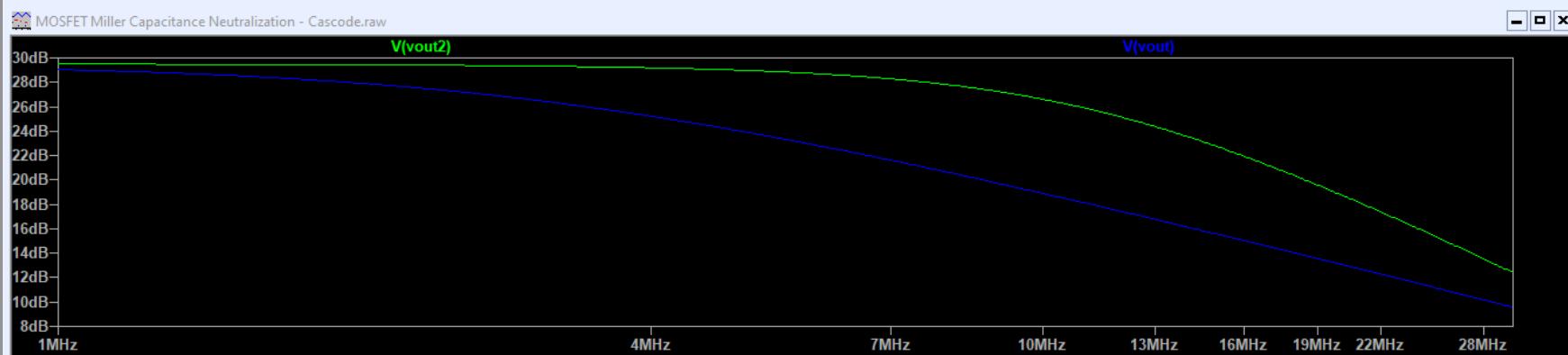

Lower Source Z

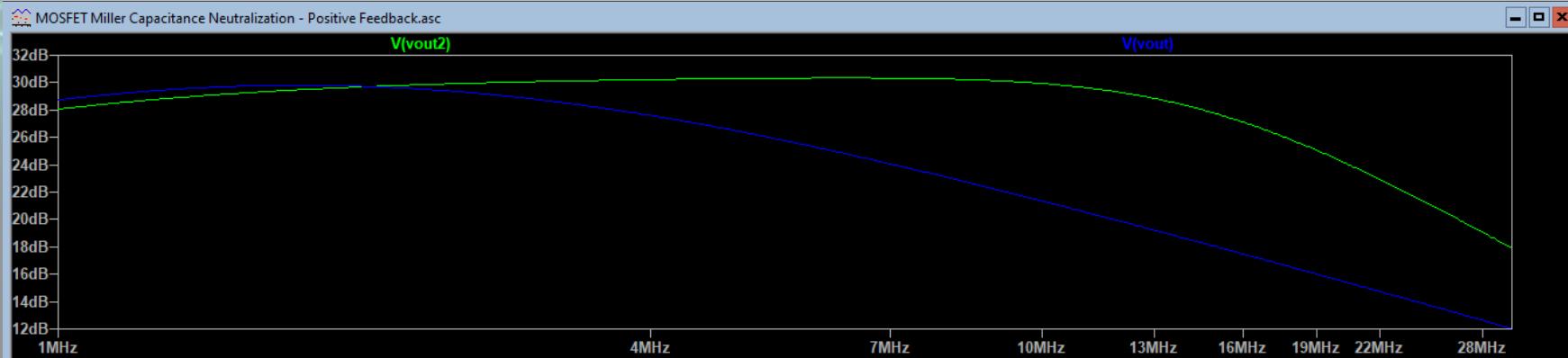

**+FEEDBACK
AMP**



CONCLUSION: RF AMPLIFIERS ARE PROBLEMATIC


1. The intrinsic capacitance of transistor limits bandwidth.

➤ Worst for high gain RF amplifiers

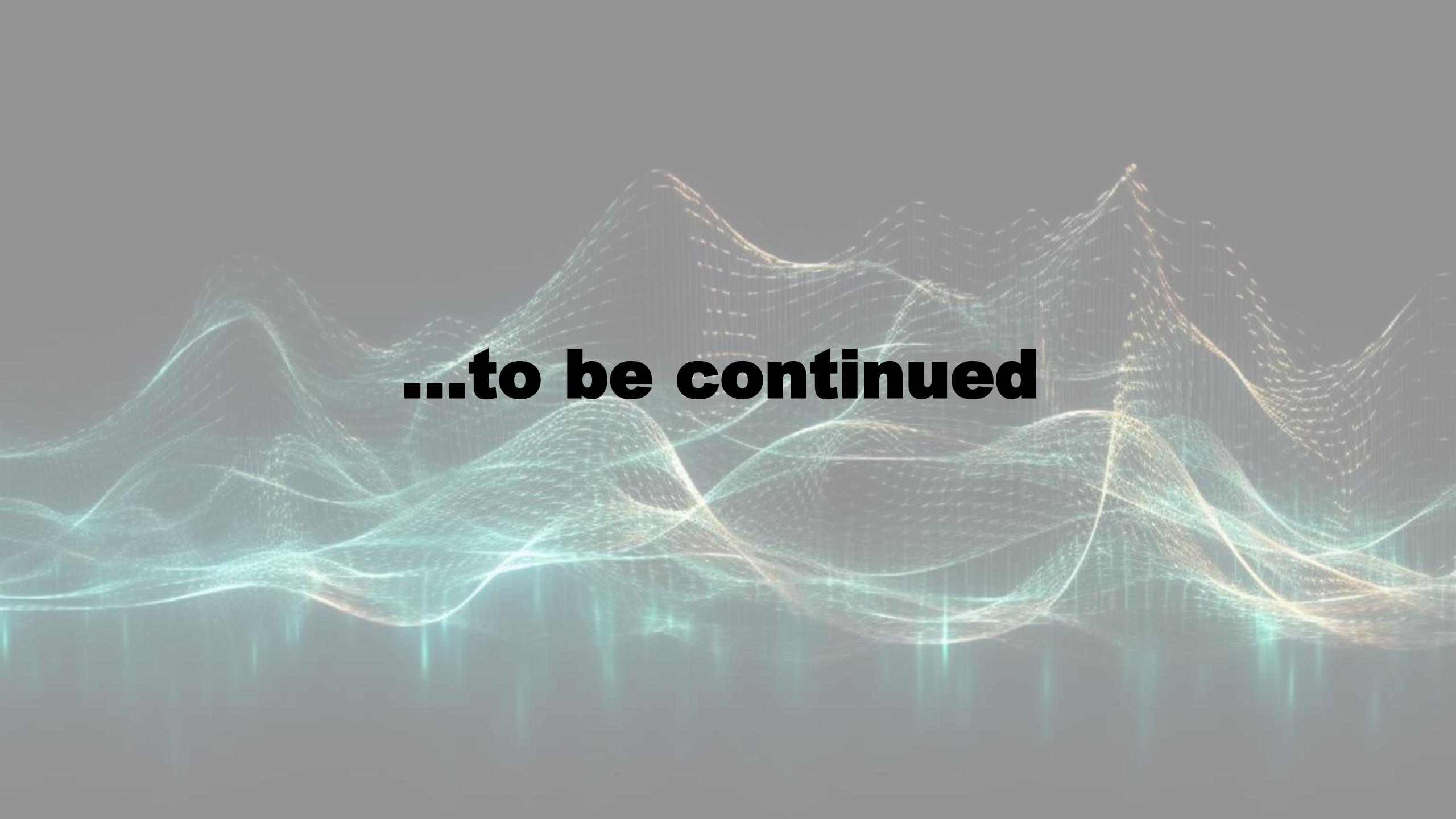2. Extend bandwidth:

- ✓ Use a RF transistor with low internal “parasitic” capacitance
- ✓ Use a non-inverting amplifier to do the heavy lifting (CASCODE/HYCAS)
- ✓ Use high current/low source impedance drive. Reduce the RC time constant.
- ✓ Reduce Gain.
 - ✓ Use negative feedback





...to be continued

RF Amplifier Negative Feedback:

How it works using math


Danger Will Robinson...



Quote Charlie Morris, ZL2CTM:

This NOT a tutorial.

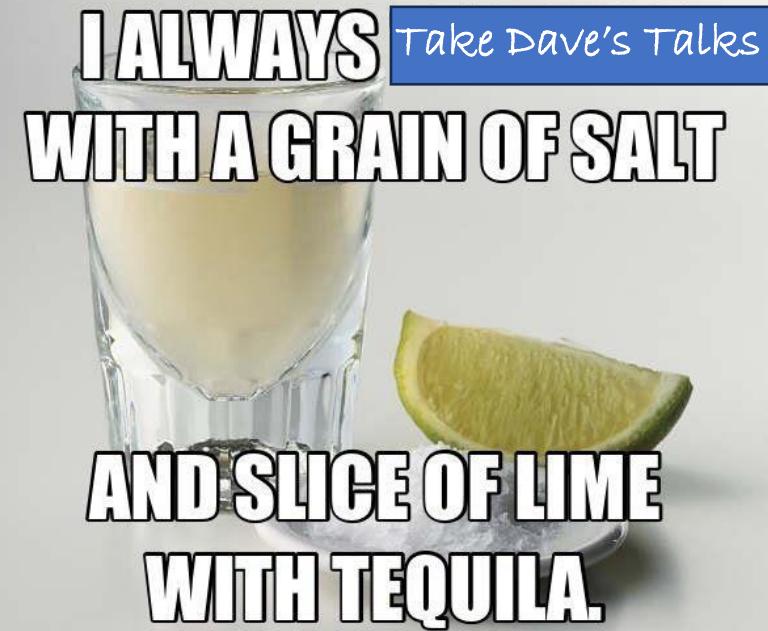It's a log of my journey. Right or wrong.





REFERENCES

#207: Basics of a Cascode Amplifier and the Miller Effect

https://youtu.be/Op_I3Ke7px0

The thumbnail shows a hand holding a blue pen over a handwritten note on lined paper. The note is titled 'BASICS OF THE CASCODE AMPLIFIER & THE MILLER EFFECT'. It includes a list of points:

- COMBINATION OF CE AMPLIFIER AND CB AMPLIFIER
- GAIN \approx CE AMPLIFIER
- USED MAINLY TO REDUCE THE MILLER EFFECT

Below the note is a schematic diagram of a cascode amplifier circuit.

w2aew 193K subscribers

Power Electronics with Dr. K 8.37K subscribers

The channel page features a background image of abstract green and white light patterns. It includes a video thumbnail for 'Power Electronics WK3_2 MOSFET Turn On Characteristics'.

EE-444/544 Power Electronics

Week 3-2

MOSFET Gate Charge and Turn-On Characteristics

Week 3-2 EE444/544 – Power Electronics

Power Electronics WK3_2 MOSFET Turn On Characteristics

<https://youtu.be/f1yt0s3gpcE>

Dr. Cristina Crespo

Semiconductor Devices: Miller's Theorem

<https://youtu.be/yM9xlbAf43Q>

The thumbnail shows a screenshot of a simulation software interface. It displays a circuit diagram with a voltage source, an operational amplifier, and two feedback paths. Below the diagram, the text 'Miller's Theorem' is visible.

Electronics with Professor Fiore 7.24K subscribers

Mateo Aboy 14.2K subscribers

The channel page features a background image of abstract green and white light patterns. It includes a video thumbnail for 'MOSFET Amplifiers'.

MOSFET Amplifiers

MOSFET High Frequency Model

4:08 / 9:45


Dr. Cristina Crespo

MOSFET High Frequency Model

<https://youtu.be/19kXfUPdF9I>

The thumbnail shows a video frame of Dr. Cristina Crespo speaking. To the right is a schematic diagram of the 'High Frequency Model of MOSFET'.

MILLER “DISTORTION”

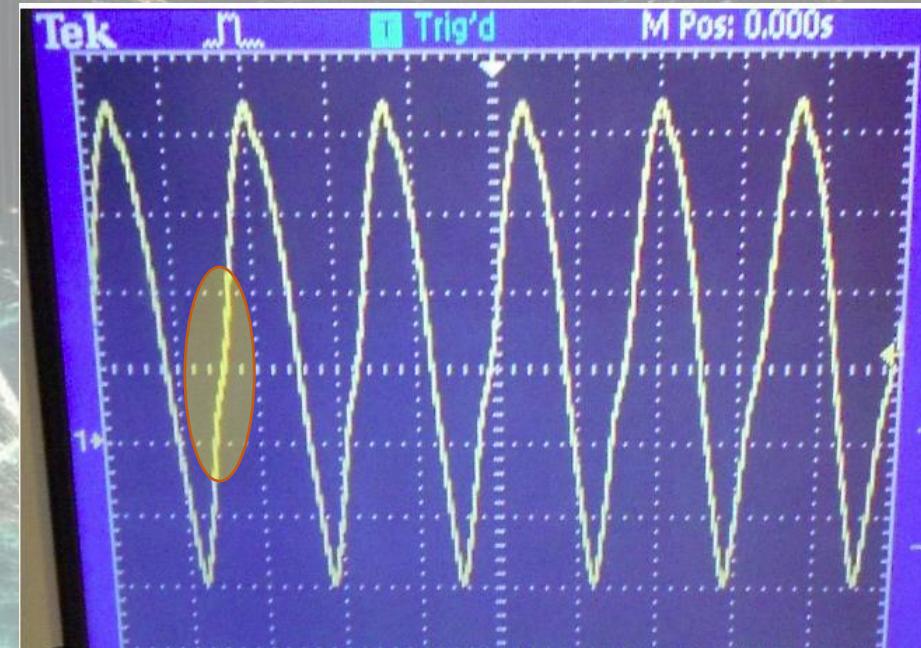

This has been exaggerated for illustration purposes

Miller Neutralization: Kick in Bag Pipes



1. **Reduce the gain hence reduce Miller Capacitance**
 - ✓ Use HYCAS or **CASCODE** amplifiers. Add common base, common gate stage
 - ✓ **Negative feedback**
2. **Increase the input drive to compensate for the low input impedance**
3. **Change the RC time constant for the internal capacitors (faster turn on)**
4. **Increase the current to reduce the charge time of the capacitors (faster turn on)**
 - ✓ Use **positive feedback**

SAME

AGENDA

1. VE3OOI Simplified Model


2. “Feedback Amplifier” Model

3. Signal Flow Charts & Mason Gain Formula



Captain, I kicked Dave in
the bag pipes..twice

GOALS

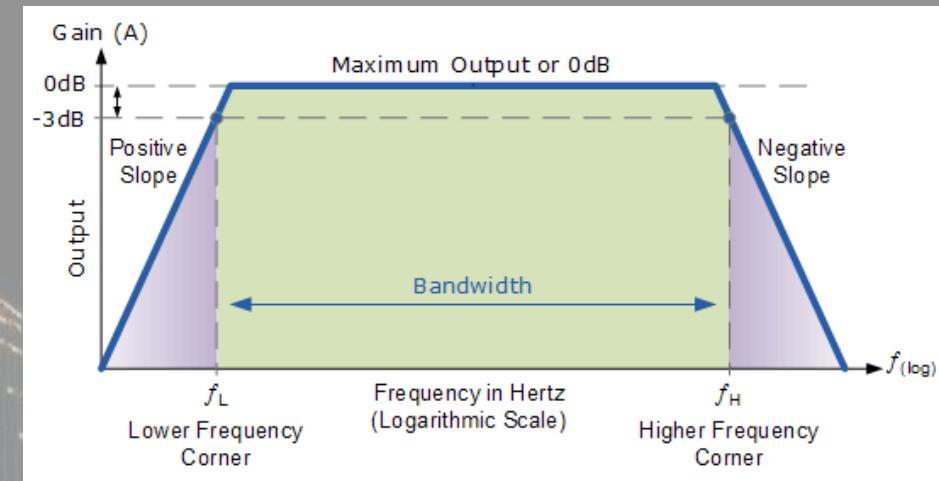

1. Need to calculate maximum gain ([Midband Analysis](#))
 - ✓ Used for Miller impedance and capacitance
2. Need to calculate amplifier cut off frequency ([3dB Frequency Analysis](#))
 - ✓ Used to ensure you have necessary performance
3. Need to calculate gain at frequency of interest ([High Frequency Analysis](#))
Notice the word "calculate"

Mid Band Analysis (Low Frequency Analysis)

3dB Frequency Analysis

Another WTF!

- I started out using 400mVp input signal for testing
- Spend weeks and weeks trying to understand why my simplified model was not working
- Learned a couple of things:
 1. If you have distortion, RMS values are skewed. Need to make sure amp is 100% linear (400mV input was overdriving MOSFET!)
 2. AC signal on a DC offset changes RMS values (painful memories of OWAEC)
 3. RMS current and voltages are scalar numbers and does not include phase. Can't add RMS signals that are out of phase.




Cannot make predictions without
Sophisticated calculations!!

Can only make rough estimates



After many months of agony....

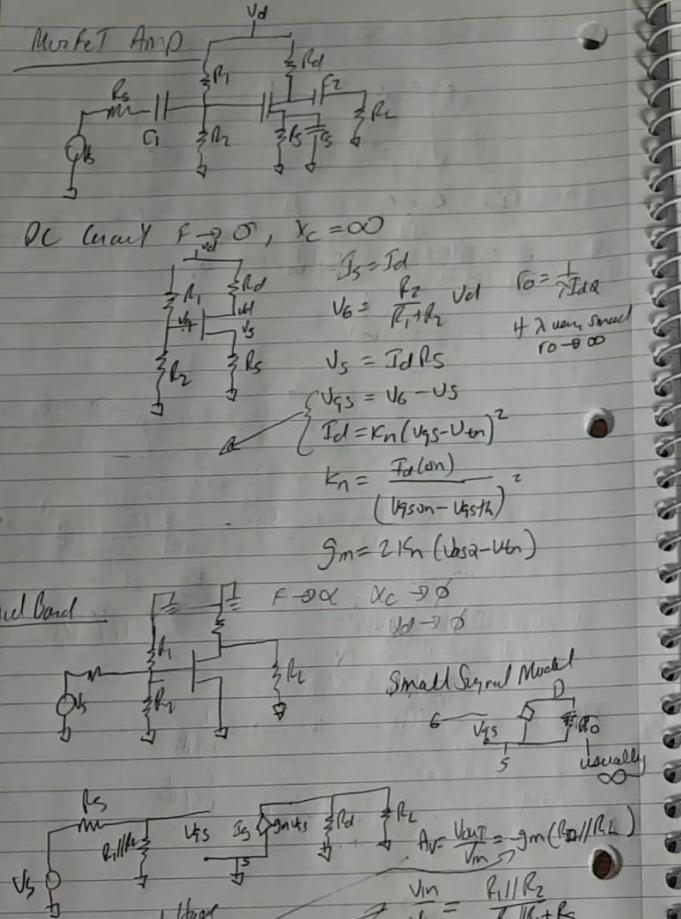

$$F_{LC_1} = \frac{L}{2\pi R_1 C_1}$$

$$F_{LC_2} = \frac{1}{2\pi R_2 C_2} \quad R_{out} = R_3 + R_L$$

$$F_{LC_S} = \frac{1}{2\pi R_S C_S} \quad R_{eq} = R_3 \parallel \frac{1}{j\omega m}$$

High Freq Model

$$C_{gd} = \frac{1}{V_{ds}}$$

$$C_{gs} = \frac{1}{V_{ds}}$$

$$C_{db} = \infty$$

$$C_{gd} \parallel C_{gs} \parallel C_{db}$$

$$C_{gd} \parallel C_{gs} \parallel C_{db} \rightarrow \infty$$

$$C_{gd} = C_{gd}(1+A), \quad C_{gs} = C_{gs}(1+A)$$

$$C_{gd} = C_{gd} + C_{gs}$$

$$C_{db} = C_{db} + C_{gd}$$

$$R_i = R_1 \parallel R_2 \parallel R_{sg}$$

$$f_{hi} = \frac{1}{2\pi R_i C_{gd}}$$

$$R_o = R_3 \parallel R_4 \parallel R_L$$

$$f_{lo} = \frac{1}{2\pi R_o C_{db}}$$



Cannot make predictions without
Sophisticated calculations!!



Can only make rough estimates

General Outcome

**How to make RF
amplifier measurements**



Simplified Model: AC MODEL

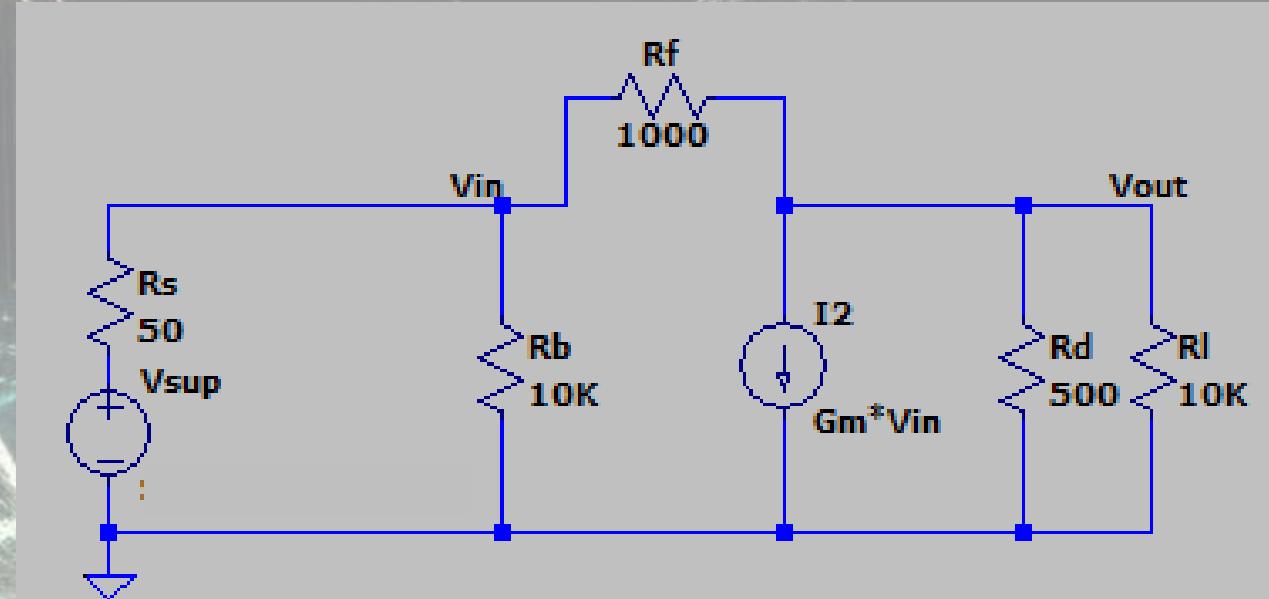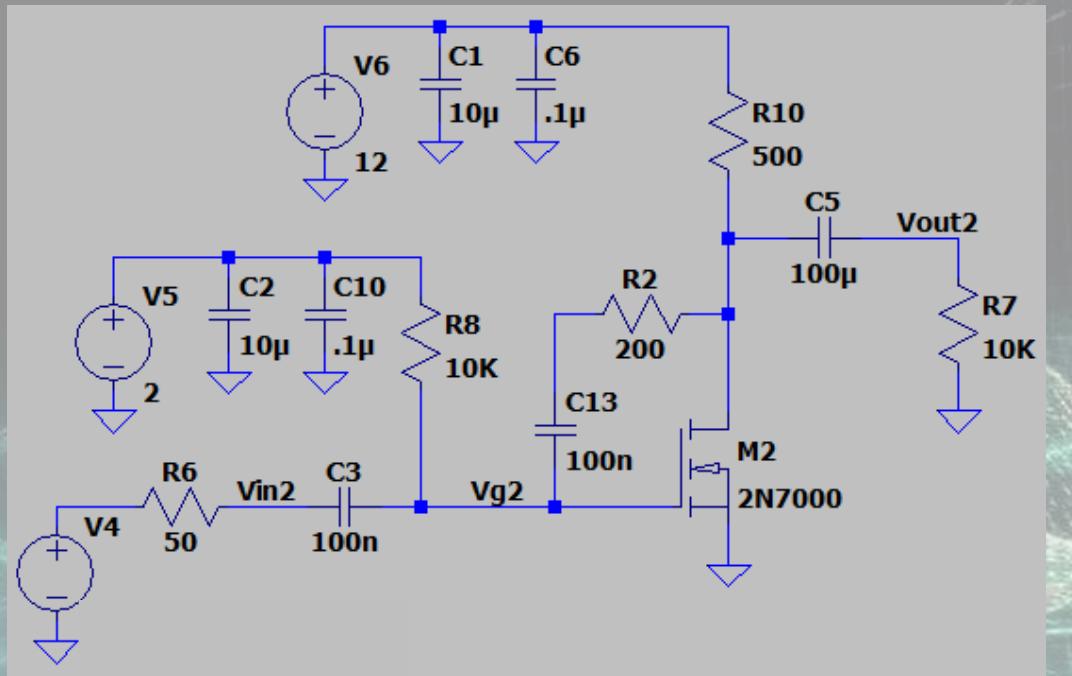


For low frequency/midband “AC” analysis:

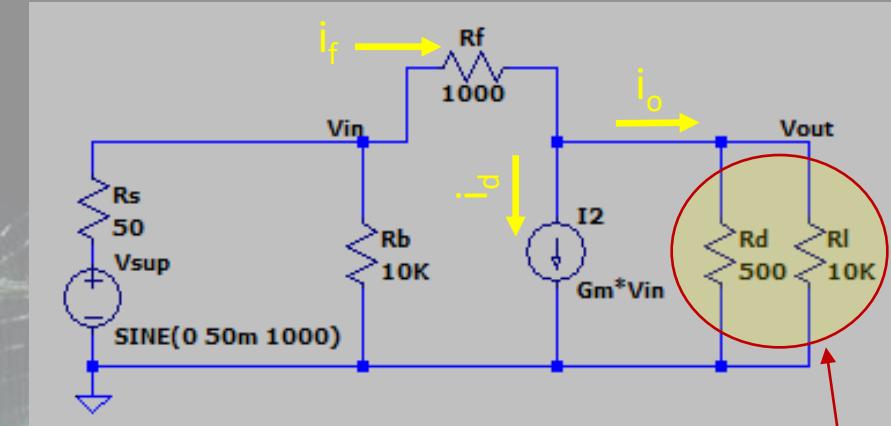1. Ground all DC sources
2. Short all DC blocking capacitors (i.e., large value caps)
3. Replace BJT or MOSFET with small signal model


Simplified Model: Gain Math

- $i_f = i_d + i_o$
- $V_g = V_{in} \text{ & } V_d = V_{out}$
 - $R_o = R_D // R_L$
 - $i_o = V_{out}/R_o$
 - $i_d = G_m V_{in}$
 - $i_f = (V_{in} - V_{out})/R_f$
- $(V_{in} - V_{out})/R_f = G_m V_{in}/R_b + V_{out}/R_o$
- $V_{in}/R_f - V_{out}/R_f = V_{out}/R_o + G_m V_{in}$
- $V_{out}(1/R_f + 1/R_o) = V_{in}/R_f - G_m V_{in} = V_{in} (1/R_f - G_m V_{in})$
- $A_v = V_{out}/V_{in} = (1/R_f - G_m V_{in}) / (1/R_f + 1/R_o)$
 - $R_f // R_o = 1 / (1/R_f + 1/R_o)$
- $A_v = (1/R_f - G_m V_{in}) R_f // R_o = (1/R_f - G_m) R_f // R_D // R_L$



$$R_o = R_D // R_L$$

Simplified Model: Gain Calculation

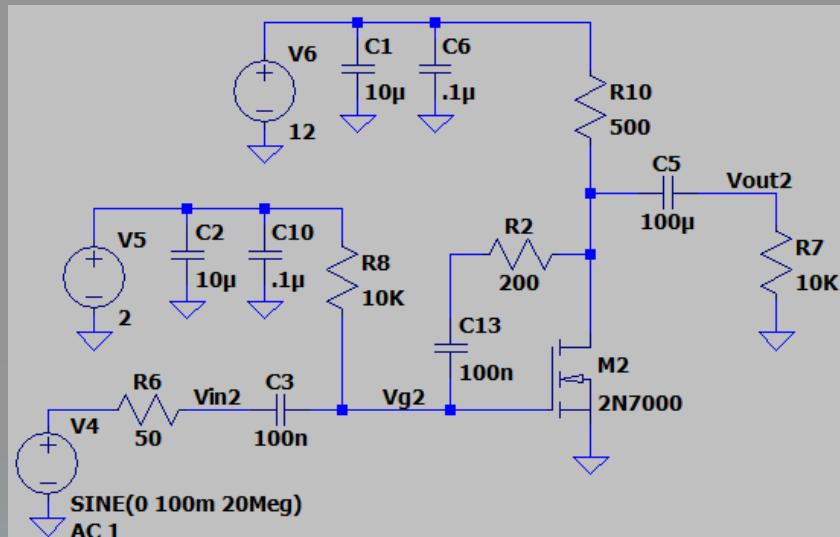

$$A_V = \left(\frac{1}{R_f} - G_m V_{in} \right) R_f // R_D // R_L$$


	RMS					
Input (Peak)	0.05	0.05	0.05	0.05	0.05	0.05
Gm	0.0663	0.0663	0.0663	0.0663	0.0663	0.0663
Cal No FB Gain	31.6	31.6	31.6	31.6	31.6	31.6
LTSpice No FB Gain	30.1	30.1	30.1	30.1	30.1	30.1
LTSpice FB Gain	4.4	8.2	14.9	18.0	20.0	24.1
FB Formula Gain	4.3	8.0	14.4	17.3	19.3	22.4
LTSpice Rin	18.6	21.8	31.4	39.4	47.4	79.1
LTSpice Rout	33.6	53.5	103.7	137.3	165.3	242.6
Rf	100	200	500	750	1000	2000
Rb	10000	10000	10000	10000	10000	10000
Rs	50	50	50	50	50	50
Ri	10000	10000	10000	10000	10000	10000
Rd	500	500	500	500	500	500
Vout	0.041889	0.0874874	0.202629	0.279525	0.343683	0.520511
Vd	3.52636	3.52786	3.53382	3.53942	3.54505	3.56435
Vg	1.99979	1.99975	1.99968	1.99964	1.99961	1.99956
Vgac	0.00953195	0.0106825	0.0135924	0.0155357	0.0171569	0.0216238
Vs	0.0353341	0.0353272	0.0353273	0.035325	0.0353223	0.0353147
Vin	0.0353341	0.0353272	0.0353273	0.035325	0.0353223	0.0353147
Vb	2	2	2	2	2	2
if	0.000513995	0.000490784	0.00043243	0.00039341	0.00036083	0.000271062
ig (Mosfet)	0.000000012	0.000000020	0.00000004	0.00000006	0.00000007	0.000000102
id (Mosfet)	0.012953400	0.012956300	0.01296650	0.01297580	0.01298500	0.013018800
is (Mosfet)	0.012953400	0.012956300	0.01296650	0.01297580	0.01298500	0.013018800
ib	0.000000953	0.000001068	0.00000136	0.00000155	0.00000172	0.000002162
is	0.000514948	0.000491853	0.00043379	0.00039496	0.00036255	0.000273224
id	0.012948000	0.012947600	0.01295030	0.01295530	0.01296150	0.012989500
il	0.000004189	0.000008749	0.00002026	0.00002795	0.00003437	0.000052051
Xc Miller at 1KHz	88609					

Av (1/Rf-gm)Rf//Ro	-4.7	-8.6	-15.7	-18.9	-21.1	-25.3
LTSpice Gain	4.4	8.2	14.9	18.0	20.0	24.1





Simplified Model: Zin Math – 1st Way

- $i_s = i_b + i_d + i_o$
 - ✓ $V_g = V_{in}$ & $V_d = V_{out}$
 - ✓ $i_b = V_{in}/R_b$
 - ✓ $i_o = V_{out}/R_o$
 - ✓ $i_d = G_m V_{in}$
- $i_s = V_{in}/R_b + G_m V_{in} + V_{out}/R_o$
- $V_{out}/R_o = i_s - V_{in}/R_b - G_m V_{in}$
- $V_{out} = i_s R_o - V_{in}/R_b R_o - G_m V_{in} R_o$
 - ✓ $i_f = (V_{in} - V_{out})/R_f$
 - ✓ $i_f = i_s - i_b = i_s - V_{in}/R_b$
 - ✓ $(V_{in} - V_{out}) = R_f i_s - R_f V_{in}/R_b$
 - ✓ $V_{out} = V_{in} - R_f i_s + R_f V_{in}/R_b$
- $V_{in} - R_f i_s + R_f V_{in}/R_b = i_s R_o - V_{in}/R_b R_o - G_m V_{in} R_o$
- $R_f i_s + i_s R_o = R_f V_{in}/R_b + V_{in}/R_b R_o + G_m V_{in} R_o$
- $i_s (R_f + R_o) = V_{in} (R_f/R_b + 1/R_b R_o + G_m R_o)$
- $Z_{in} = V_{in}/i_s = (R_f + R_o) / (R_f/R_b + 1/R_b R_o + G_m R_o) = R_b (R_f + R_o) / (R_f + R_o + G_m R_o R_b)$

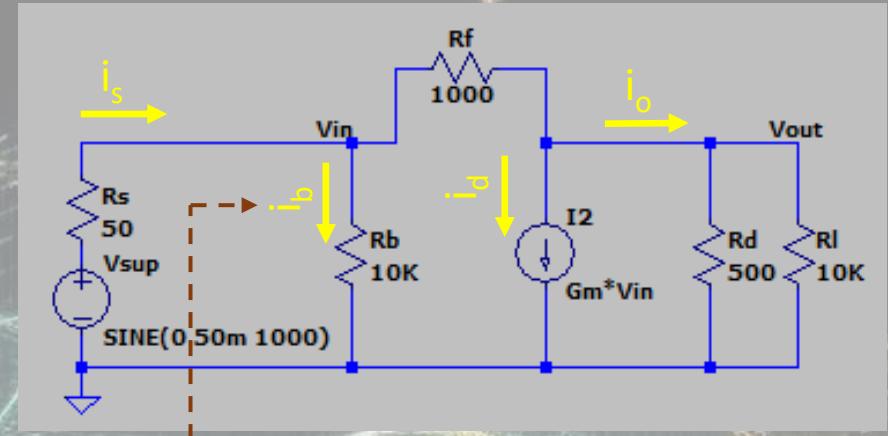


Simplified Model: Zin Math – 2nd Way

- $i_i = i_d + i_o$
 - ✓ $V_g = V_{in} \& V_d = V_{out} \& i_f = i_i$
 - ✓ $i_o = V_{out}/R_o$
 - ✓ $i_d = G_m V_{in}$
- $i_f = i_i = G_m V_{in} + V_{out}/R_o$
- $V_{out}/R_o = i_i - G_m V_{in}$
- $V_{out} = i_i R_o - G_m V_{in} R_o$
 - ✓ $i_i = i_f = (V_{in} - V_{out})/R_f$
 - ✓ $V_{out} = V_{in} - i_i R_f$
- $V_{in} - i_i R_f = i_i R_o - G_m V_{in} R_o$
- $V_{in} + G_m V_{in} R_o = i_i R_f + i_i R_o$
- $V_{in} (1 + G_m R_o) = i_i (R_f + R_o)$
- $Z_{in} = V_{in}/i_s = (R_f + R_o) / (1 + G_m R_o)$

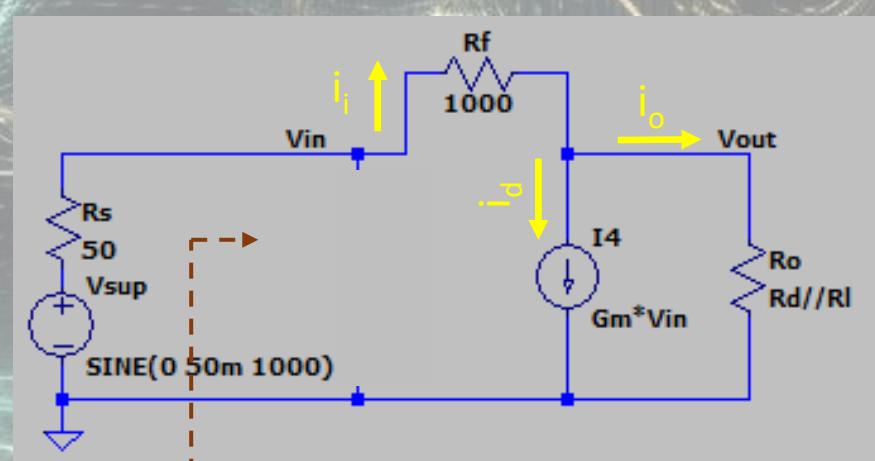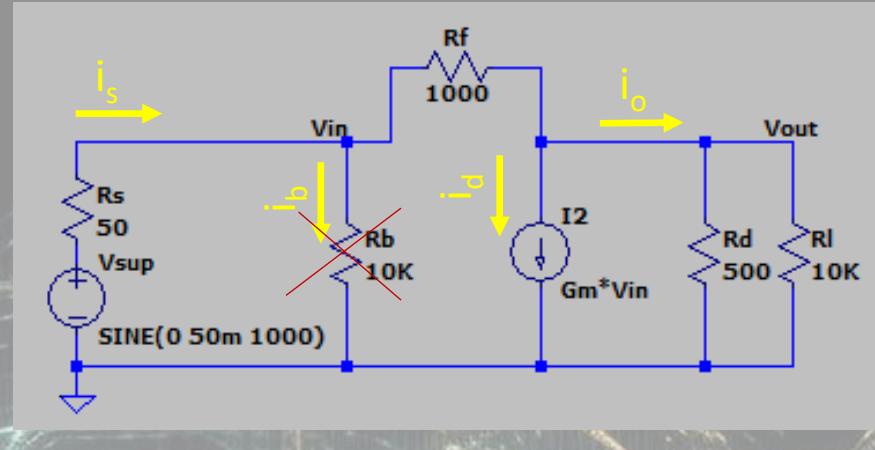

Z_{in}

Simplified Model: Zin Calculation

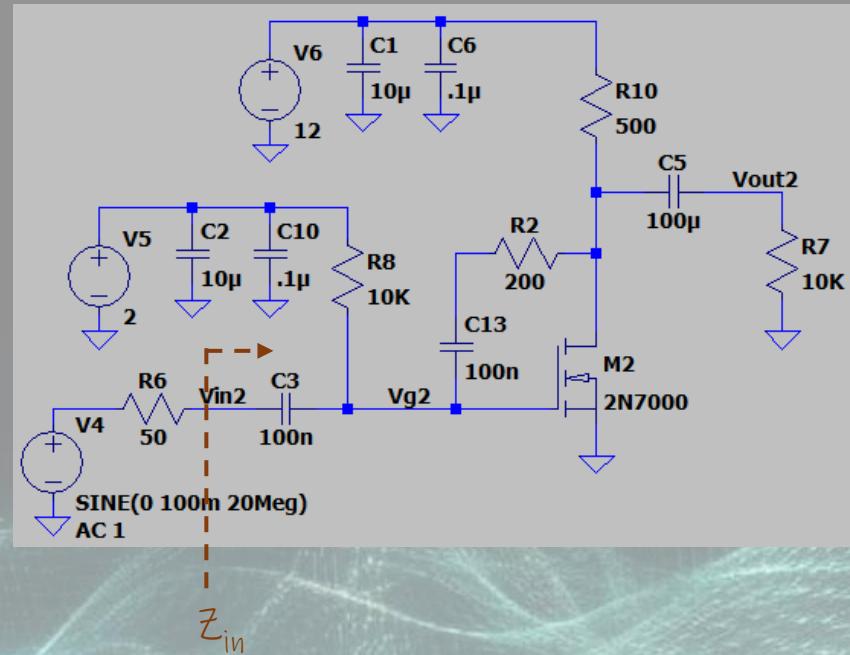

$$Z_{in} = V_{in}/i_s = R_b(R_f + R_o) / (R_f + R_o + G_m R_o R_b)$$

$$Z_{in} = V_{in}/i_s = (R_f + R_o) / (1 + G_m R_o)$$

GOOD ENOUGH



	RMS					
Input (Peak)	0.05	0.05	0.05	0.05	0.05	0.05
Gm	0.0663	0.0663	0.0663	0.0663	0.0663	0.0663
Cal No FB Gain	31.6	31.6	31.6	31.6	31.6	31.6
LTSpice No FB Gain	30.1	30.1	30.1	30.1	30.1	30.1
LTSpice FB Gain	4.4	8.2	14.9	18.0	20.0	24.1
FB Formula Gain	4.3	8.0	14.4	17.3	19.3	22.4
LTSpice Rin	18.6	21.8	31.4	39.4	47.4	79.1
LTSpice Rout	33.6	53.5	103.7	137.3	165.3	242.6
Rf	100	200	500	750	1000	2000
Rb	10000	10000	10000	10000	10000	10000
Rs	50	50	50	50	50	50
Ri	10000	10000	10000	10000	10000	10000
Rd	500	500	500	500	500	500
Vout	0.041889	0.0874874	0.202629	0.279525	0.343683	0.520511
Vd	3.52636	3.52786	3.53382	3.53942	3.54505	3.56435
Vg	1.99979	1.99975	1.99968	1.99964	1.99961	1.99956
Vgac	0.00953195	0.0106825	0.0135924	0.0155357	0.0171569	0.0216238
Vs	0.0353341	0.0353272	0.0353273	0.035325	0.0353223	0.0353147
Vin	0.0353341	0.0353272	0.0353273	0.035325	0.0353223	0.0353147
Vb	2	2	2	2	2	2
if	0.000513995	0.000490784	0.00043243	0.00039341	0.00036083	0.000271062
ig (Mosfet)	0.000000012	0.000000020	0.00000004	0.00000006	0.00000007	0.000000102
id (Mosfet)	0.012953400	0.012956300	0.01296650	0.01297580	0.01298500	0.013018800
is (Mosfet)	0.012953400	0.012956300	0.01296650	0.01297580	0.01298500	0.013018800
ib	0.000000953	0.000001068	0.00000136	0.00000155	0.00000172	0.000002162
is	0.000514948	0.000491853	0.00043379	0.00039496	0.00036255	0.000273224
id	0.012948000	0.012947600	0.01295030	0.01295530	0.01296150	0.012989500
il	0.000004189	0.000008749	0.00002026	0.00002795	0.00003437	0.000052051
Xc Miller at 1KHz	88609					

Rin Rb(Ro+Rf)/(Rf+Ro+gmRoRb)	26.2	21.4	30.8	38.7	46.5	77.8
Rin [(Ro+Rf)/(1+GmRo)]	25.2	20.8	30.0	37.6	45.3	76.0
LTSpice Rin	18.6	21.8	31.4	39.4	47.4	79.1


Simplified Model: Zout Math

- Remove Current source and short voltage source


✓ R_b is shorted and can be removed

✓ R_o and R_f are left
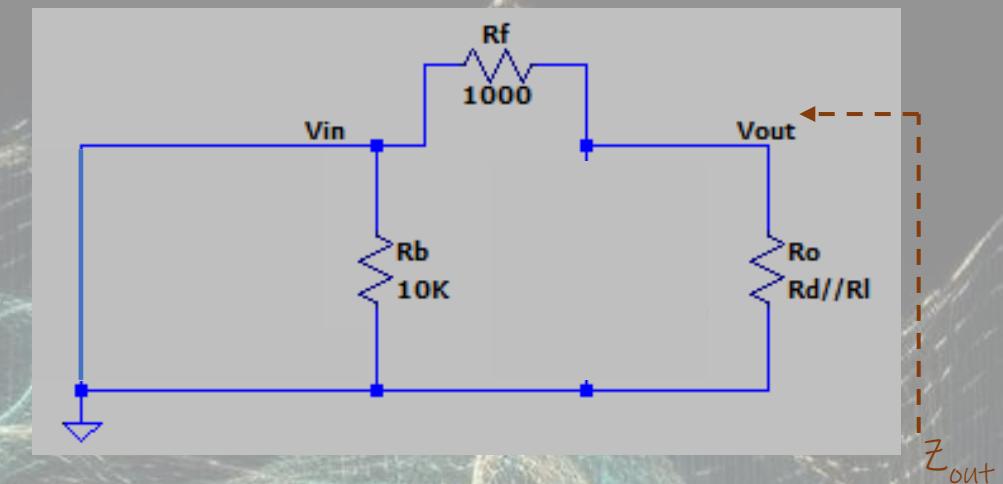
$$\bullet Z_{out} = R_f // R_o = R_f // R_D // R_L$$



Simplified Model: Zout Calculation

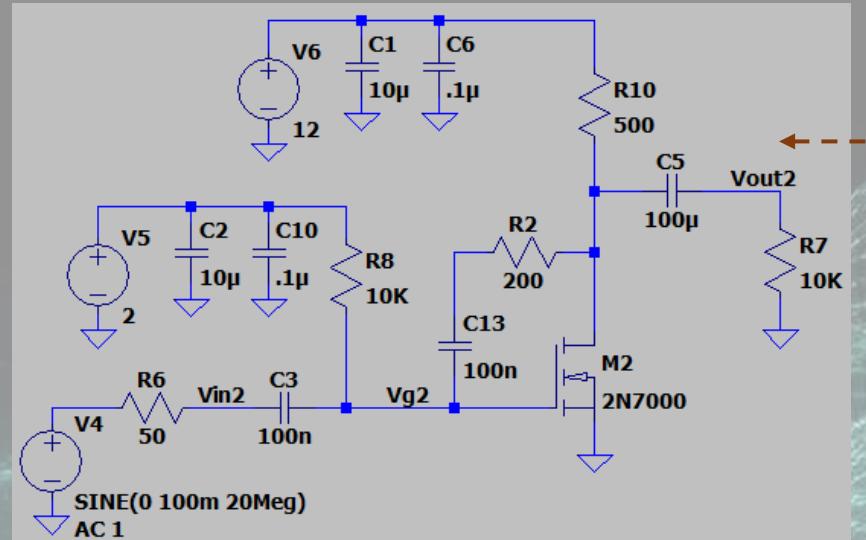


Z_{out}

$$Z_{out} = R_f // R_o = R_f // R_D // R_L$$

	RMS					
Input (Peak)	0.05	0.05	0.05	0.05	0.05	0.05
Gm	0.0663	0.0663	0.0663	0.0663	0.0663	0.0663
Cal No FB Gain	31.6	31.6	31.6	31.6	31.6	31.6
LTSpice No FB Gain	30.1	30.1	30.1	30.1	30.1	30.1
LTSpice FB Gain	4.4	8.2	14.9	18.0	20.0	24.1
FB Formula Gain	4.3	8.0	14.4	17.3	19.3	22.4
LTSpice Rin	18.6	21.8	31.4	39.4	47.4	79.1
LTSpice Rout	33.6	53.5	103.7	137.3	165.3	242.6
Rf	100	200	500	750	1000	2000
Rb	10000	10000	10000	10000	10000	10000
Rs	50	50	50	50	50	50
Ri	10000	10000	10000	10000	10000	10000
Rd	500	500	500	500	500	500
Vout	0.041889	0.0874874	0.202629	0.279525	0.343683	0.520511
Vd	3.52636	3.52786	3.53382	3.53942	3.54505	3.56435
Vg	1.99979	1.99975	1.99968	1.99964	1.99961	1.99956
Vgac	0.00953195	0.0106825	0.0135924	0.0155357	0.0171569	0.0216238
Vs	0.0353341	0.0353272	0.0353273	0.035325	0.0353223	0.0353147
Vin	0.0353341	0.0353272	0.0353273	0.035325	0.0353223	0.0353147
Vb	2	2	2	2	2	2
if	0.000513995	0.000490784	0.00043243	0.00039341	0.00036083	0.000271062
ig (Mosfet)	0.000000012	0.000000020	0.00000004	0.00000006	0.00000007	0.000000102
id (Mosfet)	0.012953400	0.012956300	0.01296650	0.01297580	0.01298500	0.013018800
is (Mosfet)	0.012953400	0.012956300	0.01296650	0.01297580	0.01298500	0.013018800
ib	0.000000953	0.000001068	0.00000136	0.00000155	0.00000172	0.000002162
is	0.000514948	0.000491853	0.00043379	0.00039496	0.00036255	0.000273224
id	0.012948000	0.012947600	0.01295030	0.01295530	0.01296150	0.012989500
il	0.000004189	0.000008749	0.00002026	0.00002795	0.00003437	0.000052051
Xc Miller at 1KHz	88609					


Zout (Ro//Rf)	82.6	140.8	243.9	291.3	322.6	384.6
LTSpice Rout	82.5	140.8	243.9	291.2	322.6	384.6

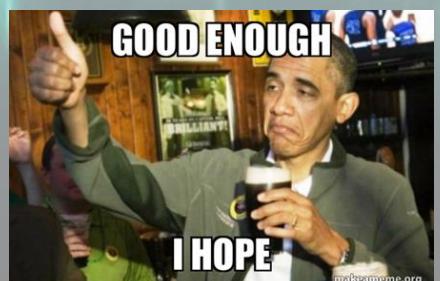

Mid Band Analysis (Low Frequency Analysis)

“Feedback Amplifier” Model

Feedback Amplifier Model: Egg Heads

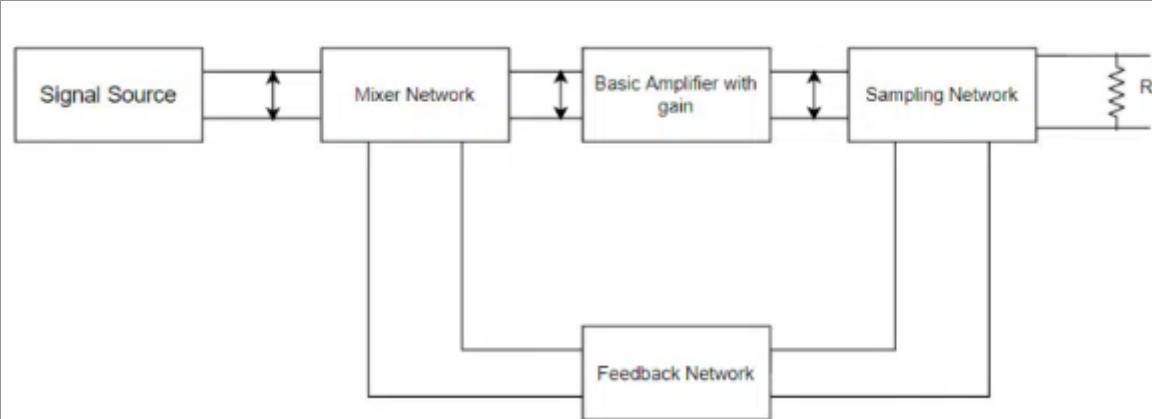


Characteristics	Types of Feedback			
	Voltage-Series	Voltage-Shunt	Current-Series	Current-Shunt
Voltage Gain	Decreases	Decreases	Decreases	Decreases
Bandwidth	Increases	Increases	Increases	Increases
Input resistance	Increases	Decreases	Increases	Decreases
Output resistance	Decreases	Decreases	Increases	Increases
Harmonic distortion	Decreases	Decreases	Decreases	Decreases
Noise	Decreases	Decreases	Decreases	Decreases

Topology	Closed-Loop Gain	Input Resistance	Output Resistance
	A_f	R_{if}	R_{of}
Voltage-Sampling Series-Mixing	$A / (1 + A\beta)$	$R_i(1 + A\beta)$	$R_o / (1 + A\beta)$
Current-Sampling Series-Mixing	$A / (1 + A\beta)$	$R_i(1 + A\beta)$	$R_o(1 + A\beta)$
Voltage-Sampling Shunt-Mixing	$A / (1 + A\beta)$	$R_i / (1 + A\beta)$	$R_o / (1 + A\beta)$
Current-Sampling Shunt-Mixing	$A / (1 + A\beta)$	$R_i / (1 + A\beta)$	$R_o(1 + A\beta)$

Beta is feedback factor or proportion of current/voltage fed back

Do you really think it was that easy?!

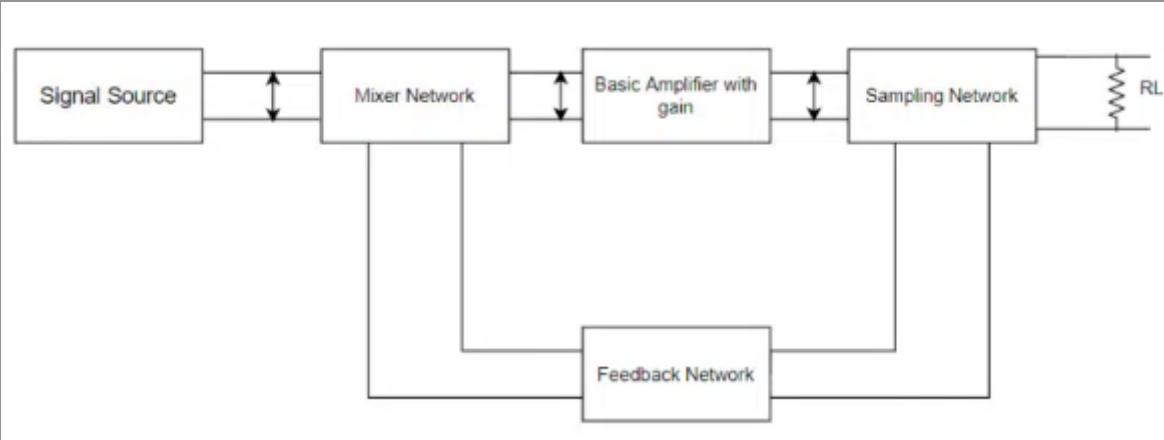

- This assumes it's a “Transresistance” amplifier and the AC/Hybrid model is different.
 - Input is a current and output is a voltage
 - Gain is $R_m = V_o/I_s$ (V_o output voltage, I_s input current)
 - Remember that V/I is a resistance hence a transresistance

I could not get this approach to work.

Gave up...life is too short



Mid Band Analysis (Low Frequency Analysis)

**Signal Flow Charts and
Mason Gain Formula**

SIGNAL FLOW CHARTS

© Copyright 2009. W. Marshall Leach, Jr., Professor, Georgia Institute of Technology, School of Electrical and Computer Engineering.

Collection of Solved Feedback Amplifier Problems

This document contains a collection of solved feedback amplifier problems involving one or more active devices. The solutions make use of a graphical tool for solving simultaneous equations that is called the Mason Flow Graph (also called the Signal Flow Graph). When set up properly, the graph can be used to obtain by inspection the gain of a feedback amplifier, its input resistance, and its output resistance without solving simultaneous equations. Some background on how the equations are written and how the flow graph is used to solve them can be found at

<http://users.ece.gatech.edu/~mleach/ece3050/notes/feedback/fdbkamps.pdf>

<https://leachlegacy.ece.gatech.edu/ece3050/notes/feedback/FBExamples.pdf>



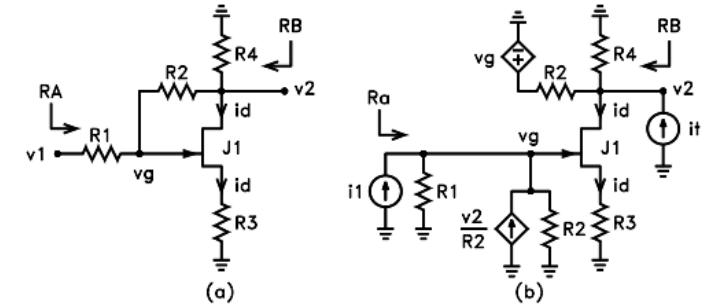


Figure 12: (a) Amplifier circuit. (b) Circuit with feedback removed.

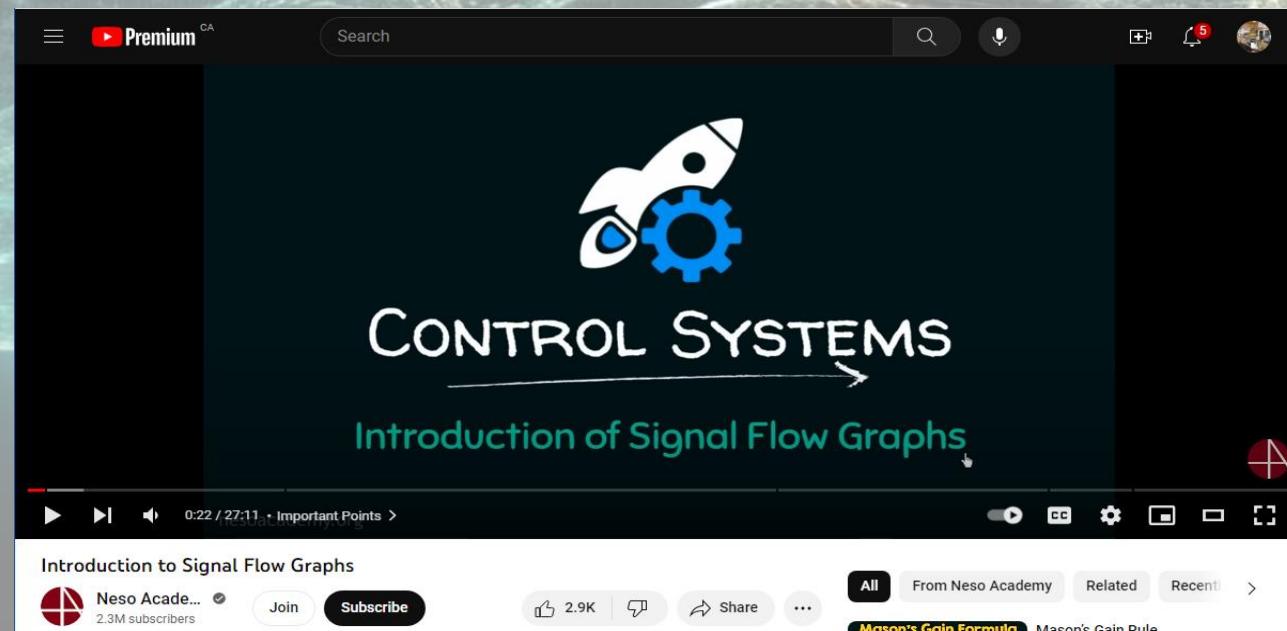

SIGNAL FLOW CHARTS
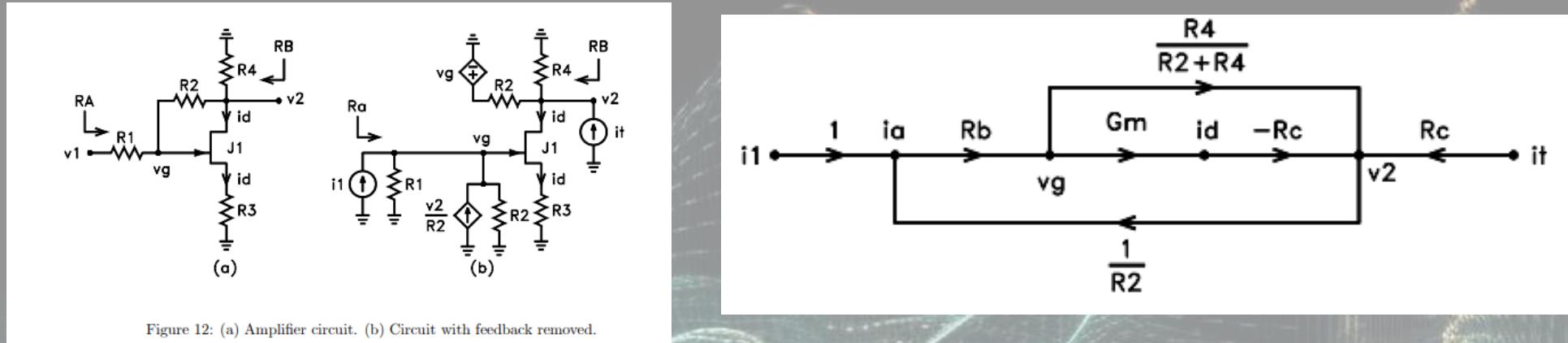
<https://leachlegacy.ece.gatech.edu/ece3050/notes/feedback/FBExamples.pdf>



For the circuit with feedback removed, we can write

$$v_g = i_1 R_b + \frac{v_2}{R_2} R_b \quad R_b = R_1 \parallel R_2 \quad i_d = G_m v_g \quad G_m = \frac{1}{r_s + R_3}$$

$$v_2 = -i_d R_c + i_t R_c + v_g \frac{R_4}{R_2 + R_4} \quad R_c = R_2 \parallel R_4$$

$$\begin{aligned} \Delta &= 1 - R_b \times \left[G_m \times -R_c + \frac{R_4}{R_2 + R_4} \right] \times \frac{1}{R_2} \\ &= 1 + R_b \times \left[G_m \times R_c - \frac{R_4}{R_2 + R_4} \right] \times \frac{1}{R_2} \end{aligned}$$


$$\begin{aligned} A &= -R_b \times \left[G_m \times R_c - \frac{R_4}{R_2 + R_4} \right] \\ &= -(R_1 \parallel R_2) \times \left[G_m \times R_2 \parallel R_4 - \frac{R_4}{R_2 + R_4} \right] \end{aligned}$$

$$R_a = \frac{v_g}{i_1} = \frac{R_b}{\Delta}$$


$$R_A = R_1 + \left(\frac{1}{R_a} - \frac{1}{R_1} \right)^{-1}$$

$$R_B = \frac{v_2}{i_t} = \frac{R_c}{\Delta}$$

Simplified Model: Zout Calculation

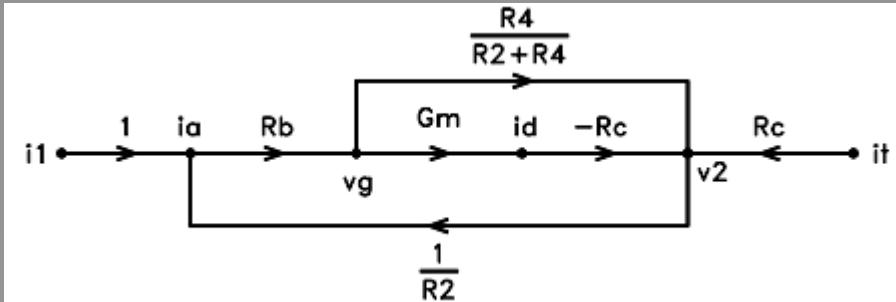

Input (Peak)	0.05	0.05	0.05	0.05	0.05	0.05
Gm	0.0663	0.0663	0.0663	0.0663	0.0663	0.0663
Cal No FB Gain	31.6	31.6	31.6	31.6	31.6	31.6
LTSpice No FB Gain	30.1	30.1	30.1	30.1	30.1	30.1
LTSpice FB Gain	4.4	8.1	14.8	17.9	20.0	24.1
FB Formula Gain	4.3	8.0	14.4	17.3	19.3	22.4
LTSpice Rin	18.7	21.9	31.5	39.5	47.4	79.2
LTSpice Rout (Input Unterminated)	15.4	15.6	16.0	16.4	16.8	18.3
LTSpice Rout (Input terminated)	33.6	53.5	103.7	137.3	165.3	242.6
Rf	100	200	500	750	1000	2000
Rb	10000	10000	10000	10000	10000	10000
Rs	0.0001	0.0001	0.0001	0.0001	0.0001	0.0001
Rl	10000	10000	10000	10000	10000	10000
Rd	500	500	500	500	500	500

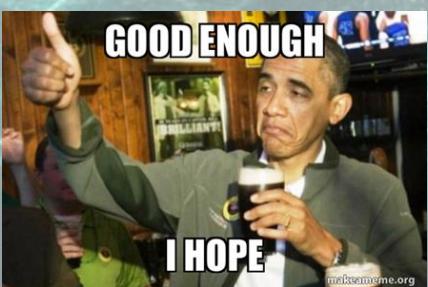

Signal Flow Chart and Mason Gain Formula						
Req	99.01	196.08	476.19	697.67	909.09	1666.67
Rc	82.64	140.85	243.90	291.26	322.58	384.62
Rd'	476.19	476.19	476.19	476.19	476.19	476.19
Det	5.61	9.46	15.94	18.60	20.15	22.09
A	-460.68	-1692.90	-7468.06	-13201.63	-19149.56	-42179.49
Beta	-0.010000	-0.005000	-0.002000	-0.001333	-0.001000	-0.000500
Gain	-4.65	-8.63	-15.68	-18.92	-21.06	-25.31
Ralpha	17.66	20.72	29.88	37.51	45.12	75.45
Rin	17.66	20.72	29.88	37.51	45.12	75.45
Rout	14.74	14.88	15.31	15.66	16.01	17.41
LTSpice Rin	18.67	21.87	31.47	39.46	47.43	79.19
LTSpice Rout (Input Unterminated)	15.44	15.59	16.04	16.41	16.78	18.26
LTSpice FB Gain	4.4	8.1	14.8	17.9	20.0	24.1

GOALS

1. Need to calculate maximum gain (**Low Frequency Analysis**)
✓ Used for Miller impedance and capacitance
2. Need to calculate amplifier bandwidth (**3dB Frequency Analysis**)
✓ Used to ensure you have necessary performance
3. Need to calculate gain at frequency of interest (**High Frequency Analysis**)

-3dB Analysis (High Frequency Cutoff)

VE3OOI Simplified Model

Simplified Model: Bandwidth



- Need to short voltage source and open current source. Separate Input side from Output side
- Need to add Miller intrinsic capacitance to input and outputs
- Need to move "Millerized" Feedback resistor to input and outputs
- Calculate 3dB cutoff frequency for LPF $F = 1/(2\pi R_{eq} C_{eq})$

For Input Side


- $C_{miller(in)} = C_{gd}(1+A) + C_{gs}$
- $R_{miller(in)} = R_f/(1+A)$
- $C_{eq} = C_{miller(in)}$
- $R_{eq} = R_{miller(in)} // R_b // R_s$
- $F_{in(3dB)} = 1/(2\pi R_{eq} C_{eq})$

For Output

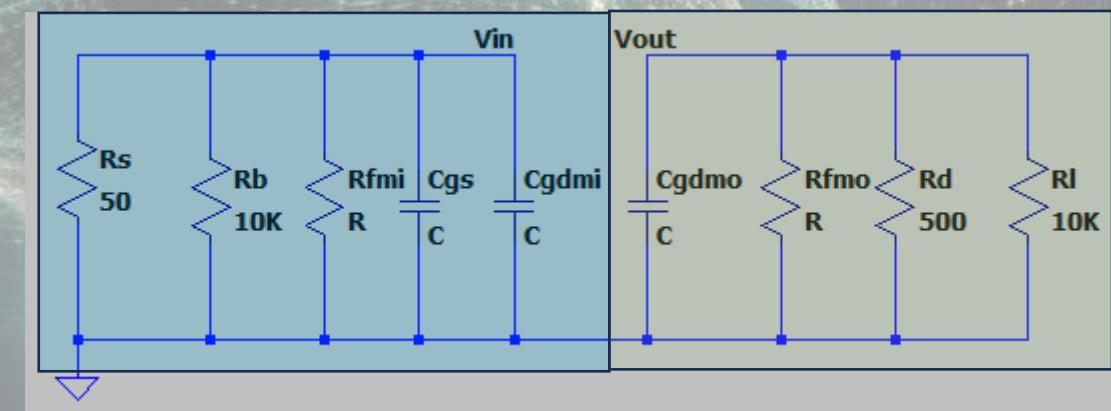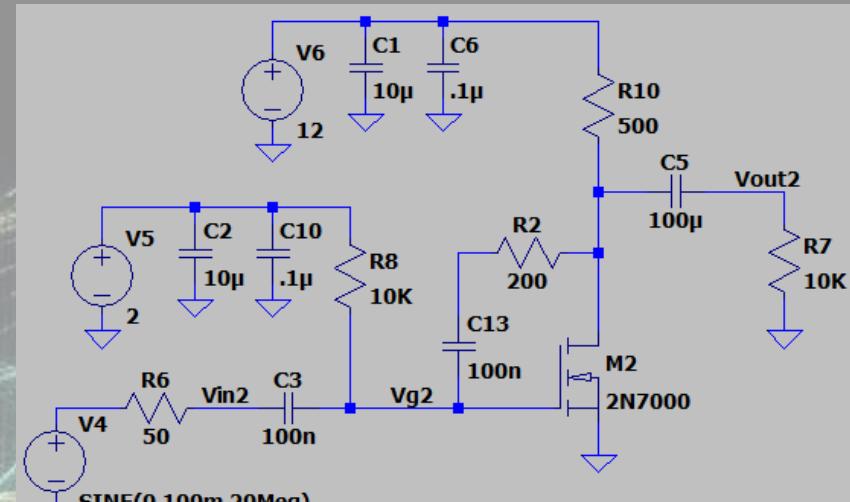- $C_{miller(out)} = C_{gd}(1+A)/A$
- $R_{miller(out)} = R_f A / (1+A)$
- $C_{eq} = C_{miller(out)}$
- $R_{eq} = R_{miller(out)} // R_d // R_L$
- $F_{out(3dB)} = 1/(2\pi R_{eq} C_{eq})$



Simplified Model: Bandwidth

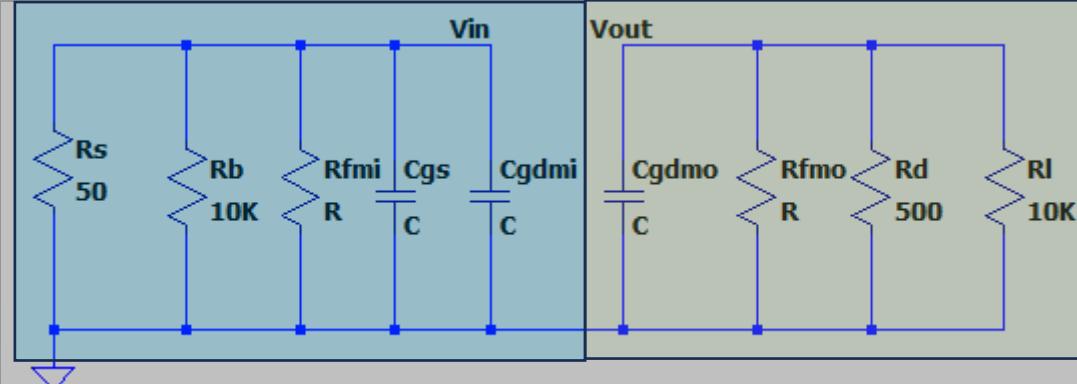

	LTSpice No FB Gain	30.1	30.1	30.1	30.1	30.1	30.1
C_{gs}		50	50	50	50	50	50
C_{gd}		19.3	19.3	19.3	19.3	19.3	19.3
R_f		100	200	500	750	1000	2000
R_b		10000	10000	10000	10000	10000	10000
R_s		50	50	50	50	50	50
R_I		10000	10000	10000	10000	10000	10000
R_d		500	500	500	500	500	500

R_f	100	200	500	750	1000	2000
Cin-Miller	600.7	600.7	600.7	600.7	600.7	600.7
Cout-Miller	19.9	19.9	19.9	19.9	19.9	19.9
Cin	650.7	650.7	650.7	650.7	650.7	650.7
Rfin-Miller	3.2	6.4	16.1	24.1	32.1	64.3
Rfout-Miller	96.8	193.6	483.9	725.9	967.9	1935.7
Rin	3.0	5.7	12.1	16.2	19.5	28.0
Rout	80.4	137.6	240.0	287.6	319.2	382.2
Fi	81.0	43.0	20.1	15.1	12.5	8.7
Fo	99.2	58.0	33.3	27.8	25.0	20.9
LTSpice Higher 3dB	63.0	34.7	15.7	11.6	9.5	6.3



LTSPICE MODELS: Bitten Again

2N7000 VDMOS (Rg=3 Vto=1.6 Rd=0 Rs=.75 Rb=.14 Kp=.17 mtriode=1.25
 Cgdmax=80p Cgdmin=12p Cgs=50p Cjo=50p
 Is=.04p mfg=Fairchild Vds=60 Ron=2 Qg=1.5n)

Model:	2n7000
Id:	1.29e-02
Vgs:	2.00e+00
Vds:	5.53e+00
Vth:	1.60e+00
Gm:	6.63e-02
Gds:	0.00e+00
Cgs:	5.00e-11
Cgd:	1.93e-11
Cbody:	1.96e-11

I used these values which I thought were fixed

ON CHARACTERISTICS

V _{GS(th)}	Gate Threshold Voltage	V _{DS} = V _{GS} , I _D = 1 mA	2N7000	0.8	2.1	3	V
		V _{DS} = V _{GS} , I _D = 250 μA	2N7002	1	2.1	2.5	
		NDS7002A					

g _{fs}	Forward Transconductance	V _{DS} = 10 V, I _D = 200 mA	2N7000	100	320	-	mS
		V _{DS} ≥ 2 V _{DS(on)} , I _D = 200 mA	2N7002	80	320	-	
		V _{DS} ≥ 2 V _{DS(on)} , I _D = 200 mA	NDS7002A	80	320	-	


C _{iss}	Input Capacitance	V _{DS} = 25 V, V _{GS} = 0 V, f = 1.0 MHz	All	-	20	50	pF	
			2N7000	2N7002	NDS7002A			
			2N7000	2N7002	NDS7002A			
C _{oss}	Output Capacitance		All	-	11	25		
			2N7000	2N7002	NDS7002A			
			2N7000	2N7002	NDS7002A			
C _{rss}	Reverse Transfer Capacitance		All	-	4	5		
			2N7000	2N7002	NDS7002A			
			2N7000	2N7002	NDS7002A			

No lead resistances specified.
 No range for Cgd provided (except for chart)

Created a custom model for testing purposes


```
.model 2N7000CUS VDMOS Vto=1.6 Kp=.17 Cgdmax=19.3p Cgdmin=19.3p Cgs=50p mfg=Fairchild Vds=60 Ron=2 Qg=1.5n)
```

Simplified Model: Bandwidth (Fixed C)

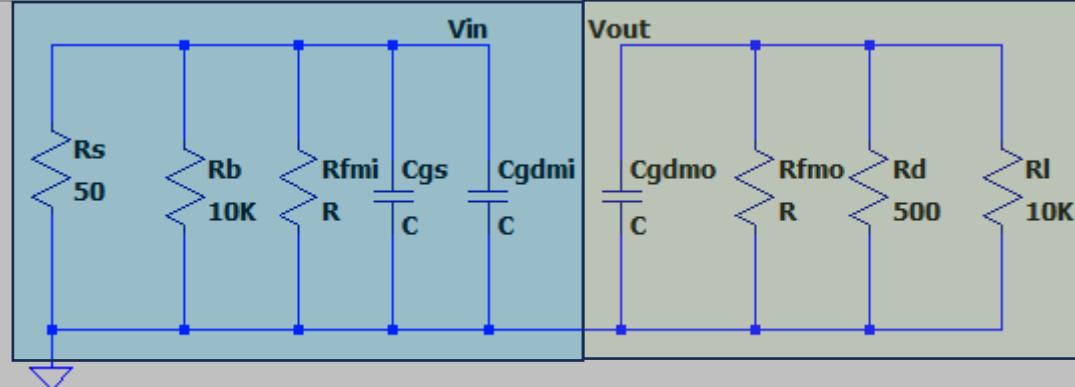

LTSpice No FB Gain	30.1	30.1	30.1	30.1	30.1	30.1
Cgs	50	50	50	50	50	50
Cgd	19.3	19.3	19.3	19.3	19.3	19.3
Rf	100	200	500	750	1000	2000
Rb	10000	10000	10000	10000	10000	10000
Rs	50	50	50	50	50	50
RI	10000	10000	10000	10000	10000	10000
Rd	500	500	500	500	500	500

Rf	100	200	500	750	1000	2000
Cin-Miller	600.7	600.7	600.7	600.7	600.7	600.7
Cout-Miller	19.9	19.9	19.9	19.9	19.9	19.9
Cin	650.7	650.7	650.7	650.7	650.7	650.7
Rfin-Miller	3.2	6.4	16.1	24.1	32.1	64.3
Rfout-Miller	96.8	193.6	483.9	725.9	967.9	1935.7
Rin	3.0	5.7	12.1	16.2	19.5	28.0
Rout	80.4	137.6	240.0	287.6	319.2	382.2
Fi - Rin	81.0	43.0	20.1	15.1	12.5	8.7
Fo	99.2	58.0	33.3	27.8	25.0	20.9
LTSpice Higher 3dB	78.0	42.3	19.4	14.1	11.6	7.6

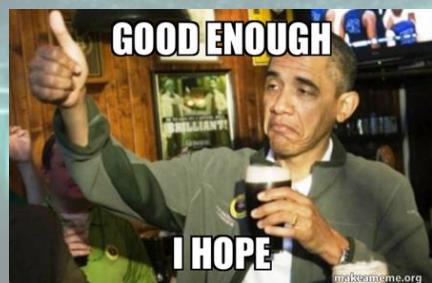


GOALS

1. Need to calculate maximum gain (**Low Frequency Analysis**)
 - ✓ Used for Miller impedance and capacitance
2. Need to calculate amplifier bandwidth (**3dB Frequency Analysis**)
 - ✓ Used to ensure you have necessary performance
3. Need to calculate gain at frequency of interest (**High Frequency Analysis**)



High Frequency Analysis

(VERY) Simplified Model



Wrap your head around this....

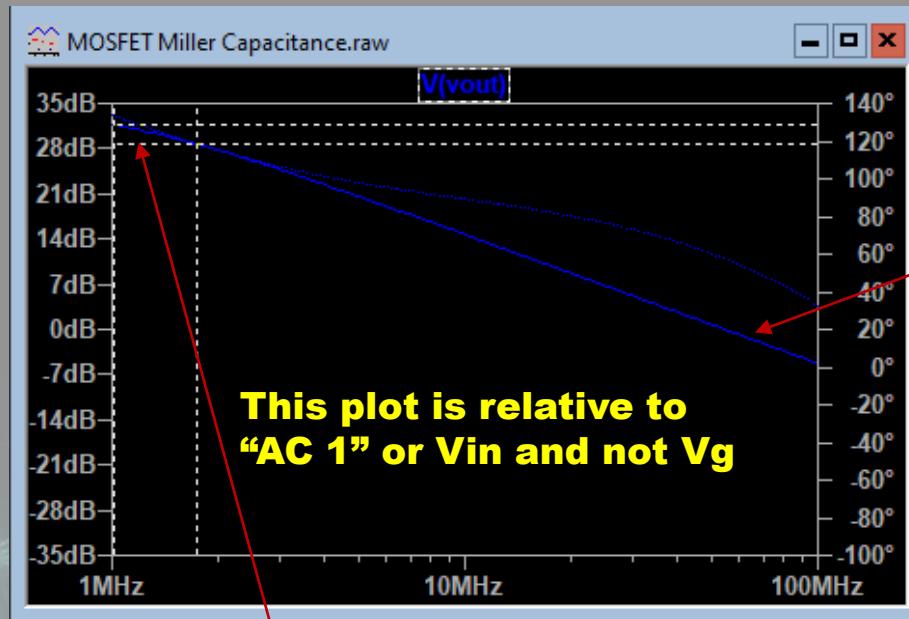

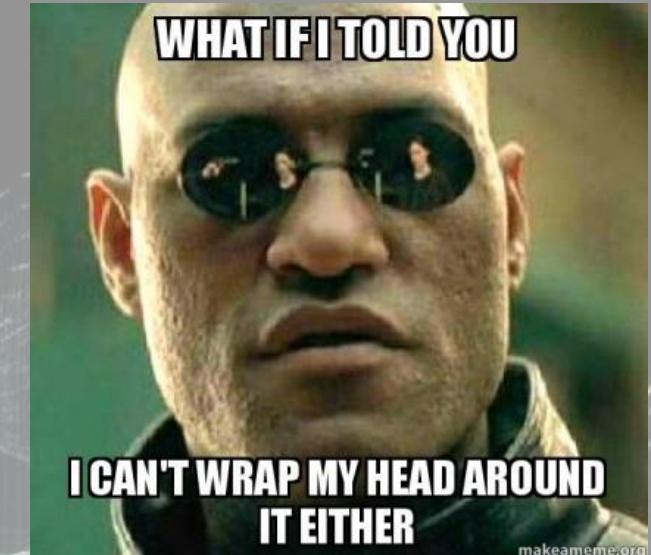
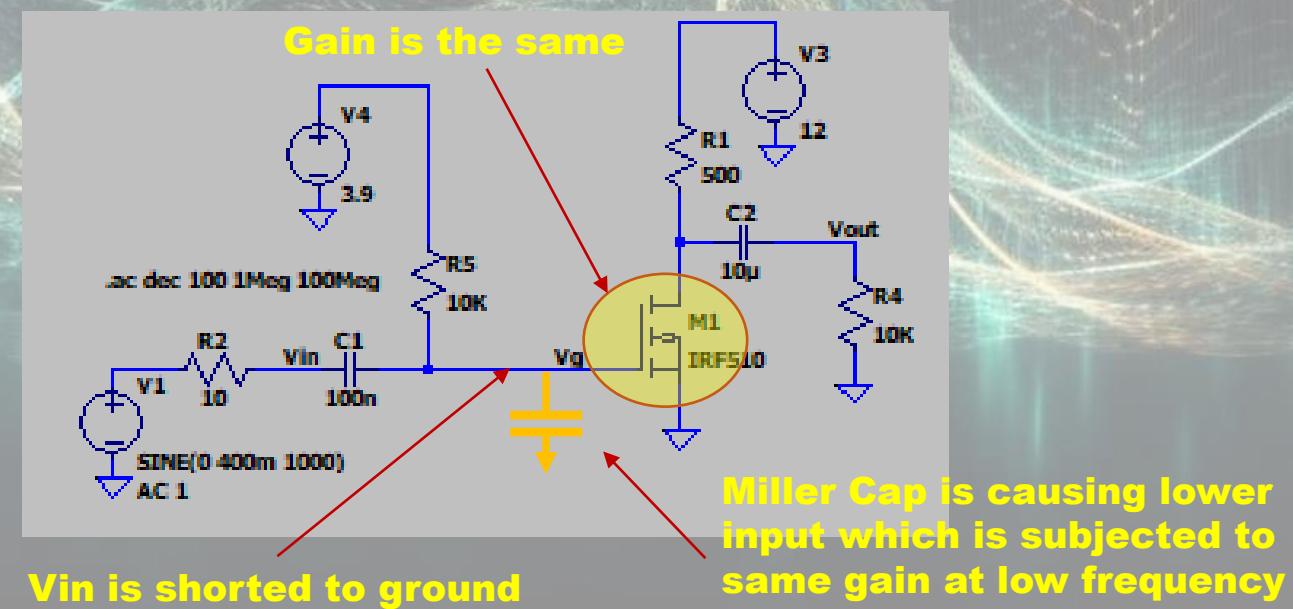
This is and **ALWAYS** will be the gain (maybe larger at lower frequencies)



VOLTAGE DIVIDER APPROXIMATION

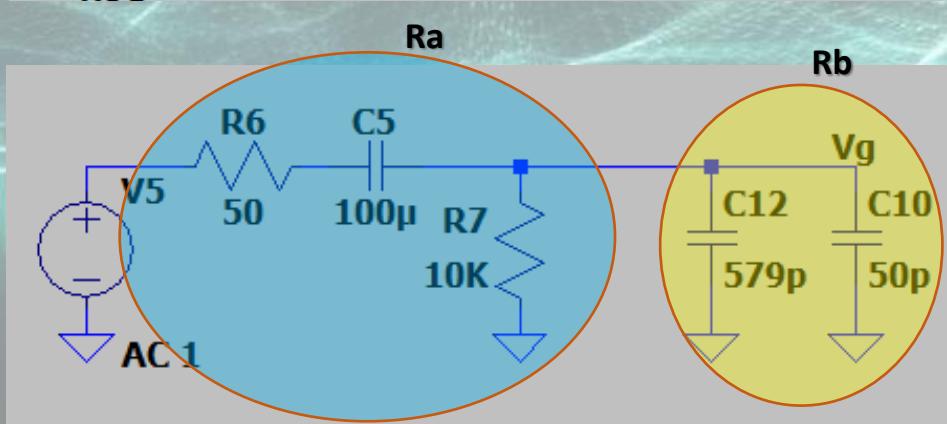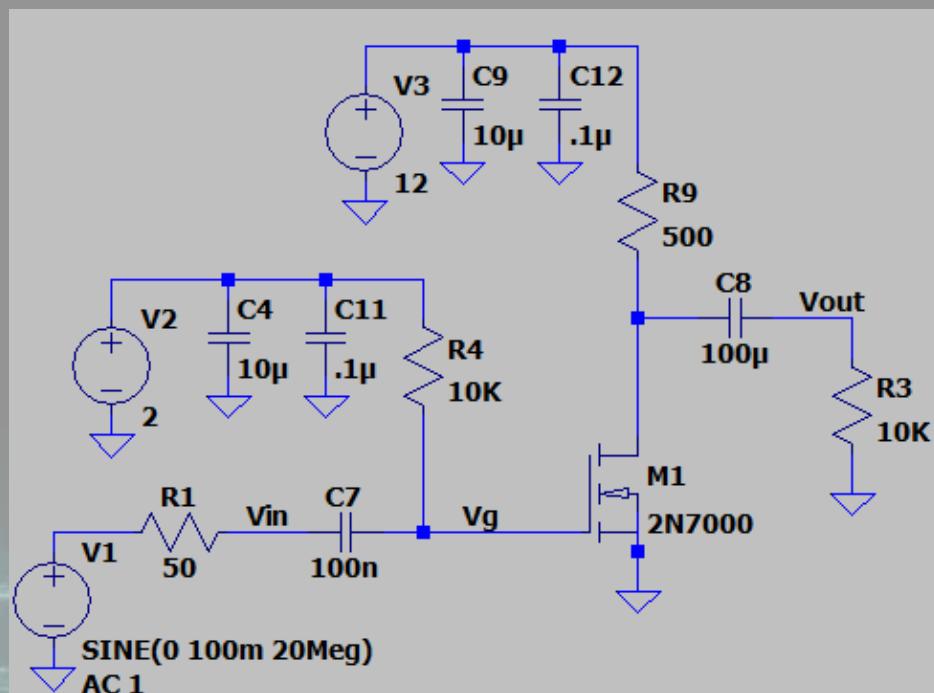


$$V_g = V_{in} * R_b / (R_a + R_b)$$

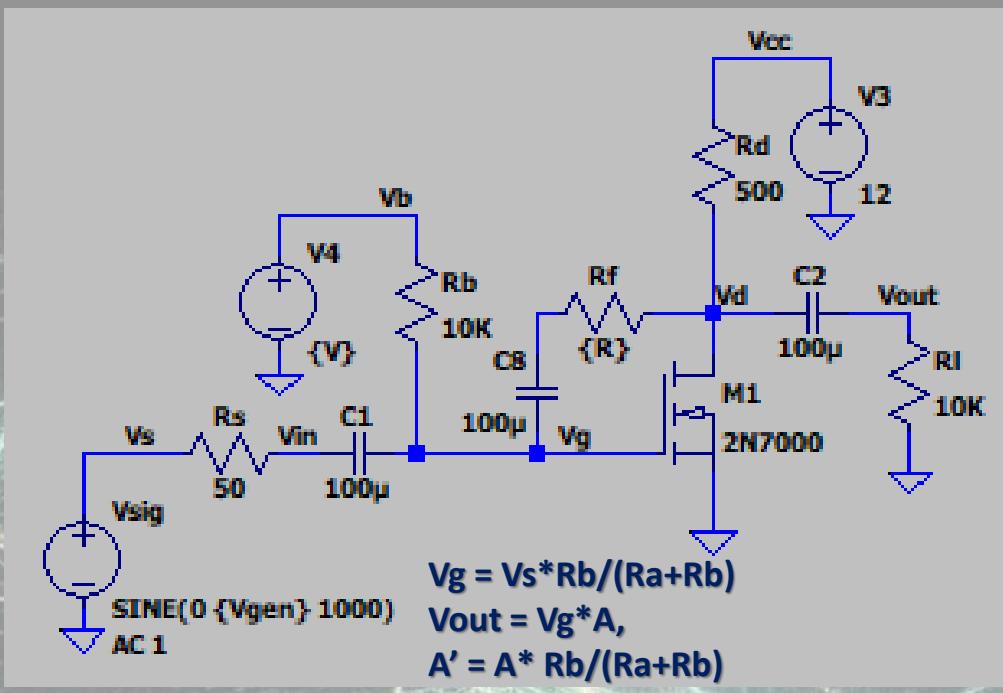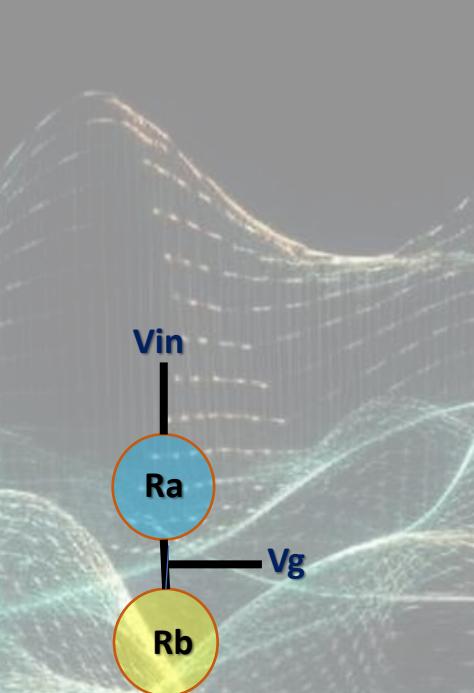

$$V_g = V_s * R_b / (R_a + R_b)$$


$$V_{out} = V_g * A$$

$$A' = A * R_b / (R_a + R_b)$$

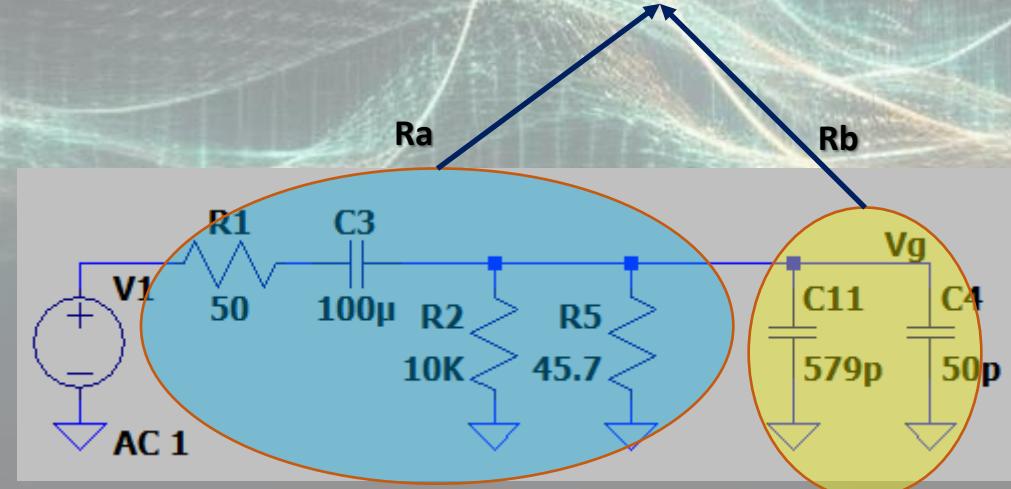

HIGH FREQUENCY ANALYSIS: No Feedback



Frequency	Gain (NF)	Rs	Rb	Cgs	Cgd	Cm	Xc	-3dB Frequency	Divider	Gain Out
1000	32.4	50	1000	50	19.3	694.2	229253	4585052	0.9998	32.4
10000	32.4	50	1000	50	19.3	694.2	22925	4585052	0.9978	32.3
20000	32.4	50	1000	50	19.3	694.2	11463	4585052	0.9957	32.2
30000	32.4	50	1000	50	19.3	694.2	7642	4585052	0.9935	32.2
50000	32.4	50	1000	50	19.3	694.2	4585	4585052	0.9892	32.0
100000	32.4	50	1000	50	19.3	694.2	2293	4585052	0.9787	31.7
200000	32.4	50	1000	50	19.3	694.2	1146	4585052	0.9582	31.0
300000	32.4	50	1000	50	19.3	694.2	764	4585052	0.9386	30.4
500000	32.4	50	1000	50	19.3	694.2	459	4585052	0.9017	29.2
1000000	32.4	50	1000	50	19.3	694.2	229	4585052	0.8210	26.6
2000000	32.4	50	1000	50	19.3	694.2	115	4585052	0.6963	22.5
3000000	32.4	50	1000	50	19.3	694.2	76	4585052	0.6045	19.6
5000000	32.4	50	1000	50	19.3	694.2	46	4585052	0.4784	15.5
10000000	32.4	50	1000	50	19.3	694.2	23	4585052	0.3144	10.2
20000000	32.4	50	1000	50	19.3	694.2	11	4585052	0.1865	6.0
30000000	32.4	50	1000	50	19.3	694.2	8	4585052	0.1326	4.3
50000000	32.4	50	1000	50	19.3	694.2	5	4585052	0.0840	2.7

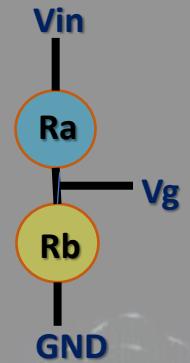

$$V_g = V_s * R_b / (R_a + R_b)$$


$$V_{out} = V_g * A,$$

$$A' = A * R_b / (R_a + R_b)$$

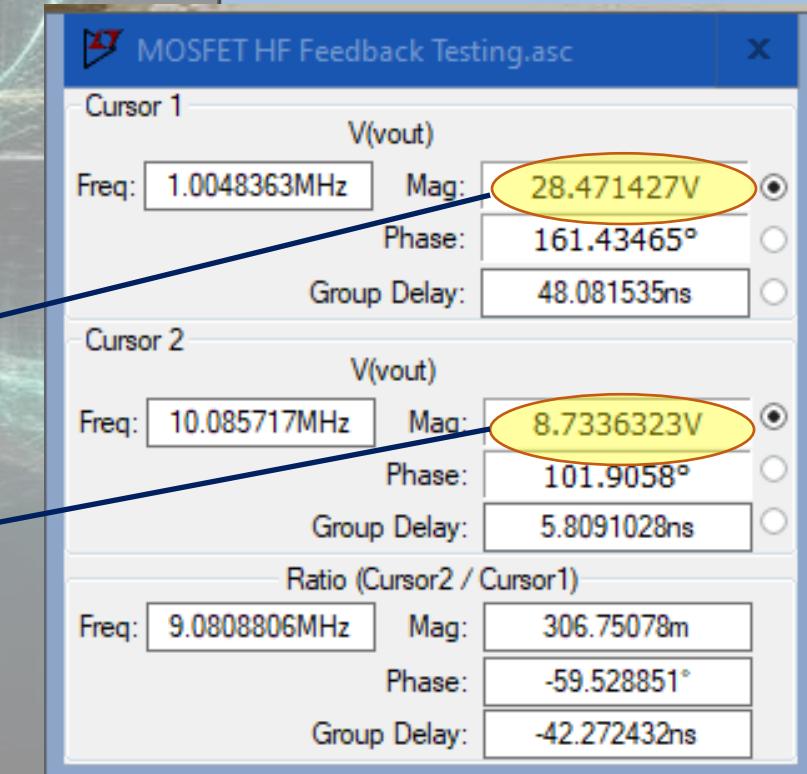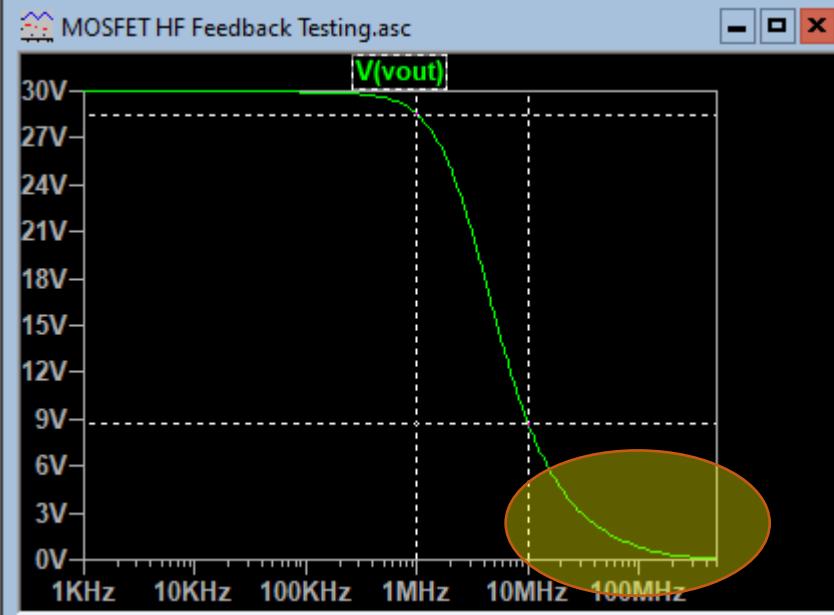

HIGH FREQUENCY ANALYSIS: 100R FB



Frequency	Gain (FB)	Rs	Rb	Ri	Rf	Cgs	Cgd	Rm	Cm	-3dB Frequency	Xc	Real	Divider	Gain Out
1000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	1726022	23.8	1.00	1.19
10000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	172602	23.8	1.00	1.19
20000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	86301	23.8	1.00	1.19
30000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	57534	23.8	1.00	1.19
50000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	34520	23.8	1.00	1.19
100000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	17260	23.8	1.00	1.19
200000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	8630	23.8	1.00	1.18
300000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	5753	23.8	1.00	1.18
500000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	3452	23.8	0.99	1.18
1000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	1726	23.8	0.99	1.17
2000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	863	23.8	0.97	1.16
3000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	575	23.8	0.96	1.14
5000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	345	23.8	0.94	1.11
10000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	173	23.8	0.88	1.04
20000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	86	23.8	0.78	0.93
30000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	58	23.8	0.71	0.84
50000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	35	23.8	0.59	0.70
60000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	29	23.8	0.55	0.65
70000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	25	23.8	0.51	0.60
80000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	22	23.8	0.48	0.56
90000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	19	23.8	0.45	0.53
100000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	17	23.8	0.42	0.50
200000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	9	23.8	0.27	0.32
300000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	6	23.8	0.19	0.23
500000000	1.19	50	10000	49.8	100	50	19.3	45.7	92.2	89701368	3	23.8	0.13	0.15

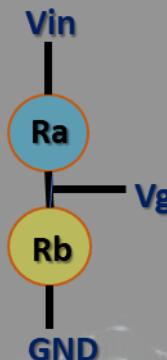

$$Vg = Vs * Rb / (Ra + Rb)$$



$$Vout = Vg * A,$$

$$A' = A * Rb / (Ra + Rb)$$

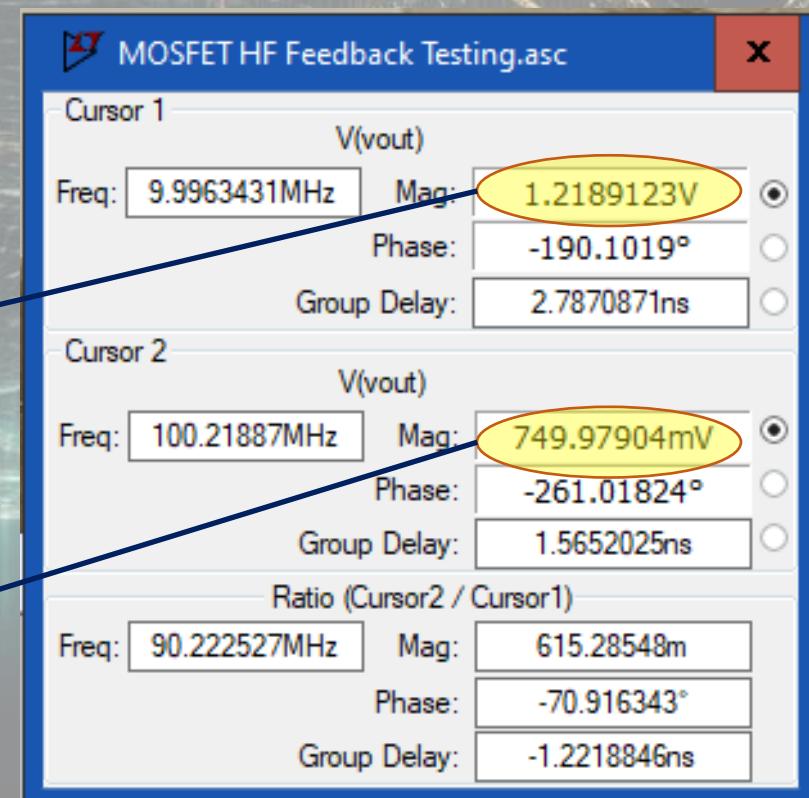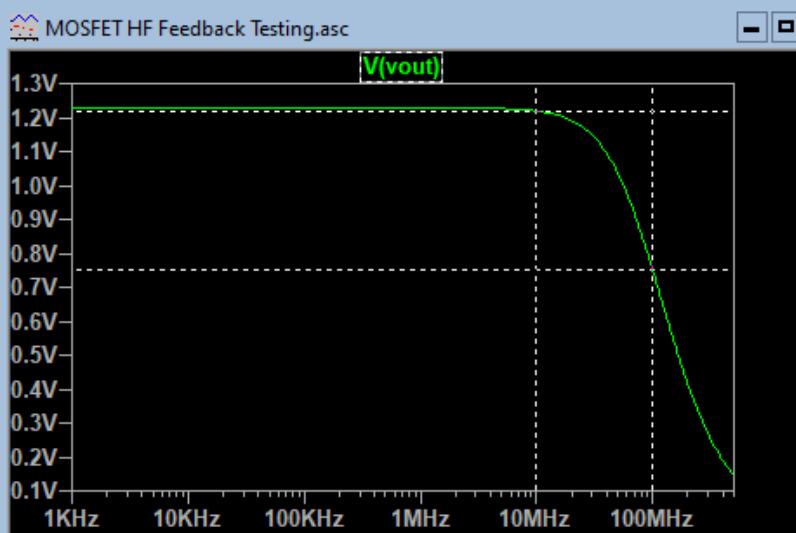

HIGH FREQUENCY ANALYSIS: 1000R FB

Frequency	Gain (FB)	Rs	Rb	Ri	Rf	Cgs	Cgd	Rm	Cm	-3dB Frequency	Xc	Real	Divider	Gain Out
1000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	601518	32.0	1.00	10.12
10000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	60152	32.0	1.00	10.11
20000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	30076	32.0	1.00	10.11
30000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	20051	32.0	1.00	10.10
50000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	12030	32.0	1.00	10.09
100000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	6015	32.0	0.99	10.06
200000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	3008	32.0	0.99	10.01
300000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	2005	32.0	0.98	9.96
500000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	1203	32.0	0.97	9.86
1000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	602	32.0	0.95	9.61
2000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	301	32.0	0.90	9.14
3000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	201	32.0	0.86	8.72
5000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	120	32.0	0.79	7.99
10000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	60	32.0	0.65	6.60
20000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	30	32.0	0.48	4.90
30000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	20	32.0	0.38	3.90
50000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	12	32.0	0.27	2.76
60000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	10	32.0	0.24	2.41
70000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	9	32.0	0.21	2.14
80000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	8	32.0	0.19	1.92
90000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	7	32.0	0.17	1.75
100000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	6	32.0	0.16	1.60
200000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	3	32.0	0.09	0.87
300000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	2	32.0	0.06	0.60
500000000	10.1	50	10000	49.8	1000	50	19.3	89.9	264.6	19380065	1	32.0	0.04	0.37

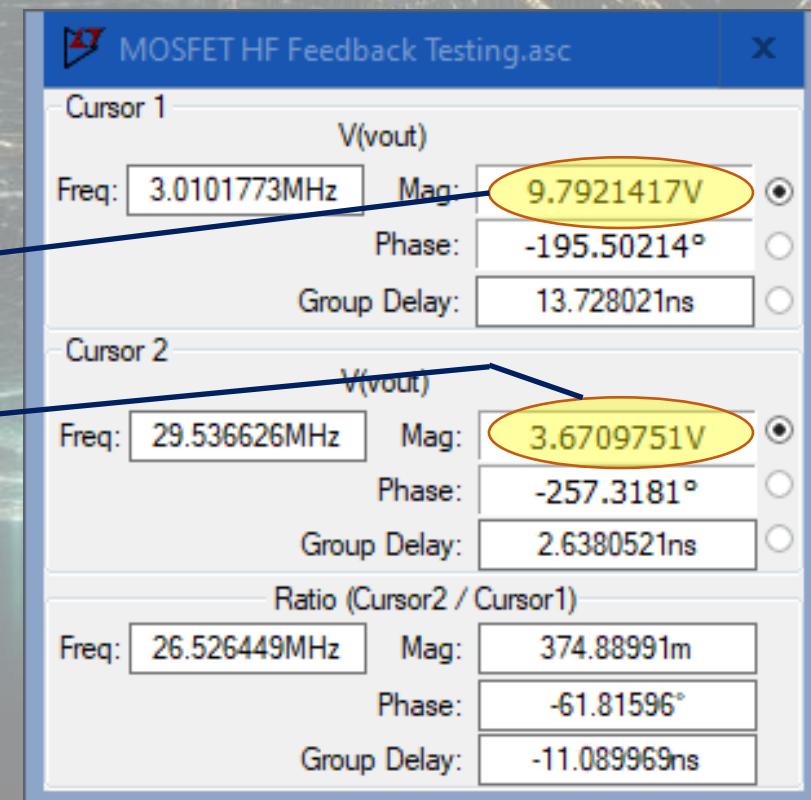
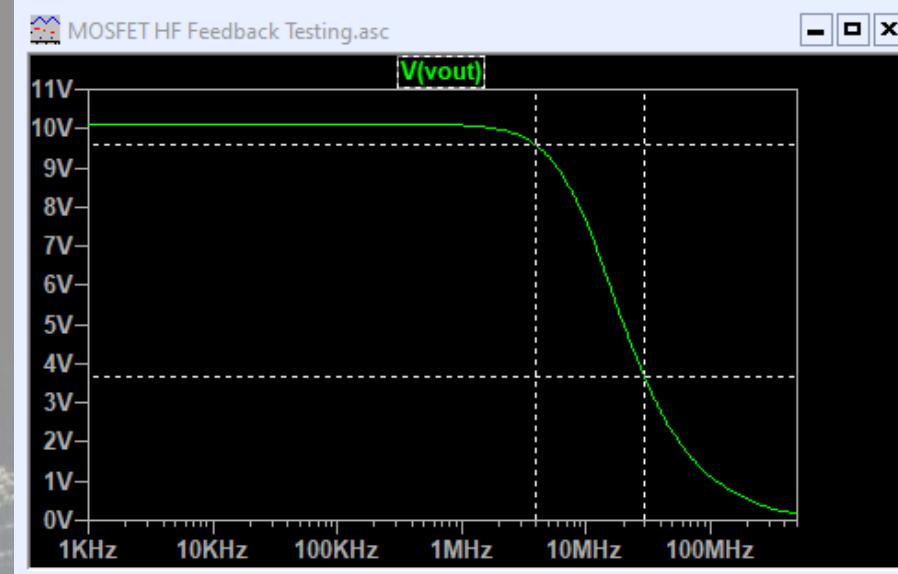


Real World Comparison

Approach

1. Build a test MOSFET Amplifier capable of “easily” changing key resistors (feedback and load)
2. Use scope to measure voltages (after used SA)
3. Calculate R_{in} , R_{out} , Gain and 3dB cutoff Frequencies

Real World Comparison: Test Setup

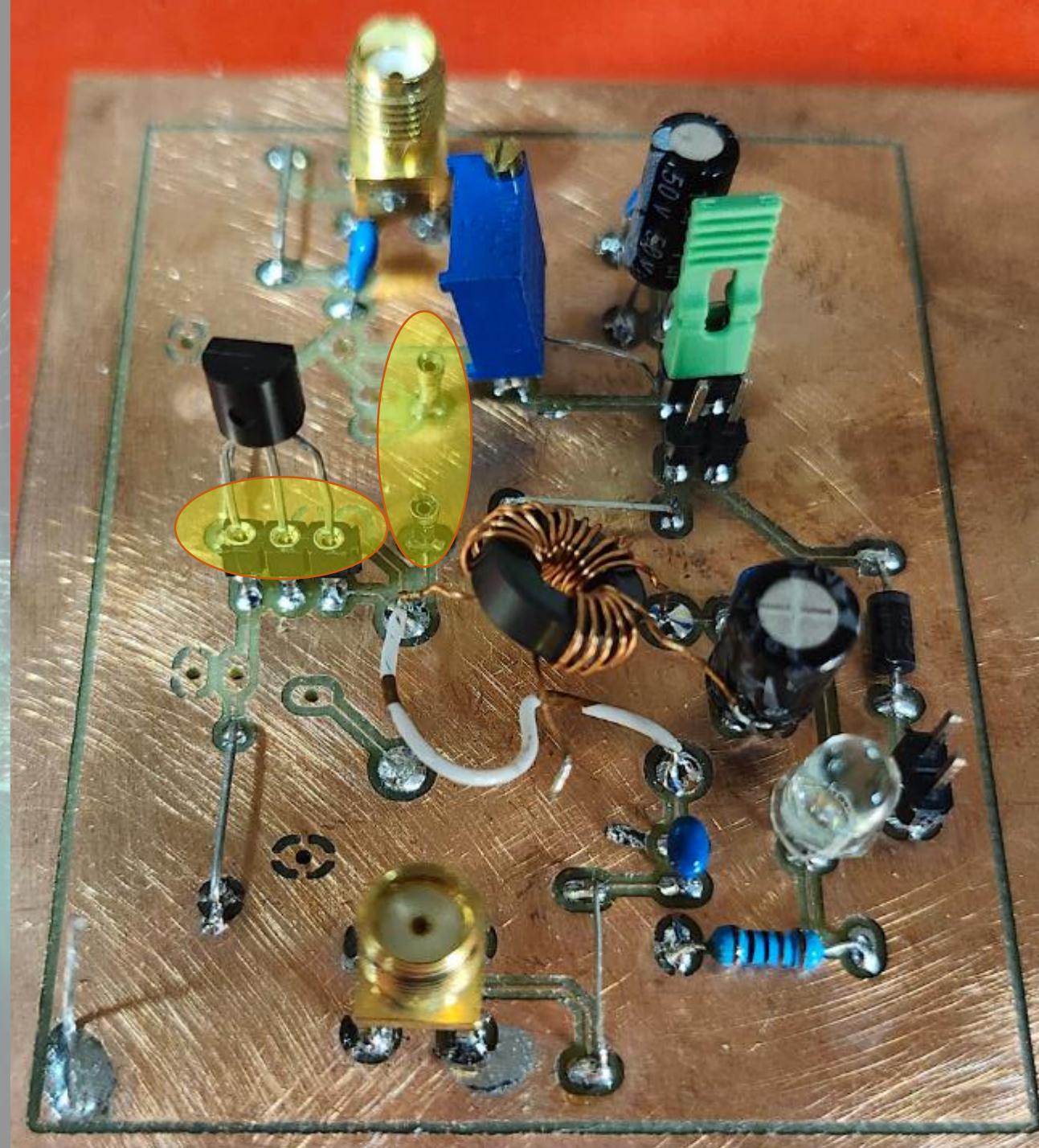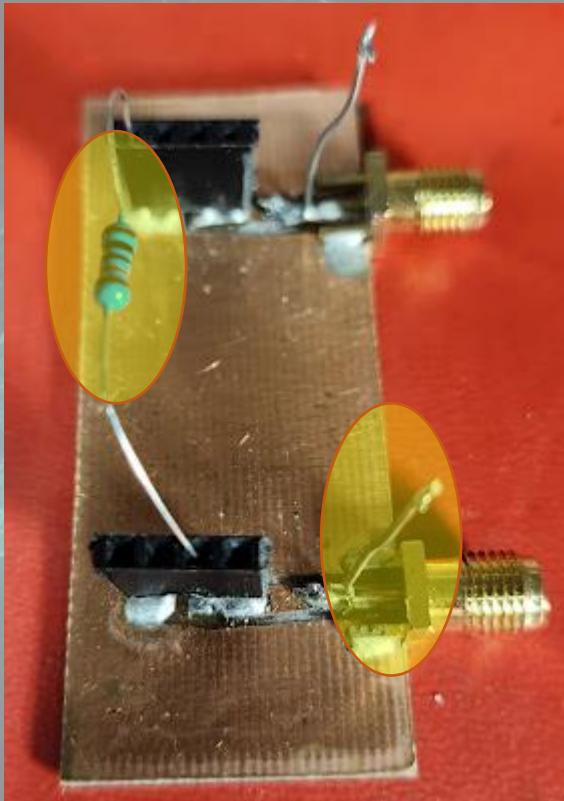

Real World Comparison: WTF!

- Used scope to measure input signal and output signal for each load and feedback resistor.
 - Need a scope to measure input/output impedance
- Method 1: Use the scope to measure output signal to identify -3dB frequencies
- Method 2: Use the SA to measure output signal (using resistor divider) to identify -3dB frequencies
- Observations:
 1. Scope and SA measurements differ significantly with -3 dB frequencies differing about 2X (e.g., 4.9 MHz vs 10.8 MHz)
 2. The SA could give accurate values for Mid Band baseline (i.e., max gain). Max gain was around 1.5 MHz and drop off below that
 3. Some Measurements vs calculations differ significantly. Operator? Equipment?



Update: How Stupid can I be?



The **half-power point** is the point at which the output **power** has dropped to half of its peak value, that is, at a level of approximately -3 dB.^{[1][a]}

Amplifiers and filters [edit]

This occurs when the output **voltage** has dropped to $1/\sqrt{2}$ (~0.707) of the maximum output voltage^[b] and the power has dropped by half.^[a] A **bandpass** amplifier will have two half-power points, while a **low-pass** amplifier or a **high-pass** amplifier will have only one.

I only realized this today!!!

General Outcome



How to make RF measurements?

Real World Comparison: Data Collection

Gain Frequency Rin Rout

	R _E	R _I	C _{in}	C _{out}	R _b	R _d	R _s	LTSPIRE Gm	r _e @ 1M 10.3nA	V _{ds} @ 1M 10.3nA	Open Loop Gain	Calculated Feedback Gain	LTSPIRE Gain @ 100KHz	Measured Gain @ 100KHz	Cir- Miller	Coil- Miller	Cir	Coil	Rfin- Miller	Rload- Miller	R _{in}	R _{out}	Calculated r _d -Zin Freq 1MHz	r _d	Measured r _d -Zin Freq 1MHz	LTSPIRE Zin [10 KHz]	Measured Zin [10KHz]	Calculated Zout [R _e -R _i]	LTSPIRE Zout [R _e -R _i]	Calculated Zout [R _e -R _i]	LTSPIRE Zout [R _e -R _i]				
BS170	1000		15.3	6.1	1000	50	500	476.2	0.000235	605	11.0	42.0	42.0	20.3	21.0	262.4	6.2	282.3	6.2	8.0	8.0	43.0	45.0	11.3	55.5	4.5	12.7	1000	357	2845	475	475	351	351	
	1000		15.3	6.1	1000	50	500	335.3	0.000235	605	11.0	23.4	23.4	19.7	20.5	185.5	6.3	285.4	6.3	8.0	8.0	43.0	39.3	15.5	75.7	6.5	18.1	1000	332	2845	333	333	333	345	
	1000		15.3	6.1	1000	50	500	142.3	0.000235	605	11.0	12.6	12.6	1.4	3.5	85.8	6.5	182.5	6.5	8.0	8.0	43.0	142.3	14.1	163.2	15.3	42.1	1000	385	2855	143	143	143	143	
	2200	10000	20	5.12	1000	50	500	476.2	0.000235	605	11.0	42.0	34.6	29.8	29.4	228.2	5.2	248.2	5.2	54.1	244.9	25.3	39.8	25.4	27.5	7.7	15.4	6.1	31	351	351	238	268	425	
	2200	10000	20	5.12	1000	50	500	335.3	0.000235	605	11.0	23.4	25.4	17.8	18.1	155.7	5.3	183.7	5.3	72.3	245.8	23.5	235.4	23.4	182.5	18.4	28.8	8.5	121	100	285	136	218	287	
	2200	200	20	5.12	1000	50	500	142.3	0.000235	605	11.0	12.6	11.0	7.3	8.1	63.7	5.5	37.7	5.5	161.7	247.7	38.8	154.8	42.0	214.5	18.4	102	242	200	154	154	118	114	268	
	1000	10000	20	5.12	1000	50	500	476.2	0.000235	605	11.0	42.0	28.1	18.5	18.5	228.2	5.2	248.2	5.2	29.2	376.1	15.0	328.1	40.5	34.8	12.5	18.7	35	58	47	323	323	213	171	173
	1000	10000	20	5.12	1000	50	500	335.3	0.000235	605	11.0	23.4	24.8	10.5	14.2	155.7	5.3	183.7	5.3	32.3	123.5	15.0	204.5	43.8	113.5	14.5	24.1	45	54	53	258	258	178	148	175
	1000	200	20	5.12	1000	50	500	142.3	0.000235	605	11.0	12.6	10.9	7.3	7.4	63.7	5.5	37.7	5.5	79.5	185.8	29.7	125.5	54.5	228.8	14.5	40.8	39	115	104	125	184	55	177	
	200	10000	20	5.12	1000	50	500	476.2	0.000235	605	11.0	42.0	11.7	7.6	7.3	228.2	5.2	248.2	5.2	4.6	185.4	4.5	188.5	150.8	219.2	>120	42.7	16	23	24	141	141	123	56	115
	200	10000	20	5.12	1000	50	500	335.3	0.000235	605	11.0	23.4	18.4	6.8	6.4	155.7	5.3	183.7	5.3	55.8	202.5	5.8	145.1	148.5	>120	40.1	18	26	23	125	125	115	53	63	
	200	200	20	5.12	1000	50	500	142.3	0.000235	605	11.0	12.6	4.5	4.4	6.3	63.7	5.5	37.7	5.5	14.7	317.7	14.5	185.5	202.5	>120	72.8	27	35	30	13	13	73	44	53	
2N7000	1000		50	15.3	1000	50	500	476.2	0.0500	325	11.0	28.0	28.0	20.2	36.0	553.9	28.0	683.9	28.0	8.0	8.0	43.0	476.2	5.2	46.7	4.5	7.0	1000	324	2145	314	475	314	445	
	1000		50	15.3	1000	50	500	335.3	0.0500	325	11.0	45.0	45.0	25.1	357.7	28.5	447.7	28.5	8.0	43.0	353.5	7.1	23.5	6.3	44.2	1000	358	2144	245	333	451				
	200		50	15.3	1000	50	500	142.3	0.0500	325	11.0	1.4	1.4	1.4	1.4	181.5	24.5	291.5	24.5	8.0	43.0	476.2	5.2	51.5	15.2	26.8	1000	386	1942	124	143	484			
	2200	10000	50	15.3	1000	50	500	476.2	0.0500	325	11.0	28.0	22.0	23.5	23.5	553.9	28.0	683.9	28.0	75.0	242.4	38.8	39.8	8.7	28.5	8.5	3.5	95	85	63	351	351	275	258	
	2200	10000	50	15.3	1000	50	500	335.3	0.0500	325	11.0	45.0	45.0	16.9	357.7	28.5	447.7	28.5	8.0	43.0	205.0	18.0	26.0	16.5	42.9	120	119	32	285	224	242	242			
	2200	200	50	15.3	1000	50	500	142.3	0.0500	325	11.0	1.4	7.8	7.8	5.3	181.5	24.5	291.5	24.5	185.8	205.7	44.8	45.8	55.1	18.0	27.7	274	228	476	194	117	113	235		
	1000	10000	50	15.3	1000	50	500	476.2	0.0500	325	11.0	28.0	18.7	18.8	23.5	553.9	28.0	683.9	28.0	34.5	365.5	28.4	318.5	42.8	25.0	14.6	44.6	52	47	35	329	329	242	165	388
	1000	10000	50	15.3	1000	50	500	335.3	0.0500	325	11.0	45.0	44.5	18.4	357.7	28.5	447.7	28.5	43.5	186.8	241.4	55.3	232.0	44.5	23.7	16.5	44.3	68	49	258	258	193	144	168	
	1000	200	50	15.3	1000	50	500	142.3	0.0500	325	11.0	1.4	7.2	7.2	5.2	181.5	24.5	291.5	24.5	185.8	182.3	32.3	28.8	23.7	134	119	32	125	125	111	31	156			
	200	10000	50	15.3	1000	50	500	476.2	0.0500	325	11.0	28.0	7.6	7.6	8.1	553.9	28.0	683.9	28.0	6.5	183.1	187.4	43.1	58.8	182.0	26	24	22	17	141	141	133	53	82	
	200	10000	50	15.3	1000	50	500	335.3	0.0500	325	11.0	45.0	6.7	6.8	8.2	357.7	28.5	447.7	28.5	3.7	187.5	201.2	43.8	59.8	183.8	23.8	27	24	21	125	125	124	51	48	
	200	200	50	15.3	1000	50	500	142.3	0.0500	325	11.0	1.4	4.5	4.5	5.5	181.5	24.5	291.5	24.5	21.5	318.4	14.3	37.4	45.1	75.6	184.4	44.7	41	34	28	83	83	42	47	



BS170 Would Not Behave

- Transistors were from China
- Parameters may be well off from LTSpice model/Datasheet
- I started to dust off my Transistor Tracer

LTSPICE MODELS: Bitten Yet Again

```
.model BS170 VDMOS VTO=1.824 RG=270 RS=1.572 RD=1.436 RB=.768 KP=.1233
Cgdmax=20p Cgdmin=3p CGS=28p Cjo=35p Rds=1.2E8 IS=5p Bv=60 Ibv=10u Tt=161.6n
```

C _{iss}	24	40
C _{oss}	17	30
C _{rss}	7	10
C _{gd}	7	10
C _{gs}	17	30
C _{ds}	10	20



ON CHARACTERISTICS (Note 1)

V _{GS(th)}	Gate Threshold Voltage	V _{DS} = V _{GS} , I _D = 1 mA	All	0.8	2.1	3	V
R _{Ds(on)}	Static Drain-Source On-Resistance	V _{GS} = 10 V, I _D = 200 mA	All	-	1.2	5	Ω
g _{FS}	Forward Transconductance	V _{DS} = 10 V, I _D = 200 mA	BS170	-	320	-	mS
		V _{DS} ≥ 2 V _{DS(on)} , I _D = 200 mA	MMBF170	-	320	-	


DYNAMIC CHARACTERISTICS

C _{iss}	Input Capacitance	V _{DS} = 10 V, V _{GS} = 0 V, f = 1.0 MHz	All	-	24	40	pF
C _{oss}	Output Capacitance		All	-	17	30	pF
C _{rss}	Reverse Transfer Capacitance		All	-	7	10	pF






Furthermore, Transistor Tracer measurements are VERY different




Real World Comparison: Findings

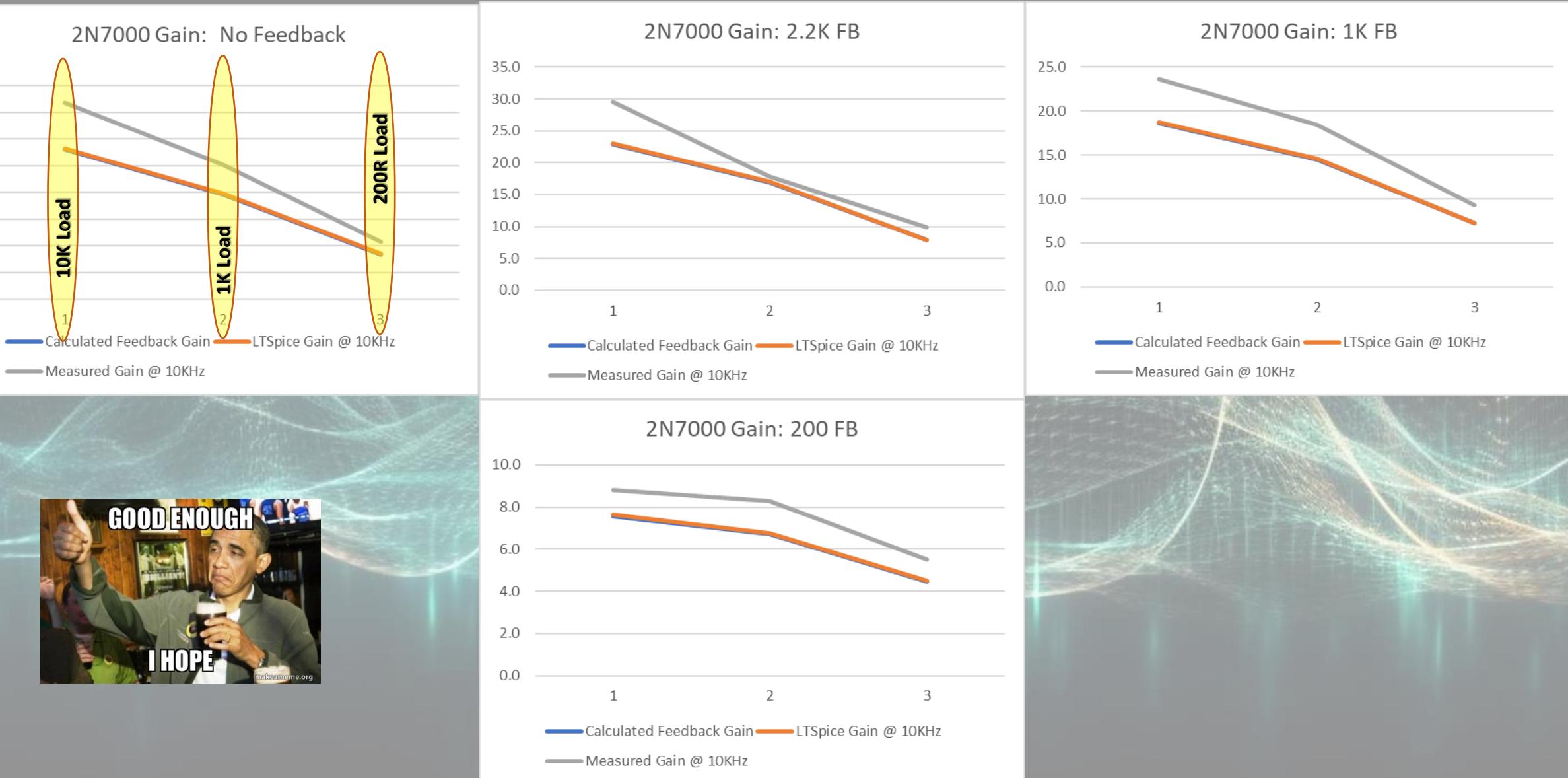


Real World Comparison: Findings

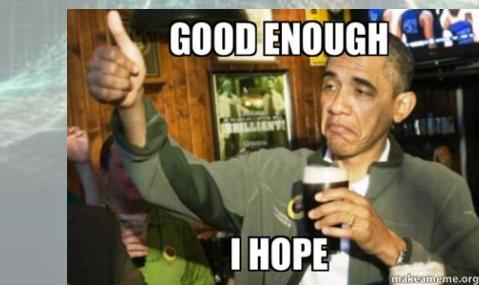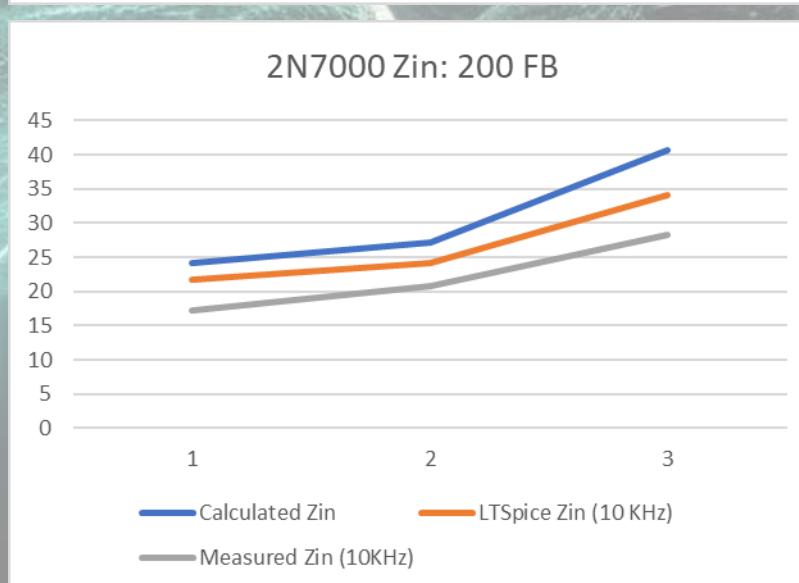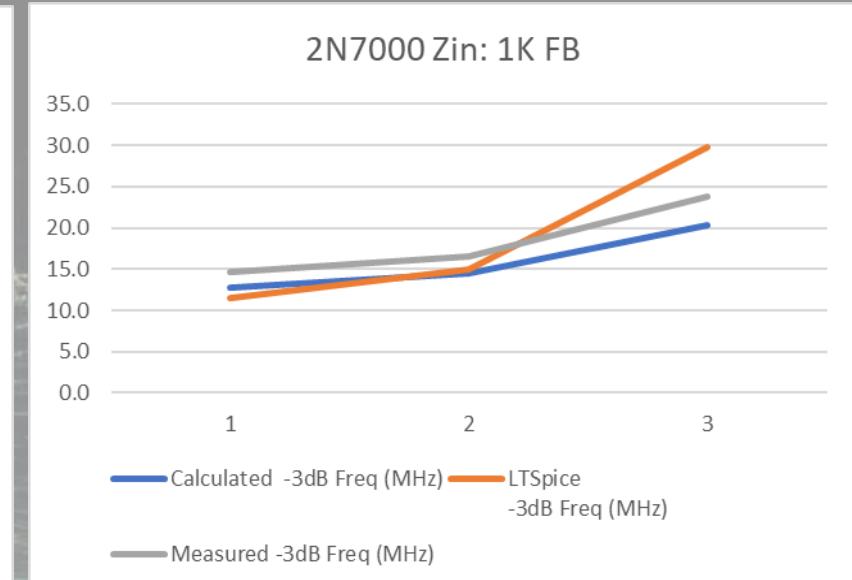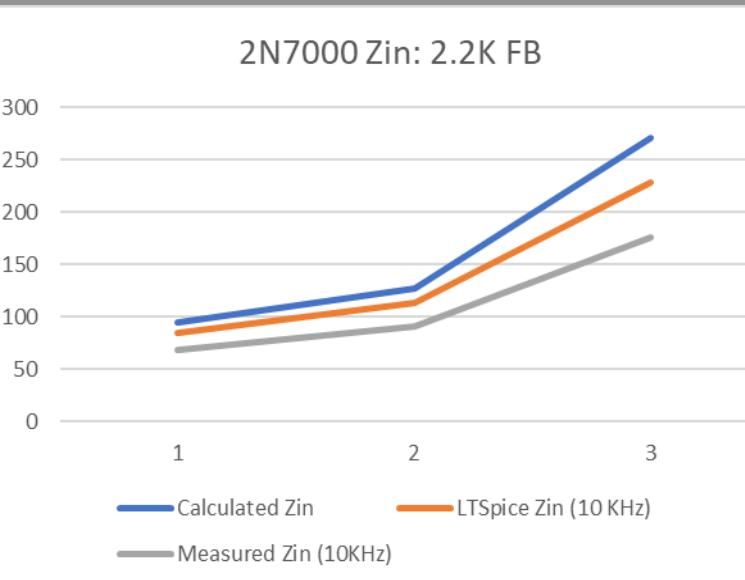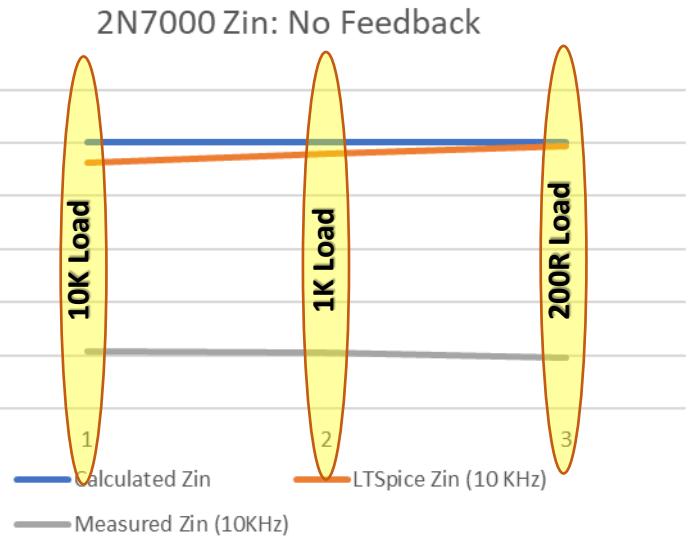

Real World Comparison: Findings

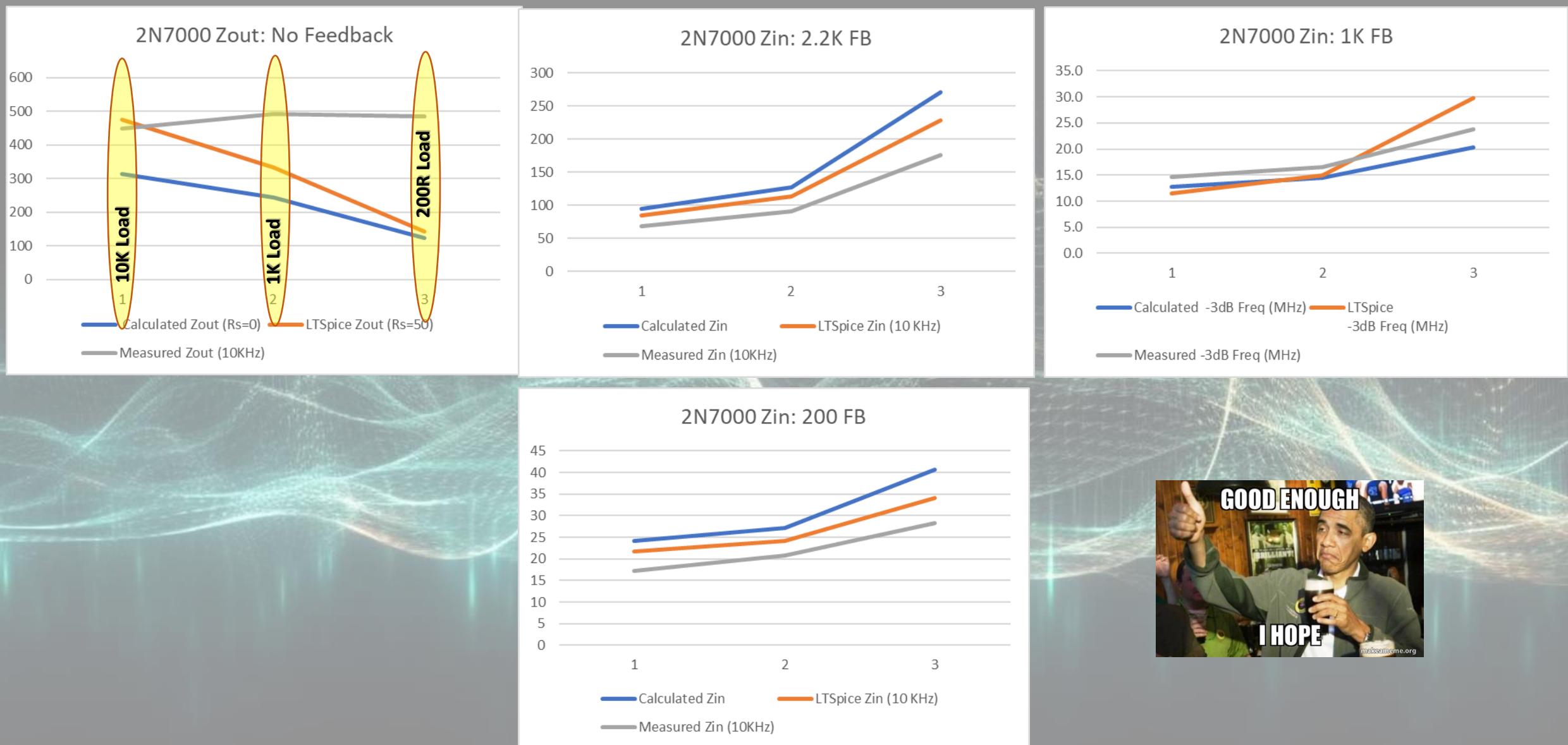

Real World Comparison: Findings

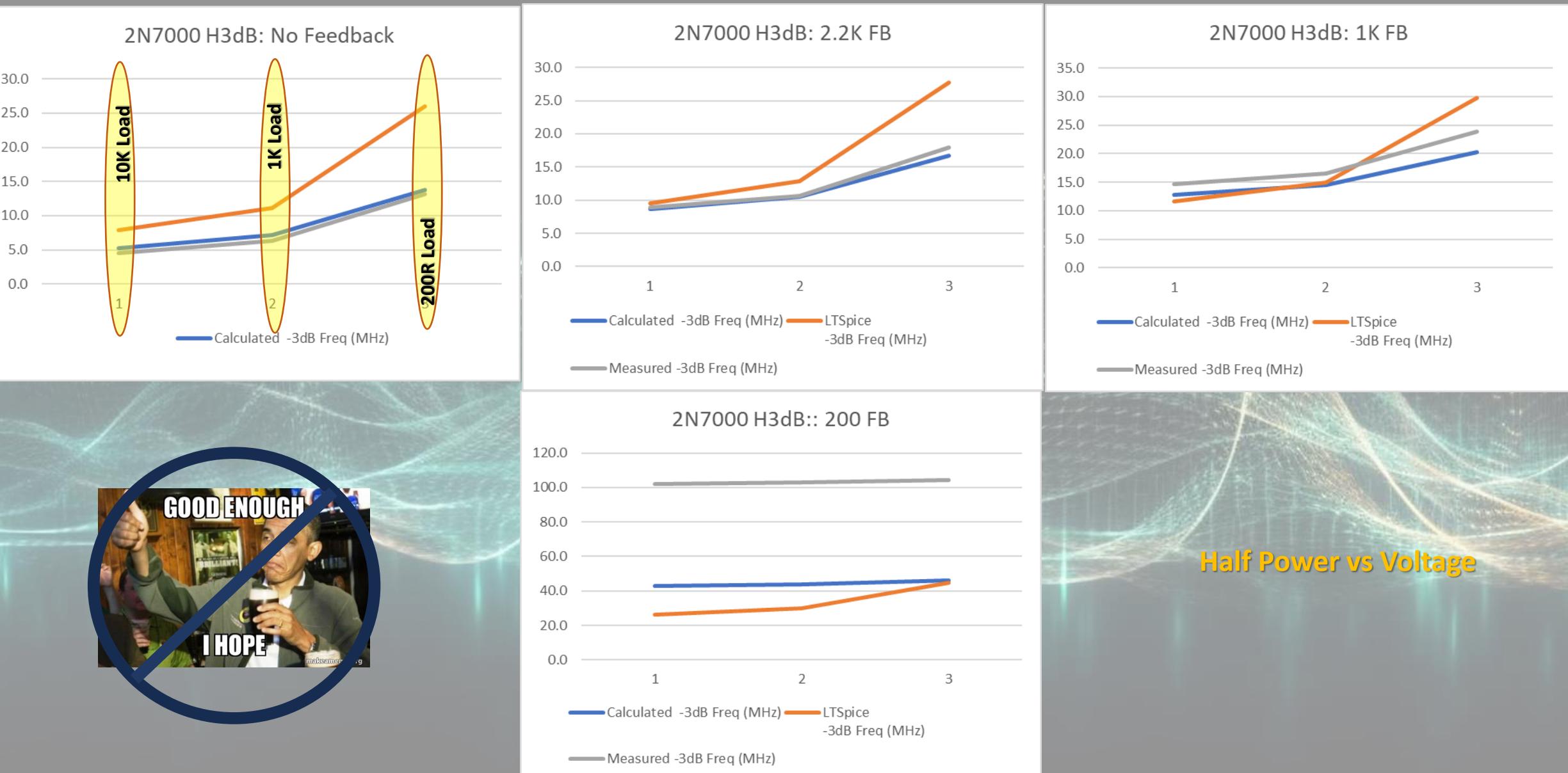

General Outcome



How to make RF measurements?

EQUATION SUMMARY

Low Frequency (well below -3dB Frequency)

- Gain:

$$\checkmark A_v = (1/R_F - G_m) R_F // R_D // R_L$$

- Input Impedance:

$$\checkmark Z_{in} = (R_F + R_O) / (1 + G_m R_O) \quad (\text{for } R_B \text{ large})$$

$$\checkmark Z_{in} = R_B (R_F + R_O) / (R_F + R_O + G_m R_O R_B)$$

- For $R_O = R_D // R_L$

- Output Impedance:


$$\checkmark Z_{out} = R_F // R_D // R_L$$

Notes:

Provided:

- ✓ Gain (without feedback) = $-G_m R_O$
- ✓ Z_{out} (without feedback) = R_O
- ✓ Z_{in} (without feedback) = R_B

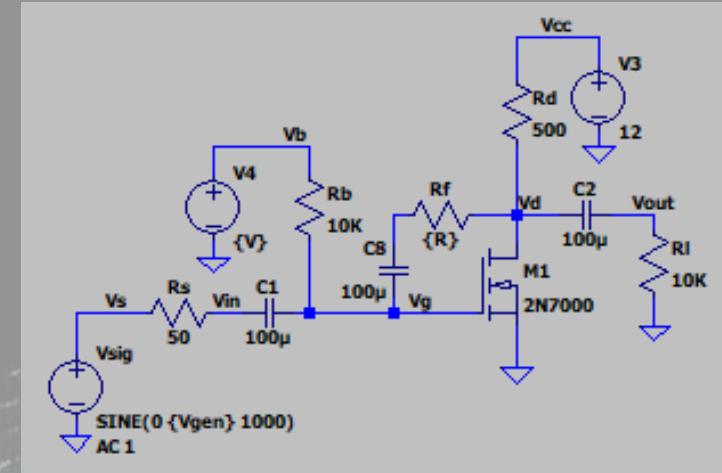1. Can solved For R_F for desired Gain (with feedback), G_m , R_D and R_L .



EQUATION SUMMARY

High Frequency (close to or beyond) -3dB Frequency)

- -3dB Cutoff Frequency


$$\checkmark F(-3\text{dB}) = 1/(2 * \pi * R_{eq} * C_{eq})$$

- For $C_{eq}(\text{input}) = C_{gd}(1+A) + C_{gs}$
- For $C_{eq}(\text{output}) = C_{gd}(1+A)/A$
- For $R_{eq}(\text{input}) = R_F/(1+A) // R_B // R_S$
- For $R_{eq}(\text{output}) = R_F A/(1+A) // R_D // R_L$

- Gain at Frequency F:

$$\checkmark A_{V(F)} = A_V * X_m / (X_m + R_i)$$

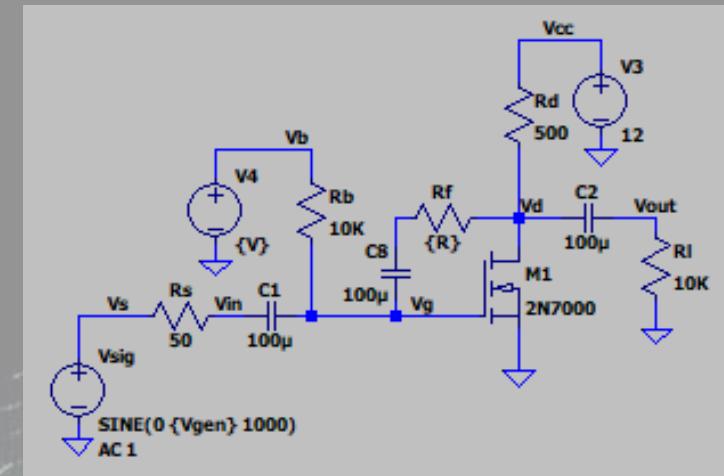- For $R_i = R_S // R_B // R_m$
- $R_m = R_F/(1+A_V)$
- $X_m = 1/(2 * \pi * F * C_{eq})$
- For $C_{eq} = C_{gs} + C_{gd} * (1+A_V)$



Notes:

1. 3dB Frequencies are an **approximation** – it's a **ballpark value**.
2. Measurement vs Calculation???



SUMMARY: RF FEEDBACK AMPLIFIERS ARE COMPLEX

HINTS and TIPS

1. Use lower gain. Multiple stages?
2. Keep input/source resistance as low as possible (more current).
3. Keep output resistance R_D and R_L as low as possible
4. Use large feedback resistors with smaller resistors for R_S R_D and R_L

$$\checkmark F(-3\text{dB}) = 1/(2 * \pi * R_{\text{eq}} * C_{\text{eq}})$$

$$\text{For } C_{\text{eq}}(\text{input}) = C_{gd}(1+A) + C_{gs}$$

$$\text{For } C_{\text{eq}}(\text{output}) = C_{gd}(1+A)/A$$


$$\text{For } R_{\text{eq}}(\text{input}) = R_F/(1+A) // R_B // R_S$$

$$\text{For } R_{\text{eq}}(\text{output}) = R_F A/(1+A) // R_D // R_L$$

Good things happen when you understand....

Dave VE3OOI (Before he went insane doing math)


MILLER EFFECT: INCREASE CURRENT

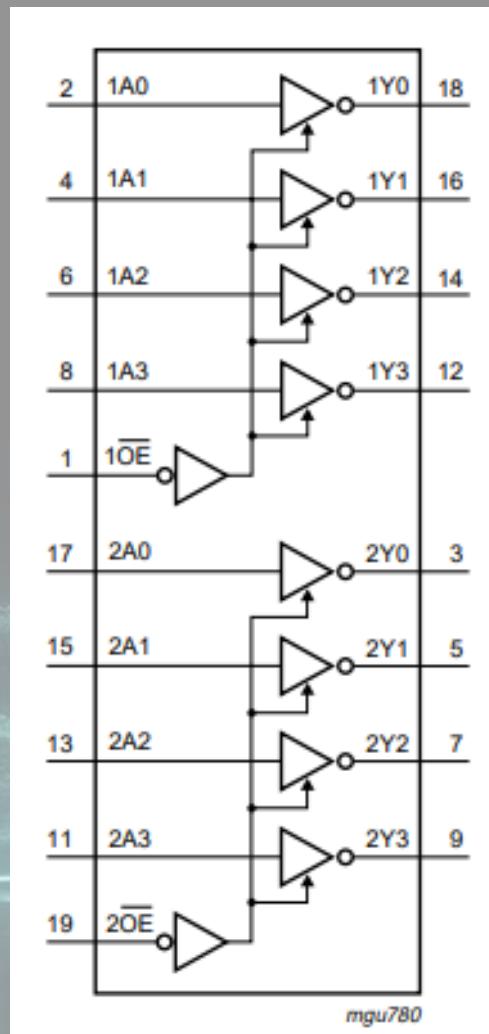

74HC240; 74HCT240

Octal buffer/line driver; 3-state; inverting

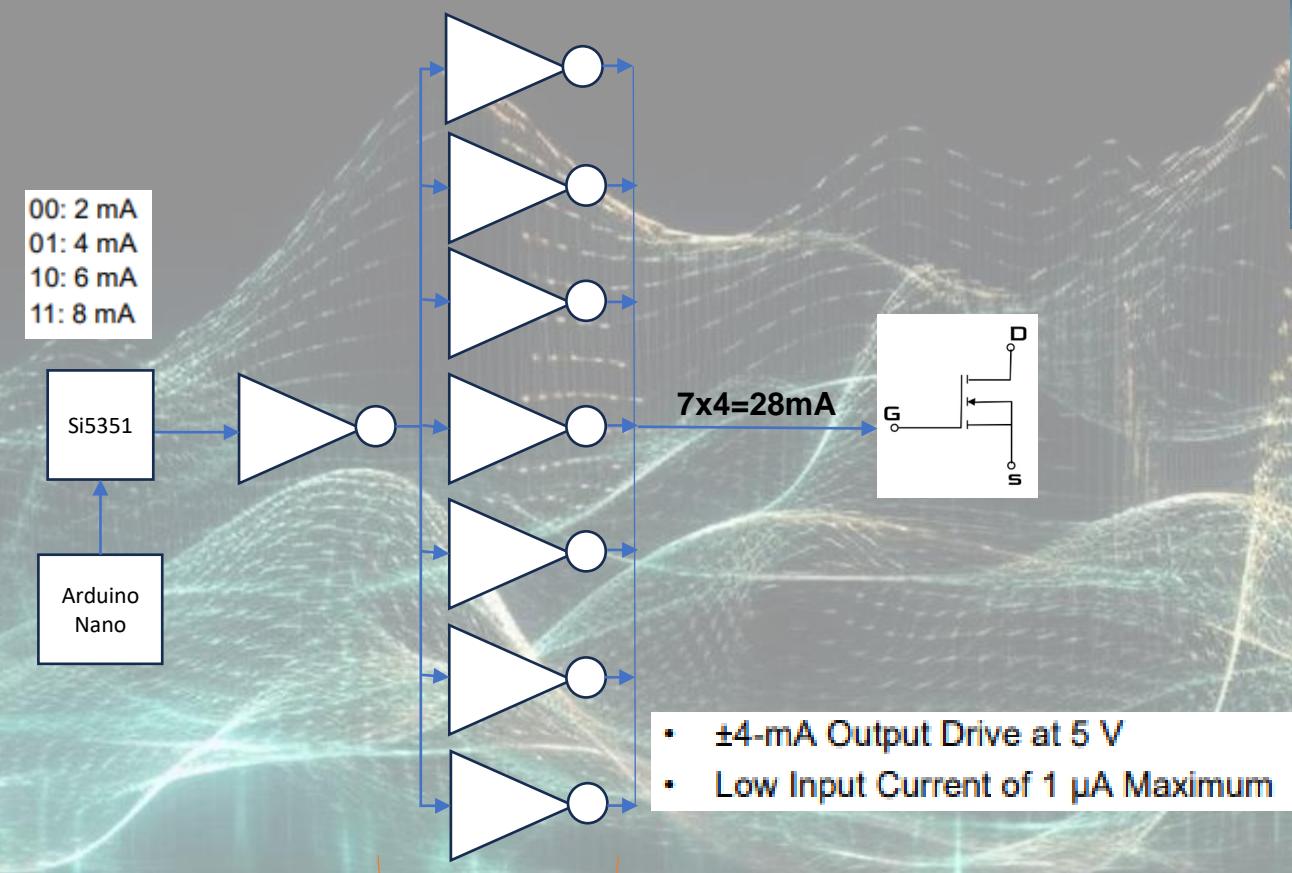The **74HC** family has High-speed CMOS circuitry, combining the speed of TTL with the very low power consumption of the




Buffer driver in parallel for greater current output.
Used for TTL Transmitters

The Si5351A/B/C features various output current drives ranging from 2 to 8 mA (default). It is recommended to configure the trace characteristics as shown in Figure 18 when an output drive setting of 8 mA is used.



Captain, we need more current...

MILLER EFFECT: INCREASE CURRENT

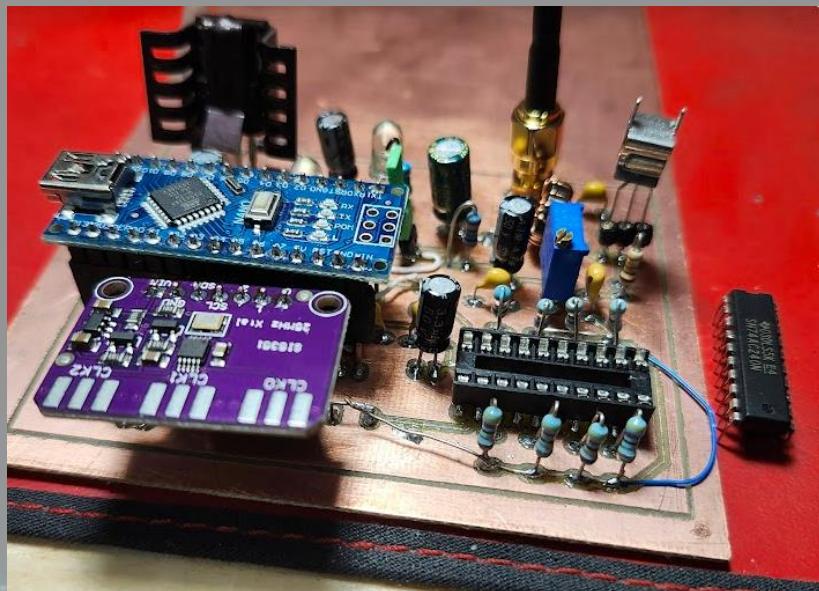


Si5351 driving BS170 MOSFET

Without 74HC240 Drivers				
Frequency (MHz)	Output (dBm)	Output (Watts)	Highest Harmonic (dBm)	Harmonic Attenuation
7	30.6	1.1	-21	-51.6
14	29.4	0.87	-21	-50.4
20	26.9	0.49	-24	-50.9
30	26.6	0.45	-24	-50.6

~8mA drive into 50R load

At least 3x
Current increase

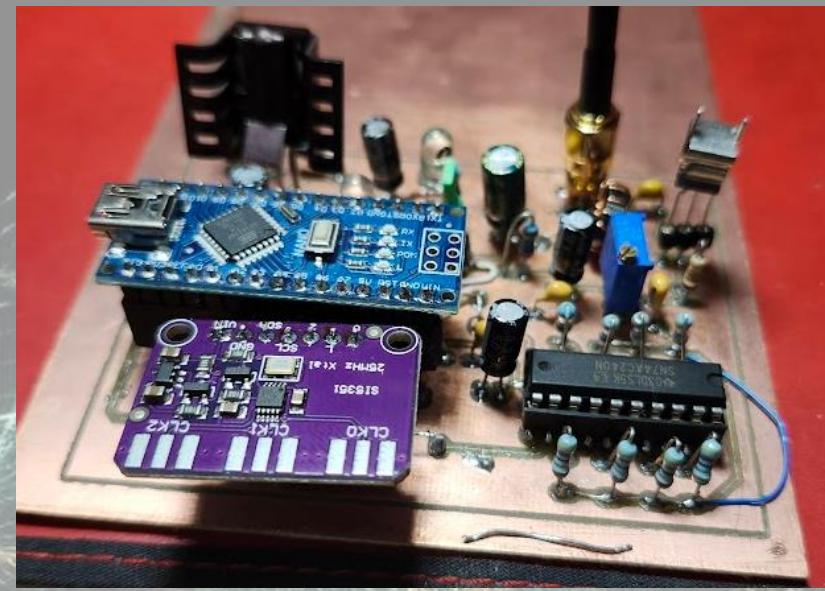Getting over 1W across HF
band with more current
from 74HC240 driver



Si5351 & 74HC140 driving BS170 MOSFET

With 74HC240 Drivers				
Frequency (MHz)	Output (dBm)	Output (Watts)	Highest Harmonic (dBm)	Harmonic Attenuation
7	32.8	1.9	-20	-52.8
14	31.8	1.5	-20	-51.8
20	31.2	1.3	-21	-52.2
30	30.5	1.1	-21	-51.5

~28mA drive into ?? load

That's all folks!